

2.2 Controlled Single phase halfwave rectifier

2.2.1 Resistive load

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d\omega t$$

$$= \frac{V_m}{2\pi} (-\cos \omega t)_{\alpha}^{\pi}$$

$$= \frac{V_m}{2\pi} (1 + \cos \alpha) \quad \text{--- (2-8)}$$

$$I_o = \frac{V_o}{R}$$

$$i = \frac{V_m}{R} \sin \omega t \quad \alpha \leq \omega t \leq \pi \quad \text{--- (2-9)}$$

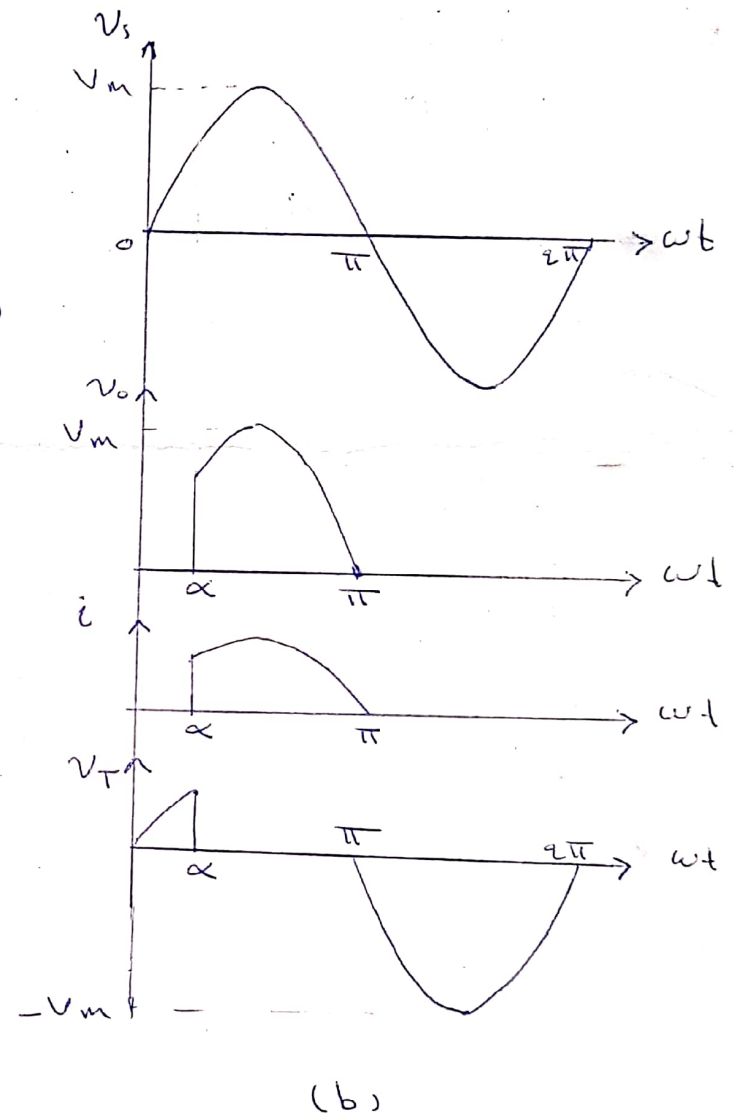
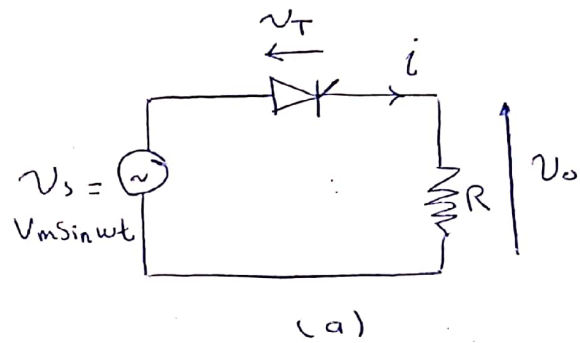


Fig. (2-5)


2.2.2 Inductive load

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\phi} V_m \sin \omega t \, d\omega t$$


$$= \frac{V_m}{2\pi} (-\cos \omega t)_{\alpha}^{\phi}$$

$$= \frac{V_m}{2\pi} (\cos \alpha - \cos \phi) \quad \dots (2.16)$$

$$I_o = \frac{V_o}{R}$$

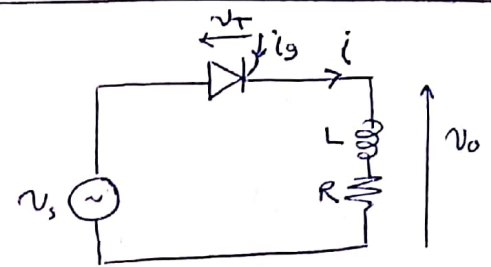

(a)

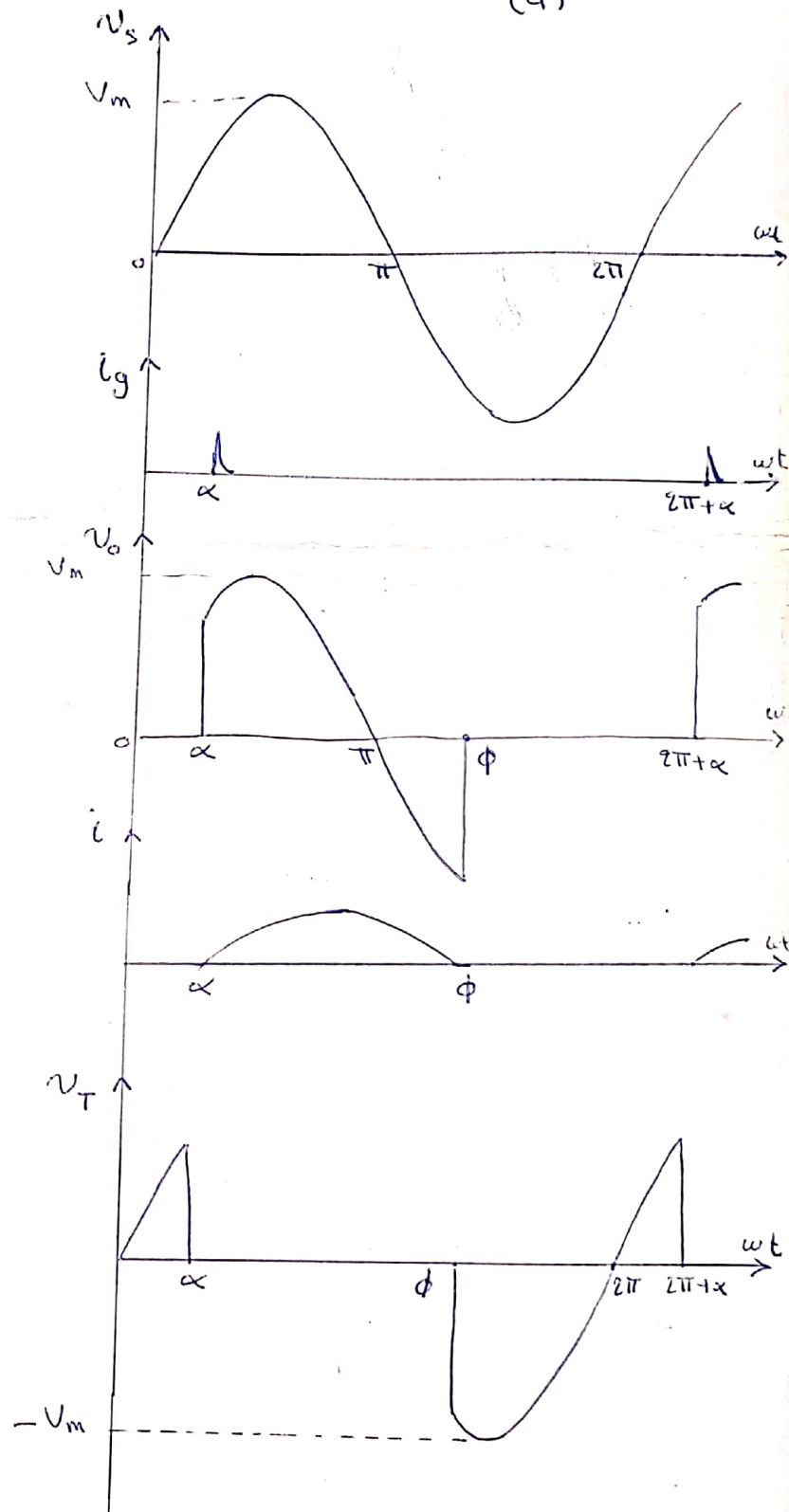

(b)


Fig. (2.6)

2-2-3 Inductive load with freewheeling diode


$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$= \frac{V_m}{2\pi} (-\cos \omega t)_{\alpha}^{\pi}$$
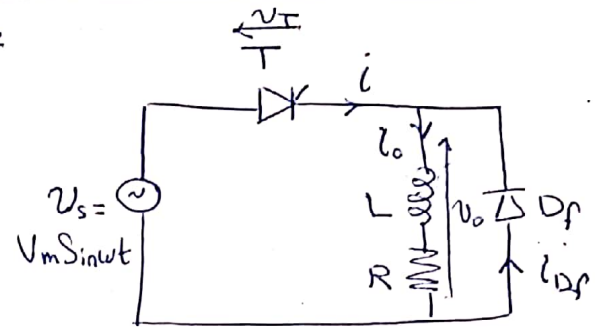
$$= \frac{V_m}{2\pi} (1 + \cos \alpha) \quad \text{--- (2.11)}$$




(a)

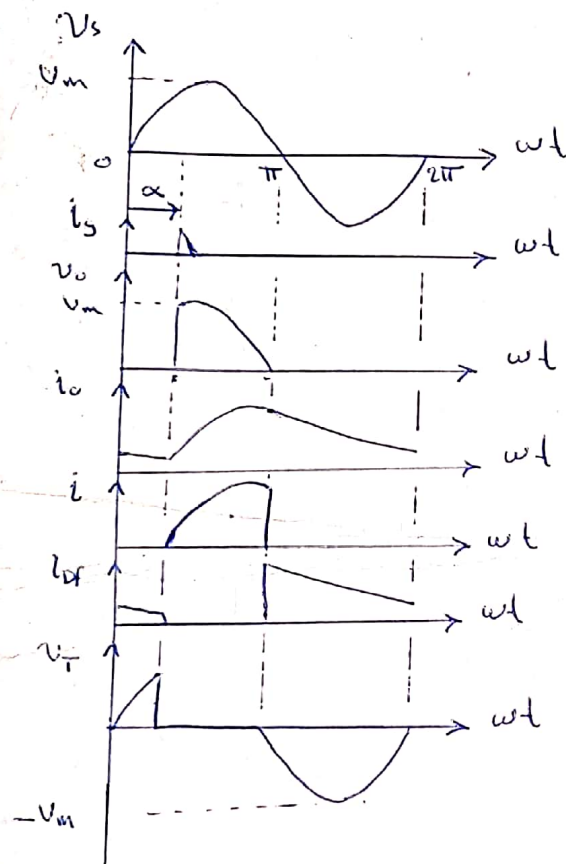

(b)

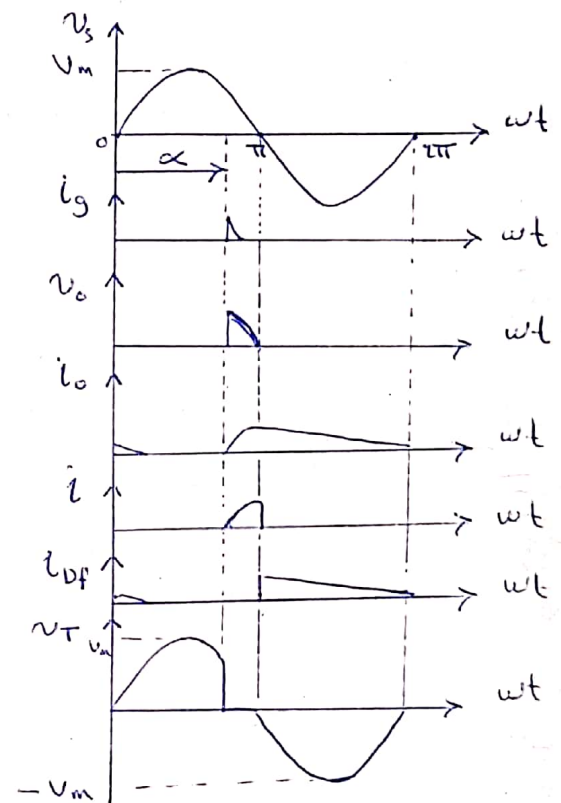small firing delay
angle
&
continuous current



(c)

Large firing delay
angle
&
discontinuous current

Fig. (2.7)