

Example: A single-phase inverter shown in figure (3.1a) supplies a 10 ohm resistance with inductance 50mH from a 340V dc source. If the bridge is operating at 50Hz, determine the load rms voltage and steady-state current waveforms with

- a square-wave output.
- a quasi-square-wave output with a 50 percent on time.

Solution

(a)

$$V_{Lrms} = +V_s = 340 \text{ V}$$

$$I_1 = -I_0 = \frac{V_s}{R} \frac{1 - e^{-\frac{R}{L}t_1}}{1 + e^{-\frac{R}{L}t_2}}$$

$$f = 50 \text{ Hz} \Rightarrow t_2 = \frac{1}{f} = \frac{1}{50} = 20 \text{ ms}$$

$$t_1 = 0.5 t_2$$

$$= 0.5 \times 20 \text{ ms} = 10 \text{ msec}$$

$$I_1 = -I_0 = \frac{340}{10} \frac{1 - e^{-\frac{10}{50 \times 10^{-3}} \times 10 \times 10^{-3}}}{1 + e^{-\frac{10}{50 \times 10^{-3}} \times 20 \times 10^{-3}}}$$

$$= 34 \frac{1 - e^{-2}}{1 + e^{-2}}$$

$$= 25.9 \text{ A}$$

$$t_x = \frac{L}{R} \ln \left(1 - \frac{I_0 R}{V_s} \right)$$

$$= \frac{50 \times 10^{-3}}{10} \ln \left(1 - \frac{-25.9 \times 10}{340} \right)$$

$$= 2.83 \text{ msec}$$

$$\text{when } V_L = V_s = 340 : i_L = \frac{V_s}{R} - \left(\frac{V_s}{R} - I_0 \right) e^{-\frac{R}{L}t}$$

$$\therefore i_L = \frac{340}{10} - \left(\frac{340}{10} + 25.9 \right) e^{-200t} = 34 - 59.9 e^{-200t}$$

When $v_L = -V_s = -340V$: $i_L = -\frac{V_s}{R} + \left(\frac{V_s}{R} + I_1\right)e^{-\frac{R}{L}t}$

$\therefore i_L = -\frac{340}{10} + \left(\frac{340}{10} + 25.9\right)e^{-200t} = -34 + 59.9e^{-200t}$ A

The mean power delivered to load = $P_L = \frac{1}{t_1} \int_0^{t_1} v_s i_L dt$

$\therefore P_L = \frac{1}{10 \times 10^{-3}} \int_0^{10m} 340 \times (34 - 59.9e^{-200t}) dt$

$= \frac{340}{10 \times 10^{-3}} \left(34t + \frac{59.9e^{-200t}}{200} \right) \Big|_0^{10 \times 10^{-3}}$

$= \frac{340}{10 \times 10^{-3}} \left(34 \times 10 \times 10^{-3} + \frac{59.9e^{-200 \times 10 \times 10^{-3}}}{200} - \frac{59.9}{200} \right)$

$= 2755$ W

(b)

Since the operation is ~~at~~ with 50 percent on-time hence:

$t_o = \frac{50}{100} \times t_1 = 0.5 \times 10m = 5msec$

$\alpha = \frac{\pi}{2}$

$V_{Lrms} = V_s \sqrt{1 - \frac{\alpha}{\pi}} = V_s \sqrt{1 - \frac{0.5\pi}{\pi}} = V_s \sqrt{\frac{1}{2}} = \frac{V_s}{\sqrt{2}} = \frac{340}{\sqrt{2}} = 240.4$ V

The steady-state load current is reached after few cycles:-

First 5ms on-period when $v_L = 340V$:-

$i_L = \frac{V_s}{R} - \left(\frac{V_s}{R} - I_0\right)e^{-\frac{R}{L}t}$, $I_0 = 0 \Rightarrow i_L = \frac{V_s}{R} - \frac{V_s}{R}e^{-\frac{R}{L}t}$

$\therefore i_L = 34 - 34e^{-200t}$ and at $t = 5ms \Rightarrow i_L = 34 - 34e^{-200 \times 5m} = 21.5$ A

$\Rightarrow I_1 = 21.5$ A

First 5ms zero period when $V_L = 0V$:-

$$i_L = I_1 e^{-\frac{R}{L}t} = 21.5 e^{-200t} \quad \text{ending with } i_L = 21.5 e^{-200 \times 5m} = 7.9 A$$

i.e $I_2 = 7.9 A$

Second 5ms on period when $V_L = -340V$:-

$$i_L = -\frac{V_s}{R} + \left(\frac{V_s}{R} + I_2\right) e^{-\frac{R}{L}t} = -34 + (34 + 7.9) e^{-200t}$$

$$= -34 + 41.9 e^{-200t} \quad \text{ending with } i_L = -34 + 41.9 e^{-200 \times 5m} = -18.6 A$$

Second 5ms zero period when $V_L = 0V$:-

$$i_L = I_1 e^{-\frac{R}{L}t} = -18.6 e^{-200t} \quad \text{ending with } i_L = -18.6 e^{-200 \times 5m} = -6.8 A$$

$\therefore I_0 = -6.8 A$

Third 5ms on period when $V_L = 340V$:-

$$i_L = \frac{V_s}{R} - \left(\frac{V_s}{R} - I_0\right) e^{-\frac{R}{L}t} = 34 - (34 - 6.8) e^{-200t} = 34 - 40.8 e^{-200t}$$

ending with $i_L = 19 A$ i.e $I_1 = 19 A$

Third 5ms zero period when $V_L = 0V$:-

$$i_L = I_1 e^{-\frac{R}{L}t} = 19 e^{-200t} \quad \text{ending with } i_L = 19 e^{-200 \times 5m} = 7 A$$

Fourth 5ms on period when $V_L = -340V$:-

$$i_L = -34 + (34 + 7) e^{-200t} \quad \text{ending with } i_L = -34 + 41 e^{-200 \times 5m} = -18.9 A$$


fourth 5ms zero period when $V_L = 0V$:-

$$i_L = -18.9 e^{-200t} \quad \text{ending with } i_L = -18.9 e^{-200 \times 5m} = -6.8 A$$


steady-state load current have been reached.

$$P_L = \frac{1}{t_1} \int_0^{t_0} V_s i_L dt = \frac{1}{0.01} \int_0^{0.005} 340 \{340 - 41 e^{-200t}\} dt = 1378 W$$


3.3 Three-phase bridge inverter

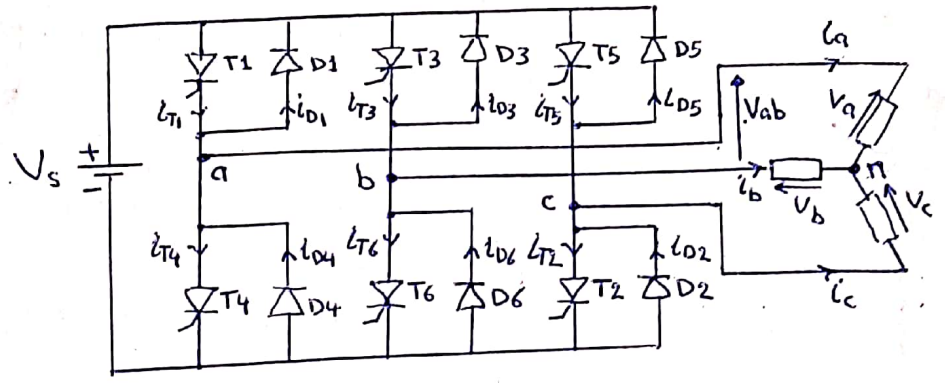

(a)

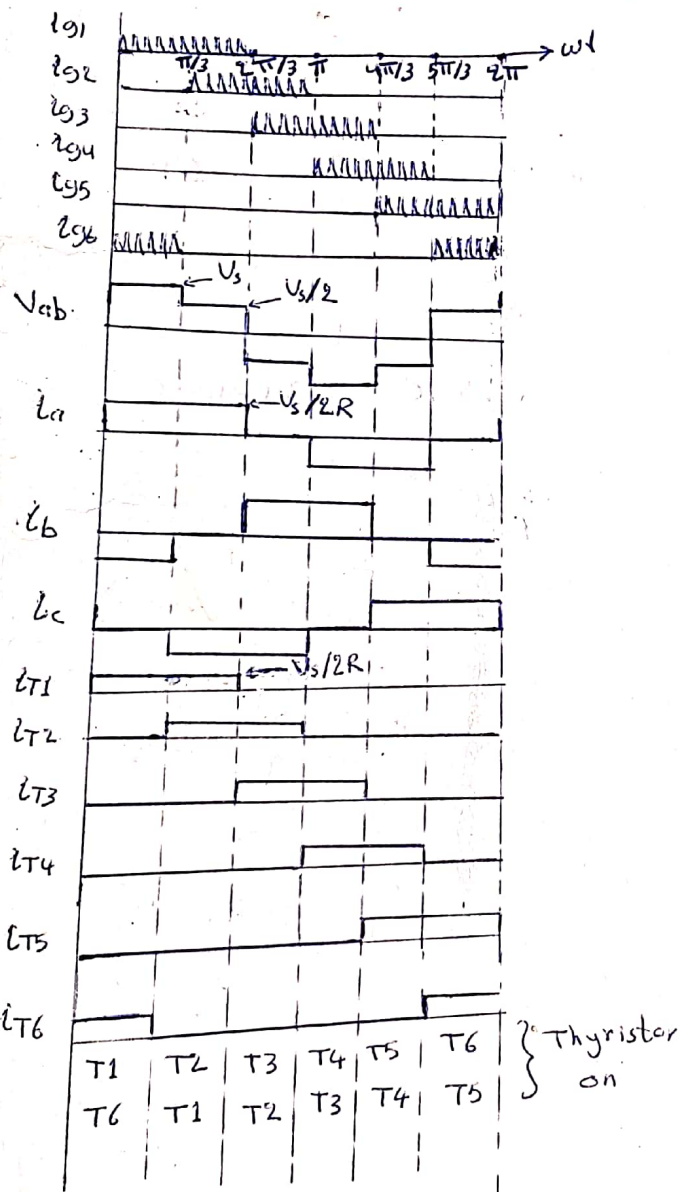

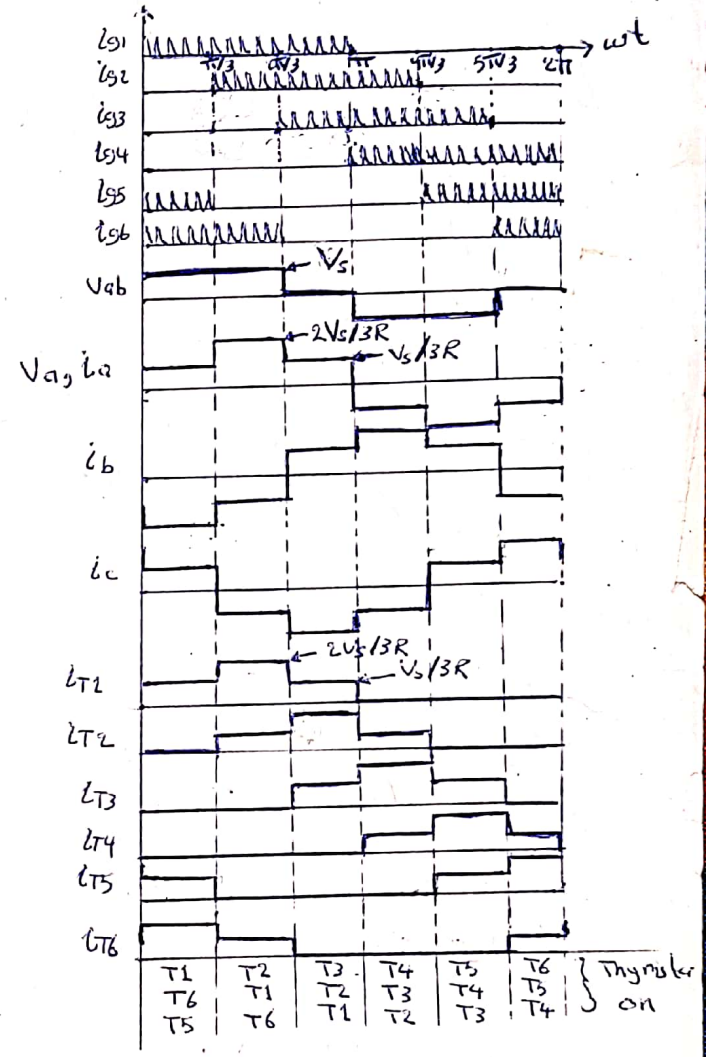(b)
 waveforms for 120° conduction
 & resistive load



(c)
 waveforms for 180° conduction
 & resistive load

Figure (3-2)