

Example 5-16 Lander p214

A three-phase bridge inverter is fed from a d.c. source of 240V. If the control is by 180° firing, quasi-square-wave output, determine the load line-current waveform at 50 Hz output given the load is (i) delta-connected, with each phase 6Ω resistance and 0.012 H inductance, (ii) star-connected, with each phase 2Ω resistance and 0.004 H inductance.

Solution

(i)

$$i_a = i_{ab} - i_{ca}$$

①

first 120°: $v_{ab} = 240V = V_s$

$$i_{ab} = \frac{V_s}{R} - \left(\frac{V_s}{R} - I_0\right) e^{-\frac{R}{L}t}, I_0 = 0$$

$$= \frac{240}{6} - \left(\frac{240}{6} - 0\right) e^{-500t}$$

$$= 40 - 40 e^{-500t}$$

at the end of this period: $-500 \times (20 \times 10^{-3} \times \frac{2}{6})$

period $i_{ab} = 40 - 40 e^{-500t}$

$$= 38.573 A$$

②

For the next 60°: $v_{ab} = 0$

$$i_{ab} = I_1 e^{-\frac{R}{L}t}$$

$$= 38.573 e^{-500t}$$

at the end of this period:

$$i_{ab} = 38.573 e^{-500 \times (20 \times 10^{-3} \times \frac{1}{6})}$$

$$= 7.285 A$$



③ For the next 120° $v_{ab} = -V_s = -240V$

$$i_{ab} = -\frac{V_s}{R} + \left(\frac{V_s}{R} + I_2\right) e^{-\frac{R}{L}t}$$

$$= -40 + (40 + 7.285) e^{-500t}$$

at the end of this period $i_{ab} = -40 + 47.285 e^{-500t}$

$$= -38.313 A$$

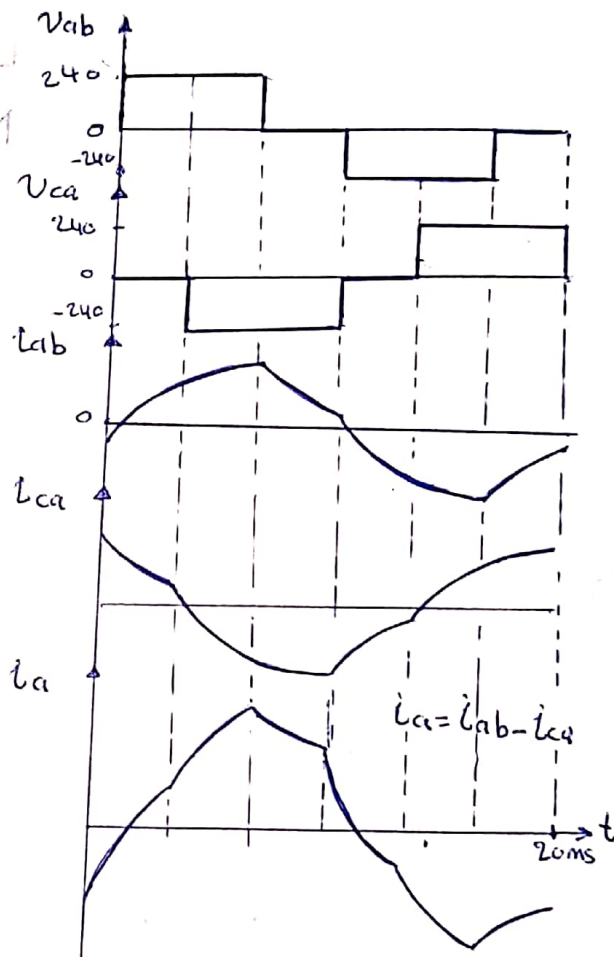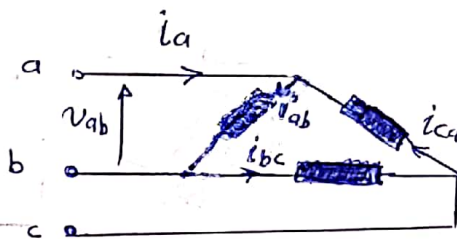

④) for the next 60° $v_{ab} = 0$

$$i_{ab} = -38.313 e^{-500t}$$

at the end of this period: $i_{ab} = -38.313 e^{-500 \times (20 \times 10^{-3} \times \frac{1}{6})} = -7.24 A$

For the next cycle the expression for the four periods will be:

- ① $i_{ab} = 40 - (40 + 7.24) e^{-500t}$ ending with $40 - 47.24 e^{-500 \times (20 \times 10^{-3} \times \frac{2}{6})} = 38.31 A$
- ② $i_{ab} = 38.31 e^{-500t}$ ending with $38.31 e^{-500 \times (20 \times 10^{-3} \times \frac{1}{6})} = 7.24 A$
- ③ $i_{ab} = -40 + (40 + 7.24) e^{-500t}$ ending with $-40 + 47.24 e^{-500 \times (20 \times 10^{-3} \times \frac{2}{6})} = -38.31 A$
- ④ $i_{ab} = -38.31 e^{-500t}$ ending with $-38.31 e^{-500 \times (20 \times 10^{-3} \times \frac{1}{6})} = -7.24 A$

i.e steady-state conditions have been reached in the second cycle.

i_{ab} for four periods is:


- first 120° : $i_{ab} = 40 - 47.24 e^{-500t}$
- next 60° : $i_{ab} = 38.31 e^{-500t}$
- next 120° : $i_{ab} = -40 + 47.24 e^{-500t}$
- next 60° : $i_{ab} = -38.31 e^{-500t}$

i_{ca} is identical to i_{ab} by displaced by 240° :

- first 60° : $i_{ca} = 38.31 e^{-500t}$
- next 120° : $i_{ca} = -40 + 47.24 e^{-500t}$
- next 60° : $i_{ca} = -38.31 e^{-500t}$
- next 120° : $i_{ca} = 40 - 47.24 e^{-500t}$

$i_a = i_{ab} - i_{ca}$ hence:-
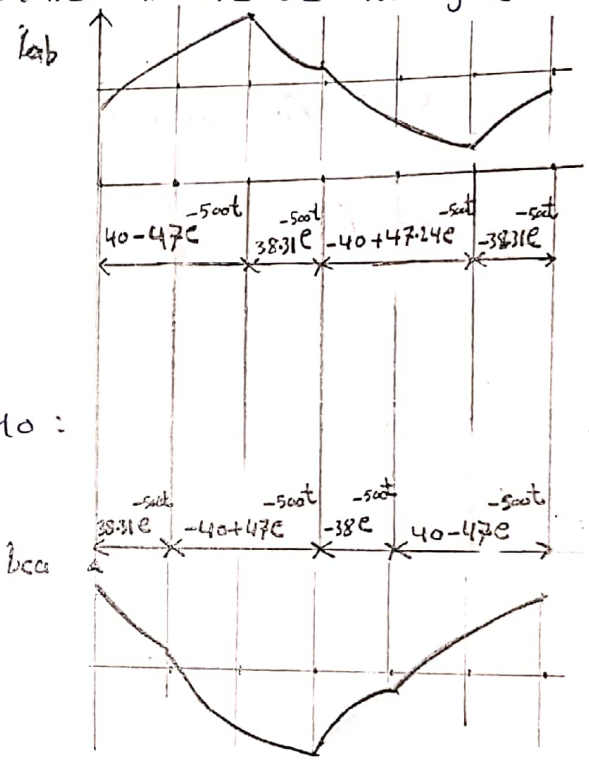
$$\begin{aligned} \text{first } 60^\circ: i_a &= 40 - 47.24 e^{-500t} - 38.31 e^{-500t} \\ \text{next } 60^\circ: i_a &= 40 - 47.24 e^{-500t} + 40 - 47.24 e^{-500t} \\ &= 40 - 47.24 e^{-500t} + 40 - 47.24 e^{-500t} \\ &= 80 - 80.922 e^{-500t} - 47.24 e^{-500t} \end{aligned}$$



$$\text{next } 60^\circ: i_a = 38.31e^{-500t} + 40 - 47.24e^{-500(t + \frac{1}{300})}$$

$$= 38.31e^{-500t} + 40 - 8.922e^{-500t}$$

$$\text{next } 60^\circ: i_a = -40 + 47.24e^{-500t} + 38.31e^{-500t}$$

$$\text{next } 60^\circ: i_a = -40 + 47.24e^{-500(t + \frac{1}{300})} - 40 + 47.24e^{-500t}$$

$$= -40 + 8.922e^{-500t} - 40 + 47.24e^{-500t}$$

$$\text{next } 60^\circ: i_a = -38.31e^{-500(t + \frac{1}{300})} - 40 + 47.24e^{-500t}$$

$$= -38.31e^{-500t} - 40 + 8.922e^{-500t}$$

(b) For star load:



① first 60°

$$i_a = \frac{V_s/3}{R} - \left(\frac{V_s/3}{R} - I_0 \right) e^{-\frac{R}{L}t}$$

$$= \frac{80}{2} - \frac{80}{2} e^{-500t}$$

$$= 40 - 40e^{-500t}$$
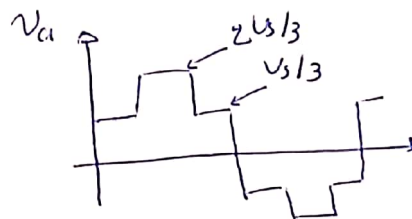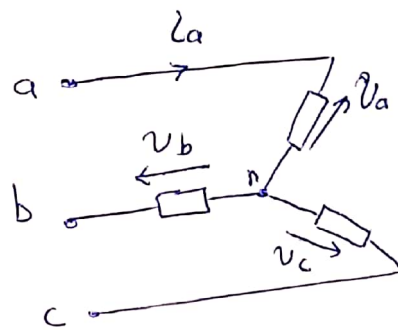
$$\text{ending with } i_a = 40 - 40e^{-500 \cdot \frac{1}{300}} = 32.445 \text{ A}$$



② next 60°

$$i_a = \frac{2V_s/3}{R} - \left(\frac{2V_s/3}{R} - I_0 \right) e^{-500t}$$

$$= \frac{160}{2} - \left(\frac{160}{2} - 32.445 \right) e^{-500t}$$

ending with $i_a = 71$

next 60° :

$$i_a = \frac{80}{2} - \left(\frac{80}{2} - 71\right)e^{-500t} \text{ ending with } i_a = 45.855 \text{ A}$$

next 60° :

$$i_a = -\frac{V_s/3}{R} + \left(\frac{V_s/3}{R} + I_2\right)e^{-\frac{R}{L}t}$$

$$= -\frac{80}{2} + \left(\frac{80}{2} + 45.855\right)e^{-500t}$$

ending with $i_a = -23.78 \text{ A}$

next 60° :

$$i_a = -\frac{160}{2} + \left(\frac{160}{2} - 23.78\right)e^{-500t}$$

ending with $i_a = -69.38 \text{ A}$

next 60° :

$$i_a = -\frac{80}{2} + \left(\frac{80}{2} - 69.38\right)e^{-500t}$$

ending with $i_a = -45.55 \text{ A}$

For the second cycle :-

first 60° : $i_a = 40 - (40 + 45.55)e^{-500t}$ ending with 23.84 A

next 60° : $i_a = 80 - (80 - 23.84)e^{-500t}$ ending with 69.39

next 60° : $i_a = 40 - (40 - 69.39)e^{-500t}$ ending with 45.55 A

next 60° : $i_a = -40 + (40 + 45.55)e^{-500t}$ ending with -23.84 A

next 60° : $i_a = -80 + (80 - 23.84)e^{-500t}$ ending with -69.39 A

next 60° : $i_a = -40 + (40 - 69.39)e^{-500t}$ ending with -45.55 A

steady-state condition have been reached.