

Example 7.1 P 382

The following test data are obtained from a 1/4 hp, ^{4 pole} 1 ϕ , 120V, 60 Hz, 1730 rpm induction motor.

Stator winding (main) resistance = 2.9 Ω

Block rotor (standstill) test: The rotor is prevented from rotating

$$V = 34 \text{ V}, I = 5 \text{ A}, P = 140 \text{ W}$$

No-load test: Motor is running freely

$$V = 120 \text{ V}, I = 3.5 \text{ A}, P = 125 \text{ W}$$


(a) Obtain the double revolving field equivalent circuit for the motor.

(b) Determine the rotational loss.

Solution

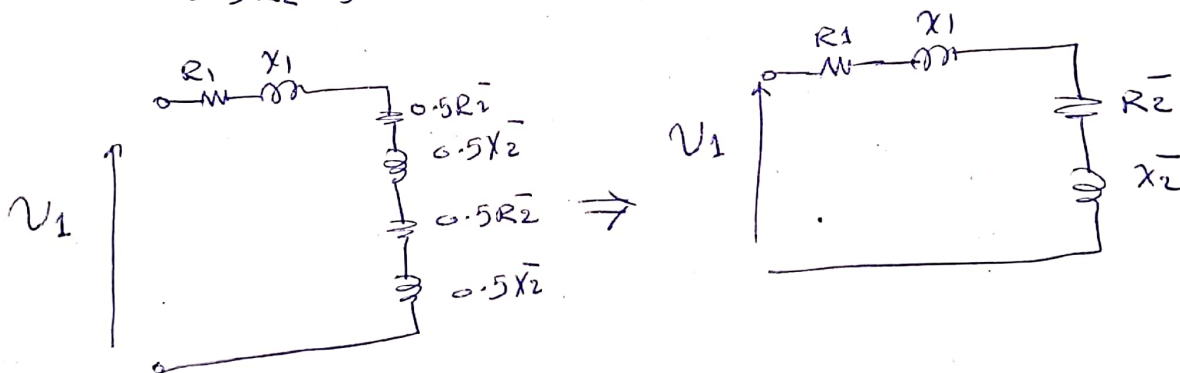(a) at $s = 1$ (standstill)

$0.5R_2 + j0.5X_2 \ll j0.5X_m$ hence the equ. ckt is



$$P = I^2 (R_1 + R_2)$$

$$140 = 5^2 (2.9 + R_2)$$

$$\Rightarrow R_2 = 2.7 \Omega$$

$$Z = \frac{V}{I} = \frac{34}{5} = 8.6 \Omega$$

$$Z = \sqrt{(R_1 + R_2)^2 + (X_1 + X_2)^2}$$

Single phase Motors

$$(x_1 + x_2)^2 = z^2 - (R_1 + R_2)^2$$

$$= 8.6^2 - (2.9 + 2.7)^2$$

$$x_1 + x_2 = 6.53 \Omega$$

assume $x_1 = x_2 = 6.53 / 2 = 3.26 \Omega$

at no load

$$\frac{0.5 R_2}{s} + j0.5 x_2 \gg j0.5 x_m$$

$$\frac{0.5 R_2}{2-s} + j0.5 x_2 \ll j0.5 x_m$$

$$\frac{0.5 R_2}{s} = 0.5 R_2 + 0.5 R_2 \left(\frac{1-s}{s} \right)$$

$$= R_{cuf} + R_{mech \cdot f}$$

$$\frac{0.5 R_2}{2-s} = 0.5 R_2 + 0.5 R_2 \frac{1-(2-s)}{2-s}$$

$$= R_{cub} + R_{mech \cdot b}$$


The mechanical power developed at no load represents rotational losses, which will include core loss.

ان $\frac{0.5 R_2}{2-s}$ هنا تمثل الخسائر الميكانيكية و لكن لا يوجد شيء

يشكل الخسائر الميكانيكية core loss لكن يوجد مقاومة R_{rot}

تمثل كل خسائر الدوران rotational loss = friction & windage + core loss

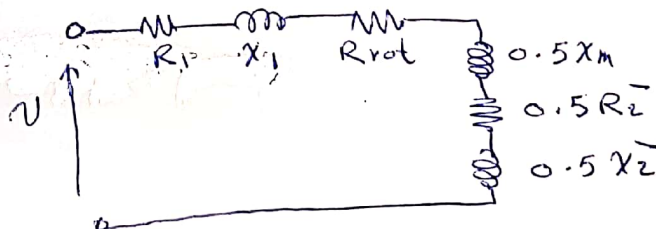المقاومة $(0.5 R_2)$ تمثل الخسائر الميكانيكية في rotor في حالة الازدحام



$$P_{NL} = I_{NL}^2 (R_1 + R_{rot} + 0.5R_2)$$

$$= I_{NL}^2 R_{NL}$$

$$R_{NL} = \frac{125}{(3.5)^2} = 10.2 \Omega$$

$$Z_{NL} = \frac{V}{I_N} = \frac{120}{3.5} = 34.3 \Omega$$

$$Z_{NL} = \sqrt{R_{NL}^2 + (X_1 + 0.5X_m + 0.5X_2)^2}$$

$$X_1 + 0.5X_m + 0.5X_2 = \sqrt{(34.3)^2 - (10.2)^2} = 32.75 \Omega$$

$$X_m = \frac{32.75 - 3.26 - 0.5 \times 3.26}{0.5}$$

$$= 55.72 \Omega$$

(b)

$$P_{NL} = I_{NL}^2 (R_1 + R_{rot} + 0.5R_2)$$

$$= I_{NL}^2 (R_1 + 0.5R_2) + I_{NL}^2 R_{rot}$$

$$= \text{copper loss} + \text{rotational loss}$$

$$I_{NL}^2 R_{rot} = P_{NL} - I_{NL}^2 (R_1 + 0.5R_2)$$

$$= 125 - (3.5)^2 (2.9 + 0.5 \times 2.7)$$

$$= 72.94$$