

## Single phase motors

Equivalent circuit of a capacitor run motor

In capacitor run and capacitor-start capacitor-run induction motor, the auxiliary winding stays in operation all the time and the motor operates as a two-phase induction motor.

As shown in figure (19), the main winding and auxiliary winding are excited by currents  $I_m$  and  $I_a$ .

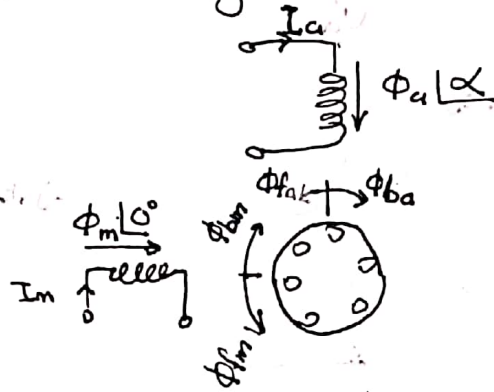


Fig (19)

The main flux  $\Phi_m$  can be resolved into two revolving

fluxes  $\Phi_{fm}$  (forward revolving) and  $\Phi_{bm}$  (backward revolving).

Similarly, the auxiliary winding flux  $\Phi_a$  is resolved into two revolving fluxes  $\Phi_{fa}$  and  $\Phi_{fb}$ . These four revolving

fluxes all induce voltages in the two windings.

The main winding can be represented by the equivalent circuit shown in figure (20a) where

$a = N_a/N_m$ . The auxiliary winding is represented

by an equivalent circuit shown in figure (20b).

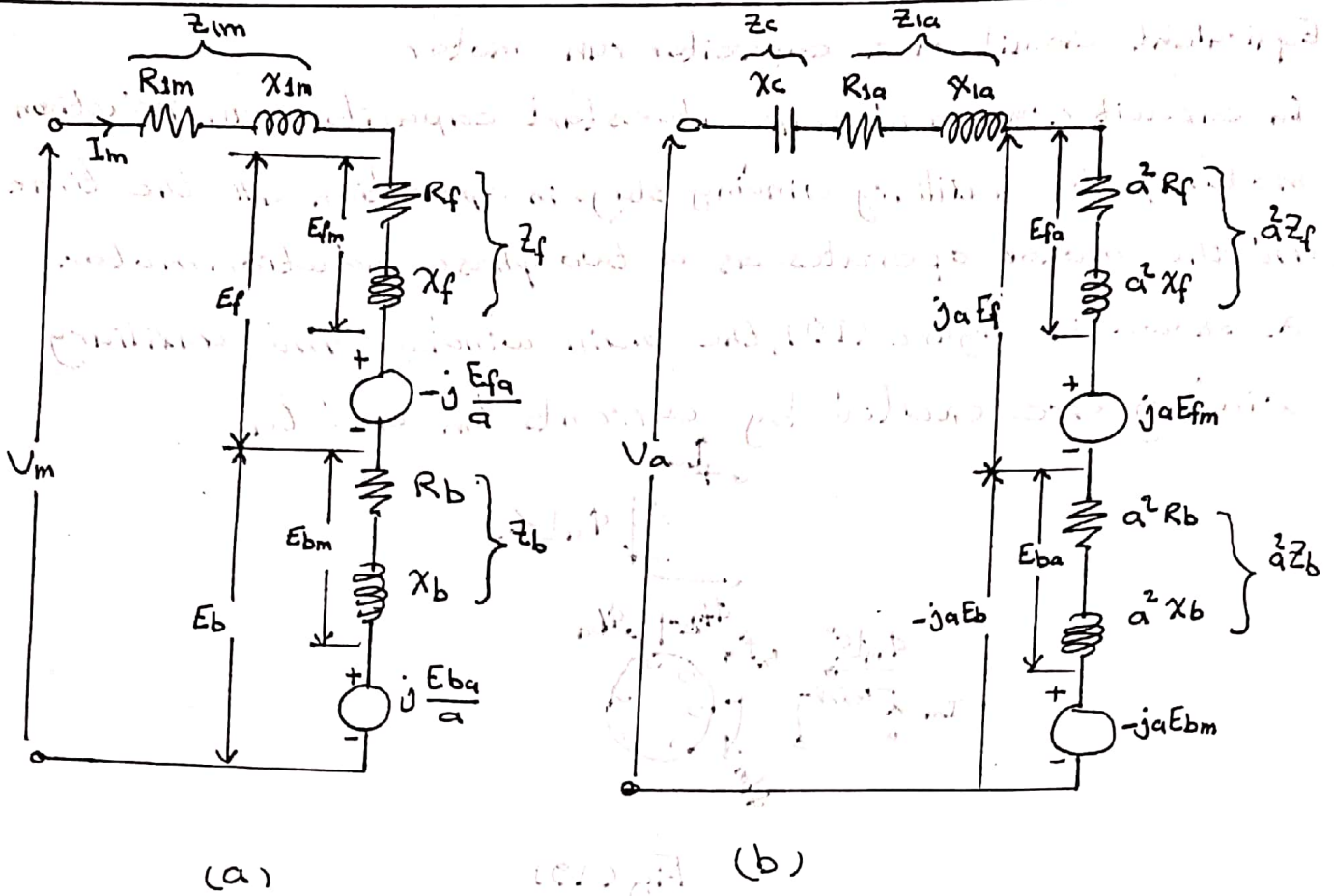


Figure (20)

$$U_m = (Z_{im} + Z_f + Z_b) I_m - j \frac{E_{fa}}{a} + j \frac{E_{ba}}{a} \quad \text{--- (1)}$$

$$V_a = (Z_c + Z_{1a} + a^2 Z_f + a^2 Z_b) I_a + ja E_{fm} - ja E_{bm} \quad \text{--- (2)}$$

where  $Z_{im} = R_{im} + jX_{im}$

$$Z_{1a} = R_{1a} + jX_{1a}$$

$$Z_c = -jX_c$$

Now:

$$E_{fa} = I_a \cdot a^2 Z_f \quad \text{--- (4)}$$

$$E_{ba} = I_a \cdot a^2 Z_b \quad \text{--- (5)}$$

$$E_{fm} = I_m \cdot Z_f \quad \text{--- (6)}$$

$$E_{bm} = I_m \cdot Z_b$$

referring rotor to the main stator winding  $Z_f = R_f$   
 $R_f = R \cdot \frac{N_m}{N_f}$   
 referring rotor to the auxiliary stator winding  $= R_f \cdot \frac{N_m}{N_a}$   
 $= R \cdot \frac{N_m}{N_f} \cdot \frac{N_a}{N_m}$   
 $= R \cdot \frac{N_a}{N_f}$

$$\text{--- (3)}$$

$$\text{--- (4)}$$

$$\text{--- (5)}$$

$$\text{--- (6)}$$

## Single phase motors

substitute equations (3) to (6) in (1) & (2):

$$V_m = (Z_{im} + Z_f + Z_b) I_m - j a (Z_f - Z_b) I_a \quad \text{--- (7)}$$

$$V_a = j a (Z_f - Z_b) I_m + (Z_c + Z_{1a} + a^2 Z_f + a^2 Z_b) I_a \quad \text{--- (8)}$$

let  $Z_M = Z_{im} + Z_f + Z_b$

$$Z_A = Z_{1a} + Z_c + a^2 Z_f + a^2 Z_b$$

hence

$$V_m = Z_M I_m - j a (Z_f - Z_b) I_a \quad \text{--- (9)}$$

$$V_a = j a (Z_f - Z_b) I_m + Z_A I_a \quad \text{--- (10)}$$

From (9) & (10),  $I_m$  &  $I_a$  can be solved:

$$I_m = \frac{V_m Z_A + j a V_a (Z_f - Z_b)}{Z_M Z_A - a^2 (Z_f - Z_b)^2} \quad \text{--- (11)}$$

$$I_a = \frac{V_a Z_M - j a V_m (Z_f - Z_b)}{Z_M Z_A - a^2 (Z_f - Z_b)^2} \quad \text{--- (12)}$$

equations (7) & (8) can be written as:-

$$V_m = I_m Z_{im} + (I_m - j a I_a) Z_f + (I_m + j a I_a) Z_b \quad \text{--- (13)}$$

$$V_a = I_a (Z_{1a} + Z_c) + j a (I_m - j a I_a) Z_f - j a (I_m + j a I_a) Z_b \quad \text{--- (14)}$$

Now:-

$$I_f = I_m - j a I_a \quad \text{--- (15)}$$

$$I_b = I_m + j a I_a \quad \text{--- (16)}$$

$$P_{gf} = I_f^2 R_f$$


$$T_f = I_f^2 R_f \quad \text{synchronous watt}$$

$$= |I_m - jaI_a|^2 R_f$$

$$= [I_m^2 + |aI_a|^2 + 2|I_a||I_m| \cos(90^\circ - \alpha)] \cdot R_f$$

$$= [I_m^2 + |aI_a|^2 + 2|I_a||I_m| \sin \alpha] \cdot R_f \quad \text{---(17)}$$

in synchronous watt

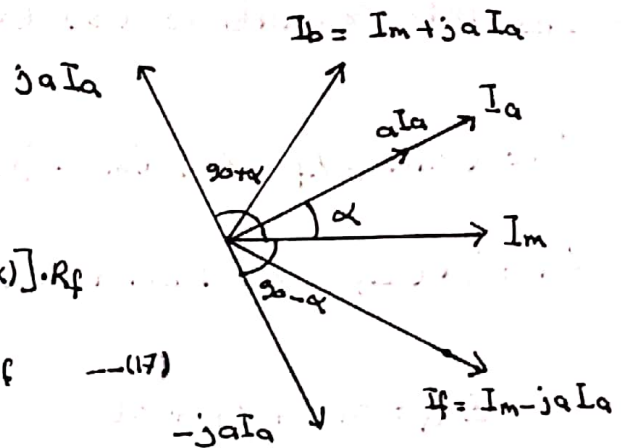

$$P_{gb} = I_b^2 R_b$$

$$T_b = I_b^2 R_b \quad \text{in synchronous watt}$$

$$= |I_m + jaI_a|^2 R_b$$

$$= [I_m^2 + |aI_a|^2 + 2|I_a||I_m| \cos(90^\circ + \alpha)] \cdot R_b$$

$$= [I_m^2 + |aI_a|^2 - 2|I_a||I_m| \sin \alpha] \cdot R_b \quad \text{syn. watt ---(18)}$$

The resultant electromagnetic torque in synchronous watt is

$$T = T_f - T_b$$

$$P_{gf} - P_{gb} = I_f^2 R_f - I_b^2 R_b$$

$$= T \quad \text{in synchronous watt}$$

$$= [I_m^2 + |aI_a|^2] (R_f - R_b) + 2|I_a||I_m| (R_f + R_b) \sin \alpha \quad \text{---(19)}$$

$$P_m = (1-s) (P_{gf} - P_{gb})$$

$$RCL = s P_{gf} + (2-s) P_{gb}$$

at starting ( $s = 1$ ):  $R_f = R_b$  hence starting torque  $T_s$  is:-

$$T_s = 2|I_a||I_m| (R_f + R_b) \sin \alpha \quad \text{syn. watt --- (20)}$$

$$T_s = \frac{2|I_a||I_m| (R_f + R_b) \sin \alpha}{\omega_s} \quad \text{N.m --- (21)}$$