

## Single phase motors

When  $I_m = -jI_a$  ( $T_b = 0$ ) and  $\alpha = 90^\circ$  the motor will operate in a balanced conditions:-


$$V_a = V_m$$

$$V_{a1} = V_a - V_c$$

$$\tan \theta_m = \frac{V_{a1}}{V_m}$$

$$I_m = I_m + I_a$$
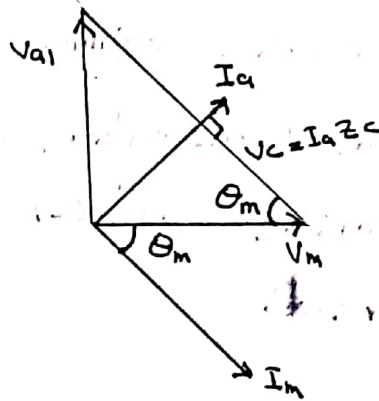
$$a = \frac{V_{a1}}{V_m}, \quad \rho \cdot a = \tan \theta_m$$



Example: Find the value of the starting capacitance for a 250W, 120V, 60 Hz induction motor that will place main and auxiliary winding currents in quadrature at starting. At standstill, motor input impedance through the main and the auxiliary windings are  $(4.5 + j3.7) \Omega$  and  $(9.5 + j3.5) \Omega$  respectively.

solution

$$\theta_m = \tan^{-1} \frac{3.7}{4.5} = 39.4^\circ$$


$$\theta_a + \theta_m = 90^\circ$$

$$\therefore \theta_a = 90^\circ - \theta_m = 90 - 39.4^\circ = 50.6^\circ$$

$$\tan \theta_a = \frac{\chi_c - 3.5}{9.5}$$

$$\begin{aligned} \Rightarrow \chi_c &= 9.5 \tan \theta_a + 3.5 \\ &= 9.5 \tan 50.6 + 3.5 \\ &= 15.07 \Omega \end{aligned}$$
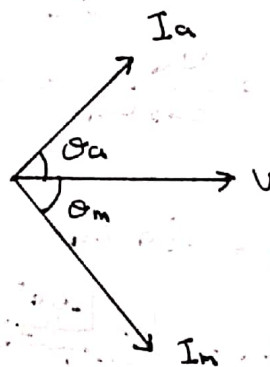
$$15.07 = \frac{1}{2\pi \times 60 C} \Rightarrow C = 176 \mu F$$




Example: A 230 V, 50 Hz, capacitor-run motor has a main winding which takes a current of 23 A at 0.5 lagging power factor when running under balanced conditions. Calculate (a) turns ratio, (b) the capacitance and capacitor voltage and (c) the power factor of the input current.

Solution

(a)

$$\theta_m = \cos^{-1} 0.5$$

$$= 60^\circ$$

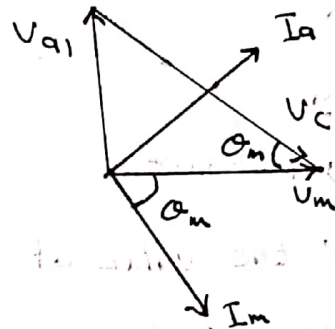

$$\tan \theta_m = \frac{V_{a1}}{V_m}, \quad a = \tan \theta_m = \tan 60 = \sqrt{3}$$

(b)

$$\cos \theta_m = \frac{V_m}{V_c}$$

$$V_c = \frac{V_m}{\cos \theta_m} = \frac{230}{\cos 60} = 460 \text{ V}$$

$$I_m = -ja I_a \Rightarrow I_a = \frac{I_m}{-ja}$$

$$\therefore I_a = \frac{23}{\sqrt{3}}$$

$$X_c = \frac{V_c}{I_a} = \frac{460}{23/\sqrt{3}} = 34.6 \, \Omega$$

$$34.6 = \frac{1}{2\pi \times 50 C} \Rightarrow C = 92 \, \mu\text{F}$$

$$(c) \quad I_m = 23 \angle -60^\circ = 11.5 - j19.92 \text{ A}$$

$$I_a = \frac{23}{\sqrt{3}} \angle 90^\circ - 60^\circ = \frac{23}{\sqrt{3}} \angle 30^\circ = 11.5 + j6.64 \text{ A}$$

$$I_{in} = I_m + I_a = 23 - j13.23 = 26.5 \angle -30^\circ \Rightarrow \text{P.f.} = \cos 30^\circ \text{ lagging}$$