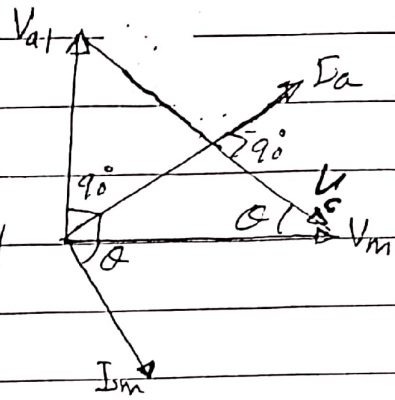


P6)

For balanced conditions,
the voltage across the auxiliary
winding V_{a1} is

$$V_{a1} = V_m - V_c = ja V_m$$



$$P = V_m I_m \cos \theta$$

$$1.25 \times 10^3 = 250 \times 12.5 \cos \theta$$

$$\cos \theta = 0.4$$

$$\theta = 66.42^\circ$$

$$\tan \theta = a = \frac{V_{a1}}{V_m}$$

$$a = \tan 66.42 = 2.29$$

$$a = \frac{N_a}{N_m} \Rightarrow N_a = a N_m = 2.29 \times 600$$

$$N_a = 1374 \text{ turns}$$

For balanced condition

$$I_b = I_m + ja I_a = 0 \text{ (only } I_f \text{ exists)}$$

$$I_m = -ja I_a$$

$$|I_m| = a |I_a|$$


$$|I_a| = \frac{|I_m|}{a} = \frac{12.5}{2.29} = 5.45 \text{ A}$$

$$\cos \theta = \frac{V_m}{V_c}$$


$$V_c = \frac{V_m}{\cos \theta} = \frac{250}{0.4} = 625 \text{ V}$$

$$VA = V_c I_a = 625 \times 5.45 = 3.40 \text{ KVA}$$

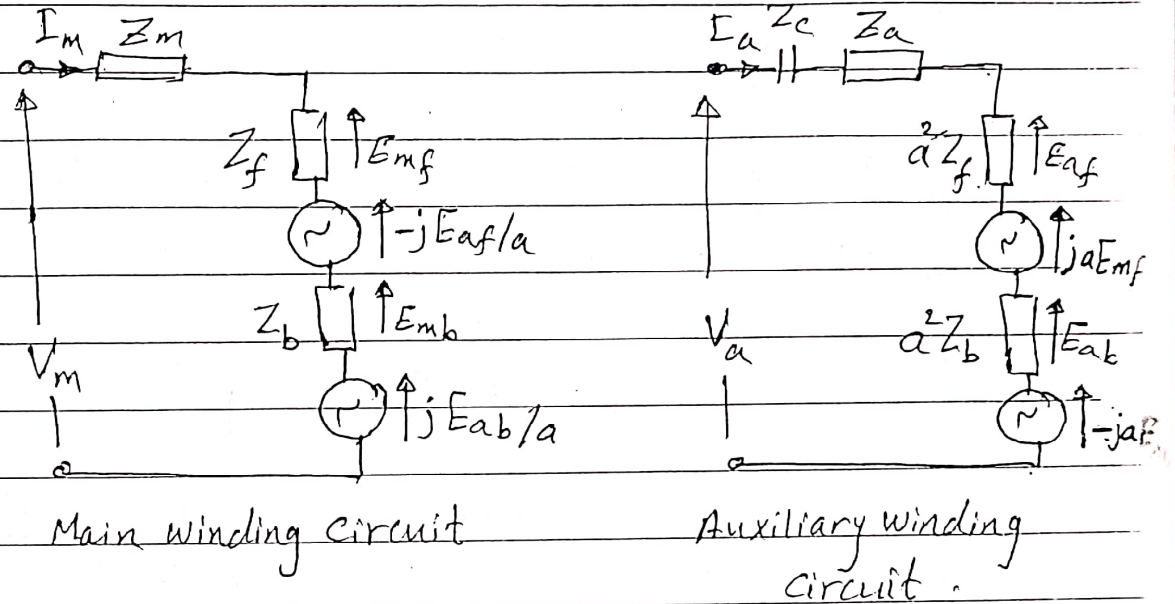Q 7) A) The equivalent circuits through main and auxiliary windings for operation with both windings, assuming the slip is "s" are shown below.



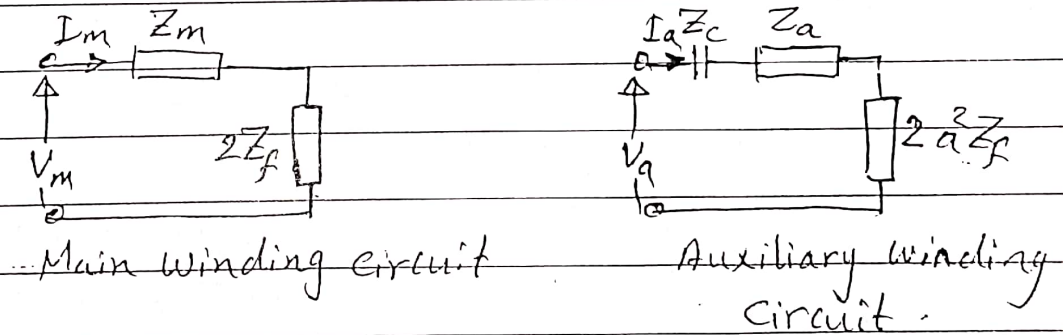for $s=1$ $Z_f = Z_b$, $E_{mf} = E_{mb}$, and $E_{af} = E_{ab}$
 The equivalent circuits are simplified.



From the above simplified circuits

$$I_m = \frac{V_m}{Z_m + 2Z_f}, \quad \text{and} \quad I_a = \frac{V_a}{Z_c + Z_a + 2a^2Z_f}$$

(12)

B) For single phase induction motor,

$$V_a = V_m = V$$

$$\frac{I_m}{I_a} = \frac{\frac{V}{Z_m + 2Z_f}}{\frac{V}{Z_c + Z_a + 2a^2 Z_f}} = \frac{Z_c + Z_a + 2a^2 Z_f}{Z_m + 2Z_f}$$

$$Z_f = Z_b = jX_{M/2} \parallel \left(\frac{R_2}{2} + jX_{L2} \right)$$

$$= j20 \parallel (2 + j2) = \frac{(2 + j2) \times j20}{2 + j2 + j20} = \frac{2.82 \angle 45^\circ \times 20 \angle 90^\circ}{22.09 \angle 84.8^\circ}$$

$$= 2.55 \angle 50.2^\circ = 1.63 + j1.95$$

For balanced condition $I_b = I_m + jaI_a = 0$

$$I_m = -jaI_a$$

$$\therefore \frac{I_m}{I_a} = -ja$$

$$\frac{I_m}{I_a} = -ja = \frac{Z_c + (3 + j3) + 2 \times 0.8^2 (1.63 + j1.95)}{(5 + j6) + 2(1.63 + j1.95)}$$

$$-j0.8 = \frac{Z_c + 5.08 + j5.49}{8.26 + j9.9}$$

$$Z_c + 5.08 + j5.49 = -j6.6 + 7.92$$

$$Z_c = -j12.09 + 2.84$$

$$X_c = \frac{1}{2\pi f C} \Rightarrow C = \frac{1}{X_c \times 2\pi f}$$

$$C = \frac{1}{12.09 \times 2\pi \times 50} = 263 \mu F$$

$$c) Z_c = (2.84 - j12.09) \Omega$$

(13)

Q8) a) $I_m = 15 \text{ A}$, $I_a = 10 \text{ A}$, $\alpha = 60^\circ$ and $a = 1.5$

$$T_f = I_f^2 R_f, T_b = I_b^2 R_b \quad (R_f = R_b \text{ at starting}).$$

$$\frac{T_f}{T_b} = \frac{[I_m^2 + a^2 I_a^2 + 2a I_a I_m \sin \alpha] R_f}{[I_m^2 + a^2 I_a^2 - 2a I_a I_m \sin \alpha] R_b}$$

$$\frac{T_f}{T_b} = \frac{15^2 + 1.5^2 \times 10^2 + 2 \times 1.5 \times 15 \times 10 \sin 60}{15^2 + 1.5^2 \times 10^2 - 2 \times 1.5 \times 15 \times 10 \sin 60}$$

$$\frac{T_f}{T_b} = \frac{839.711}{60.2885} = 13.9782$$

$$(b) \frac{T_f}{T_s} = \frac{T_f}{T_f - T_b} = \frac{[I_m^2 + a^2 I_a^2 + 2a I_m I_a \sin \alpha] R_f}{4a I_a I_m \sin \alpha R_f}$$

$$\therefore T_s = 2a I_a I_m (R_f + R_b) \sin \alpha, \text{ but } R_f = R_b \Rightarrow T_s = 4a I_a I_m R_f \sin \alpha$$

$$\frac{T_f}{T_s} = \frac{[I_m^2 + a^2 I_a^2 + 2a I_a I_m \sin \alpha] R_f}{4a I_a I_m \sin \alpha R_f} = \frac{I_f^2 R_f}{I_f^2 R_f - I_b^2 R_b}$$

$$\frac{T_f}{T_s} = \frac{839.711}{799.423} = 1.05$$