

## EXP.NO. (7)

### **A.C. Circuit with Inductance and Resistance**

**The aim of experiment:-** Measuring the inductance

#### **Theory:-**

Electricity plays an important role in medicine. There are two aspects of electricity and magnetism in medicine: electrical and magnetic effects generated inside the body.

For each value of current ( I/A) calculate the impedance in ohm:

$$Z = \frac{V}{I}$$

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + X^2}} \dots\dots\dots (2)$$

Where  $X_L$  is the inductive reactance of the coil

Since:

$$Z^2 = R^2 + X_L^2$$


A graph of  $Z^2$  against  $R^2$  will yield a straight line . The intercept (OA) gives the value of  $X_L^2$  (see diagram below)

**Thus:**

$$X_L^2 = OA = (2\pi f L)^2$$

And from this the inductance (L ) of the coil can be determined
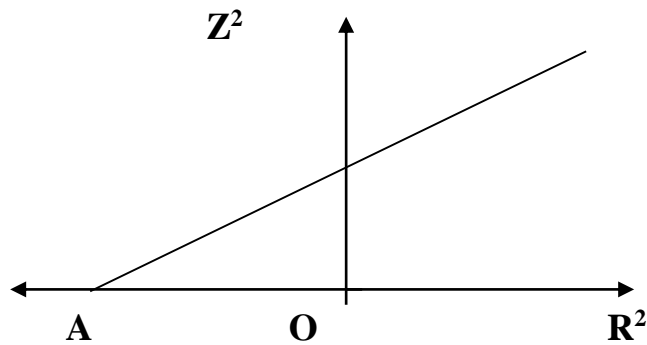
$$L = \frac{\sqrt{OA}}{2\pi f} \dots\dots\dots \text{Henry}$$




**Apparatus:-**

Low voltage A.C. source, fixed inductance, Resistance box, A.C. ammeter.

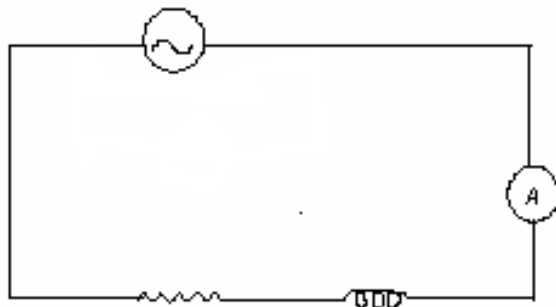**Methodology:-**

- 1-Feed the low-voltage output into the circuit connected as shown in the diagram.
- 2-Vary R and record the circuit current I as read on the A.C. ammeter at each stage.



3-Tabulate the readings:

**V= 6 Volt**

<b>R/Ω</b>	<b>I /A</b>	<b>Z=V/I</b>	<b>R<sup>2</sup></b>	<b>Z<sup>2</sup></b>
<b>0</b>				
<b>10</b>				
<b>30</b>				
<b>·</b>				
<b>·</b>				

4-plot the graph between  $Z^2$  and  $R^2$

5-Find the slope.

### **Medical application:-**

1-handheld blood analyzers, glucose monitors, and blood pressure monitors, which require switching regulators to operate at high efficiency with low –load current.

2- Capacitor series which are used in MRI application.

3- X-ray machines and laser systems, inductance combined with capacitor and resistors in high voltage circuit.

Al-mustansiriyyah