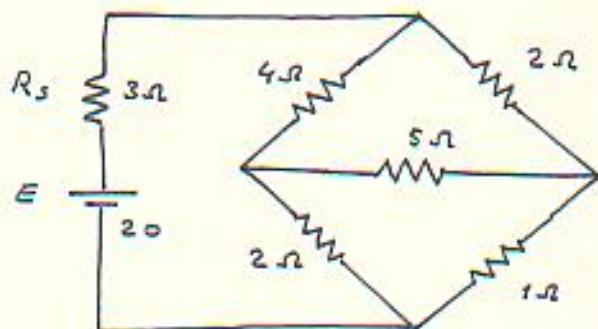


Example


For the bridge net. of the previous example, find the current in  $R_S = 3\Omega$ , using the nodal voltage method.

Solution

:



change the voltage source into a current source, then

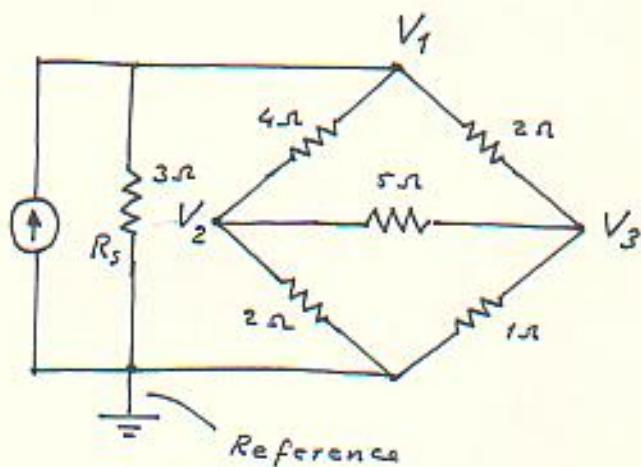For node 1:

$$\left( \frac{1}{3} + \frac{1}{4} + \frac{1}{2} \right) V_1 - \left( \frac{1}{4} \right) V_2 - \left( \frac{1}{2} \right) V_3 = \frac{20}{3}$$

For node 2:

$$\left( \frac{1}{4} + \frac{1}{2} + \frac{1}{5} \right) V_2 - \left( \frac{1}{4} \right) V_1 - \left( \frac{1}{5} \right) V_3 = 0$$

For node 3:

$$\left( \frac{1}{5} + \frac{1}{2} + \frac{1}{1} \right) V_3 - \left( \frac{1}{2} \right) V_1 - \left( \frac{1}{5} \right) V_2 = 0$$


Rearrange, and solve using determinants, then

$$V_1 = 8 \text{ V} \quad \Leftarrow \text{only } V_1 \text{ is needed to find } I_{R_S}$$

$\therefore$  No need to find  $V_2$  or  $V_3$

Practice Problem


Using the nodal voltage method, determine the current  $I$  in the circuit shown.

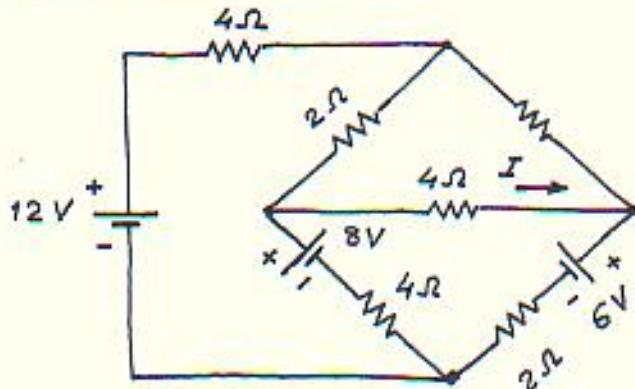Answer:

$$I = 0.25 \text{ A}$$


Practice Problem

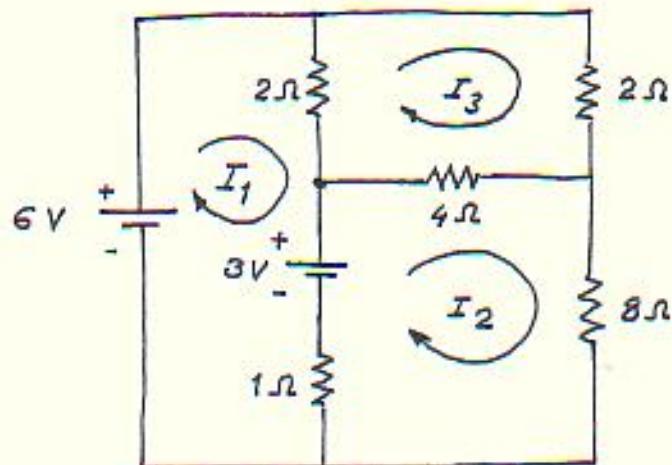: Use the loop current analysis to determine the currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit shown;



To find the current in  $R_s$ , return to the original circuit,
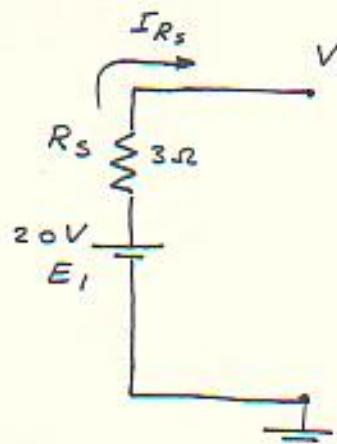
$$\begin{aligned} I_{R_s} &= \frac{E - V_1}{R_s} \\ &= \frac{20 - 8}{3} = \frac{12}{3} \\ &= 4 \text{ A}. \end{aligned}$$



Note that the same result is obtained as that in the previous example.

مهمة: حلحلة المادلة ديجياد (I\_{R\_s}) لحساب اعلاء موصول


$$I_{R_s} = \frac{E}{R_T}$$

ايقاد المادلة حسب مثمن (R\_T)  $\rightarrow$


وندبه موصول المادلة ذاتيا في المكاليم او بقين
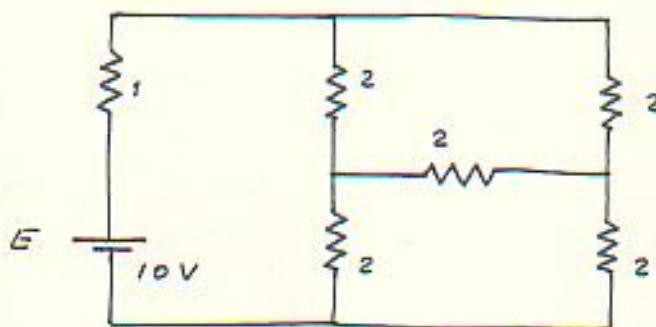
### Example

Using the loop current method find the current through the dc supply in the network shown; all resistors are in ohms.



### Solution

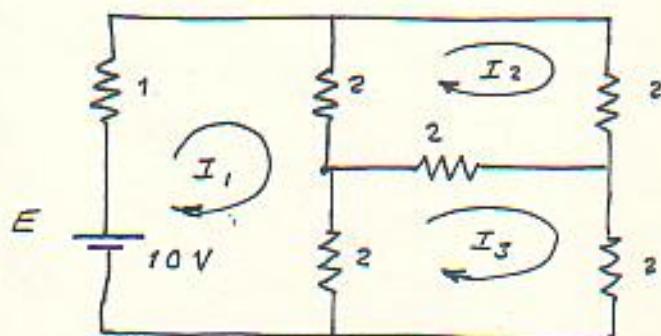

Loop 1

TSS

$$10 = (1+2+2)I_1 - (2)I_2 - (2)I_3$$

Loop 2

$$0 = (2+2+2)I_2 - (2)I_1 - (2)I_3$$

Loop 3

$$0 = (2+2+2)I_3 - (2)I_2 - (2)I_1$$

Rearrange, then we have:

$$\begin{aligned} 5I_1 - 2I_2 - 2I_3 &= 10 \\ -2I_1 + 6I_2 - 2I_3 &= 0 \\ -2I_1 - 2I_2 + 6I_3 &= 0 \end{aligned}$$


Solving using determinants, then:

$$I_1 = 3.33 \text{ A}$$

\* Solve the example using the nodal voltage method.

Example

: For the circuit shown, write the nodal equation

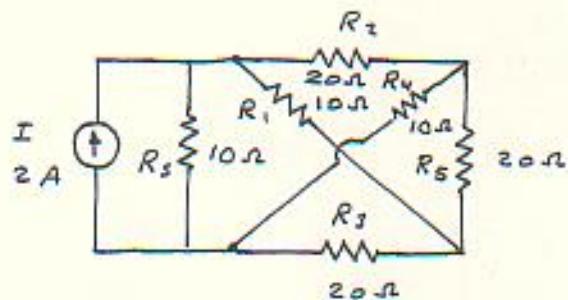Solution:

We have 3 independent nodes and a reference node as shown.

Node 1:


$$2 = V_1 \left( \frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right) - V_2 \left( \frac{1}{20} \right) - V_3 \left( \frac{1}{20} \right)$$

Node 2:

$$0 = V_2 \left( \frac{1}{20} + \frac{1}{10} + \frac{1}{20} \right) - V_1 \left( \frac{1}{20} \right) - V_3 \left( \frac{1}{20} \right)$$

Node 3:
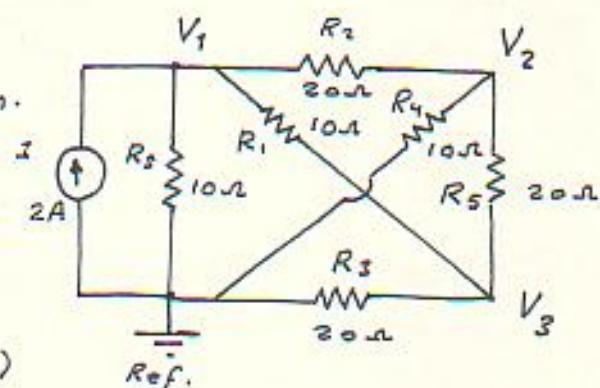
$$0 = V_3 \left( \frac{1}{10} + \frac{1}{20} + \frac{1}{20} \right) - V_2 \left( \frac{1}{20} \right) - V_1 \left( \frac{1}{20} \right)$$



Rearrange and solve.

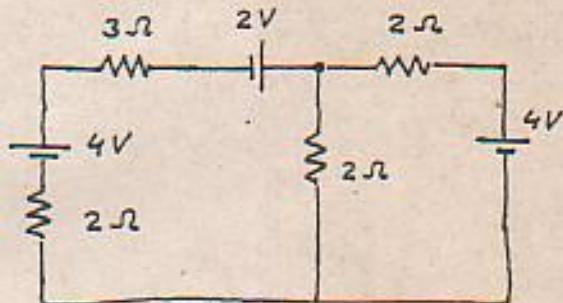
## Tutorial Sheet № 3

TS3

مذكرة: جميع أجزاء الكتاب المترافق وادلة المحلول فيه مطبوعة

Example (1)

: For the circuit shown, find the current in the  $3\Omega$  resistor using : (a) loop current method,  
(b) nodal voltage method.

Solution

(a) Using loop current method;

Loop 1


$$4 + 2 = I_1(2 + 3 + 2) - I_2(2)$$

$$\Rightarrow 7I_1 - 2I_2 = 6$$

Loop 2

$$-4 = I_2(2 + 2) - I_1(2)$$

$$\Rightarrow -2I_1 + 4I_2 = -4$$

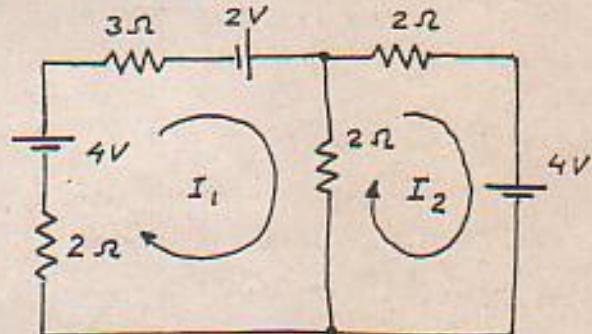


$$\therefore I_1 = \frac{\begin{vmatrix} 6 & -2 \\ -4 & 4 \end{vmatrix}}{\begin{vmatrix} 7 & -2 \\ -2 & 4 \end{vmatrix}} = \frac{(6)(4) - (-2)(-4)}{(7)(4) - (-2)(-2)} = \frac{24 - 8}{28 - 4} = \frac{16}{24}$$

$$\therefore I_1 = \frac{2}{3} \text{ A}$$

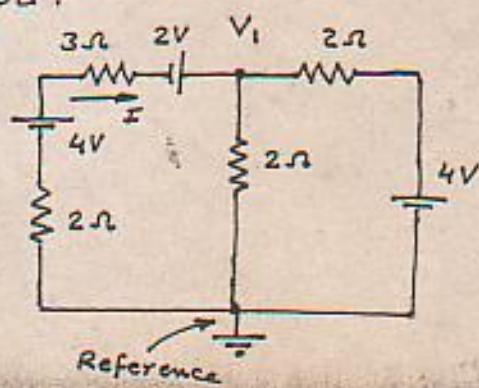(b) using nodal voltage method:

- \* There is one independent node and a reference node as shown;




\* Converting the voltage sources to current sources as shown;

\* We have only ONE independent node ( $V_1$ ),  
So we have one equation to find  $V_1$ ,

$$\therefore V_1 \left( \frac{1}{5} + \frac{1}{2} + \frac{1}{2} \right) = \frac{6}{5} + 2$$

Simplifying, we get;
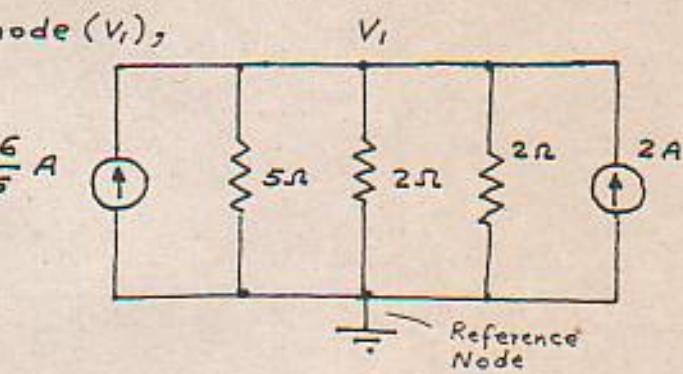
$$\Rightarrow V_1 = \frac{8}{3} \text{ V}$$



Returning to the original circuit, the current through the  $3\Omega$  resistor is :

$$I_1 = \frac{4+2-V_1}{3+2} = \frac{6 - (\frac{8}{3})}{5}$$

$$\therefore I = \frac{2}{3} \text{ A}$$

### Example

\_\_\_\_\_: Determine the current in the  $4\Omega$  resistor for the circuit shown, using loop current method. All resistor values are in Ohms.

Solution

\_\_\_\_\_  
Loop 1


$$I_1(4+1+3) - I_2(1) - I_3(3) = 24$$

Loop 2

$$I_2(1+2+12) - I_1(1) - I_3(12) = 12$$

Loop 3

$$I_3(3+12+2) - I_2(12) - I_1(3) = -10$$

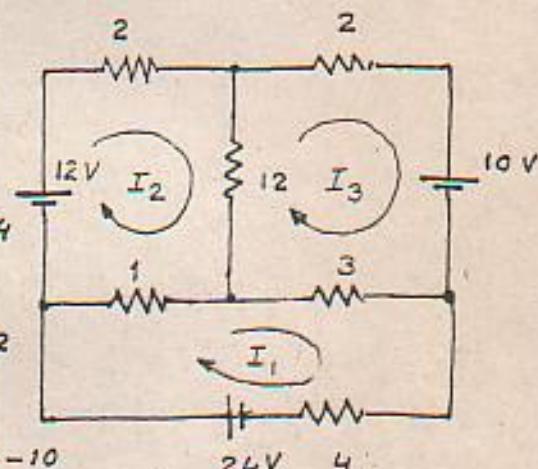

Rearrange, we get

$$8I_1 - I_2 - 3I_3 = 24$$

$$-I_1 + 15I_2 - 12I_3 = 12$$


$$-3I_1 - 12I_2 + 17I_3 = -10$$

$$I_1 = \frac{\Delta i}{\Delta} = \frac{\begin{vmatrix} 24 & -1 & -3 \\ 12 & 15 & -12 \\ -10 & -12 & 17 \end{vmatrix}}{\begin{vmatrix} 8 & -1 & -3 \\ -1 & 15 & -12 \\ -3 & -12 & 17 \end{vmatrix}} \Rightarrow I_1 = \frac{2730}{664} = 4.1 \text{ A}$$

Example

T.S.3

: Using the nodal voltage method, find the current  $I$  in the circuit shown. All resistors are in Ohms.

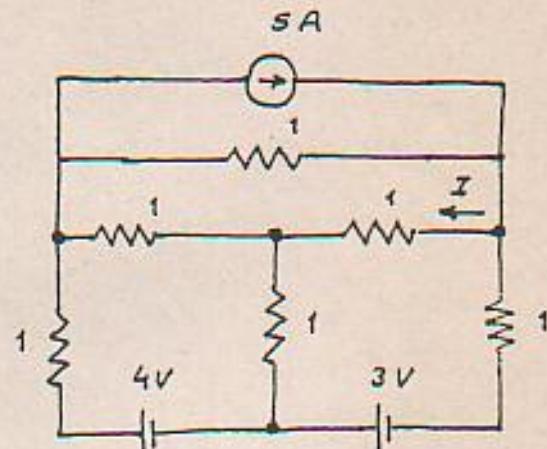Solution

\* First Convert voltage sources to current sources.

: There are three independent nodes and a reference node as shown.

For node 1

$$V_1(1+1+1) - V_2(1) - V_3(1) = 4 - 5 \\ \rightarrow 3V_1 - V_2 - V_3 = -1$$

For node 2

$$V_2(1+1+1) - V_1(1) - V_3(1) = 5 - 3 \\ \rightarrow -V_1 + 3V_2 - V_3 = 2$$


For node 3

$$V_3(1+1+1) - V_2(1) - V_1(1) = 0 \\ \rightarrow -V_1 - V_2 + 3V_3 = 0$$

$$I = \frac{V_2 - V_3}{1\Omega} = \frac{\frac{3}{4} - \frac{1}{4}}{1} = \frac{1}{2} A$$

$$\therefore I = 0.5 A$$

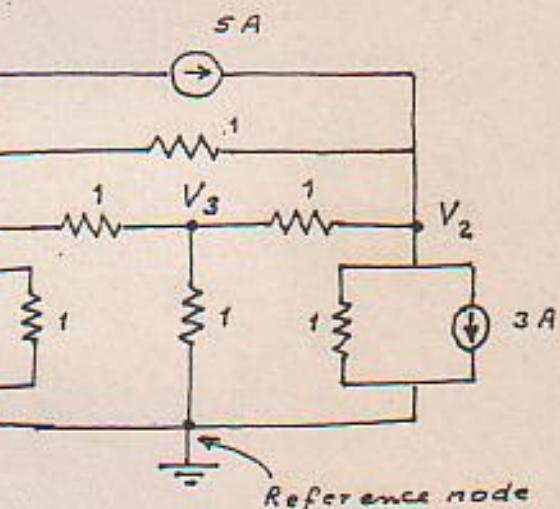طريقة الحل بال Voltages Method  
Loop current method  
درب المنهج بال Voltages



$$V_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & 0 & 3 \end{vmatrix}}{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix}} = \frac{12}{16} = \frac{3}{4} V$$


$$V_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & 2 \\ -1 & -1 & 0 \end{vmatrix}}{16} = \frac{4}{16} = \frac{1}{4} V$$

$$\therefore V_3 = \frac{1}{4} V$$

Example

TSS

For the network shown, write the nodal equations and solve for the nodal voltages.

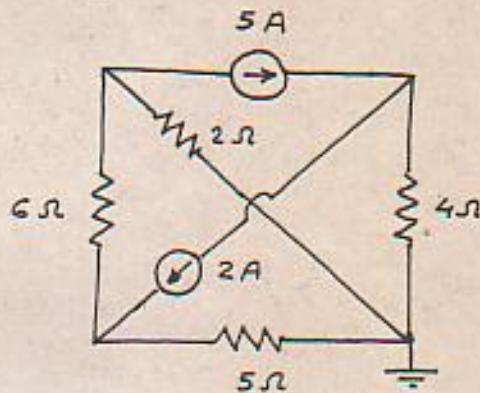Solution

There are 3 independent nodes and a reference node as shown;

- \* The independent nodes are  $V_1$ ,  $V_2$ , and  $V_3$

for node 1:


$$V_1 \left( \frac{1}{2} + \frac{1}{6} \right) - V_3 \left( \frac{1}{6} \right) = -5$$

for node 2:

$$V_2 \left( \frac{1}{4} \right) = 5 - 2 = 3$$

for node 3:
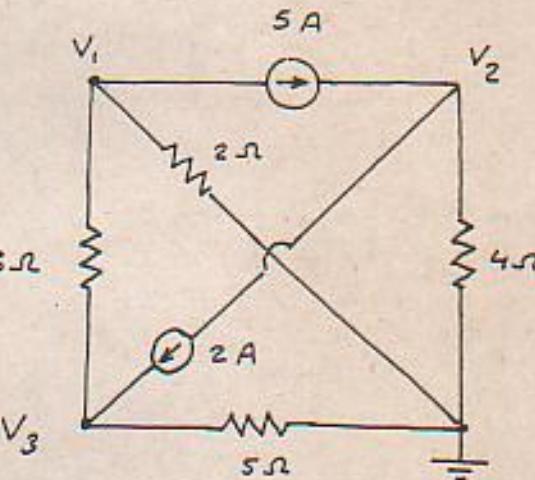
$$V_3 \left( \frac{1}{5} + \frac{1}{6} \right) - V_1 \left( \frac{1}{6} \right) = 2$$



Solving the three equations results in :

$$V_1 = -6.917 \text{ V}$$



$$V_2 = 12 \text{ V}$$

$$V_3 = 2.3 \text{ V}$$

Example

TS3

For the bridge network shown , using the loop current method find the current in  $R_5$ .

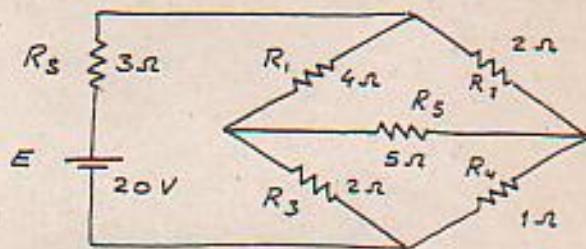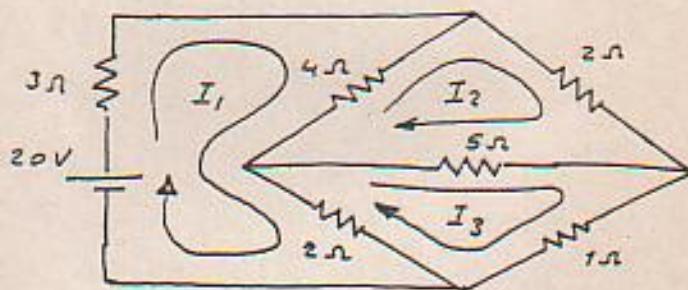SolutionLoop 1

$$I_1(3+4+2) - (4)I_2 - (2)I_3 = 20$$

Loop 2

$$I_2(4+2+5) - (4)I_1 - (5)I_3 = 0$$

Loop 3

$$I_3(2+5+1) - (2)I_1 - (5)I_2 = 0$$

Rearrange , we have :

$$\begin{aligned} 9I_1 - 4I_2 - 2I_3 &= 20 \\ -4I_1 + 11I_2 - 5I_3 &= 0 \\ -2I_1 - 5I_2 + 8I_3 &= 0 \end{aligned}$$

Solving using determinants , we have


$$I_1 = 4 \text{ A}$$

$$I_2 = 2.67 \text{ A} \quad \Rightarrow \quad \therefore I_{R_5} = I_2 - I_3$$


$$I_3 = 2.67 \text{ A} \quad \begin{aligned} &= 2.67 - 2.67 \\ &= \underline{\underline{3 \text{ A}}} \end{aligned}$$

Example

For the bridge circuit of the previous example, find the current in  $R_S = 3\Omega$ , using the nodal voltage method.

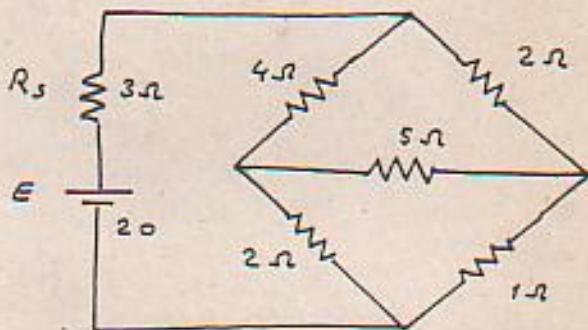Solution:

Change the voltage source into a current source, then

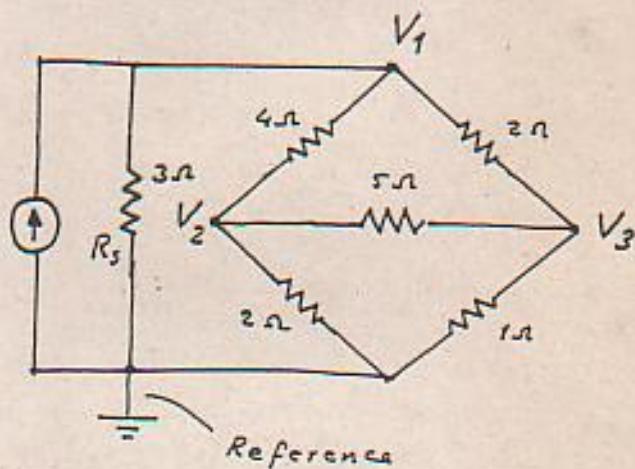For node 1

$$( \frac{1}{3} + \frac{1}{4} + \frac{1}{2} ) V_1 - ( \frac{1}{4} ) V_2 - ( \frac{1}{2} ) V_3 = \frac{20}{3}$$

For node 2

$$( \frac{1}{4} + \frac{1}{2} + \frac{1}{5} ) V_2 - ( \frac{1}{4} ) V_1 - ( \frac{1}{5} ) V_3 = 0$$

For node 3

$$( \frac{1}{5} + \frac{1}{2} + \frac{1}{1} ) V_3 - ( \frac{1}{2} ) V_1 - ( \frac{1}{5} ) V_2 = 0$$


Rearrange, and solve using determinants, then

$$V_1 = 8 \text{ V} \quad \leftarrow \text{only } V_1 \text{ is needed to find } I_{R_S}$$

$\therefore$  No need to find  $V_2$  or  $V_3$

To find the current in  $R_s$ , return to the original circuit,
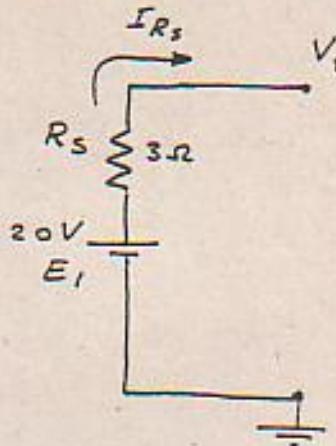
$$\begin{aligned} I_{R_s} &= \frac{E - V_1}{R_s} \\ &= \frac{20 - 8}{3} = \frac{12}{3} \\ &= 4 \text{ A} . \end{aligned}$$



Note that the same result is obtained as that in the previous example.


مقدار المقاومة المكافئ ( $R_T$ ) :

$$I_{R_s} = \frac{E}{R_T}$$


وقد يُحسب المقادير ذاتها في المقادير الباقيتين.
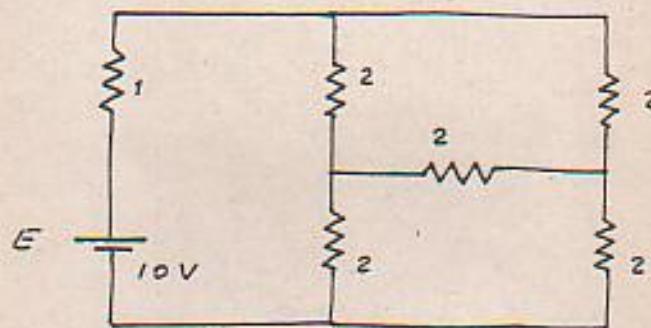
### Example

Using the loop current method find the current through the dc supply in the network shown; all resistors are in ohms.



### Solution

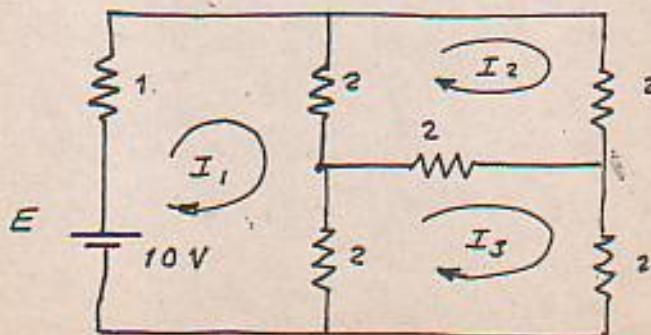

Loop 1

T53

$$10 = (1+2+2)I_1 - (2)I_2 - (2)I_3$$

Loop 2

$$0 = (2+2+2)I_2 - (2)I_1 - (2)I_3$$

Loop 3

$$0 = (2+2+2)I_3 - (2)I_2 - (2)I_1$$

Rearrange, then we have:

$$\begin{aligned} 5I_1 - 2I_2 - 2I_3 &= 10 \\ -2I_1 + 6I_2 - 2I_3 &= 0 \\ -2I_1 - 2I_2 + 6I_3 &= 0 \end{aligned}$$


Solving using determinants, then:

$$I_1 = 3.33 \text{ A}$$

\* Solve the example using the nodal voltage method.

Example

: For the circuit shown, write the nodal equation

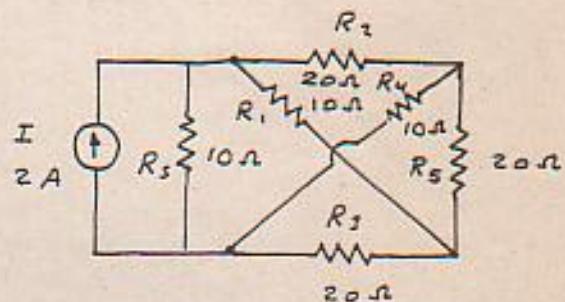Solution

We have 3 independent nodes and a reference node as shown.

Node 1


$$2 = V_1 \left( \frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right) - V_2 \left( \frac{1}{20} \right) - V_3 \left( \frac{1}{10} \right)$$

Node 2

$$0 = V_2 \left( \frac{1}{20} + \frac{1}{10} + \frac{1}{20} \right) - V_1 \left( \frac{1}{20} \right) - V_3 \left( \frac{1}{20} \right)$$

Node 3
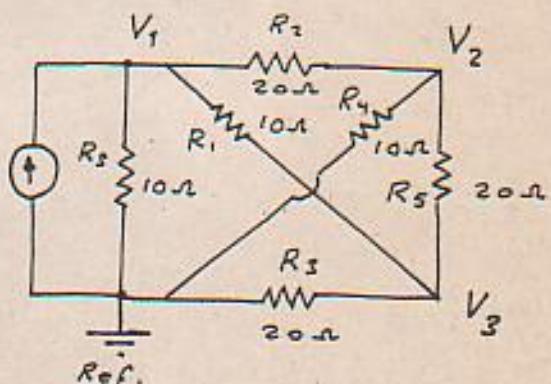
$$0 = V_3 \left( \frac{1}{10} + \frac{1}{20} + \frac{1}{20} \right) - V_2 \left( \frac{1}{20} \right) - V_1 \left( \frac{1}{10} \right)$$



Rearrange and solve.

## 4. Circuit Theorems

EE4


### 3.1 Superposition Theorem

Definition : The theorem states that, "the current through (or the voltage across) an element in a linear bilateral network is equal to the algebraic sum of the currents (or voltages) produced independently by each source.

- \* To apply this theorem to find the current (or voltage) in a certain part of a network, remove the sources of the network and find the current (or voltage) in the existence of only one source each time. The resultant current (or voltage) will be the algebraic sum of currents (or voltages) due to all sources when acting independently once at a time.
- \* Removing the sources means: SHORT CIRCUITING the voltage source and OPEN CIRCUITING the current source.

#### Example

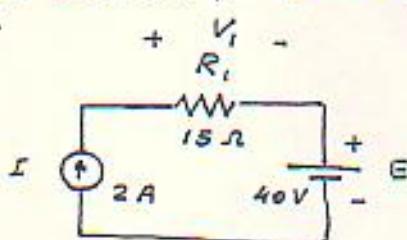
Problem : Using the superposition theorem, determine  $V_i$  for the network shown.


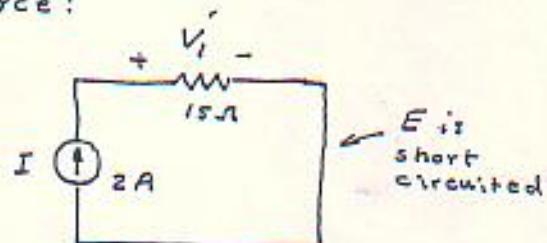
#### Solution


\* Due to the current source:

$$\begin{aligned} V'_i &= IR_i \\ &= (2)(15) \\ &= 30 \text{ V} \end{aligned}$$



\* Due to the voltage source:
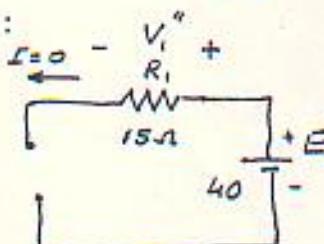
$$\begin{aligned} V''_i &= I_i R_i \\ &= (0)(15) \\ &= 0 \text{ V} \end{aligned}$$




$$\begin{aligned} \therefore V_i &= V'_i + V''_i \\ &= 30 - 0 = 30 \text{ V} \end{aligned}$$

Example

EE4

: Using the superposition theorem, determine the current through the  $4\Omega$  resistor for the network shown.

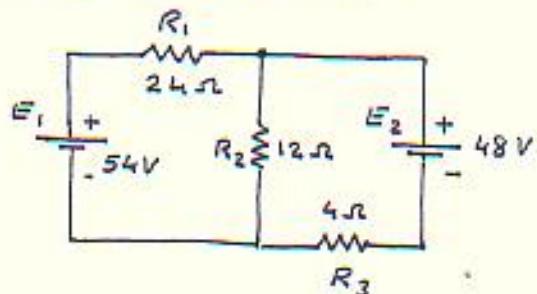
Solution

: Consider the effect of  $E_1$ ,

$$I = \frac{E_1}{R_T} = \frac{-54}{27} = 2A$$

Using the current division rule  $\therefore$
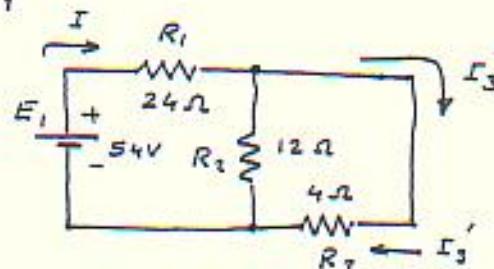
$$\begin{aligned} \therefore I'_3 &= I \frac{R_2}{R_2 + R_3} \\ &= 2 \frac{12}{12 + 4} = \underline{1.5 A} \end{aligned}$$




$$\begin{aligned} R_T &= (R_2 // R_3) + R_1 \\ &= (12 // 4) + 24 = 3 + 24 \\ &= 27 \Omega \end{aligned}$$

\* Consider the effect of  $E_2$ :

$$I = I''_3 = \frac{E_2}{R_T}$$

$$\begin{aligned} R_T &= (24 // 12) + 4 \\ &= 8 + 4 \\ &= 12 \Omega \end{aligned}$$

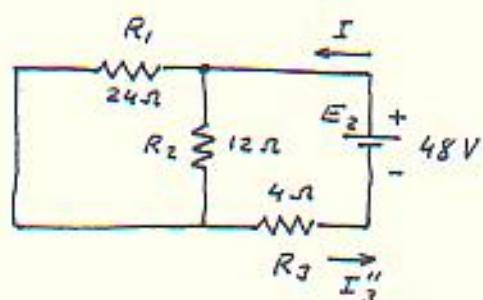
$$\therefore I''_3 = \frac{48}{12} = \underline{4 A}$$



$$\begin{aligned} \therefore I_3 &= I''_3 - I'_3 \\ &= 4 - 1.5 = \underline{2.5 A} \quad (\text{in the direction of } I''_3). \end{aligned}$$

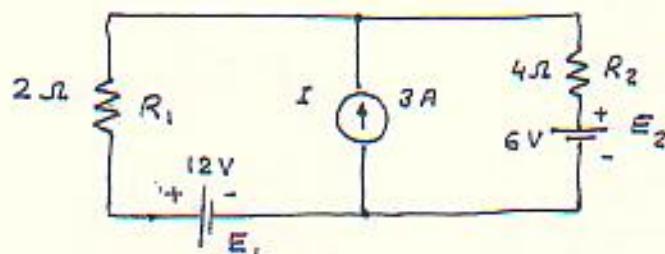Example

: Using the superposition theorem, find the current through the  $2\Omega$  resistor of the network shown.



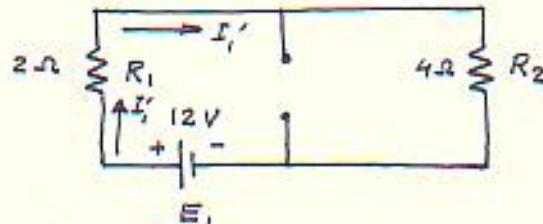
Solution

EE4

\* The effect of  $E_1$ 

Remove the voltage source  $E_2$  (short circuited) and the current source  $I$  (open circuited); the network will be as shown:

$$\therefore I'_1 = \frac{E_1}{R_T} = \frac{12}{2+4} = 6A$$

\* The effect of  $E_2$ 


: removing  $E_1$  &  $I$ , the network will be as shown:

$$\therefore I''_1 = \frac{E_2}{R_T} = \frac{6}{2+4} = 1A$$


\* The effect of  $I$ 

: removing  $E_1$  and  $E_2$ , the network will be as shown:
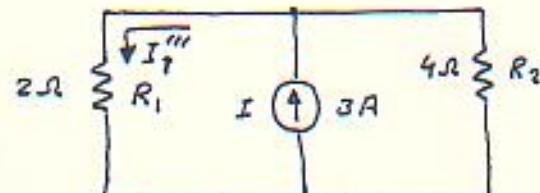
$$\therefore I'''_1 = I \cdot \frac{R_2}{R_1 + R_2} = (3) \frac{4}{4+2} = 2A$$



$$\therefore I_1 = \underbrace{I''_1}_{\substack{\text{same} \\ \text{direction}}} + \underbrace{I'''_1}_{\substack{\text{opposite} \\ \text{direction}}} - I'_1 \Rightarrow I_1 = 1 + 2 - 1 = 1A$$

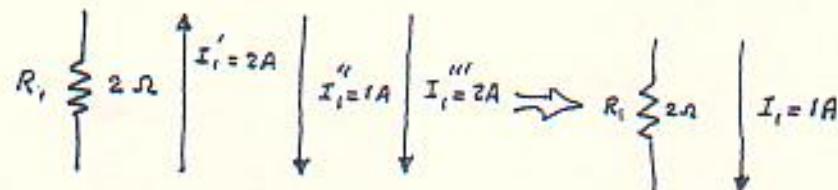
Resulting current in  $R_2$

### 3.2 Thevenin's Theorem

EE4

Thevenin's theorem states that "Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a voltage source and a series resistor."

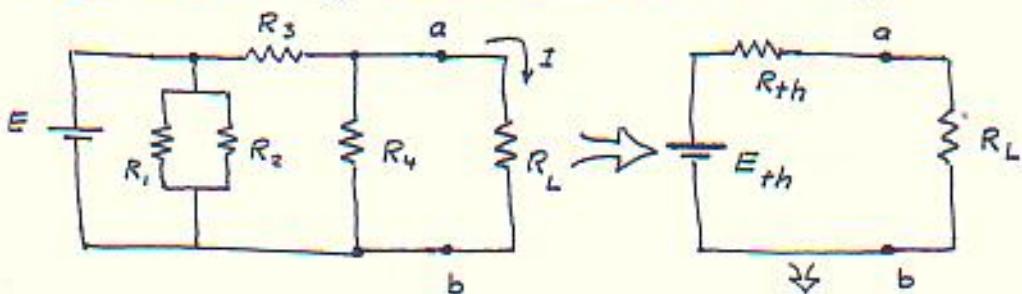Consider the network shown, it can be replaced by the voltage source  $E_{th}$  and the series resistor  $R_{th}$ :



\* To find  $I$  through the resistance  $R_L$

$$\Rightarrow I = \frac{E_{th}}{R_{th} + R_L}$$

\* Steps to find  $E_{th}$  and  $R_{th}$ :

#### STEP 1

: Remove that portion of the network across which the Thevenin's equivalent circuit is to be found.

#### STEP 2

: Mark the terminals of the remaining two-terminal network.

#### STEP 3 ( $R_{th}$ )

: Calculate  $R_{th}$  by first setting all sources to zero (voltage sources are replaced by short circuits and current sources are replaced by open circuits), and finding the resultant resistance between the two marked terminals.

#### STEP 4 ( $E_{th}$ )

: Calculate  $E_{th}$  by first returning all sources to their original positions and finding the open circuit voltage between the marked terminals.


#### STEPS

: Draw the Thevenin's equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.


Example

EE4

: Using Thevenins theorem, find the current in the  $R_L = 10\ \Omega$  of the network shown.

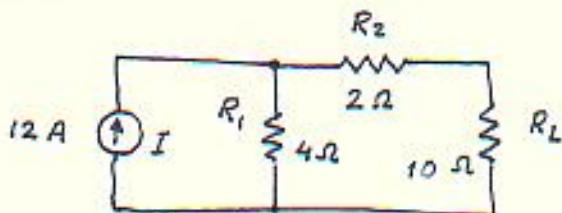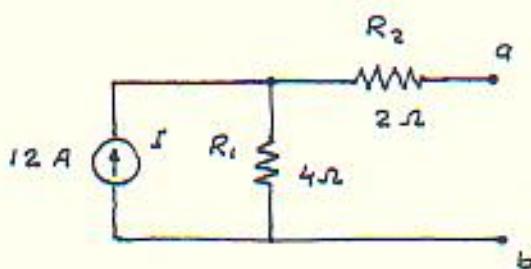
Solution

steps 1 and 2 :

step 3

:  $R_{th} = ?$

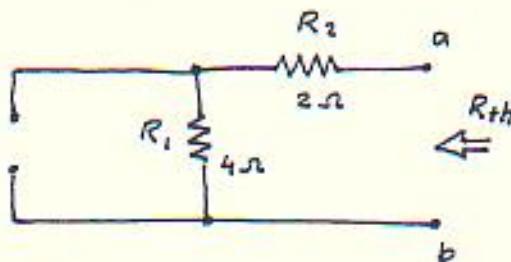Remove the current source I, then calculate  $R_{th}$  between the terminals a and b;



$$\therefore R_{th} = R_1 + R_2 = 4 + 2 = 6\ \Omega$$

step 4

:  $E_{th} = ?$

Return the current source to its original position then determine  $E_{th}$  across the open circuit terminals a and b.

$I_2 = 0$   
 $\Rightarrow I_2 R_2 = 0$

Then


$$E_{th} = I_1 R_1 - I_2 R_2$$

$$= I_1 R_1 = 12(4)$$

$$= 48\ V$$


step 5

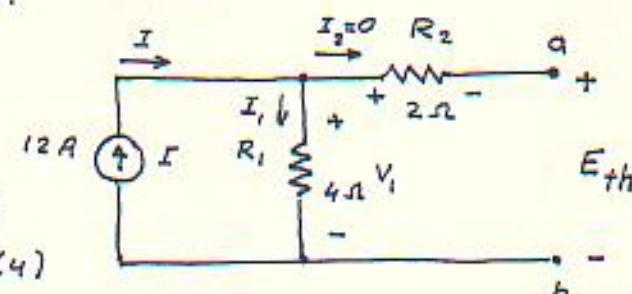: Draw the Thevenin equivalent circuit representing the network between points a and b with  $R_L$  added.



$$\therefore I = \frac{E_{th}}{R_{th} + R_L}$$


$$= \frac{48}{6 + 10} = 3 A$$

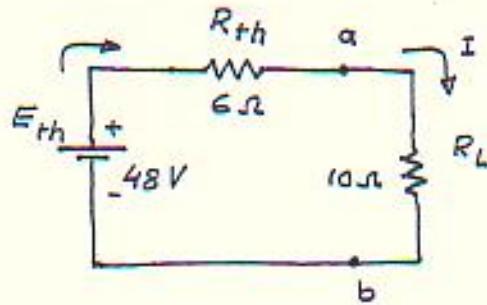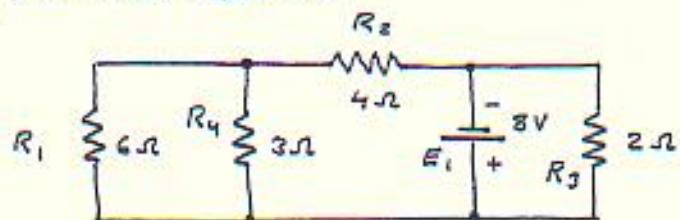


EE4

Example

For the circuit shown, find the current in the 3-Ω resistor using Thévenin's theorem.


Solution

Step 1 and 2:

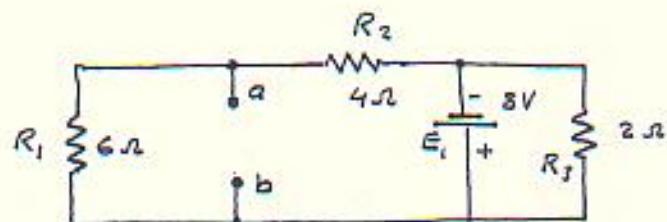

Step 3  $R_{th} = ?$

:

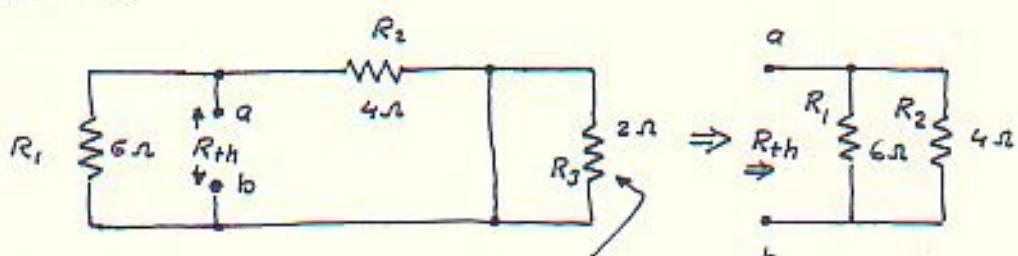


$$\therefore R_{th} = \frac{6(4)}{6+4} = 2.4 \Omega \quad R_3 \text{ short circuited}$$

$$R_{th} = 6//4 = 2.4 \Omega$$

Step 4


:  $E_{th} = ?$

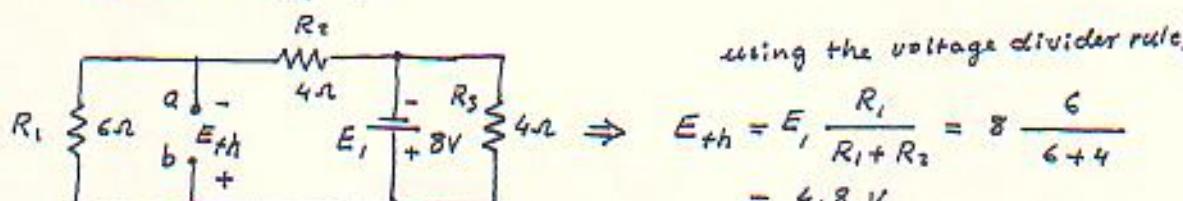

using the voltage divider rule,

$$E_{th} = E_i \cdot \frac{R_1}{R_1 + R_2} = 8 \cdot \frac{6}{6+4} = 4.8 V$$


Step 5

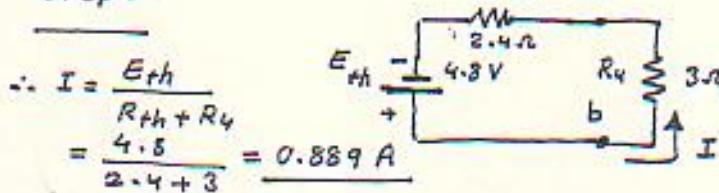
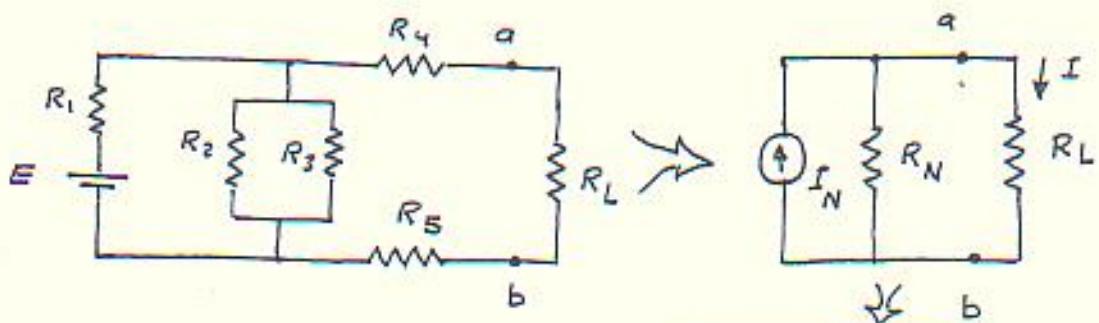
### 3.3. Norton's Theorem

: Norton's theorem states that " Any two terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor."

Consider the network shown , it can be replaced by the current source  $I_N$  and the parallel resistor  $R_N$  ;



To find the current through  $R_L \Rightarrow$

$$I = \frac{I_N R_N}{R_N + R_L}$$

#### How to find $I_N$ and $R_N$

##### STEP 1

: Remove that portion of the network across which the Norton equivalent circuit is found .

##### STEP 2

: Mark the terminals of the remaining two-terminal network .

##### STEP 3 ( $R_N$ )

: Calculate  $R_N$  by first removing all the sources ( voltage sources replaced by short circuits and current sources replaced by open circuits ) and then finding the resultant resistance between the two marked terminals .

##### STEP 4 ( $I_N$ )


: Calculate  $I_N$  by first returning all sources to their original position and then finding the short circuit current between the marked terminals .

##### STEP 5

: Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit .


Relation between Norton equivalent circuit and Thevenin's equivalent circuit

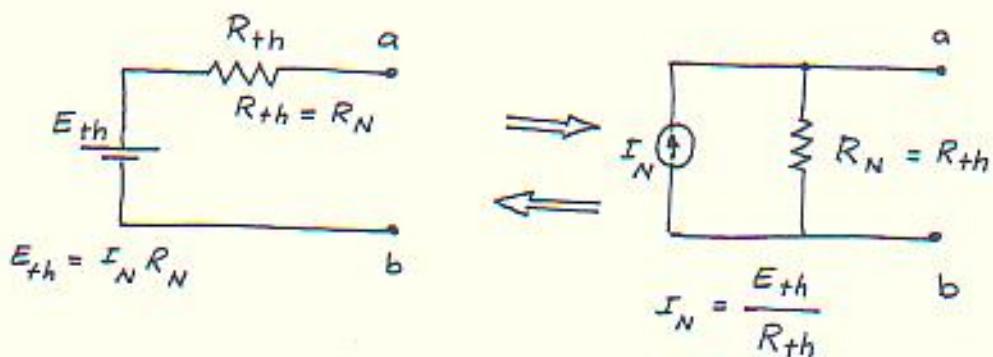: The Norton and Thevenin equivalent circuits can also be found from each other by using the source transformation previously discussed, as shown;



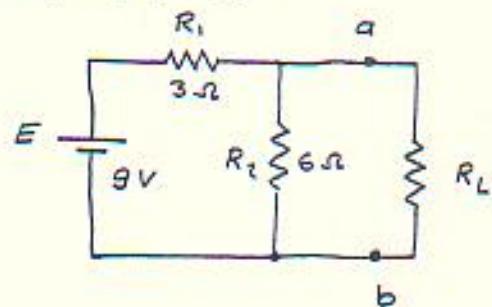
### Example

: For the circuit shown, find the Norton equivalent circuit for the network to the left of (a-b).




### Solution

: steps 1 and 2

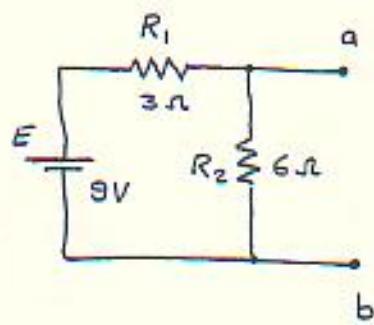

Step 3       $R_N = ?$


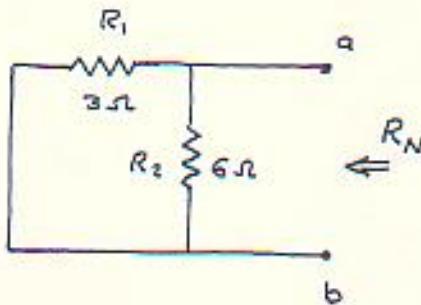
$$\begin{aligned} R_N &= R_1 // R_2 \\ &= \frac{3(6)}{3+6} \\ &= 2\Omega \end{aligned}$$



STEP 4

$$I_N = ?$$


$$I_N = I = \frac{E}{R_1} = \frac{9}{3} = 3 \text{ A}$$

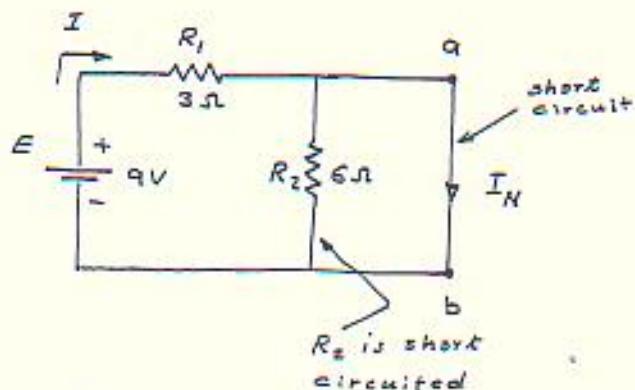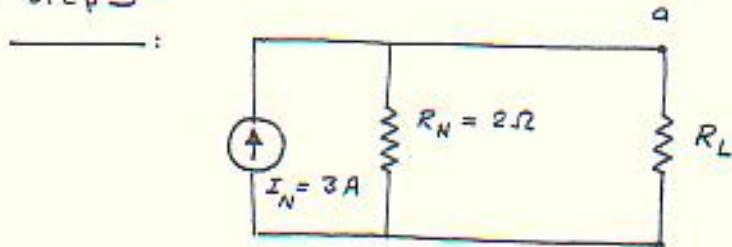Step 5


which is the Norton equivalent circuit of the network.


Note

Thevenin's theorem can be determined by Norton's theorem as shown :



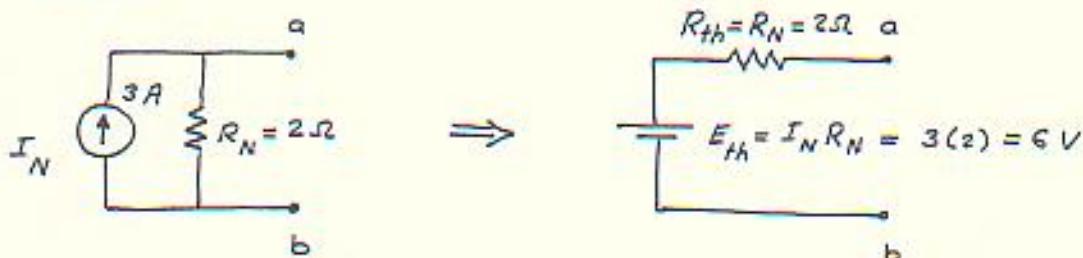
Example

Using Norton theorem find the current through the load resistor  $R_L$  in the network shown .

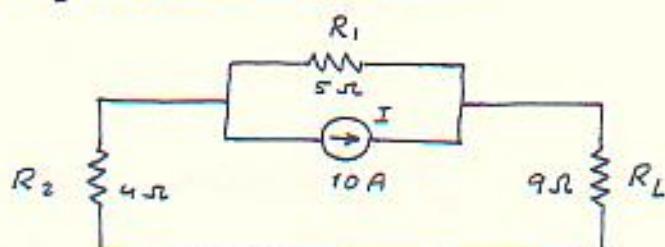

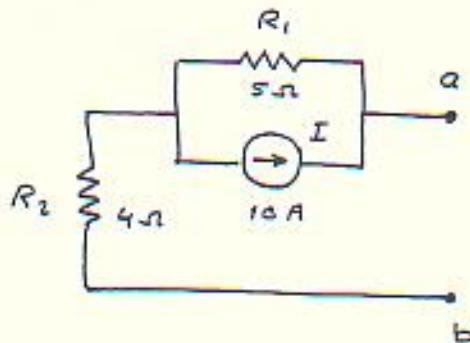SolutionStep 1 : Step 1 and 2Step 3 :  $R_N = ?$ 

$$\begin{aligned} R_N &= R_1 + R_2 \\ &= 5 + 4 \\ &= 9 \Omega \end{aligned}$$

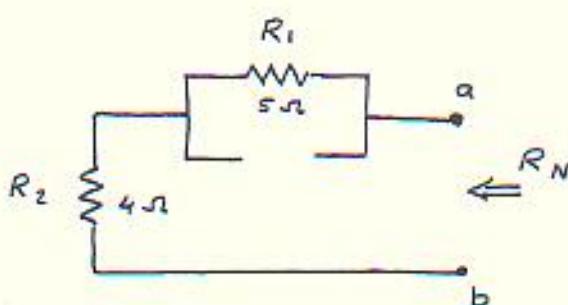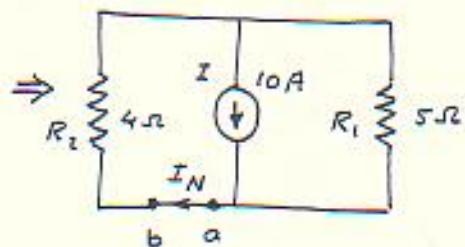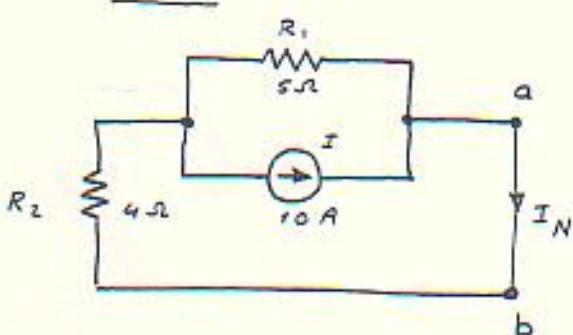Step 4 :  $I_N = ?$ 

$$\therefore I_N = I \cdot \frac{R_1}{R_1 + R_2}$$

$$= 10 \cdot \frac{5}{5+4}$$

$$= 5.556 \text{ A}$$


+ Step 5

$$\therefore I = \frac{I_N}{2} = 2.778 \text{ A}$$
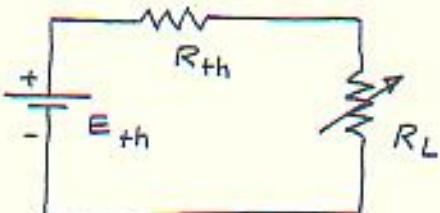
### 3.4 Maximum Power Transfer Theorem

: The maximum power transfer theorem states the following:

- \* A load will receive maximum power from a linear bilateral dc network when its total resistive value is exactly equal to the Thevenin resistance of the network as seen by the load."




For maximum power transfer  $\Rightarrow$

$$R_{th} = R_L$$

$$I = \frac{E_{th}}{R_{th} + R_L}$$
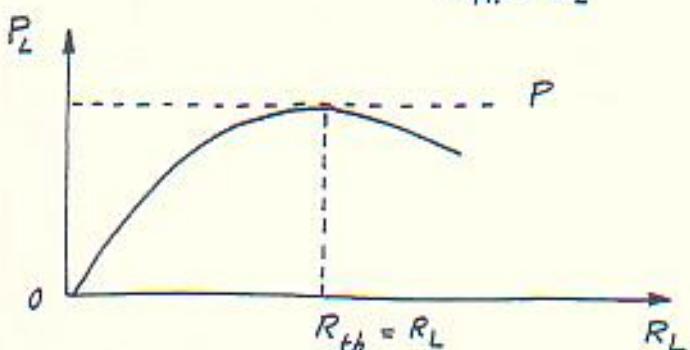
$$P_L = I^2 R_L = \left( \frac{E_{th}}{R_{th} + R_L} \right)^2 R_L$$



$\therefore P_{max} \Rightarrow \text{at } R_{th} = R_L$


$$P_{max} = \left( \frac{E_{th}}{2 R_{th}} \right)^2 R_{th} = \frac{E_{th}^2}{4 R_{th}}$$

$$\therefore P_{max} = \frac{E_{th}^2}{4 R_{th}}$$

\* When dealing with Norton equivalent circuit, maximum power transfer takes place when:

$$R_N = R_L$$

That is;

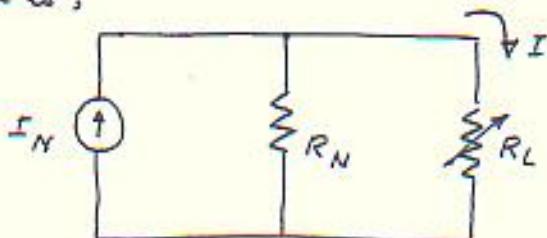

Max. power transfer at

$$R_N = R_L$$

$$P_L = I^2 R_L$$

$$= (I_N \cdot \frac{R_N}{R_N + R_L}) \cdot R_L$$

$$\therefore P_{L_{\max}} = \left( I_N \cdot \frac{R_N}{2R_N} \right)^2 R_N$$


$$= \frac{I_N^2 R_N}{4}$$

$$P_{L_{\max}} = \frac{I_N^2 R_N}{4}$$



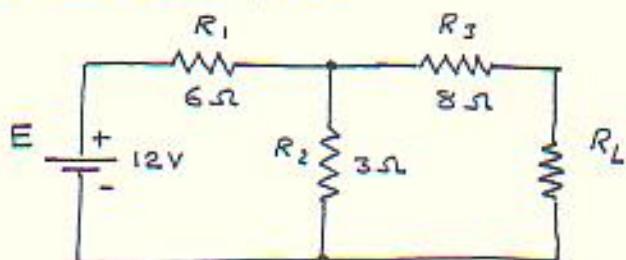
### Example

For the network shown, determine the value of  $R_L$  for maximum power transfer, and calculate the power delivered under these conditions.



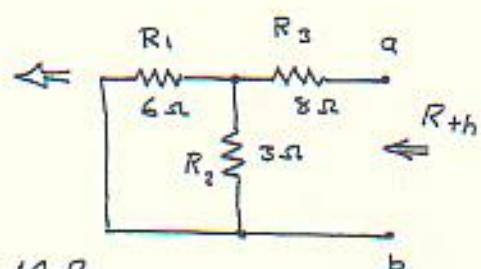
### Solution

$$\begin{aligned} * R_{th} &= (R_1 // R_2) + R_3 \\ &= \frac{6 \times 3}{6 + 3} + 8 \\ &= 10 \Omega \end{aligned}$$



$\therefore$  For max. power the value of  $R_L = R_{th} = 10 \Omega$

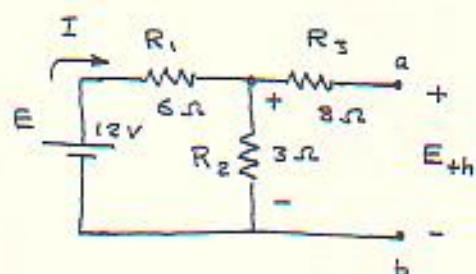
$$\begin{aligned} * E_{th} &= \frac{E \cdot R_2}{R_1 + R_2} \\ &= \frac{12 \times 3}{6 + 3} = 4V \end{aligned}$$




$$\therefore P_{L_{\max}} = \frac{E_{th}^2}{4R_{th}} = \frac{(4)^2}{4(10)} = 0.4W$$

Example

: Find the value of  $R_L$  in the network shown, for maximum power to  $R_L$  and determine the maximum power.

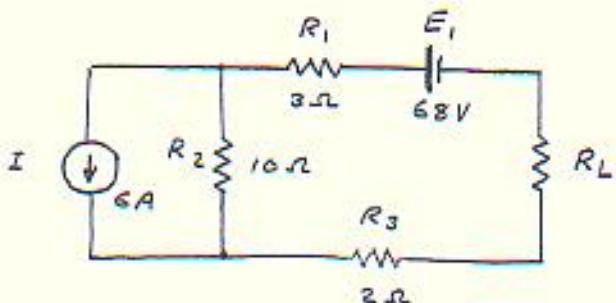Solution

:  $R_{th}$

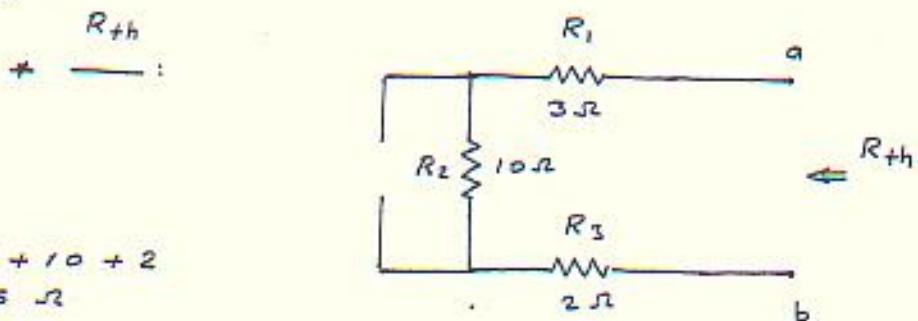


$$R_{th} = 3 + 10 + 2 \\ = 15 \Omega$$

$\therefore$  For max power transfer

$$R_L = R_{th} = 15 \Omega$$


:  $E_{th}$

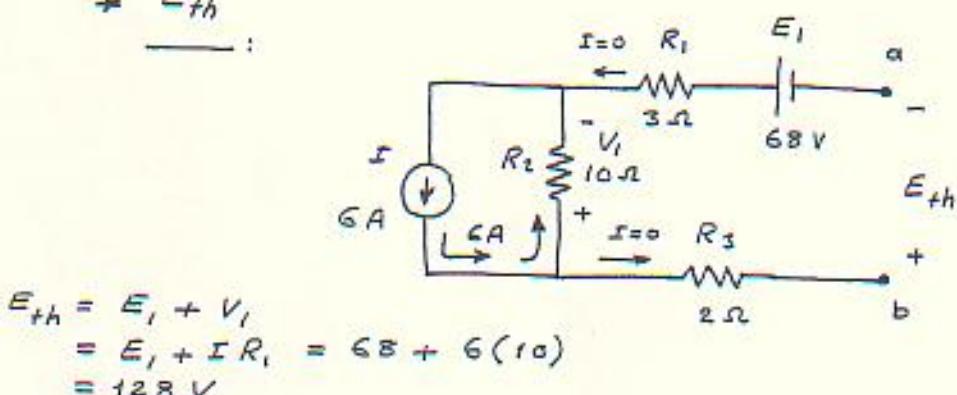

$$E_{th} = E_1 + V_1 \\ = E_1 + I R_1 = 68 + 6(10) \\ = 128 V$$

$$\therefore P_{L\max} = \frac{E_{th}^2}{4R_{th}} = \frac{(128)^2}{4(15)} = 273.07 W$$

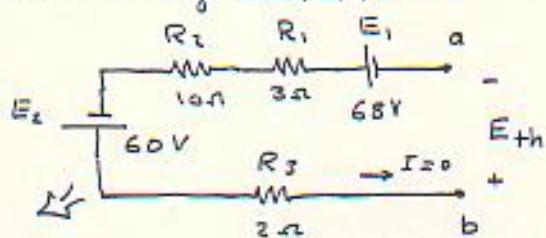The current source can be converted into a voltage source:



$$R_{th} = R_1 + R_2 + R_3 \\ = 3 + 10 + 2 \\ = 15 \Omega$$

$$R_L = R_{th} = 15 \Omega \text{ for max. power}$$

$$E_{th} = 68 + 60 = 128 V$$


### 3.5 Reciprocity Theorem

The reciprocity theorem is applicable only to a single-source networks. The theorem states that:

"The current  $I$  in any branch of a network due to a single voltage source  $E$  anywhere else in the network, will equal the current through the branch in which the source was originally located if the source is placed in the branch in which the current  $I$  was originally measured."

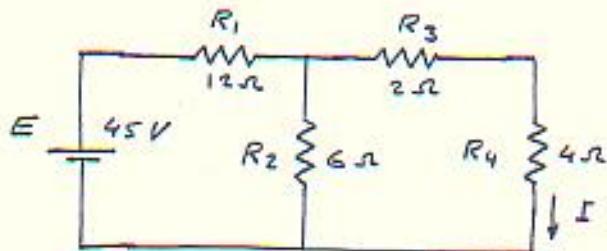
#### Example

For the network shown, determine the current  $I$ . Is the reciprocity theorem satisfied?



#### Solution

:

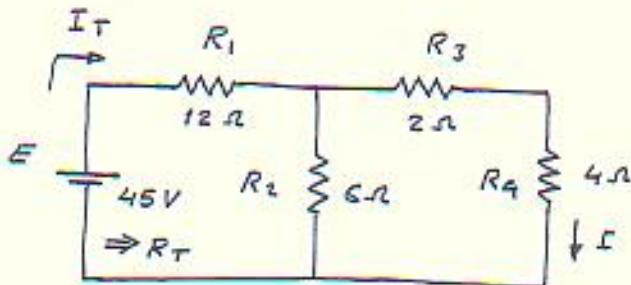

$$I_T = \frac{E}{R_T}$$

$$= \frac{45}{15} = 3 \text{ A}$$


$$\therefore I = \frac{3}{2} = 1.5 \text{ A}$$

$$R_T = [(R_3 + R_4) // R_2] + R_1$$

$$= \frac{2+4}{6} + 12 = 15 \Omega$$

$$= 3 + 12 = 15 \Omega$$

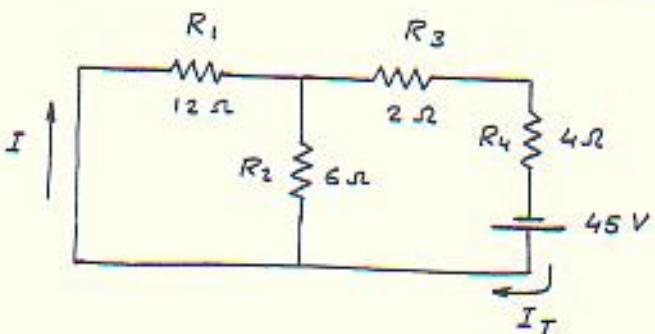To check the reciprocity, place  $E$  in the branch of the current  $I$ , and calculate the current in the branch where  $E$  was originally exist.



$$I_T = \frac{E}{R_T}$$

$$= \frac{45}{10}$$

$$\therefore I_T = 4.5 \text{ A}$$

$$R_T = (R_1 // R_2) + R_3 + R_4$$

$$= \frac{12(6)}{12+6} + 2 + 4 = 4 + 2 + 4$$

$$\therefore R_T = 10 \text{ ohms}$$

Finding  $I$  ?

$$I = I_T \frac{R_2}{R_1 + R_2} = 4.5 \frac{6}{12 + 6}$$

$$\therefore I = 1.5 \text{ A}$$


Since  $I = 1.5 \text{ A}$

$\therefore$  The reciprocity theorem is satisfied.

**مدونة : جميع انشطة المكتبات ليرجعى راسملته ملحوظة .**
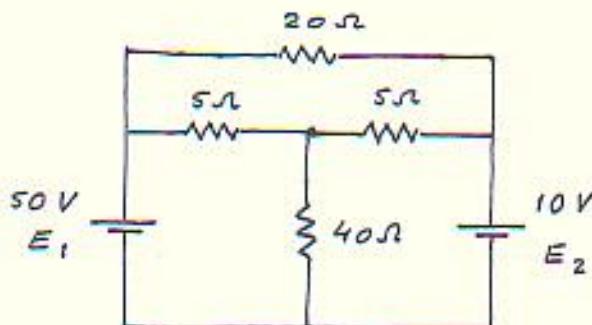
### Example


Use the superposition theorem, find the current in the  $40\ \Omega$  resistor of the circuit shown.




### Solution

2

### # The effect of $E$ ,

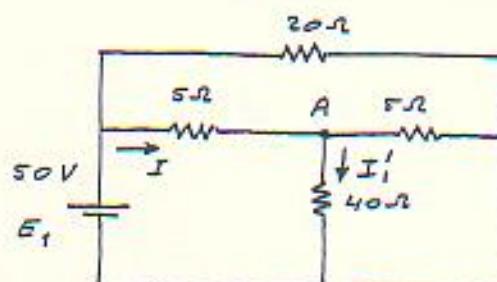

5/1140

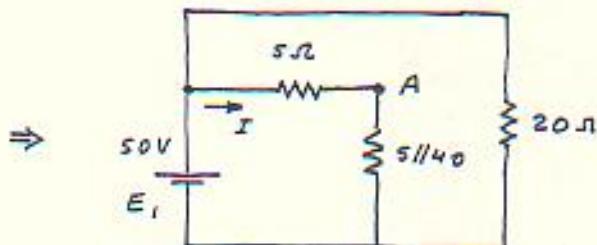

$$51140 = 4,44 \pi$$

$$\therefore I = \frac{50}{5 + 4.44} = 5.296 \text{ A}$$


$$\therefore I_1' = I \frac{s}{s+40} = 5.296 \frac{s}{45} = 0.589 A$$

### \* The effect of $E_2$

$$I = \frac{10}{(51140) + 5} = 1.059 \text{ A}$$

$$I''_1 = I \frac{5}{40+5} = 1.059 \frac{5}{45}$$

$$= 0.118 A$$

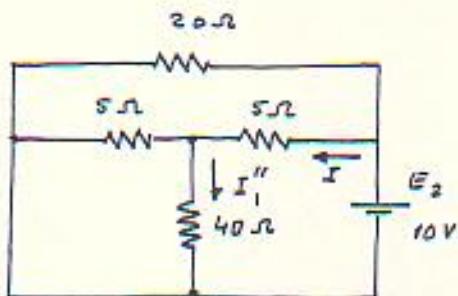


$$\therefore I_1 = I'_1 + I''_1 = 0.589 + 0.118 = 0.707 \text{ A}$$


Example

TS4

For the circuits shown, calculate the current through the  $9\ \Omega$  resistor using the superposition theorem.

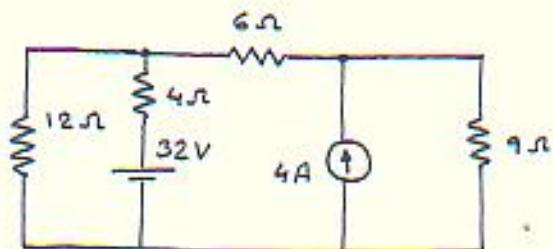Solution

\* The effect of the voltage source

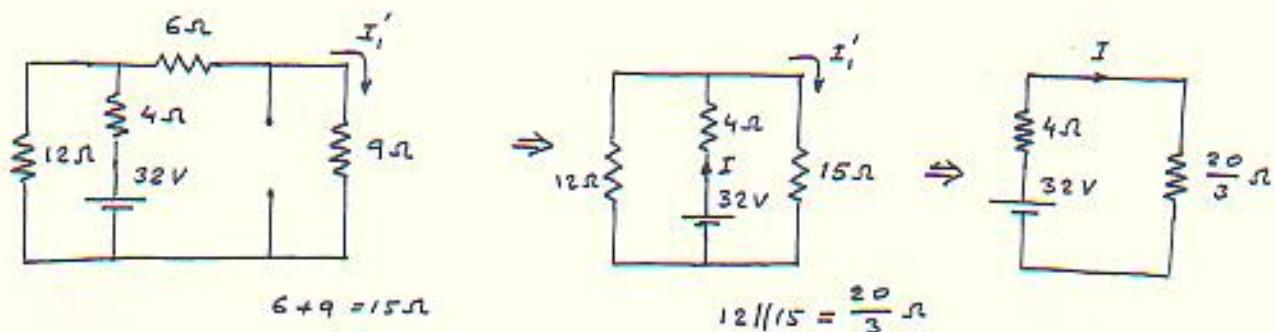


$$R_T = 4 + \frac{20}{3} = \frac{32}{3}\ \Omega$$

$$\therefore I = \frac{E}{R_T} = \frac{32}{(32/3)} = 3\ A$$

$$\therefore I'_1 = I \cdot \frac{12}{12+15} = \frac{4}{3}\ A$$

\* The effect of the current source

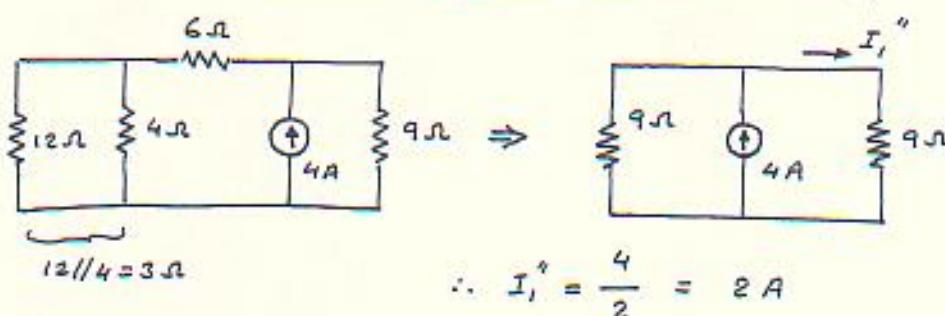


$$\therefore I_1 = I'_1 + I''_1 = \frac{4}{3} + 2 = \frac{10}{3}\ A$$

**Example**

TS4

Using the superposition theorem, find the value of the output voltage  $V_o$  in the circuit shown.

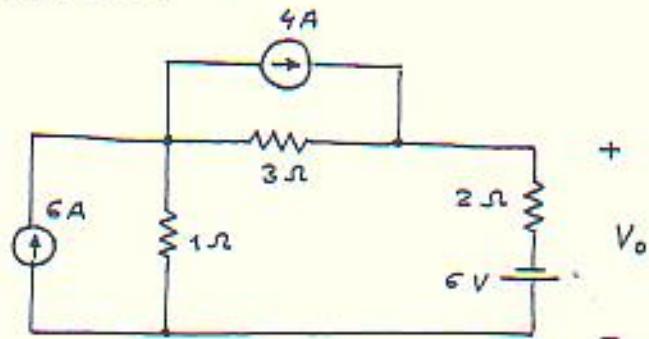
**Solution**

# Effect 6A source

Using the current divider rule:

$$I_1' = 6 \cdot \frac{1}{(1+2+3)} \\ = 1 \text{ A}$$
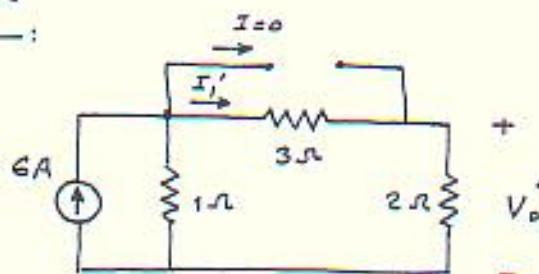
$$\therefore V_o' = I_1'(2) = 2 \text{ V}$$




# Effect of 4A source

current  
divider  
rule

$$\therefore I_1'' = 4 \cdot \frac{3}{(1+2)+3} \\ = 2 \text{ A}$$

$$\therefore V_o'' = I_1''(2)$$

$$= 4 \text{ V}$$

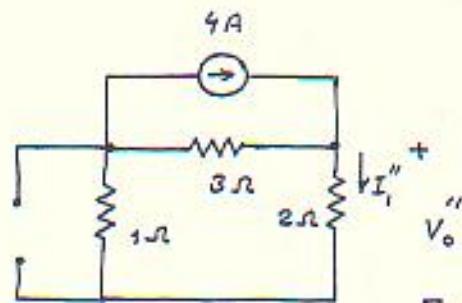


# Effect of 6V-source

$$I_1''' = \frac{6}{1+3+2} = 1 \text{ A}$$

$$\therefore V_2 = I_1'''(2) = 2 \text{ V}$$

$$\therefore V_o''' = E - V_2 = 6 - 2 = 4 \text{ V}$$

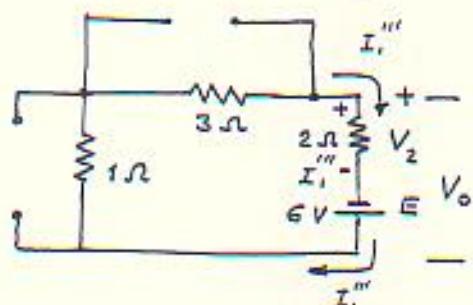
$$\therefore V_o = V_o' + V_o'' - V_o''' = 2 + 4 - 4 \\ = 2 \text{ V}$$



Example


TS4

: Use the superposition theorem to find the voltage  $V_{ab}$  in the circuit shown.

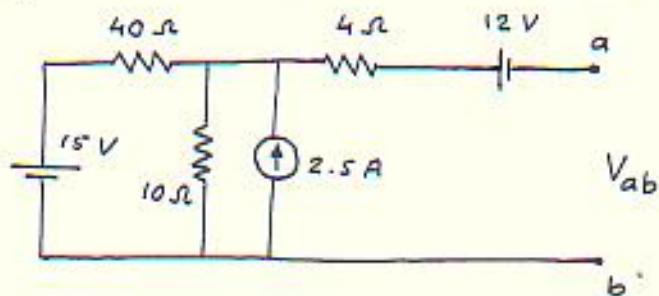Solution

\* The effect of the 15V - source
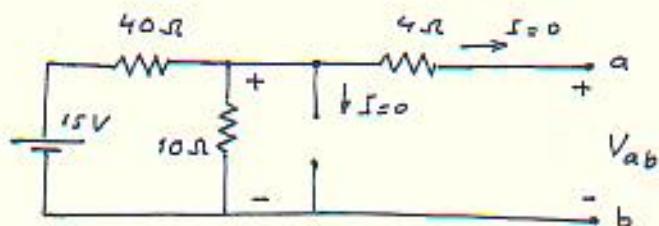
$$\therefore V'_{ab} = 15 \frac{10}{10+40} = 3 \text{ V}$$




$V_{ab}$  = voltage across 10Ω resistor

\* The effect of 2.5A - source


$$40//10 = 8\Omega$$
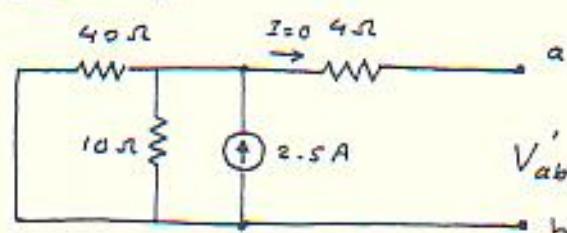
$$\therefore V_{ab} = 8 \times 2.5 = 20 \text{ V}$$



or convert the current source to a voltage source then:

$$V_{ab} = E - V_{10\Omega}$$

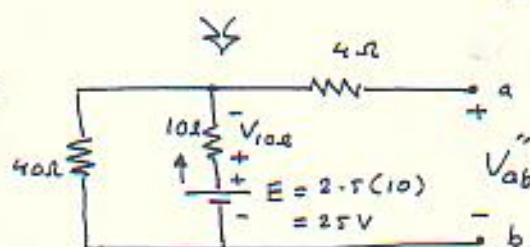

$$V_{10\Omega} = E \frac{10}{10+40} = 25 \frac{10}{50} = 5 \text{ V}$$


$$\therefore V_{ab} = 25 - 5$$

$$= 20 \text{ V}$$

\* The effect of 12V - source

$$\therefore V_{ab} = V'_{ab} + V''_{ab} - V'''_{ab}$$

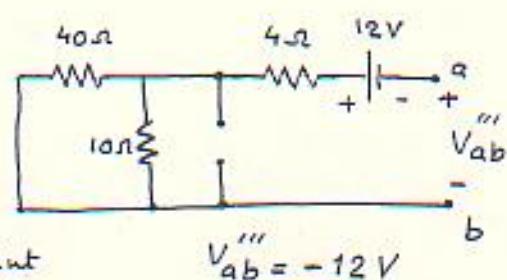
$$= 3 + 20 - 12 = 11 \text{ V} \quad \text{with point } a(+ve)$$




Example

TS4


Use the Thevenin's theorem to find the current in the  $3\Omega$  resistor in the network shown.

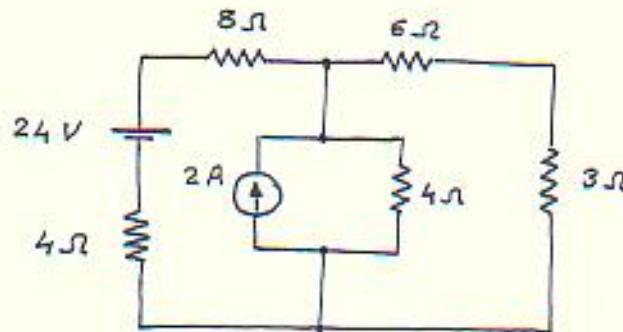Solution

$E_{th} = ?$

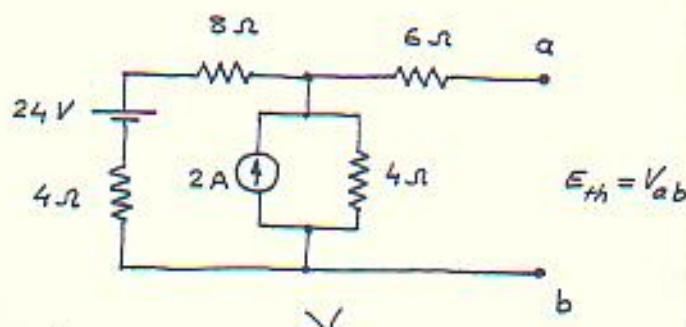

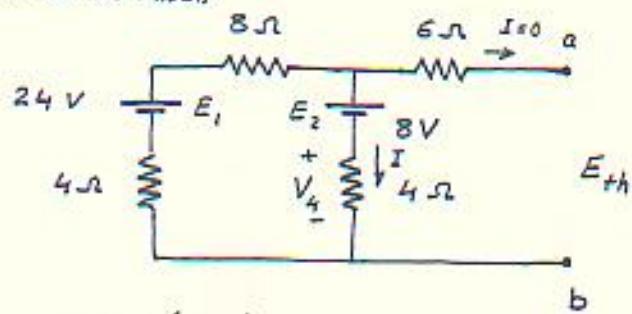\* convert the current source  
to voltage source as shown



$$V_4 = I(4\Omega)$$


$$I = \frac{E_1 - E_2}{4 + 8 + 4} = \frac{24 - 8}{16} = 1A$$

$$\therefore V_4 = (1)(4) = 4V$$


$$\therefore E_{th} = 8 + 4 = 12V$$

$R_{th} = ?$

$$R_{th} = [(8+4)/4] + 6 \\ = 9\Omega$$

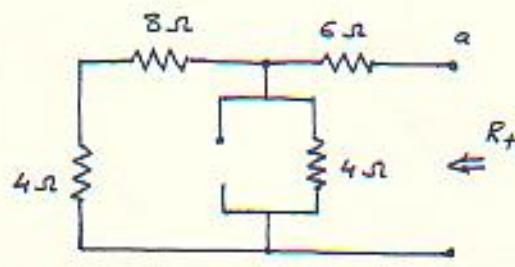
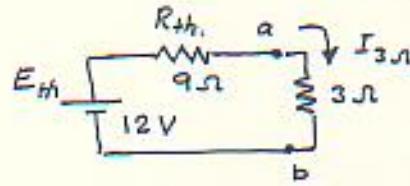
$$\therefore I_{3\Omega} = \frac{12}{9+3} \\ = 1A$$




Note: Repeat this example to find the value of  $R_L$  for max. power transfer and compute  $P_{max}$


Example

TS4

For the network shown, what is the value of  $R_L$  for maximum power transfer condition? Calculate this power.

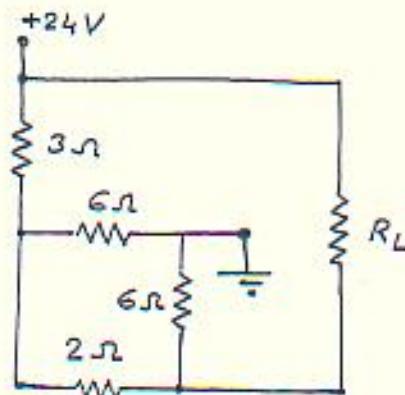Solution


The circuit is redrawn to be as shown;

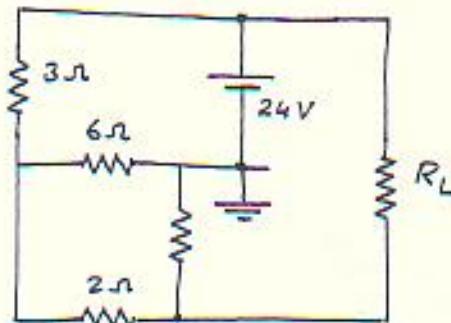

$$E_{th} = ?$$

$$\begin{aligned} E_{th} &= 24 - V_{ab} \\ &= 24 - I_1(4\Omega) \end{aligned}$$

$$I_T = \frac{E}{R_T}$$

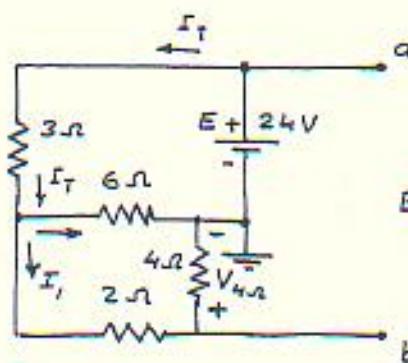

$$E_{th} = V_{ab}$$

$$R_T = [(2+4)//6] + 3 = 6\Omega$$

$$\therefore I_T = \frac{24}{6} = 4A \quad \xrightarrow{3} \quad I_1 = \frac{4}{2} = 2A$$

$$\therefore E_{th} = 24 - 2(4) = 16V$$


$$\# R_{th} = ?$$

$$\begin{aligned} R_{th} &= [(3//6)+2]//4 \\ &= 2\Omega \end{aligned}$$

$$R_L = R_{th}$$

for maximum power transfer

$$\therefore R_L = 2\Omega$$

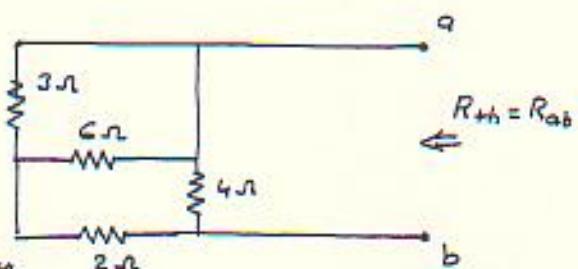

$P_{L\max}$  = max. power transferred to the load resistance  $R_L$


T54

$$P_{L\max} = \frac{E_{th}^2}{4R_{th}}$$

$$= \frac{(16)^2}{4(2)} = 32 \text{ W}$$
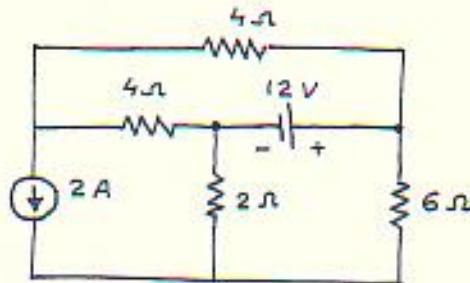
### Example

Use the Thevenin's theorem to find the current flowing through the  $6\Omega$  resistor in the network shown.



### Solution

$E_{th} = ?$

\_\_\_\_\_ :



$$E_{th} = E - V_{2\Omega}$$

$$= 12 - (2)(2) = 8 \text{ V}$$

$R_{th} = ?$

\_\_\_\_\_ :


$$R_{th} = 2 \Omega$$

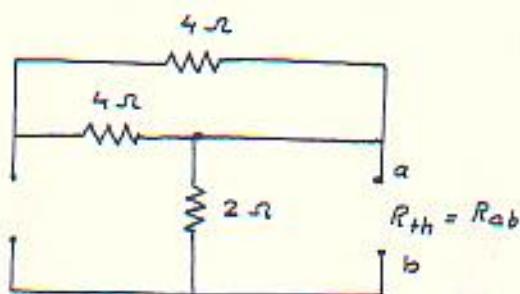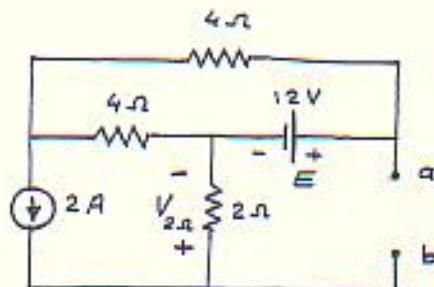

$$\therefore I_{6\Omega} = \frac{E_{th}}{R_{th} + 6}$$

$$= \frac{8}{2 + 6}$$

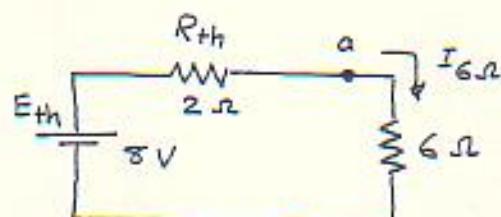
$$\therefore \frac{I}{6\Omega} = 1 \text{ A}$$



Example


TS 4

For the circuit shown, find the value of the current passing through the  $5\Omega$  resistor using Norton's theorem. Calculate the power absorbed by this resistor.

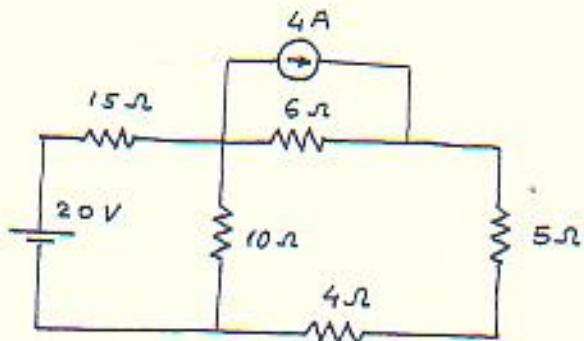Solution

$$\text{---} : R_N = ?$$
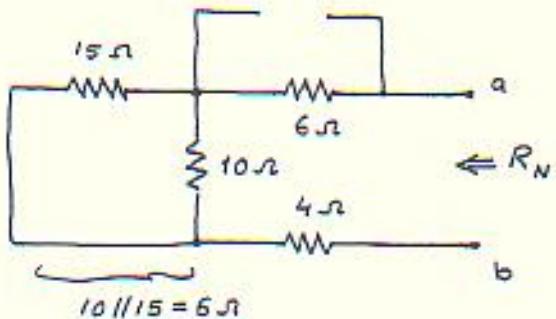
$$R_N = (15//10) + 6 + 4 \\ = 16 \Omega$$





$$I_{SC} = ?$$

--- We have two sources; we can use superposition theorem to find the resulting  $I_{SC}$ .

Effect of 4A source

current  
divider  
rule
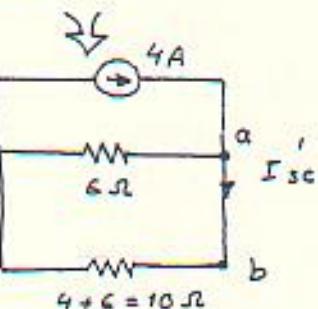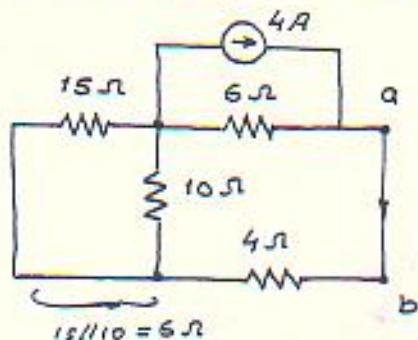
$$I'_{SC} = 4 \cdot \frac{6}{6+10} = \frac{4(6)}{16} \\ = \frac{3}{2} = 1.5 \text{ A}$$



Effect of 20V source

$$I_T = \frac{E}{R_T}$$


$$R_T = [(6+4)/10] + 15$$

$$\therefore I_T = \frac{20}{20} = 1 \text{ A}$$

$$\therefore I_{sc}' = \frac{I_T}{2} = \frac{1}{2} = 0.5 \text{ A}$$

$$\therefore I_N = I_{sc}' + I_{sc}'' = 1.5 + 0.5 = 2 \text{ A}$$
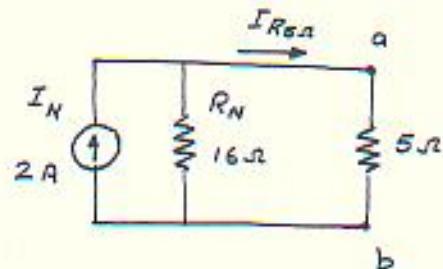
$$\begin{aligned} \therefore I_{R_{5\Omega}} &= I_N \frac{R_N}{R_N + R_{5\Omega}} \\ &= 2 \frac{16}{16+5} = 1.52 \text{ A} \end{aligned}$$




$$\text{and the power } P = I_{R_{5\Omega}}^2 \cdot R_{5\Omega}$$

$$= (1.52)^2 \cdot (5) = 11.6 \text{ W}$$

نقطة: إذا تم توصيل دائرة غير متوازنة بمحرك ذو معاين على الشبكة  $E_{th}$  فإنها توليد طاقة.

Example

- For the circuit shown, obtain the condition for power transfer to the load  $R_L$ . Hence determine the maximum power transferred.

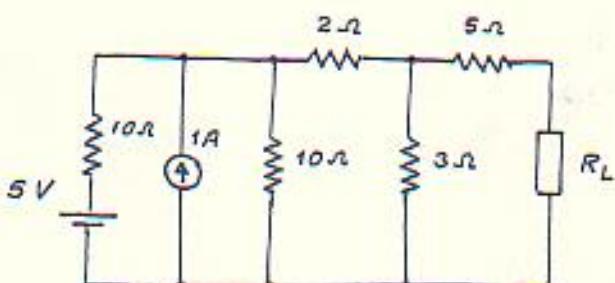
Solution

The condition for max. power transfer is  $R_L = R_{th}$  of the eez.

$$R_{th} = ?$$

$$R_{th} = 7.1 \Omega \Rightarrow$$
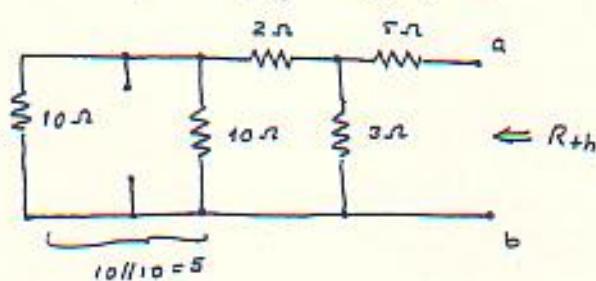
$$\therefore R_L = 7.1 \Omega \text{ for max. power transfer}$$




To calculate  $P_{L_{max}}$  (max. power transfer),  $E_{th}$  must be determined.


TS4

$$P_{L_{max}} = \frac{E_{th}^2}{4R_{th}}$$

$$\therefore E_{th} = ?$$

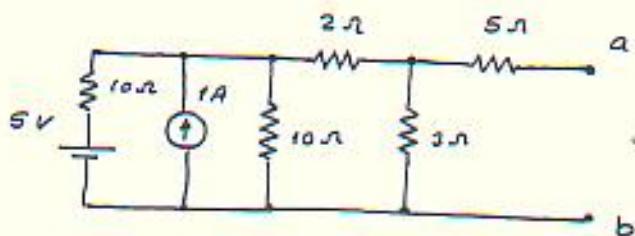

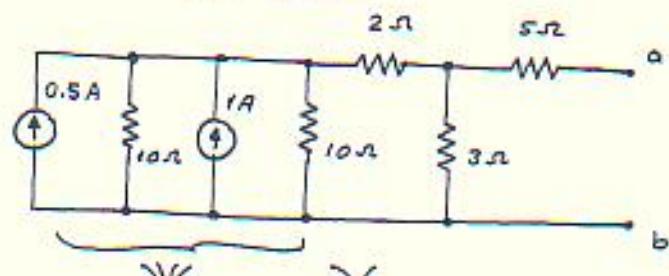
convert the voltage source  
into a current source



$$\therefore I_{R_{2\Omega}} = 1.5 \cdot \frac{5}{2+3} = 0.75 \text{ A}$$


$$\therefore E_{th} = 0.75(3) = 2.25 \text{ V}$$
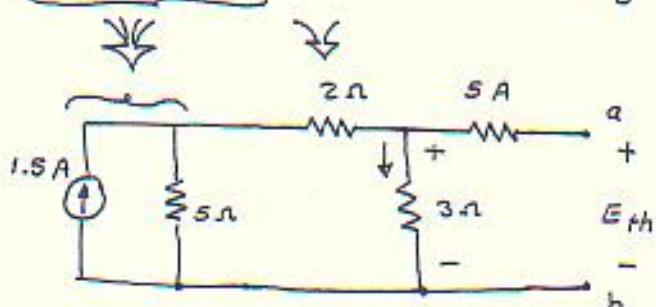
$$\therefore P_{L_{max}} = \frac{(2.25)^2}{4(7.1)} = 0.178 \text{ W} = 178 \text{ mW}$$


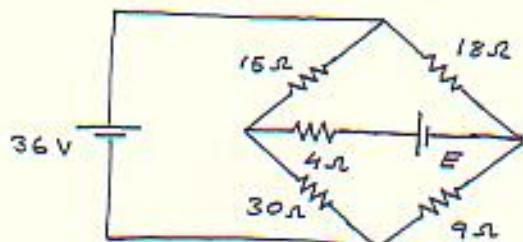
### Example

For the circuit shown, find the current flowing through the 4Ω resistor when : (a)  $E = 2 \text{ V}$ , (b)  $E = 12 \text{ V}$ , (c)  $E = 20 \text{ V}$




### Solution

Since it is required to determine the current in the same branch many times, it convenient to use Thevenin's theorem.

$$R_{th} = ?$$


Ans:

$$\begin{aligned} R_{th} &= (15//30) + (18//9) \\ &= 16 \Omega \end{aligned}$$

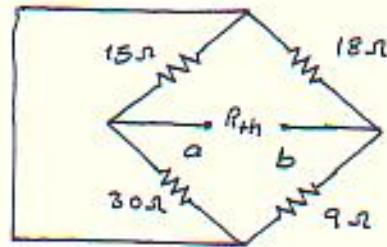

TS4

25

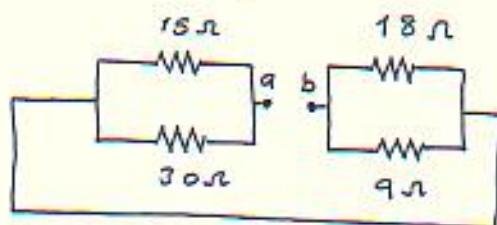


$$E_{th} = V_{ab} = V_a - V_b$$

using voltage divider rule

$$\begin{aligned} V_b &= 36 \frac{9}{9+18} \\ &= 12 V \end{aligned}$$

also,
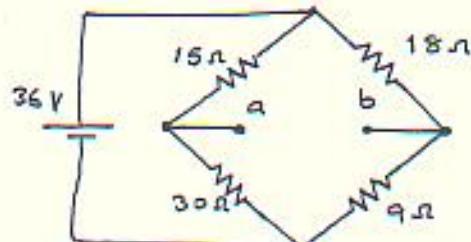
$$\begin{aligned} V_a &= 36 \frac{30}{30+15} \\ &= 24 V \end{aligned}$$




$$\text{then: } \therefore E_{th} = V_a - V_b = 24 - 12 = 12 V$$

∴ Thevenin's equivalent circuit of the network is :

$$\begin{aligned} \therefore I &= \frac{E_{th} - E}{R_{th} + 4} \\ &= \frac{12 - E}{16 + 4} = \frac{12 - E}{20} \end{aligned}$$
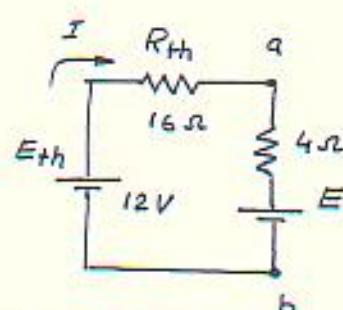
$$\therefore I = * \text{ for } E = 2 V$$



$$\begin{aligned} * \text{ for } E = 12 V &\quad \therefore I = \frac{12 - 12}{20} = 0 A \\ &\quad \therefore I = \frac{12 - 12}{20} = 0 A \end{aligned}$$

$$\therefore I = \frac{12 - 12}{20} = 0 A$$



$$* \text{ for } E = 20 V$$

$$\therefore I = \frac{12 - 20}{20} = -0.4 A \quad (\text{in the reversed direction.})$$

Example

TS 4


Find the Norton equivalent circuit for the portion of the network to the left of (a-b) in the circuit shown.

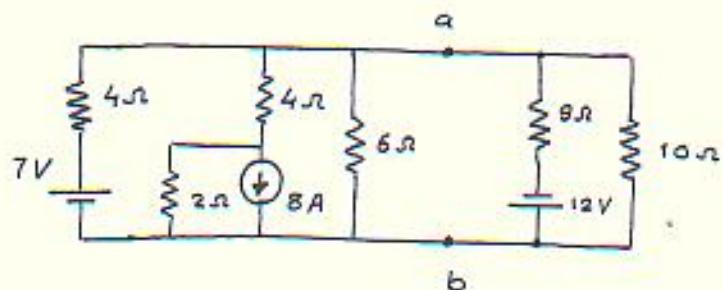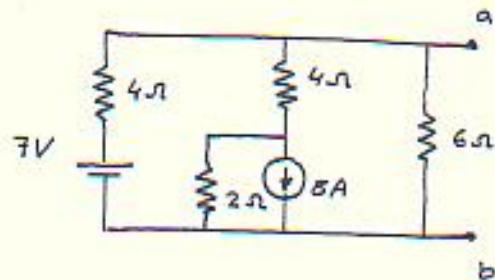Solution

$$R_N = ?$$

$$R_N = 6//6//4$$

$$= 1.714 \Omega$$

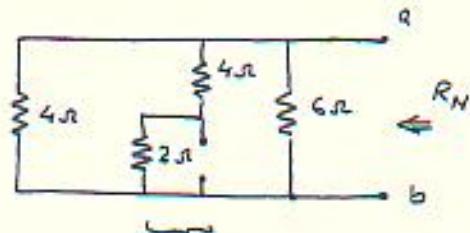


$$I_N = ?$$

We have 2 sources, it is recommended to use the superposition theorem to find  $I_N$

أولاً: نطبق المبدأ الثاني  
نأخذ المصادر الأخرى

- Effect of 7V source
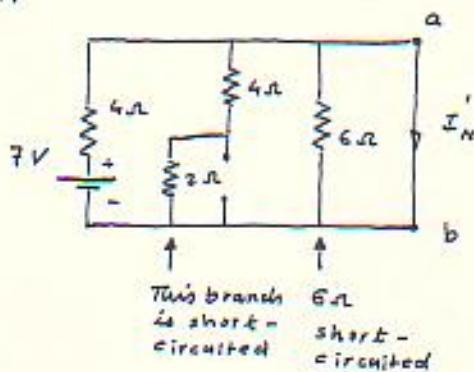
$$\therefore I'_N = \frac{7}{4} = 1.75 A$$




- Effect of BA source

TS4


current  
divider  
rule
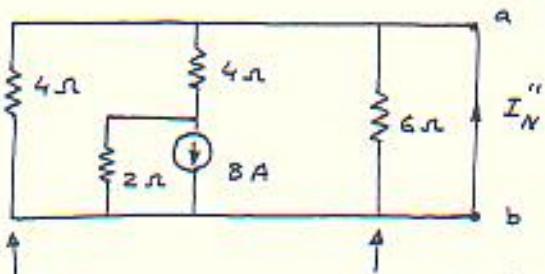
$$\therefore I_N'' = 8 \frac{2}{2+4} \\ = 2.667 \text{ A}$$



$$\therefore I_N = I_N' - I_N'' = 2.667 - 1.75 \quad \text{short circ.} \\ = 0.917 \text{ A} \quad (\text{in the direction of } I_N').$$

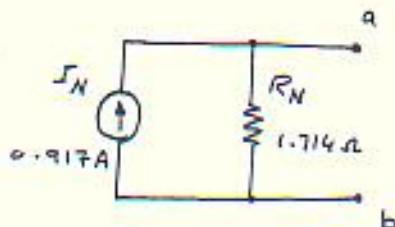
$\therefore$  The Norton equivalent circuit of the portion of the network to the left of (a-b) is:



(Thévenin) අවා මුදල් නිරූපණය යොමු කළ ඇති විට පෙනීම.

Example

For the circuit shown, find the current through the 20V voltage source using Thévenin's theorem.

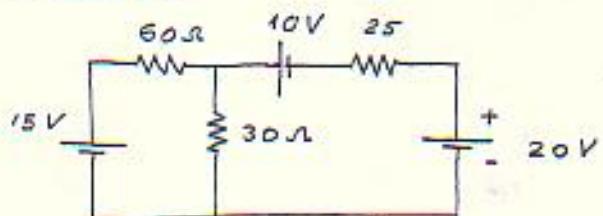
Solution

$E_{th} = ?$

$$E_{th} = I(30) - 10$$

$$\therefore E_{th} = 5 - 10 \quad I = \frac{15}{60 + 30} = \frac{1}{6}$$

$$= -5 \text{ V}$$

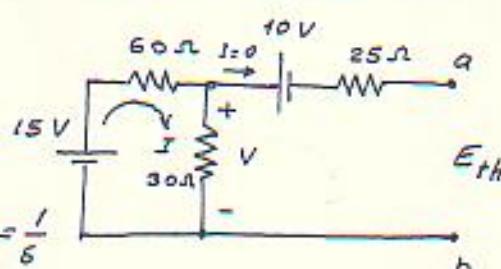

$$\text{or } E_{th} = V - 10$$

$$\begin{aligned} \text{Voltage divider rule} \quad V &= 15 \frac{30}{30+60} \\ &= 5 \text{ V} \end{aligned}$$



$$\therefore E_{th} = 5 - 10 = -5 \text{ V}$$

$R_{th} = ?$ :


$$R_{th} = (60//30) + 25$$

$$= 45 \Omega$$


TS4

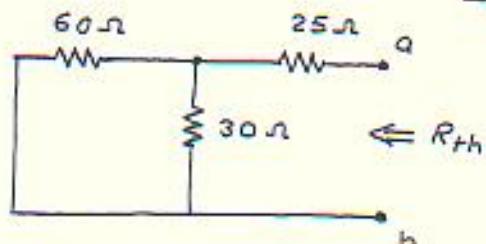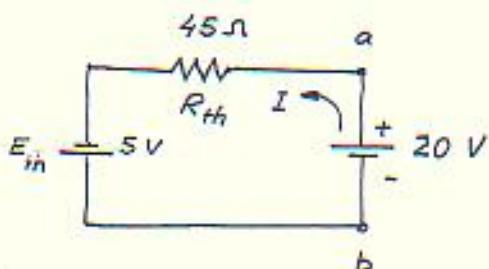∴ Thevenin equivalent circuit of the network is :

$$\therefore I = \frac{20+5}{45} = \frac{25}{45} = 0.56 A$$

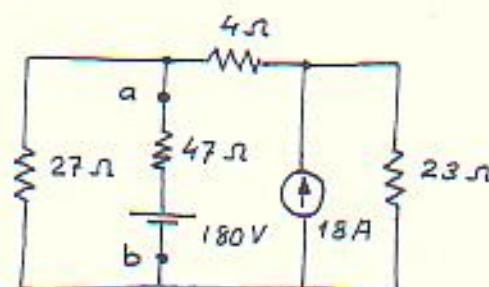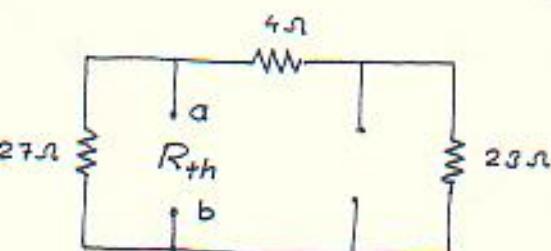Example: In the circ. shown, find the current through the branch a-b using Thevenin's theorem.Solution:  $R_{th} = ?$ :

$$R_{th} = (\underbrace{4+23}_{27}) // 27$$



$$\therefore R_{th} = \frac{27}{2} = 18.5 \Omega$$


$$E_{th} = ?$$

:

$$E_{th} = I(27\Omega)$$

$$= 7.67(27)$$

$$= 207 \text{ V}$$

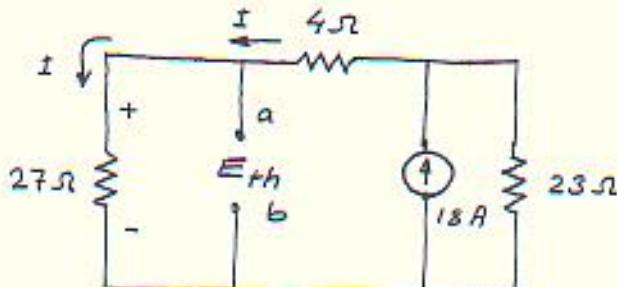


TS4

$$\leftarrow I = 18 \frac{23}{(4+27)+23} = 18 \frac{23}{54}$$

$$= 7.67 \text{ A}$$

∴ Thevenin equivalent circuit is:
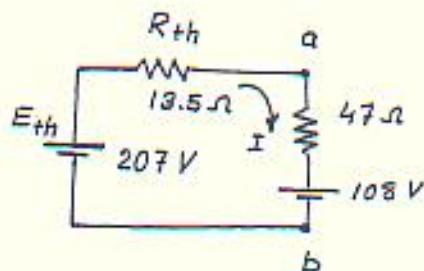
$$\begin{aligned} \therefore I &= \frac{E_{th} - 108}{R_{th} + 47} \\ &= \frac{207 - 108}{13.5 + 47} \\ &\Rightarrow I = 1.64 \text{ A} \end{aligned}$$





### Example

: Using Norton's theorem, find the current through the branch  $a-b$  in the circuit shown.
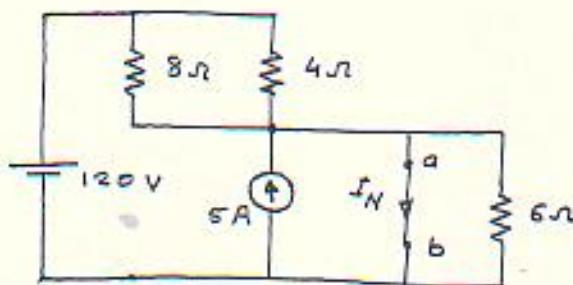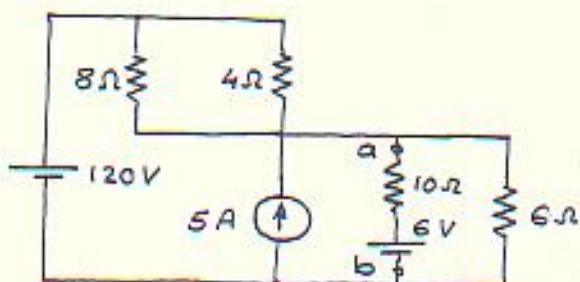
### Solution

$$I_N = ?$$

\* We have two source in the circuit shown, so we can use the superposition theorem to determine  $I_N$ .




\* Effect of 18V source

TS4

$$I'_N = \frac{120}{2.67}$$

$$= 45 \text{ A}$$

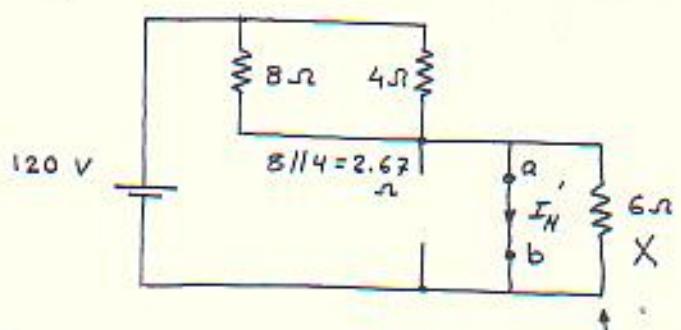

\* Effect of 5A source


short-circuited

$$\therefore I''_N = 5 \text{ A}$$

in the same  
direction

$$\therefore I_N = I'_N + I''_N$$


$$= 45 + 5 = 50 \text{ A}$$

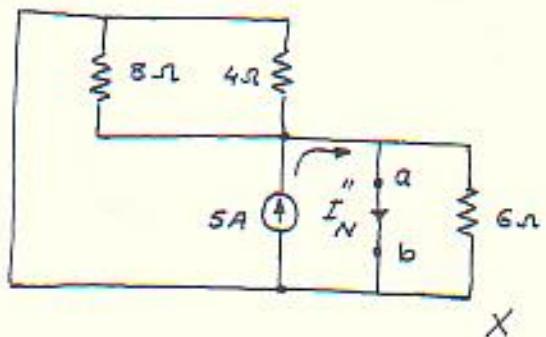

$$R_N = ?$$

$$R_N = (8//4)//6$$


$$= 1.846 \Omega$$

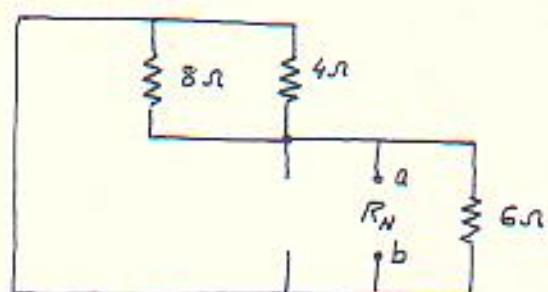


$\therefore$  Norton equivalent circuit is:

$$\therefore I = \frac{92.3 - 6}{1.846 + 10}$$

$$= 7.29 \text{ A}$$

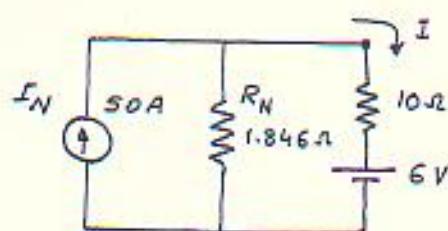


convert to  
voltage source

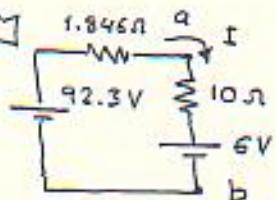


Example

TS4

For the network shown, determine the current  $I$ .  
Is the reciprocity theorem satisfied?

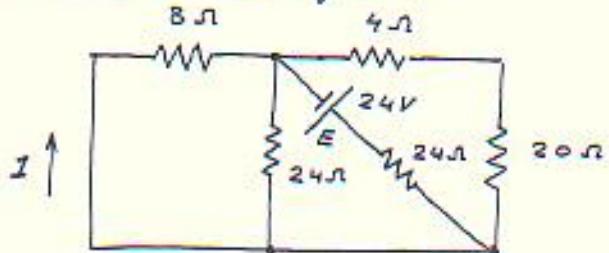
Solution

The circuit is redrawn to be as shown:

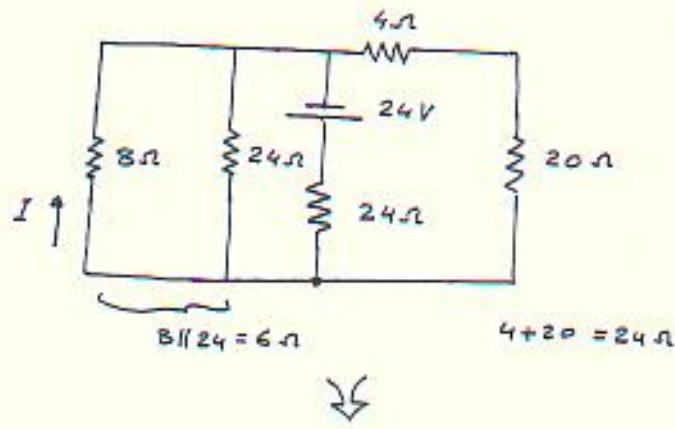

$$R_T = (6 \parallel 24) + 24$$

$$= 28.8 \Omega$$

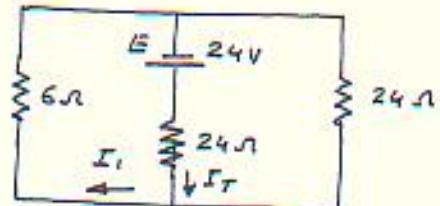

$$\therefore I_T = \frac{E}{R_T} = \frac{24}{28.8}$$

$$= 0.833 A$$

$$\therefore I_1 = I_T \frac{24}{24+6} = 0.833 \frac{24}{30} = 0.666 A$$


$$\Rightarrow I = I_1 \frac{24}{8+24} = 0.666 \frac{24}{32} = 0.5 A$$

Reciprocity!

$$\therefore I_T = \frac{E}{R_T} = \frac{24}{16} = 1.5 A$$

$$\text{and } I_1 = I_T \frac{24}{24+12} = 1 A$$

$$\therefore I = \frac{I_1}{2} = 0.5 A$$

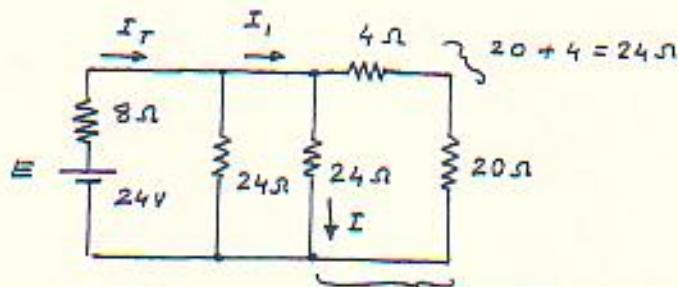

$$R_T = 8 + 8 \leftarrow \quad 24 \parallel 24 = 12 \Omega$$


$$= 16 \Omega \quad 24 \parallel 12 = 8 \Omega$$

Hence, the reciprocity theorem is satisfied

Example

TS4

For the circuit shown, determine the voltage  $V$ . Is the reciprocity theorem satisfied?

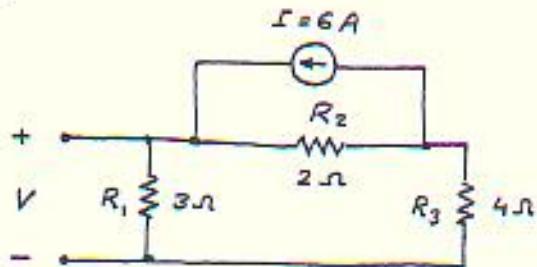Solution

$$V = ?$$

$$V = I_1 R_1$$

$$I_1 = \frac{I(2)}{(3+4)+2}$$

$$\Rightarrow I_1 = \frac{6 \times 2}{9} = \frac{12}{9} = 1.333 \text{ A}$$


$$\therefore V = (1.333)(3)$$

$$= \underline{4V}$$

Reciprocity!

$$I_1 = \frac{I}{R_1 + (R_2 + R_3)}$$

$$= \frac{6}{3 + (2+4)} = 2 \text{ A}$$

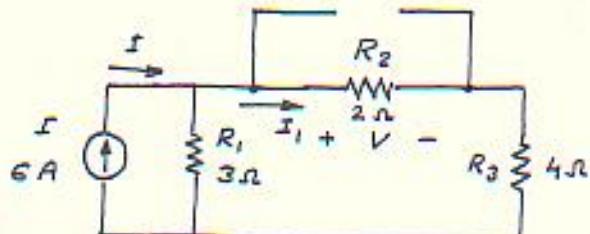


$$\therefore V = I_1 R_2 = 2(2) = \underline{4V}$$

 $\therefore$  Reciprocity theorem is satisfied.

Example

TSA


For the network shown determine the value of  $R_L$  to achieve maximum power transfer condition to  $R_L$ . Calculate this maximum power.

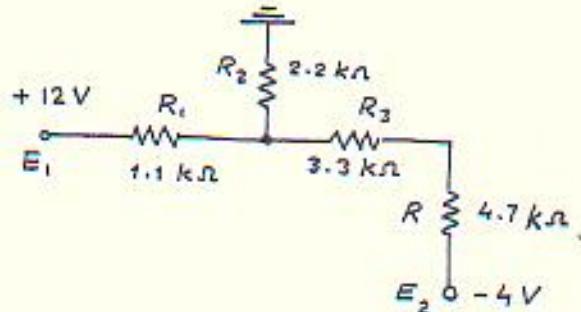Solution

The circuit is redrawn to be as shown;

For max. power transfer

$$R_L = R_{th}$$

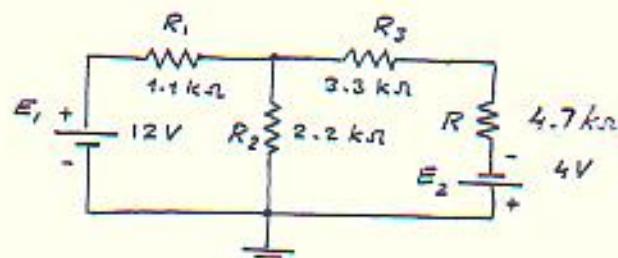


$R_{th}$ :

$$R_{th} = (R_1 \parallel R_2) + R_3$$

$$= 4.033 \text{ k}\Omega$$

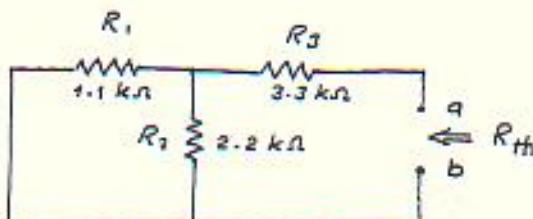$\therefore R_L = 4.033 \text{ k}\Omega$  for max power transfer




$E_{th}$ :

$$E_{th} = E_2 + V_2$$

$$V_2 = 12 \frac{2.2 \times 10^3}{(1.1 + 2.2) \times 10^3}$$

$$\therefore V_2 = 3 \text{ V}$$
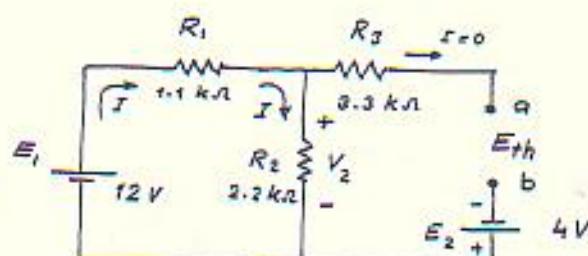
$$\therefore E_{th} = 4 + 3 = 12 \text{ V}$$



$$\therefore P_{L\max} = \frac{E_{th}^2}{4R_{th}} = \frac{(12)^2}{4(4.033) \times 10^3}$$


$$= 9.93 \times 10^{-3} \text{ W}$$

$$= 9.93 \text{ mW}$$

Example

TS4

For the circuit shown, find the value of the resistor  $R_1$ , such that the resistor  $R_4$  will receive maximum power.

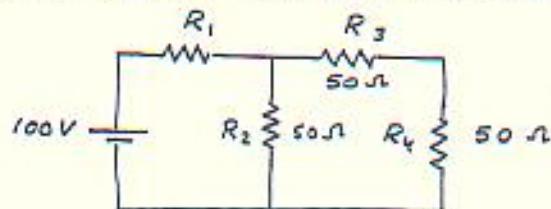
Solution

Since  $R_4$  receive maximum power, then:

$$\therefore R_4 = R_{th}$$

$$\therefore R_{th} = 50\Omega$$
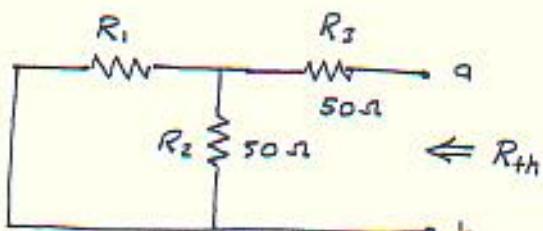
$$\begin{aligned} R_{th} &= (R_1 \parallel R_2) + R_3 \\ &= \frac{R_1 * R_2}{R_1 + R_2} + R_3 \end{aligned}$$



$$\therefore 50 = \frac{R_1(50)}{R_1 + 50} + 50$$

$$\frac{50R_1}{R_1 + 50} = 0 \Rightarrow 50R_1 = 0$$

$$\therefore R_1 = 0$$


or

$$R_1 + 50 = 0 \Rightarrow R_1 = -50$$

$$\therefore R_1 = 0 \quad (\text{short circuit})$$

-ve sign  
neglected

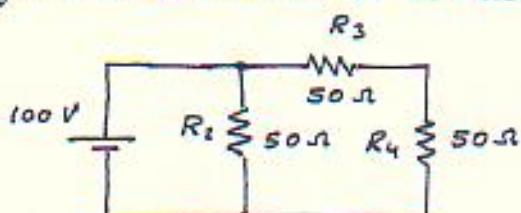$\therefore$  For maximum power transfer, the circ. will be as shown:



**Practice Problem**


TS4

: For the circuit shown, find the current through the  $1\Omega$  resistor using;


- (a). the superposition theorem,
- (b). the nodal voltage method,
- (c). the loop current method.
- (d). Thevenin's theorem.
- (e). Norton's theorem.

**Answer**

:  $I_{1\Omega} = 0.6 \text{ A}$

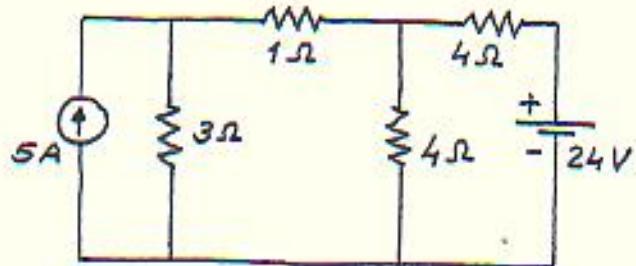**Practice Problem**


: Find the current through the  $8\Omega$  resistor in the circuit shown, using the superposition theorem.

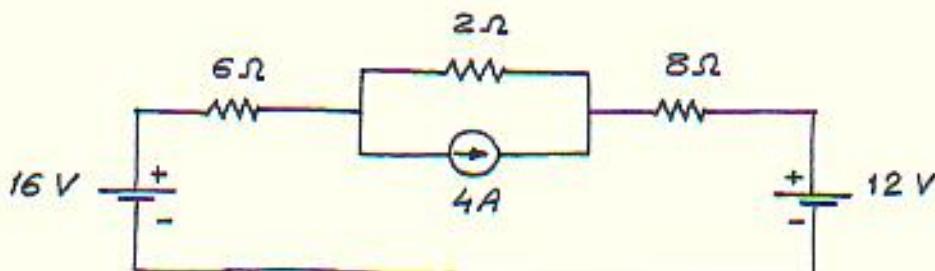**Answer**

:  $I = 0.75 \text{ A}$

**Practice Problem**

: Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown, then find the current  $I$ .

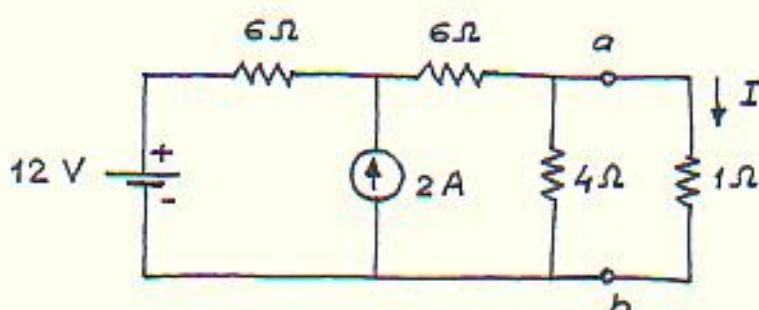
**Answer**

:  $\frac{V_{th} = 6V}{R_{th} = 3\Omega} \Rightarrow I = 1.5 \text{ A}$

TS4


Example

Find the Thevenin's equivalent circuit of the circuit shown to the left of the terminals  $a-b$ . Then find the current through  $R_L = 6, 16, \text{ and } 36 \Omega$ .

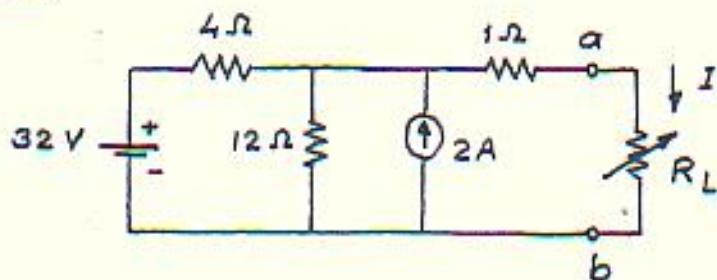Solution

\_\_\_\_\_ :

$$\oplus R_{th} = ?$$

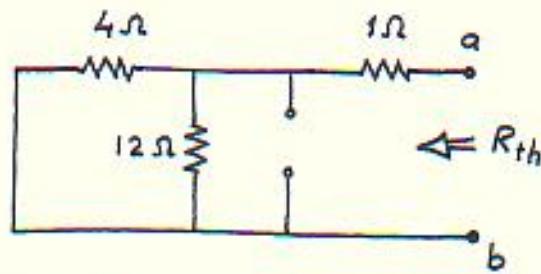


$$R_{th} = (4//12) + 1$$

$$= \frac{4 \times 12}{4+12} + 1 = \frac{48}{16} + 1 = 4 \Omega$$

$$\oplus V_{th} = ?$$

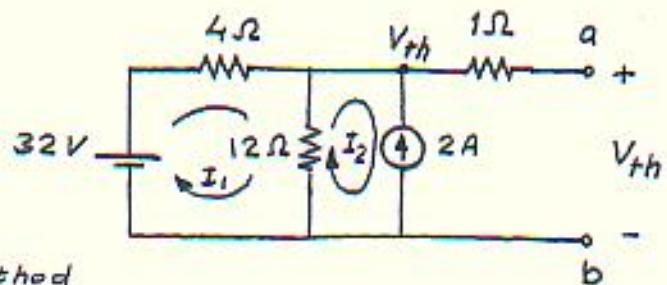هذه الطريقة خطأ  
قيمة  $V_{th}$  راسية (أو المتر)  
المذكورة هنا ليست بواحدة.



# Using loop method

$$\underline{\text{Loop 1}} \quad 32 = I_1(4+12) - I_2(12)$$

$$\underline{\text{Loop 2}} \quad I_2 = -2 A$$

$$\therefore 32 = I_1(16) - (-2)(12)$$

$$\Rightarrow I_1 = \frac{32 - 24}{16} = \frac{8}{16} = 0.5 A$$

$$\therefore V_{th} = (I_1 - I_2)(12\Omega)$$

$$= (0.5 + 2)(12) = \underline{\underline{30 V}}$$




T84

الحلقة كنوز استهلاك الـ (Nodal method) بدتحبيب مصدر المولدة اولاً  
ثم تيار يحصل على المقاومة المدنية :

∴ There is one node, which is  $V_{th}$ ,  
then


$\Rightarrow V_{th} \left( \frac{1}{4} + \frac{1}{12} \right) = 8 + 2$

$\therefore V_{th} (3 + 1) = 120$

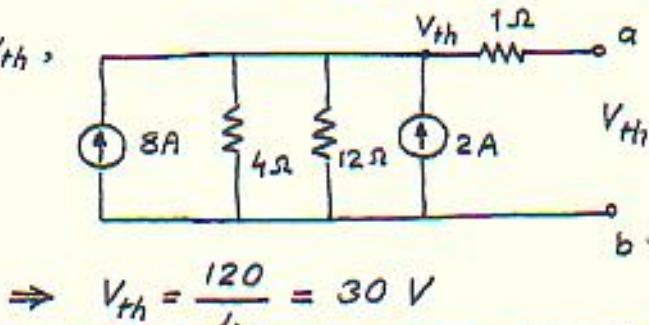

∴ The Thévenin's equivalent circ. is :
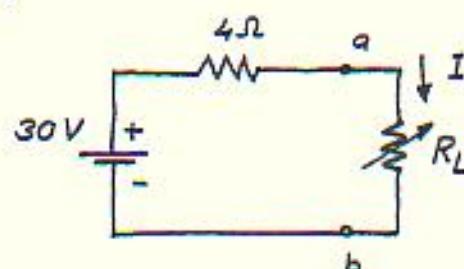
$$\therefore I = \frac{V_{th}}{R_{th} + R_L}$$



So;

$$\text{When } R_L = 6\Omega$$

$$\Rightarrow I = \frac{30}{4+6} = 3A$$

$$\text{When } R_L = 16\Omega$$


$$\Rightarrow I = \frac{30}{4+16} = 1.5A$$

$$\text{When } R_L = 36\Omega$$

$$\Rightarrow I = \frac{30}{4+36} = 0.75A$$
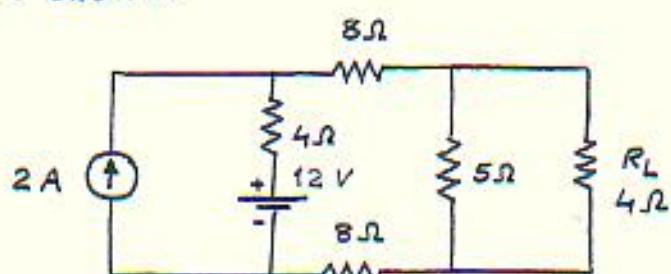
### Example

: Using Norton's theorem, find the current through  $R_L$  in the circuit shown.



### Solution

:

$$\therefore R_N = ?$$

$$\therefore R_N = 5 // (8 + 4 + 8)$$

$$= \frac{5 \times 20}{5 + 20} = 4\Omega$$

