


Per unit System

Eq. pow 1

The solution of an interconnected power system having several different voltage levels requires the cumbersome transformation of all impedance to a single voltage level. However, power system engineers have devised the per-unit system such that the various physical quantities such as power, voltage, current and impedance are expressed as a decimal fraction or multiples of base quantities.

In this system, the different voltage levels disappear, and a power network involving generators, transformers and lines (of different voltage levels) reduces a system of simple impedance. The per unit value of any quantity is defined as
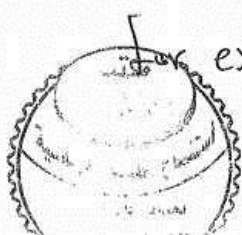
$$\text{Quantity in per unit} = \frac{\text{actual quantity}}{\text{base value quantity}} \quad \text{--- (1)}$$



For example : $S_{pu} = \frac{S}{S_B}$; $V_{pu} = \frac{V}{V_B}$

$$I_{pu} = \frac{I}{I_B} ; Z_{pu} = \frac{Z}{Z_B}$$

where S_{pu} : per unit apparent power

S : actual apparent power

S_B : Base " "

V_{pu} : per unit voltage

V : actual voltage

V_B : Base voltage

I_{pu} : per unit current

I : actual current

I_B : Base current

Z_{pu} : per unit impedance

Z : actual impedance

Z_B : Base impedance

where the numerator (actual values) are phasor quantities or complex values and the denominators (base values) are always real number

A minimum of four base quantities are required to completely define a per unit system: volt-ampere, voltage, current and impedance.

Usually, the 3- ϕ base volt-ampere S_B or MVA_B and the line-to-line base voltage V_B or kV_B are selected.

Base current and base impedance are then dependent on S_B and V_B and must obey the circuit law.

These are given by:

$$I_B = \frac{S_B}{\sqrt{3} V_{B \text{ Line}}}$$

$$Z_B = \frac{V_B / \sqrt{3}}{I_B} \Rightarrow Z_B = \frac{V_B / \sqrt{3}}{\frac{S_B}{\sqrt{3} V_B}}$$

$$Z_B = \frac{V_B^2}{S_B} = \frac{kV_B^2}{MVA_B}$$

Then $S_{pu} = V_{pu} I_{pu}^*$

$$V_{pu} = Z_{pu} I_{pu}$$

The complex Load power $S_{L(3\phi)}$ can be defined as

$$S_{L(3\phi)} = 3 V_P I_P^*$$

I_P : Load current per pha
 V_P : Load voltage per pha

$$I_P = \frac{V_P}{Z_P}$$

$$Z_P = \frac{V_P}{I_P} = \frac{V_P}{\left(\frac{S_{L(3\phi)}}{3V_P} \right)^*}$$

Impedance are calculate per phase

$$Z_p = \frac{V_p}{\frac{S_{L(3\phi)}^*}{3V_p^*}} = \frac{3V_p^* V_p^*}{S_{L(3\phi)}^*}$$

$$Z_p = \frac{3|V_p|^2}{S_{L(3\phi)}^*} = \frac{V_{Line}^2}{S_{L(3\phi)}^*} = \frac{V_{LL}^2}{S_{L(3\phi)}^*}$$

$$\therefore Z_p = \frac{V_{LL}^2}{S_{L(3\phi)}^*}$$

$$Z_{pu} = \frac{Z_p}{Z_B} = \frac{\frac{V_{LL}^2}{S_{L(3\phi)}^*}}{\frac{V_B^2}{S_B}}$$

$$Z_{pu} = \frac{V_{LL}^2}{V_B^2} * \frac{S_B}{S_{L(3\phi)}^*}$$

$$Z_{pu} = \frac{V_{pu}^2}{S_{L(pu)}^*}$$

$S_L =$ Load apparent power

* Change of Base

For power system analysis, all impedances must be expressed in per unit on a common system base. To accomplish this, an arbitrary base for apparent power is selected; for example, 100 MVA.

Then the voltage base must be selected.

Once a voltage base has been selected for a point in a system, the remaining voltage bases are no longer independent; they are determined by the various transformer turns ratios.

For example, if on a low-voltage side of $\frac{34.5 \text{ kV}}{115 \text{ kV}}$ transformer the base voltage of 36 kV is selected.

The base voltage on the high-voltage side must be

$$36 \times \frac{115}{34.5} = 120 \text{ kV}$$

where $\frac{N_2}{N_1} = \frac{VB_2}{VB_1}$



Normally we try to select the voltage bases that are the same as the nominal values.

Let Z_{pu}^{old} be the per-unit impedance on the power base S_B^{old} and the voltage V_B^{old}

$$Z_{pu}^{old} = \frac{Z_{\Omega}}{Z_B^{old}} = Z_{\Omega} \frac{S_B^{old}}{(V_B^{old})^2}$$

Expressing Z_{Ω} to a new power base and a new voltage base, results in the new per unit impedance

$$Z_{pu}^{new} = \frac{Z_{\Omega}}{Z_B^{new}} = Z_{\Omega} \frac{S_B^{new}}{(V_B^{new})^2}$$

$$Z_{pu}^{new} = \frac{Z_{pu}^{old}}{\frac{S_B^{old}}{(V_B^{old})^2}} \times \frac{S_B^{new}}{(V_B^{new})^2} =$$


$$Z_{pu}^{new} = Z_{pu}^{old} \cdot \left(\frac{S_B^{new}}{S_B^{old}} \right) \left(\frac{V_B^{old}}{V_B^{new}} \right)^2$$

* The advantage of per-unit system.

7

- 1- The per-unit system gives us a clear idea of relative magnitudes of various quantities, such as voltage, current, power and impedance.
- 2- The per-unit impedance of equipment of the same general type based on their own ratings fall in a narrow range regardless of rating of the equipment. Whereas their impedance in ohms vary greatly with the rating.
- 3- The per-unit values of impedance, voltage and current of a transformer are the same regardless of whether they are referred to the primary or the secondary side. This is a great advantage since the different voltage levels disappear and the entire system reduces to a system of simple impedance.
- 4- The per-unit system are ideal for the computerized analysis and simulation of complex power system problem.
- 5- The ckt law are valid in per-unit system and the power and the voltage equations are simplified since the factor $\sqrt{3}$ and 3 are eliminated in per-unit.

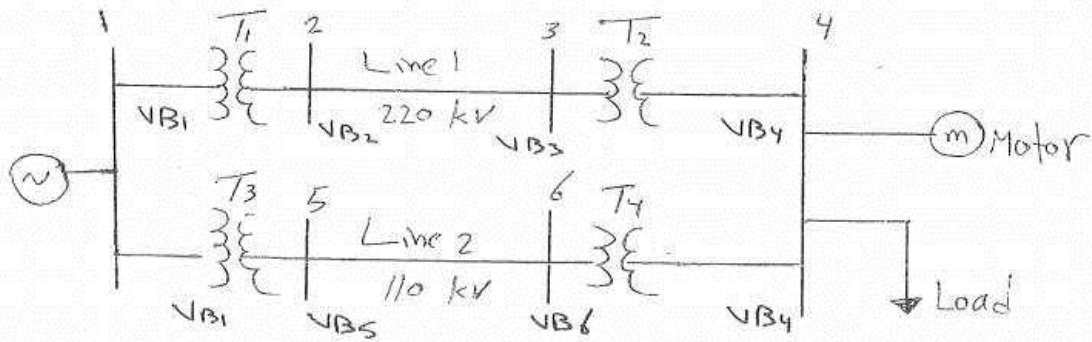ex1) The one-line diagram of a 3- ϕ power system is shown in the fig. below :-



Select a Common base of 100 MVA and 22 kV on the generator side.

Draw an impedance diagram in per unit.

The data for each device is given below :-

G :	90 MVA	22 kV	$X = 18\%$
T_1 :	50 MVA	22/220 kV	$X = 10\%$
T_2 :	40 MVA	220/11 kV	$X = 6\%$
T_3 :	40 MVA	22/110 kV	$X = 6.4\%$
T_4 :	40 MVA	110/11 kV	$X = 8\%$
Motor :	66.5 MVA	10.45 kV	$X = 18.5\%$ 0.8 Lag. P.f

The 3- ϕ load at bus 4 absorbs 57 MVA, 0.6 P.f Lag. at 10.45 kV. Line 1 and Line 2 have a reactance of 48.4 and 65.43 Ω respectively.

- The voltage bases must be determined for all sections of the network.

- The generator rated voltage is given at the base voltage at bus 1

$$V_{B1} = V_{G1} = 22 \text{ kV}$$

$$V_{B2} = 22 * \left(\frac{220}{22} \right) = 220 \text{ kV}$$

where

$$\frac{N_2}{N_1} = \frac{V_{B2}}{V_{B1}}$$

$$\frac{220}{22} = \frac{V_{B2}}{22} \Rightarrow V_{B2} = 22 * \left(\frac{220}{22} \right) = 220 \text{ kV}$$

$$V_{B2} = V_{B3} = 220 \text{ kV}$$

$$V_{B4} = 220 \left(\frac{11}{220} \right) = 11 \text{ kV}$$

$$V_{B3} = 22 \left(\frac{110}{22} \right) = 110 \text{ kV}$$

$$V_{B6} = V_{B3} = 110 \text{ kV}$$

$$V_{B4} = 110 * \left(\frac{11}{110} \right) = 11 \text{ kV}$$

$$X_{\text{new}} = X_{\text{old}} \left(\frac{S_{B \text{ new}}}{S_{B \text{ old}}} \right) \left(\frac{V_{B \text{ old}}}{V_{B \text{ new}}} \right)^2$$

$$X_{G1} = 0.18 \left(\frac{100}{90} \right) \left(\frac{22}{22} \right)^2 = 0.2 \text{ pu}$$

$$X_{T1} = 0.1 * \left(\frac{100}{50} \right) \left(\frac{22}{22} \right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary side} \\ \text{of Transformer 1} \\ \text{i.e.: Low voltage} \\ \text{side.} \end{array} \right.$$

OR

$$X_{T1} = 0.1 * \left(\frac{100}{50} \right) \left(\frac{220}{220} \right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 1} \\ \text{i.e.: High voltage} \\ \text{side.} \end{array} \right.$$

$$X_{T2} = 0.6 * \left(\frac{100}{40} \right) \left(\frac{220}{220} \right)^2 = 0.15 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary} \\ \text{side of} \\ \text{Transformer 2} \\ \text{i.e.: High voltage} \\ \text{side.} \end{array} \right.$$

OR

$$X_{T2} = 0.6 * \left(\frac{100}{40} \right) \left(\frac{11}{11} \right)^2 = 0.15 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 2} \\ \text{i.e.: Low} \\ \text{voltage side} \end{array} \right.$$

$$X_{T3} = 0.064 * \left(\frac{100}{40} \right) \left(\frac{22}{22} \right)^2 = 0.16 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary} \\ \text{side of} \\ \text{Transformer 3} \\ \text{i.e.: Low} \\ \text{voltage side} \end{array} \right.$$

OR

$$X_{T3} = 0.064 * \left(\frac{100}{40} \right) \left(\frac{110}{110} \right)^2 = 0.16 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 3} \end{array} \right.$$

$$X_{T4} = 0.08 \left(\frac{100}{40} \right) \left(\frac{110}{110} \right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary side} \\ \text{of Transformer 4} \\ \text{i.e.: High Voltage} \\ \text{side.} \end{array} \right.$$

OR

$$X_{T4} = 0.08 \left(\frac{100}{40} \right) \left(\frac{110}{110} \right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 4} \\ \text{i.e.: Low Voltage} \\ \text{side.} \end{array} \right.$$

$$X_{\text{motor}} = 0.185 \left(\frac{100}{65.5} \right) \left(\frac{10.45}{11} \right)^2 = 0.2 \text{ pu}$$

$$Z_{\text{Line 1}}^B = \frac{V_{B \text{ Line 1}}^2}{S_B} = \frac{(V_{B2} \text{ or } V_{B3})^2}{S_B} = \frac{220^2}{100} = 484 \Omega$$

$$Z_{\text{Line 2}}^B = \frac{V_{B \text{ Line 2}}^2}{S_B} = \frac{(V_{B5} \text{ or } V_{B6})^2}{S_B} = \frac{110^2}{100} = 121 \Omega$$

$$X_{\text{Line 1}}^{\text{pu}} = \frac{\text{actual}}{\text{Base}} = \frac{48.4}{484} = 0.1 \text{ pu} = j0.1 \text{ pu}$$


$$X_{\text{Line 2}}^{\text{pu}} = \frac{\text{actual}}{\text{Base}} = \frac{65.43}{121} = 0.54 \text{ pu} = j0.54 \text{ pu}$$

$$S_{\text{Load}} = 57 \angle 53.13^{\circ} \text{ MVA} \quad \left\{ \begin{array}{l} 0.6 \text{ Lag. P.F.} \end{array} \right.$$

where :-

Lag. P.F. { inductive Load }

12

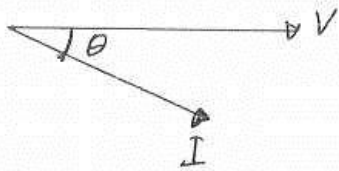

$$V = VL \angle 0 \quad ; \quad I = IL \angle -\theta$$

$$S_{3\phi} = \sqrt{3} V_{\text{line}} I_{\text{line}}^* \quad \text{or} \quad 3 V_P \hat{I}_P^*$$

$$\begin{aligned} S_{3\phi} &= \sqrt{3} V (IL \angle -\theta)^* \\ &= \sqrt{3} V IL \angle \theta = \sqrt{3} (VL \angle \theta) \end{aligned}$$


$$= \sqrt{3} (VI \cos \theta + j VI \sin \theta)$$

$$= \sqrt{3} VI \cos \theta + j \sqrt{3} VI \sin \theta$$

$$= P + jQ$$

where $P = \sqrt{3} VI \cos \theta$

$Q = \sqrt{3} VI \sin \theta$

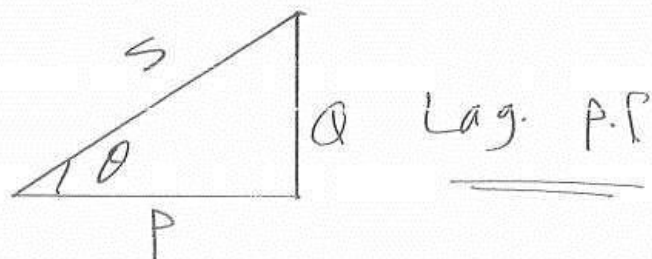

$$S = |S| \angle +\theta$$

Lag p.f. \Rightarrow


$$S_{3\phi} = 57 \angle +53.13^\circ \text{ MVA}$$

$$Z_{\text{Load actual}} = \frac{V_{L-L}^2}{S_{3\phi}} = \frac{10.45^2 \text{ kV}}{57 \angle -53.13 \text{ MVA}} = 1.1495 + j1.1532 \Omega$$

$$Z_{B \text{ Load}} = \frac{V_{B \text{ Load}}^2}{S_B} = \frac{11 \text{ kV}^2}{100 \text{ MVA}} = 1.21 \Omega$$

$$Z_{\text{Load pu}} = \frac{\text{actual}}{\text{Base}} = \frac{1.1495 + j1.1532}{1.21} = 0.95 + j1.2667 \text{ pu}$$

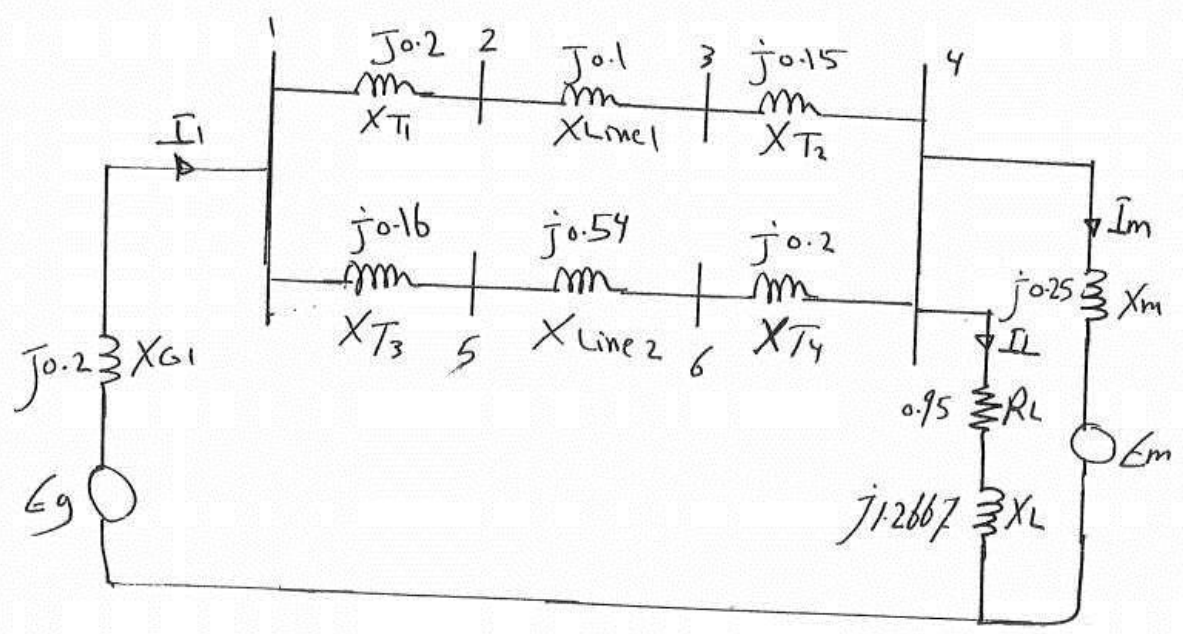The per unit equivalent ckt is shown in Fig. below



ex₂) If the motor in ex₁ operate at full-load¹⁴
 0.8 p.f Lag leading at terminal voltage
 of 10.45 kV.

- 1- Determine the voltage at the generator bus bar (bus 1)
- 2- Determine the generator and the motor internal emfs.


Sol)

The per-unit voltage at bus 4, taken as reference is

$$V_4 = \frac{\text{actual}}{\text{Base}} = \frac{10.45}{11} = 0.95 \angle 0 \text{ pu}$$


The apparent power of motor at 0.8 lead p.f
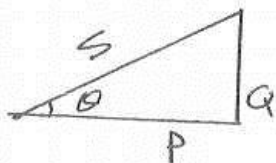
$$S_m = \frac{\text{actual}}{\text{Base}} = \frac{66.5 \angle -36.8}{100} = 0.665 \angle -36.87 \text{ pu}$$



Lag p.f

$$S = S \angle +\theta$$

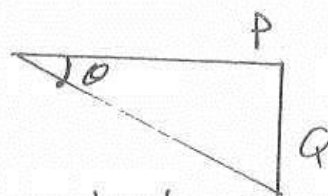

lead p.f

$$S = S \angle -\theta$$

$$S_{pu} = V_{pu} I_{pu}^*$$

The current drawn by the motor is

$$\bar{I}_m = \frac{S_m^*}{V_m^*} \quad \left\{ \text{where } S_m = V_m \bar{I}_m^* \right.$$

$$\bar{I}_m = \frac{0.665 \angle 36.87^\circ}{0.95 \angle 0^\circ} = 0.56 + j0.42 \text{ pu}$$

The current drawn by the Load is

$$\bar{I}_L = \frac{V_4}{Z_L} = \frac{0.95 \angle 0^\circ}{0.95 + j1.2667} = 0.36 - j0.48 \text{ pu}$$

The current drawn from bus 4

$$I = \bar{I}_m + \bar{I}_L = \bar{I}_1 \quad \left\{ \text{current of } G \right\}$$

$$= (0.56 + j0.42) + (0.36 - j0.48) = 0.92 - j0.06 \text{ pu}$$

The equivalent reactance of the parallel branches is


$$X = \frac{0.45 * 0.9}{0.45 + 0.9} = 0.3 \text{ pu}$$

The generator terminal voltage

$$\begin{aligned} V_1 &= V_4 + ZI \\ &= 0.95 \angle 0^\circ + j0.3(0.92 - j0.06) = 0.968 + j0.276 \\ &= 1 \angle 15.91^\circ \end{aligned}$$

$$= 1 * 22 \text{ kV} = 22 \angle 15.91^\circ \text{ kV}$$

ex 3)

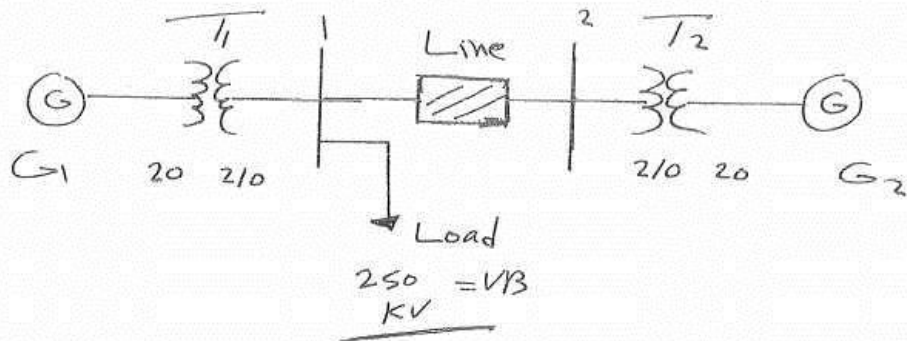

G_1	90 MVA	20 kV	$X = 0.09 \text{ pu}$
T_1	80 MVA	20/210	$X = 0.16 \text{ pu}$
T_2	80 MVA	210/20	$X = 0.2 \text{ pu}$
G_2	90 MVA	18 kV	$X = 0.06 \text{ pu}$
Line	210 kV		$X = 120 \Omega$
Load	210 kV		$S = 48 + j64$

Choose base MVA as 100 MVA and base voltage of 250 kV at the Load bus

Sol) The base voltage = 250 kV at the Load bus bar

$$V_{B_{\text{Load}}} = 250 \text{ kV}$$

$$V_{B_2} \text{ at bus } \underline{2} = 250 \text{ kV}$$

$$V_{B_{G_2}} = 250 + \left(-\frac{20}{210} \right) = 23.8 \text{ kV}$$

17

$$V_{BG1} = 250 + \left(\frac{20}{210} \right) = 23.8 \text{ kV}$$

$$X_{G1} = X_{old} \left(\frac{S_B^{new}}{S_B^{old}} \right) \left(\frac{V_B^{old}}{V_B^{new}} \right)^2$$

$$X_{G1} = 0.09 \left(\frac{100}{90} \right) \left(\frac{20}{23.8} \right)^2 = 0.0706 \text{ pu}$$

$$X_{G2} = 0.06 \left(\frac{100}{90} \right) \left(\frac{18}{23.8} \right)^2 = 0.038 \text{ pu}$$

$$X_{T1} = 0.16 \left(\frac{100}{80} \right) \left(\frac{20}{23.8} \right)^2 = 0.141 \text{ pu} \left\{ \begin{array}{l} \text{on primary} \\ \text{side} \end{array} \right.$$

OR

$$X_{T1} = 0.16 \left(\frac{100}{80} \right) \left(\frac{210}{250} \right)^2 = 0.141 \text{ pu} \left\{ \begin{array}{l} \text{on secondary} \\ \text{side} \end{array} \right.$$

$$X_{T2} = 0.2 * \left(\frac{100}{80} \right) \left(\frac{210}{250} \right)^2 = 0.176 \text{ pu} \left\{ \begin{array}{l} \text{on primary} \\ \text{side} \end{array} \right.$$

OR

$$X_{T2} = 0.2 * \left(\frac{100}{80} \right) \left(\frac{20}{23.8} \right)^2 = 0.176 \text{ pu} \left\{ \begin{array}{l} \text{on} \\ \text{secondary} \\ \text{side} \end{array} \right.$$

$$X_{B_{Line}} = \frac{V_B^2 \text{ Line}}{S_B} = \frac{250^2}{100} = 625 \text{ } \Omega$$

$$X_{pu \text{ Line}} = \frac{\text{actual}}{\text{base}} = \frac{120}{625} = 0.192 \text{ pu}$$

$$X_{\text{Load actual}} = \frac{V_{LL}^2}{S_{3\phi}^*} = \frac{210^2}{48 - j64} = 378 + j504 \text{ } \Omega \quad 188$$

$$X_{\text{Load B}} = \frac{V_{B \text{ Load}}^2}{S_B} = \frac{250^2}{100} = 625$$

$$X_{\text{pu Load}} = \frac{\text{actual}}{\text{Base}} = \frac{378 + j504}{625} = 0.6048 + j0.806 \text{ pu}$$

