

By Assist Lecturer: Besma Nazar

Digital Systems

References:-

- 1- Digital fundamentals by Floyd.
- 2- Digital Design by Morris Mano.
- 3- Digital logic cct. analysis & design by Victor p. Nelson.
- 4- Digital Design Principles & practice by John F. Wakerly.
- 5- Digital Electronics principles, Devices and Applications by Anil.



2016


1-

Number Systems :-

The study of number systems is important from the viewpoint of understanding how data are represented before they can be processed by any digital system including a digital computer.

A number system consists of an ordered set of symbols, called (digits) and the total number of digits allowed in the number system is called the (radix (r)) or (base) of the number system.

Number systems commonly used in digital system design and computer programming include decimal (r=10), binary (r=2), octal (r=8), and hexadecimal (r=16). Any number in a given system may have both an integer part and a fractional part, which are separated by a radix point (.). The place values or weights of different digits in the integer part of the number are given by r^0, r^1, r^2, r^3 and so on, starting with the digit adjacent to the radix point. For the fractional part, these are r^{-1}, r^{-2}, r^{-3} and so on, again starting with the digit next to the radix point.

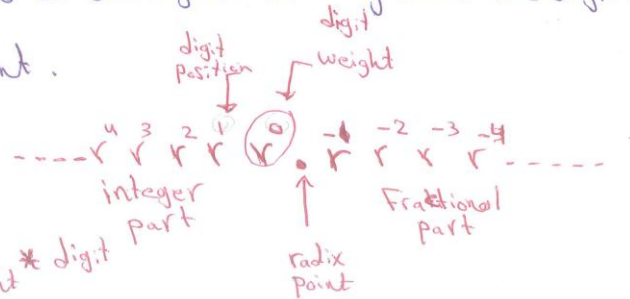


* Note =


digit value = digit weight * digit

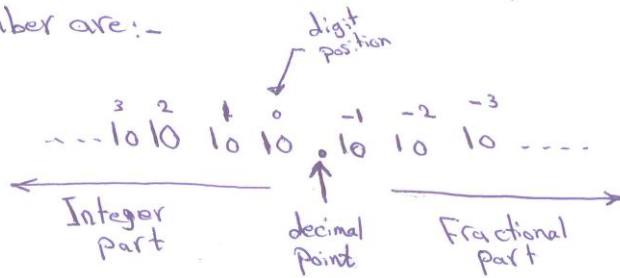1.1. Decimal Number System: —

The decimal number system is aradix (10) number system and therefore has 10 different digits or symbols. There are (0, 1, 2, 3, 4, 5, 6, 7, 8, 9). The weights of different digits in a mixed decimal number are:-



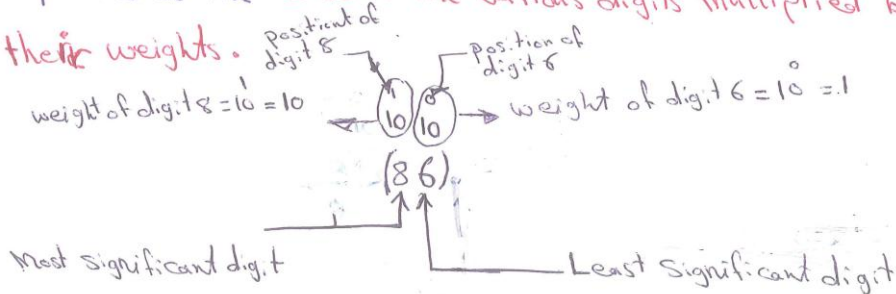The value or magnitude of a given decimal number can be expressed as the **Sum of the various digits multiplied by their weights.**



$$\begin{aligned} \text{Value of digit 8} &= 8 \times 10^1 = 8 \times 10 = 80 \\ \text{Value of digit 6} &= 6 \times 10^0 = 6 \times 1 = 6 \end{aligned} \quad \Bigg] \rightarrow 80 + 6 = 86$$

Asst. Lect: Besma Nazar.

(3)

Ex1: - Express each of the following decimal numbers as a sum of the values of each digit.

a) $(47)_{10}$

b) $(568.23)_{10}$

Solution: -

a) 47

$$\begin{matrix} 1 & 0 \\ 10 & 10 \end{matrix}$$

$$47 = 47$$

$$\begin{aligned} 47 &= (4 \times 10^1) + (7 \times 10^0) \\ &= (4 \times 10) + (7 \times 1) \\ &= 40 + 7 \end{aligned}$$

b) 568.23

$$\begin{matrix} 2 & 1 & 0 & \text{decimal} & -1 & -2 \\ 10 & 10 & 10 & \text{point} & 10 & 10 \\ & & & \downarrow & & \\ & & & 568.23 & & \end{matrix}$$

$$\begin{aligned} 568.23 &= (5 \times 10^2) + (6 \times 10^1) + (8 \times 10^0) + (2 \times 10^{-1}) + (3 \times 10^{-2}) \\ &= (5 \times 100) + (6 \times 10) + (8 \times 1) + (2 \times 0.1) + (3 \times 0.01) \\ &= 500 + 60 + 8 + 0.2 + 0.03 \end{aligned}$$

Ex2: - What weight does the digit 7 have in each of the following numbers?

a) $(7051)_{10}$

b) $(58.72)_{10}$

Solution: -

$$\begin{matrix} 3 & 2 & 1 & 0 \\ 10 & 10 & 10 & 10 \end{matrix}$$

a) -

$$\begin{matrix} 1 & 0 & 5 & 1 \\ 10 & 10 & 10 & 10 \\ 7 & 0 & 5 & 1 \\ 58.72 \end{matrix}$$


the weight of 7 is $= 10^3$

the weight of 7 is $= 10^{-1}$
 $= 0.1$

2) Binary Number System :-

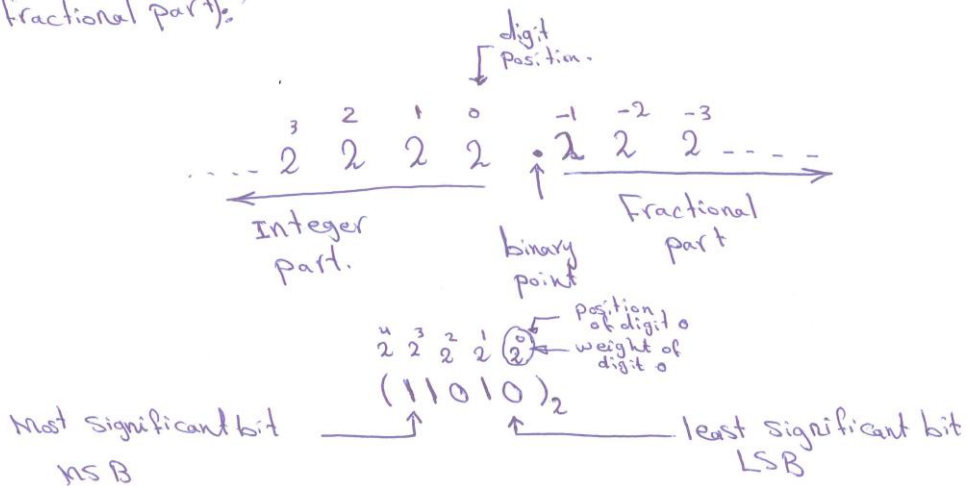(4)

The binary number system is a radix(2) number system with (0 and 1) as the two independent digits. A binary digit is called a bit. Starting from the binary point, the place values or weight of different bits in mixed binary number are $2^0, 2^1, 2^2$ and so on (for the integer part) and $2^{-1}, 2^{-2}, 2^{-3}$ and so on (for the fractional part).



$$\begin{aligned} \text{Value} &= (1 \times 2^4) + (1 \times 2^3) + (0 \times 2^2) + (1 \times 2^1) + (0 \times 2^0) \\ &= (1 \times 16) + (1 \times 8) + (0 \times 4) + (1 \times 2) + (0 \times 1) \end{aligned}$$

Note: The largest decimal number that can be represented in binary with n bits equal to $2^n - 1$.

For example :- with five bits ($n=5$) the largest decimal number

$$2^5 - 1 = 31$$

and with six bits ($n=6$)

$$\text{largest decimal number} = 2^6 - 1 = 63$$

Asst Lect: Basma Nozar.

(5)

Ex 3: - Determine the weight for the five first bits in binary system :-


Solution: -

| | | | | | |
|-------|-------|-------|-------|-------|---------|
| b_5 | b_4 | b_3 | b_2 | b_1 | bit_0 |
| 4 | 3 | 2 | 1 | 0 | |
| 2 | 2 | 2 | 2 | 2 | 2 |
| ↓ | ↓ | ↓ | ↓ | ↓ | ↓ |
| 16 | 8 | 4 | 2 | 1 | |

Ex 4: - Determine the weight of the 1 in the binary number


$(10000)_2$

Solution: -

 


Ex 5: - Determine the weight of each bit that is at in the following fractional binary number $(0.1011)_2$.

Solution: -

 

 (1-3) Octal Number System: -

The octal number system has a radix of (8) and therefore has eight distinct digits. The independent digits are (0, 1, 2, 3, 4, 5, 6, 7). The weights of different digits in mixed octal number are: -



$$\begin{array}{c} 1 \\ 8 \end{array} \begin{array}{c} \text{Position of digit } 7 \\ \text{weight of digit } 7 \end{array} \\ (27)_8$$

⑥

$$27 = (2 \times 8^1) + (7 \times 8^0) \\ \text{Value} = (2 \times 8) + (7 \times 1)$$

Note: - Counting in octal is similar to counting in decimal, except that the digits 8 and 9 are not used. To distinguish octal numbers from decimal numbers, we will use the subscript 8 to indicate an octal number. For instance, $(15)_8$, $(7)_8$, $(22)_8$. Sometime you may see an "o" or a "Q" following an octal number.

(14) Hexadecimal Number System: -

The hexadecimal number system is radix (16) number system and its 16 basic digits are (0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F).

The first ten digits are borrowed from the decimal system. The letters A, B, C, D, E, F are used for digits 10, 11, 12, 13, 14, 15 respectively.

The weights of different digits in a mixed hexadecimal number are

$$\begin{array}{ccccccc} \dots & 3 & 2 & 1 & 0 & -1 & -2 & -3 & \dots \\ \dots & 16 & 16 & 16 & 16 & 16 & 16 & 16 & \dots \\ \leftarrow & & & & & \uparrow & & & \rightarrow \\ \text{Integer} & & & & & \text{hexadecimal} & & & \text{Fractional} \\ \text{point} & & & & & \text{point} & & & \text{point} \end{array}$$

$$\begin{array}{cccc} 2 & 1 & 0 & -1 \\ 16 & 16 & 16 & 16 \\ (FD4.E)_{16} \end{array}$$

$$\begin{aligned} &= (F \times 16^2) + (D \times 16^1) + (4 \times 16^0) + (E \times 16^{-1}) \\ &= (15 \times 16^2) + (13 \times 16^1) + (4 \times 16^0) + (14 \times 16^{-1}) \\ &= (15 \times 256) + (13 \times 16) + (4 \times 1) + (14 \times 0.0625) \end{aligned}$$

Asst Lect. : Besma Nazar.

⑦

Note: - To avoid confusion hexadecimal numbers with decimal number or another numbers we will use the subscript 16 to indicate hexadecimal numbers. Sometimes you may see an "h" following a hexadecimal number.

H.w1: - What weight does the digit 0 have in each of the following numbers ?

a) $(51.03)_{10}$

b) $(11011)_2$

c) $(703 \cdot 12)_8$

d) $(F2E.10A)_{16}$.

H.w2: - How many bits are required to represent the following decimal numbers ?

a) 17

b) 49

c) 114

d) 205

2. Conversion between Systems: -

(8)

1. Finding the Decimal Equivalent: -

The decimal equivalent of a given number in another number system is given by the sum of all the digits multiplied by their respective weights. The integer and fractional parts of the given number should be treated separately. Binary to decimal, octal to decimal and hexadecimal to decimal conversions are illustrated below: -

2.1 Binary to Decimal Conversion: -

Ex 6: Convert the following binary numbers to decimal: -

- a) 11001 b) 110.001 c) 0.111

Solution: -

$$\begin{aligned} \text{a) } (11001)_2 &\rightarrow (25)_{10} \\ &\begin{array}{cccccc} 2^4 & 2^3 & 2^2 & 2^1 & 2^0 & \\ & & & & & 2^{-1} \\ & & & & & 2^{-2} \\ & & & & & 2^{-3} \\ & & & & & 2^{-4} \\ & & & & & 2^{-5} \end{array} \\ &\quad 1 \ 1 \ 0 \ 0 \ 1 \\ &\quad (1 \times 2^4) + (1 \times 2^3) + (0 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) \\ &\quad (1 \times 16) + (1 \times 8) + (0 \times 4) + (0 \times 2) + (1 \times 1) = (25)_{10} \end{aligned}$$

$$\begin{aligned} \text{b) } (110.001)_2 &\rightarrow (6.125)_{10} \\ &\begin{array}{cccccc} 2^2 & 2^1 & 2^0 & 2^{-1} & 2^{-2} & 2^{-3} \\ & & & & & 2^{-4} \\ & & & & & 2^{-5} \\ & & & & & 2^{-6} \\ & & & & & 2^{-7} \end{array} \\ &\quad 1 \ 1 \ 0 . \ 0 \ 0 \ 1 \\ &\quad (1 \times 2^2) + (1 \times 2^1) + (0 \times 2^0) + (0 \times 2^{-1}) + (0 \times 2^{-2}) + (1 \times 2^{-3}) \\ &\quad (1 \times 4) + (1 \times 2) + (0 \times 1) + (0 \times 0.5) + (0 \times 0.25) + (1 \times 0.125) \\ &\quad = (6.125)_{10} \end{aligned}$$

$$\begin{aligned} \text{c) } (0.111)_2 &= (0.875)_{10} \\ &\begin{array}{cccc} 2^{-1} & 2^{-2} & 2^{-3} & 2^{-4} \\ & & & 2^{-5} \\ & & & 2^{-6} \\ & & & 2^{-7} \end{array} \\ &\quad 0 . \ 1 \ 1 \ 1 \\ &\quad (0 \times 2^0) + (1 \times 2^{-1}) + (1 \times 2^{-2}) + (1 \times 2^{-3}) \\ &\quad = (0 \times 1) + (1 \times 0.5) + (1 \times 0.25) + (1 \times 0.125) = (0.875)_{10} \end{aligned}$$

2.2: Octal-to-Decimal Conversion:-

(9)

Ex. 7:- Convert the following octal number to decimal:-

a) $(73)_8$

b) $(31.6)_8$

Solution:-

a) $(73)_8 \rightarrow (59)_{10}$

$\begin{matrix} 1 & 0 \\ 8 & 8 \end{matrix}$

$7 \quad 3$

$(7 \times 8^1) + (3 \times 8^0)$

$(7 \times 8) + (3 \times 1) = (59)_{10}$

b) $(31.6)_8 \rightarrow (25.75)_{10}$

$\begin{matrix} 1 & 0 & -1 \\ 8 & 8 & 8 \end{matrix}$

$3 \quad 1 \quad 6$

$(3 \times 8^1) + (1 \times 8^0) + (6 \times 8^{-1})$

$(3 \times 8) + (1 \times 1) + (6 \times 0.125) = (25.75)_{10}$

2.3: Hexadecimal-to-Decimal Conversion:-Ex. 8:- Convert the following hexadecimal numbers to decimal:-

a) $(1C)_{16}$

b) $(F5.AB85)_{16}$

Solution:-

a) $(1C)_{16} \rightarrow (28)_{10}$

$\begin{matrix} 1 & 0 \\ 16 & 16 \end{matrix}$

$1 \quad C$

$(1 \times 16^1) + (C \times 16^0)$

$(1 \times 16) + (12 \times 1) = (28)_{10}$

b) $(F5.AB85)_{16} \rightarrow (245.67)_{10}$

$\begin{matrix} 1 & 0 & -1 & -2 & -3 & -4 \\ 16 & 16 & 16 & 16 & 16 & 16 \end{matrix}$

$F \quad 5 \quad A \quad B \quad 8 \quad 5$

$(F \times 16^1) + (5 \times 16^0) + (A \times 16^{-1}) + (B \times 16^{-2}) + (8 \times 16^{-3}) + (5 \times 16^{-4})$

$(15 \times 16) + (5 \times 1) + (10 \times 0.0625) + (11 \times 0.0039) + (8 \times 0.00024) + (5 \times 0.000015)$

$= (245.67)_{10}$

H.w.:- Convert the following numbers to decimal:- (10)

- a) $(1001.0101)_2$ b) $(137.21)_8$ c) $(1E0.2A)_{16}$

3. Decimal-to-Binary Conversion:-

There are two ways to convert from a decimal number to a binary number:-
 (3-1) Sum of weights methods
 (3-2) Repeated division by 2 method.

(3-1) Sum of weights method:-

Exq.:- Convert the following decimal numbers to binary:-

- a) $(12)_{10}$ b) $(0.625)_{10}$ c) $(1.25)_{10}$

Solution:-

a) $(12)_{10} \rightarrow (1100)_2$

| | | | | | |
|---|----|---|---|---|---|
| | 4 | 3 | 2 | 1 | 0 |
| | 2 | 2 | 2 | 2 | 2 |
| ∴ | 16 | 8 | 4 | 2 | 1 |
| | | 1 | 1 | 0 | 0 |

$(1 \times 8) + (1 \times 4) = (12)_{10}$

b) $(0.625)_{10} \rightarrow (0.101)_2$

| | | | | |
|--|---|-----|------|-------|
| | 0 | -1 | -2 | -3 |
| | 2 | 0.5 | 0.25 | 0.125 |
| | 0 | 1 | 0 | 1 |

$(1 \times 0.5) + (1 \times 0.125) = (0.625)_{10}$

c) $(1.25)_{10} \rightarrow (1.01)_2$

| | | | |
|--|---|-----|------|
| | 0 | -1 | -2 |
| | 2 | 0.5 | 0.25 |
| | 1 | 0 | 1 |


$(1 \times 1) + (1 \times 0.25) = (1.25)_{10}$

3-2:- Repeated division by 2-method:-


Ex.10:- Convert the following decimal numbers to binary:-

- a) $(2)_{10}$ c.) $(0.625)_{10}$ d.) $(1.25)_{10}$ b) $(41)_{10}$


e) $(123.61)_{10}$

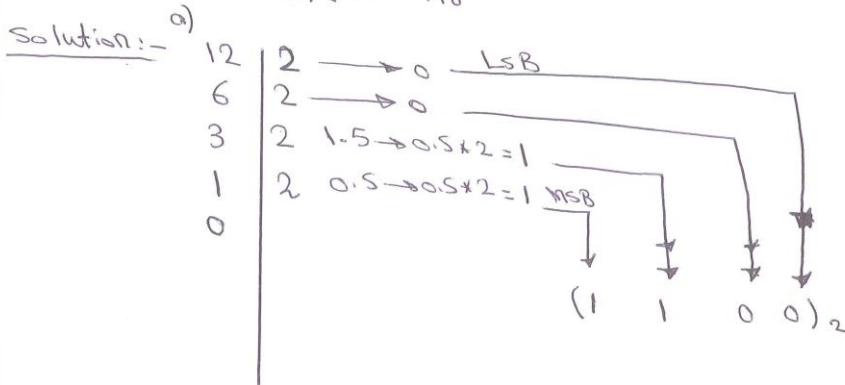


b) $(41)_{10} \rightarrow (101001)_2$

 


c) $(0.625)_{10} \rightarrow (0.101)_2$

 

d) $(1.25)_{10} \rightarrow (1.01)_2$

 

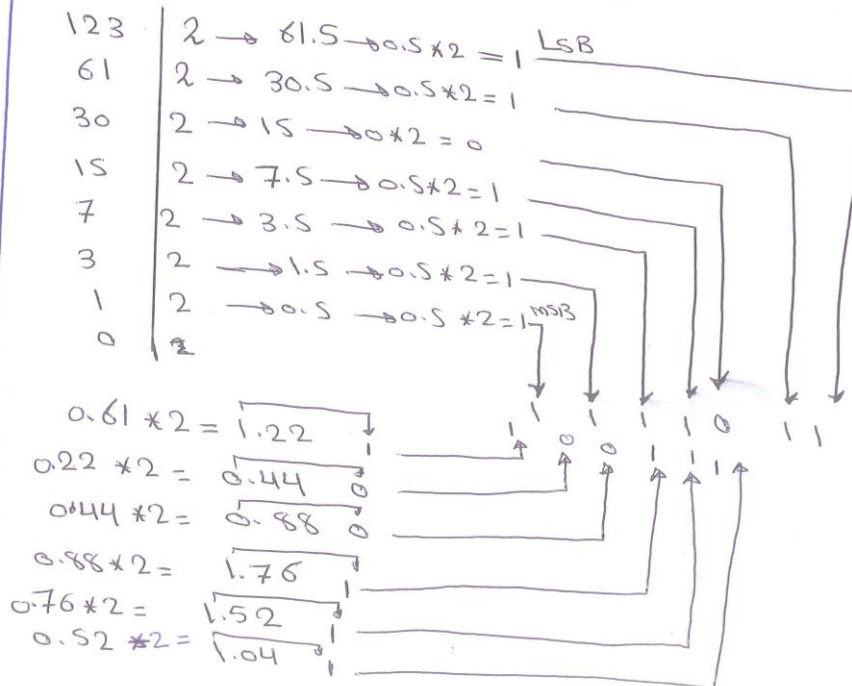e) $(123.61)_{10} \rightarrow (1111011.100111)_2$



4-Decimal-to-Octal Conversion:-

There are two ways to convert from decimal to octal:-

(4.1) Sum of weights methods

(4.2) Repeated Division by 8.

4.1:- Sum of weights method:-

Ex 1.1:- Convert the following decimal numbers to octal:-

a) 14

b) 12.25

Solution:-

$$a) (14)_{10} \rightarrow (16)_8$$

$$1 \times 8^1$$

$$6 \times 8^0$$

$$1 \times 8^0$$

$$(1 \times 8) + (6 \times 1) = (14)_{10}$$

$$b) (12.25)_{10} \rightarrow (14.2)_8$$

$$2 \times 8^2 + 4 \times 8^1 + 2 \times 8^0 = 128 + 32 + 2 = 162$$

$$1 \times 8^1 + 4 \times 8^0 = 8 + 4 = 12$$

$$1 \times 8^0 + 4 \times 8^{-1} = 1 + 0.5 = 1.5$$

$$(1 \times 8) + (4 \times 1) + (2 \times 0.125) = (12.25)_{10}$$

4.2:- Repeated Division by 8:-


Ex 1.2:- Convert the following decimal number to octal:-

a) 14

b) 12.25

Solution:-

$$\begin{array}{r|l} 14 & 8 \rightarrow 1.75 \rightarrow 0.75 \times 8 = 6 \\ 1 & 8 \rightarrow 0.125 \rightarrow 0.125 \times 8 = 1 \\ 0 & \end{array}$$

 

$$b) (12.25)_{10} \Rightarrow (14.2)_8$$

$$\begin{array}{r|l} 12 & 8 \rightarrow 1.5 \\ 1 & 8 \rightarrow 0.125 \\ 0 & \end{array} \quad \begin{array}{l} 0.5 \times 8 \rightarrow 4 \\ 0.125 \times 8 \rightarrow 1 \end{array} \quad \begin{array}{l} \text{LSD} \\ \text{MSD} \\ \downarrow \\ 4 \end{array}$$

$$0.25 \times 8 = 2$$

5- Decimal to Hexadecimal Conversion:-

There are two ways to convert from decimal to hexadecimal:

(5-1) Sum of weights method.

(5-2) Repeated Division by 16.

(5-1) Sum of weights method:-

Ex 13:- Convert the following decimal numbers to hexadecimal:

a) $(650)_{10}$

b) $(213.0625)_{10}$

Solution:-

a) $(650)_{10} \rightarrow (28A)_{16}$

$$\begin{array}{r} 2 \quad 1 \quad 0 \\ 16 \quad 16 \quad 16 \\ 256 \quad 16 \quad 1 \\ (2 \quad 8 \quad A)_{16} \\ (2 \times 256) + (8 \times 16) + (A \times 1) \\ (2 \times 256) + (8 \times 16) + (10 \times 1) = (650)_{10} \end{array}$$

b) $(213.0625)_{10} \rightarrow (D5.1)_{16}$

$$\begin{array}{r} 1 \quad 0 \quad -1 \\ 16 \quad 16 \quad 16 \\ 16 \quad 1 \quad 0.0625 \\ (D \quad 5 \quad 1)_{16} \\ (16 \times D) + (5 \times 1) + (1 \times 0.0625) \\ (16 \times 13) + (5 \times 1) + (1 \times 0.0625) = (213.0625)_{10} \end{array}$$

(5-2) Repeated Division by 16:-

(15)


(Ex.14) Convert the following decimal numbers to hexadecimal:-

a) $(650)_{10}$



b) $(245.67)_{10}$

Solution:-

a) $(650)_{10} \rightarrow (28A)_{16}$

 

  b) $(245.67)_{10} \rightarrow (F5.AB85)_{16}$



H.w:- Convert each of the following decimal numbers to binary, octal and hexadecimal numbers by using

(a) sum of weight method and (b) Repeated of division

(a) 27

(b) 915

(c) 0.375

(d) 0.65

(e) 174.25

(f) 250.8

6. Binary - Octal and Octal - Binary Conversions :-

An octal number can be converted into binary equivalent by replacing each octal digit with its three-bit binary equivalent because the $(8 = 2^3)$. A binary number can be converted into an equivalent octal number by splitting the integer and fractional parts into groups of three bits, starting from binary point on both sides. The 0s can be added to complete the outside groups if needed.

Ex 15 :- Convert each of the following Octal numbers to Binary

a) $(13)_8$ (b) $(7526)_8$ (c) $(1.52)_8$

Solution :-

(a) $(13)_8 \rightarrow (1011)_2$

$$\begin{array}{c} 13 \\ \uparrow \uparrow \\ \text{---} 001 \ 011 \\ \downarrow \downarrow \end{array}$$

(b) $(7526)_8 \rightarrow (111101010110)_2$

$$\begin{array}{c} 7526 \\ \downarrow \downarrow \downarrow \downarrow \\ 111 \ 101 \ 010 \ 110 \end{array}$$

(c) $(1.52)_8 \rightarrow (1.10101)_2$

$$\begin{array}{c} 1.52 \\ \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \\ \text{---} 001 \ . \ 10101 \end{array}$$


Table (1)
Octal / Binary Conversion

| Octal Digit | Binary |
|-------------|--------|
| 0 | 000 |
| 1 | 001 |
| 2 | 010 |
| 3 | 011 |
| 4 | 100 |
| 5 | 101 |
| 6 | 110 |
| 7 | 111 |


Ex. 16: - Convert each of the following binary number to Octal (17)

 - a) $(110101)_2$ b) $(11010000100)_2$ c) $(1110100.0100111)_2$
 d) $(110101.1)_2$ e) $(10101.001)_2$


Solution: - a) $(110101)_2 \rightarrow (65)_8$



 
b) $(11010000100)_2 \rightarrow (3204)_8$



 
c) $(1110100.0100111)_2 \rightarrow (164.234)_8$



d) $(110101.1)_2 \rightarrow (65.1)_8$

 

e) $(10101.001)_2 \rightarrow (25.1)_8$

 


7- Hex - Binary and Binary - Hex Conversions: -

A hexadecimal number can be converted into its binary equivalent by replacing each hex digit with its four-bit binary equivalent because the $(16 = 2^4)$. A binary number can be converted into an equivalent hexadecimal number by splitting the integer and fractional parts into groups of four bits starting from the binary point on both sides. The 0s can be added to complete the outside groups if needed.

Ex 17:- Convert each of the following hexadecimal numbers to binary: - (18)

 - a) $(10A4)_{16}$ b) $(CF8E)_{16}$ c) $(2B.A)_{16}$

Solution:- a) $(10A4)_{16} \rightarrow (100010101000)_2$



b) $(CF8E)_{16} \rightarrow (1100111110001110)_2$


 


Table 2: Hex/Binary Conv.

| Hex digit | Binary Digit |
|-----------|--------------|
| 0 | 0000 |
| 1 | 0001 |
| 2 | 0010 |
| 3 | 0011 |
| 4 | 0100 |
| 5 | 0101 |
| 6 | 0110 |
| 7 | 0111 |
| 8 | 1000 |
| 9 | 1001 |
| A | 1010 |
| B | 1011 |
| C | 1100 |
| D | 1101 |
| E | 1110 |
| F | 1111 |

c) $(2B.A)_{16} \rightarrow (101011.101)_2$

 

Ex 18:- Convert the following binary numbers to hexadecimal:-

- a) $(110010101010111)_2$ b) $(1111100010110101)_2$
 c) $(101100011011.1111010)_2$

Solution:- a) $(110010101010111)_2 \rightarrow (CA57)_{16}$

b) $(1111100010110101)_2 \rightarrow (3F169)_{16}$

c) $(101100011011.1111010)_2 \rightarrow (2C6B.F2)_{16}$

8. Hex-Octal and Octal to Hex Conversions:-

(19)

For hexadecimal-octal conversion, the given hex number is firstly converted into its binary equivalent which is further converted into its octal equivalent.

Hex number \rightarrow Binary number \rightarrow Octal number

For octal-hexadecimal conversion, the octal number may first be converted into equivalent binary number and then the binary number transformed into its hex equivalent.

Octal number \rightarrow Binary number \rightarrow Hex number

Ex. 19:- Find the octal equivalent of $(2F.C4)_{16}$ and the hex equivalent of $(762.013)_8$.

Solution:- $(2F.C4)_{16} \rightarrow (0010\ 1111.1100\ 0100)_2 \rightarrow (57.62)_8$
 $(762.013)_8 \rightarrow (0111\ 1010.000\ 001\ 011)_{000} \rightarrow (F2.058)_{16}$

(H.w) (1):- Convert the following binary numbers to octal, hexadecimal and decimal numbers:-

a) $(1101)_2$ b) $(0.101)_2$ c) $(0.01101)_2$ d) $(10101.11)_2$

(H.w) (2):- Convert the following octal numbers to binary, hexadecimal and decimal numbers:-

a) $(65)_8$ b) $(240.51)_8$ c) $(2000)_8$ d) $(177777)_8$

(H.w) (3):- Convert each of the following hexadecimal numbers to binary, octal and decimal numbers:-

a) $(4F)_{16}$ b) $(F8.A7)_{16}$ c) $(2000)_{16}$ d) $(2064)_{16}$

Arithmetic operation: $\begin{matrix} \nearrow \text{Addition} \\ \searrow \text{Subtraction} \end{matrix}$

1. Addition: -

(a) Binary Addition: -

The basic rules of binary addition are as follows: -

- ① $0+0=0$
- ② $0+1=1$
- ③ $1+0=1$
- ④ $1+1=0$ with a carry of 1 to the next most significant bit.
- ⑤ $1+1+1=1$ with a carry of 1 to the next most significant bit.

Ex: - Add the following binary numbers: -

- a) $11+11$ b) $100+10$ c) $111+11$ d) $110+100$

Solution: - a) $11+11=(110)_2$

$$\begin{array}{r} ① \\ 11 \\ + \\ 11 \\ \hline (110)_2 \end{array}$$

b) $100+10=(110)_2$

$$\begin{array}{r} 100 \\ + \\ 010 \\ \hline (110)_2 \end{array}$$

c) $111+11=(1010)_2$

$$\begin{array}{r} ① \quad ① \\ 111 \\ + \\ 011 \\ \hline (1010)_2 \end{array}$$

d) $110+100=(1010)_2$

$$\begin{array}{r} 110 \\ + \\ 100 \\ \hline (1010)_2 \end{array}$$

(B) Octal Addition: - 1) If the sum result ≥ 8 , subtract 8 and carry 1

Ex: - Add the following numbers: -

a) $(57)_8 + (432)_8$

b) $(4163)_8 + (7520)_8$

Solution: - a) $(57)_8 + (432)_8 = (511)_8$

$$\begin{array}{r} \text{Carry} \rightarrow 0 \text{ } 0 \\ \text{Carry} \rightarrow 0 \text{ } 57 \\ \underline{432} + \\ (511)_8 \end{array}$$

b) $(4163)_8 + (7520)_8 = (13703)_8$

$$\begin{array}{r} 0 \\ 4163 \\ \underline{7520} + \\ (13703)_8 \end{array}$$

(C) Hexadecimal Addition: - 1) A=10, B=11, C=12, D=13, E=14, F=15
2) If the sum result ≥ 16 , subtract 16 and carry 1

Ex: - Add the following numbers: -

a) $(58)_{16} + (4B)_{16}$

b) $(2A58)_{16} + (71D0)_{16}$

Solution: - a) $(58)_{16} + (4B)_{16} = (A3)_{16}$

$$\begin{array}{r} 0 \\ 58 \\ \underline{4B} + \\ (A3)_{16} \end{array}$$

b) $(2A58)_{16} + (71D0)_{16} = (9C28)_{16}$

$$\begin{array}{r} 0 \\ (2A58) \\ \underline{(71D0)} + \\ (9C28)_{16} \end{array}$$

(H.w): - Add the following numbers: -

a) $(110101)_2 + (11001)_2$

b) $(175214)_8 + (152405)_8$

c) $(4F1A5)_{16} + (88D5)_{16}$

Complements:—

Complement are used in digital computer for simplifying the subtraction operation and for logical manipulation. There are two types of complements for each base- r system. The first is referred to as the r 's complement and the second as the $(r-1)$'s complement.

1- Binary Number Complements:—

In the binary number system we have the 1's and 2's complements.

The 1's complement of a binary number is obtained by replacing 0s with 1s and 1s with 0s.

$$\begin{array}{l} 0 \rightarrow 1 \\ 1 \rightarrow 0 \end{array}$$

For example, the 1's complement of $(10010110)_2$ is $(01101001)_2$

The 2's complement of a binary number is obtained by adding 1's to its 1's complement. or right to left copy bits through 1st logic 1, then invert. $2's \text{ complement} = 1's \text{ complement} + 1$

For example, the 2's complement of $(10010110)_2$ is $(01101010)_2$

Ex:— Find the 1's complement of the following numbers:—

a) $(1011000)_2$

b) $(0101101)_2$

solution:—

a) $\begin{array}{r} 1011000 \\ \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \text{1's} \\ (0100111)_2 \text{ complement} \end{array}$

b) $\begin{array}{r} 0101101 \\ \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \text{1's} \\ (1010010)_2 \text{ complement} \end{array}$

Ex:- Find the 2^s Complement of the following numbers -

a) $(1011010100)_2$

b) $(1101101001)_2$

Solution:- a) $(1011010100)_2$

First method $2^s = 1^s + 1$

1st complement = 0100101011

2^s complement = $(0100101100)_2$

~~XXXXXXXXXX~~

Second method:-
 $\begin{array}{ccccccc} & \xrightarrow{\text{1's complement}} & & \xrightarrow{\text{unchange}} & & & \\ 1 & 0 & 1 & 1 & 0 & 1 & 0 & 1 & 0 & 0 \\ & \downarrow & & & \downarrow & & & & & \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 & 0 & 1 & 1 \\ & & & & & & & & & \downarrow \\ & & & & & & & & & 0 \end{array}$

b) $(1101101001)_2$

First method = $2^s = 1^s + 1$

1^s complement = 0010010110

2^s complement = $(0010010111)_2$

Second method:-
 $\begin{array}{ccccccc} & \xrightarrow{\text{1's complement}} & & \xrightarrow{\text{unchange}} & & & \\ 1 & 1 & 0 & 1 & 1 & 0 & 1 & 0 & 0 & 1 \\ & \downarrow & & & \downarrow & & & & & \\ 0 & 0 & 1 & 0 & 0 & 1 & 0 & 1 & 1 & 0 \\ & & & & & & & & & \downarrow \\ & & & & & & & & & 1 \end{array}$

2- Decimal numbers Complements:-

In the Decimal number system we have the 9^s and 10^s complements.

The 9^s complement of a given decimal number is obtained by subtracting each digit from 9.

For example:- Find the 9^s complement of $(2496)_{10}$

$$\begin{array}{r} 9999 \\ - 2496 \\ \hline 7503 \end{array}$$

9^s complement $(7503)_{10}$

The 10^s Complement is obtained by adding '1' to the 9^s complement.

10^s complement = 9^s complement + 1

(24)

For example: Find the 10's complement of $(2496)_{10}$

$$\begin{array}{r} 9999 \\ 2496 \\ \hline 9's \text{ complement} \rightarrow 7503 \\ \phantom{9's \text{ complement}} \\ \phantom{9's \text{ complement}} \\ \phantom{9's \text{ complement}} \\ \hline 10's \text{ complement} (7504)_{10} \end{array}$$

Ex:- Find the 9's and 10's complement of the following numbers:-

a) $(546700)_{10}$ b) $(012398)_{10}$

Solution:- a) $(546700)_{10}$ b) $(012398)_{10}$

$$\begin{array}{r} 999999 \\ 546700 - \\ \hline 9's \text{ comp. } (453299)_{10} \\ \phantom{9's \text{ comp.}} \phantom{(453299)_{10}} \\ \phantom{9's \text{ comp.}} \phantom{(453299)_{10}} \\ \hline 10's \text{ comp. } (453300)_{10} \end{array} \quad \begin{array}{r} 999999 \\ 012398 - \\ \hline 9's \text{ comp. } (987601)_{10} \\ \phantom{9's \text{ comp.}} \phantom{(987601)_{10}} \\ \phantom{9's \text{ comp.}} \phantom{(987601)_{10}} \\ \hline 10's \text{ comp. } (987602)_{10} \end{array}$$

3- Octal number Complements:-

In the octal system, we have the 7's and 8's complements.

The 7's complement of a given octal number is obtained by subtracting each octal digit from 7.

For example: the 7's complement of $(562)_8$ would be:-

$$\begin{array}{r} 777 \\ 562 - \\ \hline 7's \text{ complement } (215)_8 \end{array}$$

The 8's complement is obtained by adding 1 to the 7's complement.

$$\boxed{8's \text{ complement} = 7's \text{ complement} + 1}$$

For example: the 8's complement of $(562)_8$ would be:-

$$\begin{array}{r} 777 \\ 562 - \\ \hline 7's \text{ comp. } (215)_8 \\ \phantom{7's \text{ comp.}} \\ \phantom{7's \text{ comp.}} \\ \hline 8's \text{ comp. } (216)_8 \end{array}$$

Ex:- Find the 7's and 8's complement for the following

Number :- $(6572)_8$

Solution :-

$$\begin{array}{r} 7777 \\ 6572 - \\ \hline 7's \text{ complement } (1205)_8 \\ \phantom{7's \text{ complement }} + \\ \hline 8's \text{ complement } (1206)_8 \end{array}$$

4- Hexadecimal Number Complements:- $A=10; B=11; C=12$
 $D=13; E=14; F=15$

The 15's and 16's complements are defined with respect to the hexadecimal number system.

The 15's complement is obtained by subtracting each hex digit from 15. For example:- the 15's complement of $(3BF)_{16}$ would be

$$\begin{array}{r} 15 \ 15 \ 15 \\ 3 \ B \ F - \\ \hline (C \ 4 \ 0)_{16} \end{array}$$

The 16's complement is obtained by adding '1' to the 15's complement

$$\boxed{16's \text{ complement} = 15's \text{ complement} + 1}$$

For example: the 16's complement of $(2AE)_{16}$ would be

$$\begin{array}{r} 15 \ 15 \ 15 \\ 2 \ A \ E - \\ \hline 15's \text{ complement } (D \ 5 \ 1)_{16} \\ \phantom{15's \text{ complement }} \phantom{(D \ 5 \ 1)_{16}} + \\ \hline 16's \text{ complement } (D \ 5 \ 2)_{16} \end{array}$$

Ex:- Find the 15's and 16's complement of the following numbers:-

$$\begin{array}{r} \text{ABF8} \\ 15 \ 15 \ 15 \ 15 \\ A \ B \ F \ 8 - \\ \hline 15's \text{ complement } (5 \ 4 \ 0 \ 7)_{16} \\ \phantom{15's \text{ complement }} \phantom{(5 \ 4 \ 0 \ 7)_{16}} + \\ \hline 16's \text{ complement } (5 \ 4 \ 0 \ 8)_{16} \end{array}$$

2- Subtraction:-

The direct method of subtraction through in elementary schools uses the borrow concept. This method, works well when people perform subtraction with paper and pencil. However, when subtraction is implemented with digital H/W, the method is less efficient than the method that uses complements.

The subtraction of two r -digit numbers $M-N$ can be done as follows: \leftarrow

1- If we use $(r-1)$'s complement [1's, 9's, 7's, 15's]: \leftarrow

a) For $M-N$, if $M \geq N$, the sum produce an end carry which can be added to the sum and this is referred to as an end around carry.

b) For $M-N$, if $M < N$, the sum does not produce an end carry and to obtain the answer in a familiar form, take the $(r-1)$'s complement of the sum and place a negative sign in front.

2- If we use r 's complement [2's, 10's, 8's, 16's]: \leftarrow

a) For $M-N$, if $M \geq N$, the sum produce an end carry which can be discarded ~~and~~

b) For $M-N$, if $M < N$, the sum does not produce an end carry and to obtain the answer in familiar form, take the r 's complement of the sum and place a negative sign in front.

Ex: Subtract the following binary number by use 1's and 2's

Complement :-

a) $(1010100)_2 - (1000011)_2$

b) $(1000011)_2 - (1010100)_2$

Solution:-
use 1's complement

use 2's complement

a) $(1010100)_2 - (1000011)_2$

$$\begin{array}{r}
 1010100 \\
 - 1000011 \\
 \hline
 011100 \\
 + 011100 \\
 \hline
 10010000 \\
 \text{cy} \rightarrow 1 \\
 \hline
 \text{result} = (0010001)_2
 \end{array}$$

$$\begin{array}{r}
 1010100 \\
 - 1000011 \\
 \hline
 011100 \\
 + 011101 \\
 \hline
 10010001 \\
 \text{2's comp} \rightarrow \\
 \hline
 \text{result} = (0010001)_2
 \end{array}$$

b) $(1000011)_2 - (1010100)_2$

use 1's complement

use 2's complement

$$\begin{array}{r}
 1000011 \\
 - 1010100 \\
 \hline
 0101011 \\
 + 0101011 \\
 \hline
 1101110 \\
 \text{1's comp} \rightarrow \\
 + 0010001 \\
 \text{add (1)} \rightarrow \\
 \hline
 \text{result} = -(0010001)_2
 \end{array}$$

$$\begin{array}{r}
 1000011 \\
 - 1010100 \\
 \hline
 0101011 \\
 + 0101011 \\
 \hline
 1101110 \\
 \text{2's comp} \rightarrow \\
 + 0010001 \\
 \text{add (1)} \rightarrow \\
 \hline
 \text{result} = -(0010001)_2
 \end{array}$$

Ex:- Using 9's and 10's Complement subtract:-

a) $(72532)_{10} - (3250)_{10} =$ b) $(3250)_{10} - (72532)_{10}$

Solution:-

a) $(72532)_{10} - (3250)_{10}$

9's complement

$$\begin{array}{r}
 \xrightarrow{\text{9's comp.}} \quad 72532 \\
 \quad \quad \quad 03250 - \\
 \hline
 \quad \quad \quad 72532 \\
 \text{9's comp.} \quad \rightarrow \quad 96749 + \\
 \hline
 \quad \quad \quad 169281 \\
 \text{cy} \quad \quad \quad \rightarrow \quad 1 + \\
 \hline
 \text{result} = (69282)_{10}
 \end{array}$$

10's complement

$$\begin{array}{r}
 \xrightarrow{\text{10's comp.}} \quad 72532 \\
 \quad \quad \quad 03250 - \\
 \hline
 \quad \quad \quad 72532 \\
 \text{10's comp.} \quad \rightarrow \quad 96750 + \\
 \hline
 \quad \quad \quad 69282 \\
 \text{cy} \quad \quad \quad \rightarrow \quad 1 + \\
 \hline
 \text{result} = (69282)_{10}
 \end{array}$$

b) $(3250)_{10} - (72532)_{10}$

9's complement

$$\begin{array}{r}
 \xrightarrow{\text{9's comp.}} \quad 03250 \\
 \quad \quad \quad 72532 - \\
 \hline
 \quad \quad \quad 03250 \\
 \text{9's comp.} \quad \rightarrow \quad 27467 + \\
 \hline
 \quad \quad \quad 30717 \\
 \text{9's comp.} \quad \rightarrow \quad 69282 \\
 \text{add (-)} \quad \rightarrow \quad -(69282)_{10} \\
 \hline
 \text{result} = -(69282)_{10}
 \end{array}$$

10's complement

$$\begin{array}{r}
 \xrightarrow{\text{10's comp.}} \quad 03250 \\
 \quad \quad \quad 72532 - \\
 \hline
 \quad \quad \quad 03250 \\
 \text{10's comp.} \quad \rightarrow \quad 27468 + \\
 \hline
 \quad \quad \quad 30718 \\
 \text{10's comp.} \quad \rightarrow \quad (69282) \\
 \text{add (-)} \quad \rightarrow \quad -(69282)_{10} \\
 \hline
 \text{result} = -(69282)_{10}
 \end{array}$$

Ex:- Subtract the following octal number by use 7's and 8's complement. -

a) $(256)_8 - (341)_8$

Solution:- 7's complement

$$\begin{array}{r}
 256 \\
 341 - \\
 \hline
 0256 \\
 7's \text{ comp. } \rightarrow 436 + \\
 \hline
 714 \\
 7's \text{ comp. } \rightarrow 063 \\
 \text{add(-)} \rightarrow -(63)_8 \\
 \hline
 \text{result} = -(63)_8
 \end{array}$$

8's complement

$$\begin{array}{r}
 256 \\
 341 - \\
 \hline
 0256 \\
 8's \text{ comp. } \rightarrow 437 + \\
 \hline
 705 \\
 8's \text{ comp. } \rightarrow 063 \\
 \text{add(-)} \rightarrow -(63)_8 \\
 \hline
 \text{result} = -(63)_8
 \end{array}$$

Ex:- Subtract the following hexadecimal number by use 15's and 16's complement:-

a) $(592)_{16} - (3A5)_{16}$

Solution:- 15's complement

$$\begin{array}{r}
 592 \\
 3A5 - \\
 \hline
 592 \\
 15's \text{ comp. } \rightarrow C5A + \\
 \hline
 11EC \\
 \rightarrow 1 + \\
 \hline
 \text{result} = (1ED)_{16}
 \end{array}$$

16's complement

$$\begin{array}{r}
 592 \\
 3A5 - \\
 \hline
 592 \\
 16's \text{ comp. } \rightarrow C5B + \\
 \hline
 1ED \\
 \text{cy } \times \text{ but } \\
 \hline
 \text{result} = (1ED)_{16}
 \end{array}$$

Ex: Subtract the following number by use 1's and 2's

complement:-

a) $(-3)_{10} + (4)_{10}$ b) $(-3)_{10} + (+4)_{10}$

Solution:-

a) $(-3)_{10} + (4)_{10}$

1's Complement

$$\begin{array}{r}
 \text{Binary } \rightarrow 011 \\
 \text{1's comp.} \rightarrow 100 \\
 \hline
 \begin{array}{r}
 -3 \\
 4 + \\
 \hline
 011 \\
 100 \\
 \hline
 1000 \\
 \text{cy } \rightarrow 1 + \\
 \hline
 \text{result} = (001)_2
 \end{array}
 \end{array}$$

2's Complement

$$\begin{array}{r}
 \text{Binary } \rightarrow 011 \\
 \text{2's comp.} \rightarrow 101 \\
 \hline
 \begin{array}{r}
 -3 \\
 4 + \\
 \hline
 011 \\
 100 \\
 \hline
 101 \\
 100 \\
 \hline
 \text{cy } \rightarrow 001 \\
 \text{result} = (001)_2
 \end{array}
 \end{array}$$

b) $(-3)_{10} + (-4)_{10}$

1's Complement

$$\begin{array}{r}
 \text{Binary } \rightarrow 0011 \\
 \text{1's comp.} \rightarrow 1100 \\
 \hline
 \begin{array}{r}
 -3 \\
 -4 + \\
 \hline
 0011 \\
 0100 \\
 \hline
 1100 \\
 1000 \\
 \hline
 10111 \\
 \text{1's comp.} = 0111 \\
 \text{result} = -(1111)
 \end{array}
 \end{array}$$

2's Complement

$$\begin{array}{r}
 \text{Binary } \rightarrow 0011 \\
 \text{2's comp.} \rightarrow 1100 \\
 \hline
 \begin{array}{r}
 -3 \\
 -4 + \\
 \hline
 0011 \\
 0100 \\
 \hline
 1101 \\
 1100 \\
 \hline
 11001 \\
 \text{2's comp.} = 0111 \\
 \text{result} = -(1111)
 \end{array}
 \end{array}$$

H.W: Find the following:-

a) $(1001001)_2 - (101110)_2$ using 1's & 2's complement.

b) $(341)_8 - (256)_8$ using 7's & 8's complement.

c) $(9F1B)_{16} - (4A36)_{16}$ using 15's & 16's complement.

d) $(-18)_6 + (-37)_{10}$ using 1's & 2's complement.

Binary Codes:-

Codes have been used for security reasons, so that others will not be able to read the message. There are many types of codes, each one of them have 4-bits, but the weight must be chosen in such a way that these sums is not greater than 15 and less than 9.

BCD (8421) code:-

The binary coded decimal (BCD) is a type of binary code used to represent a given decimal number in an equivalent binary form. BCD-to-decimal and decimal-to-BCD conversions are very easy and straightforward. The BCD equivalent of a decimal number is written by replacing each decimal digit in integer and fractional parts with its four-bit binary equivalent. Table below gives the four bit code for one decimal digits:-

| Decimal Symbol | BCD digit 8 4 2 1 |
|----------------|----------------------|
| 0 | 0 0 0 0 |
| 1 | 0 0 0 1 |
| 2 | 0 0 1 0 |
| 3 | 0 0 1 1 |
| 4 | 0 1 0 0 |
| 5 | 0 1 0 1 |
| 6 | 0 1 1 0 |
| 7 | 0 1 1 1 |
| 8 | 1 0 0 0 |
| 9 | 1 0 0 1 |

- Note:-
- ① It is important to realize that BCD numbers are decimal numbers and not binary numbers although they use bits in their representation.
 - ② It is unable to decode binary numbers greater than 9. (The binary combination 1000 through 1111 are not used and have no meaning in the BCD code) because the decimal system do not have greater than 9.

(33)

Ex:- Convert each of the following decimal numbers to BCD code:

a) $(185)_{10}$ b) $(23.15)_{10}$ c) $(2469)_{10}$

Solution:- a) $(185)_{10}$
 $(0001\ 1000\ 0101)_{BCD}$

b) $(23.15)_{10}$
 $(0010\ 0011 . 0001\ 0101)_{BCD}$

c) $(2469)_{10}$
 $(0010\ 0100\ 0110\ 1001)_{BCD}$

Ex:- Convert each of the following BCD codes to decimal:
 *(H.w) and binary

a) $(0011\ 0101\ 0001)_{BCD}$ b) $(0010\ 1001 . 0111\ 0101)_{BCD}$

Solution:- a) $(0011\ 0101\ 0001)_{BCD} \rightarrow (351)_{10}$
 $\downarrow \quad \downarrow \quad \downarrow$
 3 5 1

b) $(0010\ 1001 . 0111\ 0101)_{BCD} \rightarrow (29.75)_{10}$
 $\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$
 2 9 . 7 5

H.w:- Convert the following decimal number to BCD code and binary number:

a) 171.625 b) 171

- Other Decimal Codes:-

Many different codes can be formulated by arranging four bits into 16 distinct combinations. The representative codes are shown in table below.

Each code uses only 10 out of a possible 16-bit combinations that can be arranged with four bits. The other six unused combinations have no meaning and should be avoided.

| Decimal digit | 2421 [*] | 84-2-1 | 7421 | 6311 | 5421 | 4221 | Excess-3 |
|---------------|-------------------|--------|------|-------|------|-------|----------|
| 0 | 0000 | 0000 | 0000 | 0000 | 0000 | 0000 | 0011 |
| 1 | 0001 | 0111 | 0001 | 0001 | 0001 | 0001 | 0100 |
| 2 | 0010 | 0110 | 0010 | 0010 | 0010 | 0010 | 0101 |
| 3 | 0011 | 0101 | 0011 | 0100 | 0011 | 0011 | 0110 |
| 4 | 0100 | 0100 | 0100 | 0110* | 0100 | 1000 | 0111 |
| 5 | 0101 | 1011 | 0101 | 0111 | 1000 | 0111* | 1000 |
| 6 | 1100 | 1010 | 0110 | 1000 | 1001 | 1100 | 1001 |
| 7 | 1101 | 1001 | 1000 | 1001 | 1010 | 1101 | 1010 |
| 8 | 1110 | 1000 | 1001 | 1011 | 1011 | 1110 | 1011 |
| 9 | 1111 | 1111 | 1010 | 1100 | 1100 | 1111 | 1100 |

Note:- (1) The BCD and the 2421 codes are weighted codes. In weighted codes, each position is assigned a weighting factor in such a way that each digit can be evaluated by adding the weights to all the 1's in the coded combination. The 84-2-1 code is an example of assigning both positive and negative weights to decimal code:-

$(6)_{10} = (0110)_{BCD} = (0 \times 8) + (1 \times 4) + (1 \times 2) + (0 \times 1)$
 $(7)_{10} = (1101)_{2421} = (2 \times 1) + (4 \times 1) + (2 \times 0) + (1 \times 1)$
 $(2)_{10} = (0110)_{84-2-1} = (8 \times 0) + (4 \times 1) + (-2 \times 1) + (-1 \times 0)$

(2) The EX-3 code is a digital code obtained by adding three to each decimal digit and then converting the result to 4 bit binary. It is unweight code. It is example of self-complementing codes. The 9's complement is obtained directly by changing 1's to 0's and 0's to 1 in the code. $(395)_{10} \rightarrow (0110 \ 1100 \ 1000)_{EX3}$
 $(604)_{10} \rightarrow (1001 \ 0011 \ 0111)_{EX3}$

Ex: - Convert the following decimal numbers: -

(35)

a) $(16)_{10} \rightarrow 8421$ code

b) $(7)_{10} \rightarrow 2421$ code

c) $(395)_{10} \rightarrow \text{EX-3}$ code.

Solution: -

a) $(16)_{10} \rightarrow (0001\ 0110)_{8421}$

b) $(7)_{10} \rightarrow (1101)_{2421}$

c) $(395)_{10} \rightarrow (0110\ 1100\ 1000)_{\text{EX-3}}$

H.W: - Write the following decimal number in 4221 and 5421 codes
 $(98.16)_{10}$


Gray Code: -

The Gray code is unweighted and is not an arithmetic code; that is, there are no specific weights assigned to the bit positions. The important feature of the Gray code is that it exhibits only a single bit change from one code word to the next in sequence. This property is important in many applications, such as shaft position encoders, where error susceptibility increases with the number of bits changes between adjacent numbers in a sequence. Like binary numbers, the Gray code can have any number of bits. In going from decimal 3 to decimal 4, the Gray code changes from 0010 to 0110 while the binary code change from 0011 to 0100, a change of three bits.

 a) Binary to Gray code Conversion: -

The MSB in the Gray code is the same as the corresponding MSB in the binary number. Going from left to right, add each adjacent pair of binary code bit to get the next Gray code bit. Discard carries.


Ex:- Convert the binary number (10110) to Gray code:-



 b) Gray to Binary Conversion:-

The MSB in the binary code is the same as the corresponding bit in the Gray code. Add each binary bit generated to the Gray code bit in the next adjacent position. Discard carries.

Ex:- Convert the Gray code (11011) to binary:-



H.w(1): List the 4-bit Gray code for decimal numbers from 0 to 15.

- H.w(2):
- (a) Convert binary 101101 to Gray code
 - (b) Convert Gray code 100111 to binary.

Logic Gates:-


Circuits used to process digital signals are called (logic gates).

Logic symbols are used to identify these ccts. The seven gates that are the fundamental logic elements in digital system are shown below:-

| Logic Function | Logic gate symbol | Truth table | Boolean Expression | | | | | | | | | | | | |
|-----------------------------------------------------|-------------------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------|---|--------|---|----|---------------|----|---|----|---|-------------------------------------------------------|---|---------------|
| 1- Inverter or NOT | | <table border="1"> <tr><td colspan="2">input</td><td>output</td></tr> <tr><td>A</td><td></td><td>F = \bar{A}</td></tr> <tr><td>0</td><td></td><td>1</td></tr> <tr><td>1</td><td></td><td>0</td></tr> </table> | input | | output | A | | F = \bar{A} | 0 | | 1 | 1 | | 0 | $F = \bar{A}$ |
| input | | output | | | | | | | | | | | | | |
| A | | F = \bar{A} | | | | | | | | | | | | | |
| 0 | | 1 | | | | | | | | | | | | | |
| 1 | | 0 | | | | | | | | | | | | | |
| 2- AND | | <table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>0</td></tr> <tr><td>01</td><td>0</td></tr> <tr><td>10</td><td>0</td></tr> <tr><td>11</td><td>1</td></tr> </table> | AB | F | 00 | 0 | 01 | 0 | 10 | 0 | 11 | 1 | $F = A \cdot B$ <small>AND ('·')</small> | | |
| AB | F | | | | | | | | | | | | | | |
| 00 | 0 | | | | | | | | | | | | | | |
| 01 | 0 | | | | | | | | | | | | | | |
| 10 | 0 | | | | | | | | | | | | | | |
| 11 | 1 | | | | | | | | | | | | | | |
| 3- NAND (AND-NOT) | | <table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>1</td></tr> <tr><td>01</td><td>1</td></tr> <tr><td>10</td><td>1</td></tr> <tr><td>11</td><td>0</td></tr> </table> | AB | F | 00 | 1 | 01 | 1 | 10 | 1 | 11 | 0 | $F = \overline{A \cdot B}$ <small>OR ('+')</small> | | |
| AB | F | | | | | | | | | | | | | | |
| 00 | 1 | | | | | | | | | | | | | | |
| 01 | 1 | | | | | | | | | | | | | | |
| 10 | 1 | | | | | | | | | | | | | | |
| 11 | 0 | | | | | | | | | | | | | | |
| 4- OR | | <table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>0</td></tr> <tr><td>01</td><td>1</td></tr> <tr><td>10</td><td>1</td></tr> <tr><td>11</td><td>1</td></tr> </table> | AB | F | 00 | 0 | 01 | 1 | 10 | 1 | 11 | 1 | $F = A + B$ <small>EX-OR ('⊕')</small> | | |
| AB | F | | | | | | | | | | | | | | |
| 00 | 0 | | | | | | | | | | | | | | |
| 01 | 1 | | | | | | | | | | | | | | |
| 10 | 1 | | | | | | | | | | | | | | |
| 11 | 1 | | | | | | | | | | | | | | |
| 5- NOR (OR-NOT) | | <table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>1</td></tr> <tr><td>01</td><td>0</td></tr> <tr><td>10</td><td>0</td></tr> <tr><td>11</td><td>0</td></tr> </table> | AB | F | 00 | 1 | 01 | 0 | 10 | 0 | 11 | 0 | $F = \overline{A + B}$ <small>EX-NOR ('⊙')</small> | | |
| AB | F | | | | | | | | | | | | | | |
| 00 | 1 | | | | | | | | | | | | | | |
| 01 | 0 | | | | | | | | | | | | | | |
| 10 | 0 | | | | | | | | | | | | | | |
| 11 | 0 | | | | | | | | | | | | | | |
| 6- Exclusive OR EX-OR (XOR) | | <table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>0</td></tr> <tr><td>01</td><td>1</td></tr> <tr><td>10</td><td>1</td></tr> <tr><td>11</td><td>0</td></tr> </table> | AB | F | 00 | 0 | 01 | 1 | 10 | 1 | 11 | 0 | $F = A \oplus B$ $= AB' + A'B$ | | |
| AB | F | | | | | | | | | | | | | | |
| 00 | 0 | | | | | | | | | | | | | | |
| 01 | 1 | | | | | | | | | | | | | | |
| 10 | 1 | | | | | | | | | | | | | | |
| 11 | 0 | | | | | | | | | | | | | | |
| 7- Exclusive NOR EX-NOR (EX-OR-NOT) (XNOR) | | <table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>1</td></tr> <tr><td>01</td><td>0</td></tr> <tr><td>10</td><td>0</td></tr> <tr><td>11</td><td>1</td></tr> </table> | AB | F | 00 | 1 | 01 | 0 | 10 | 0 | 11 | 1 | $F = A \odot B$ $= AB + A'B'$ | | |
| AB | F | | | | | | | | | | | | | | |
| 00 | 1 | | | | | | | | | | | | | | |
| 01 | 0 | | | | | | | | | | | | | | |
| 10 | 0 | | | | | | | | | | | | | | |
| 11 | 1 | | | | | | | | | | | | | | |











Note:- $A \oplus B = \overline{A \odot B}$
 $A \odot B = \overline{A \oplus B}$

 Ex:- Write the boolean algebra expression of the following ccts:-



Universal Gates:-

          NAND and NOR gates have the property that they indivi. dually can be used to hardware-implement a logic circuit corresponding to any given Boolean expression. That is, it is possible to use either only NAND gates or only NOR gates to implement any Boolean expression.



Ex: - Implement the following Functions by using NAND gates only:-


a) $F_1 = A\bar{B} + \bar{A}B\bar{C}$

b) $F_2 = AB + C\bar{D}$

Solution:- Mixed gates

a)


$F_1 = A\bar{B} + \bar{A}B\bar{C}$

 

Mixed gates


NAND gates

 $F_1 = \overline{\overline{A\bar{B} + \bar{A}B\bar{C}}}$
 $F_1 = \overline{A\bar{B}} \cdot \overline{\bar{A}B\bar{C}}$




NAND gates

b) $F_2 = AB + C\bar{D}$

 

 $F_2 = \overline{\overline{AB + C\bar{D}}}$
 $F_2 = \overline{AB} \cdot \overline{C\bar{D}}$



1- NOT gate $F_1 = \overline{A} \cdot A$

2- AND gate $F_2 = \overline{\overline{AB}} = \overline{\overline{A} + \overline{B}}$

3- NAND gate $F_3 = \overline{AB} = \overline{A} + \overline{B}$

4- OR gate $F_4 = \overline{\overline{A+B}}$

5- EX-OR:- $F_5 = \overline{AB + \bar{A}\bar{B}}$
 $= \overline{AB} \cdot \overline{\bar{A}\bar{B}}$
 $= \overline{A}\bar{B} + A\bar{B}$

6- EX-NOR = $\overline{F_5}$




Ex: - Implement following function by using NOR gates only:-

$$F = (A + \bar{B}) \cdot (\bar{A} + c)$$

Solution: -

Mixed gates

 
$$F = (A + \bar{B}) \cdot (\bar{A} + c)$$



NOR gates

$$F = \overline{\overline{(A + \bar{B}) \cdot (\bar{A} + c)}}$$
 
$$F = \overline{(A + \bar{B}) + (\bar{A} + c)}$$



Combinational logic circuits:-

Digital systems are composed of combinations of logic gates described by a truth table and Boolean expression or logic symbol diagram. In combination logic, the output of the circuit depends only on the inputs to the circuit.

- De Morgan's Theorem:-

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

Laws and Rules of boolean algebra:-

- 1- $A+B = B+A$
- 2- $AB = BA$] \rightarrow Commutative Laws
- 3- $A+(B+C) = (A+B)+C$
- 4- $A(BC) = (AB)C$] \rightarrow Associative Laws
- 5- $A(B+C) = AB+AC$ \rightarrow Distributive Law.

- 6- $A+0 = A$
- 7- $A+1 = 1$
- 8- $A+A = A$
- 9- $A+\bar{A} = 1$
- 10- $A \cdot 0 = 0$
- 11- $A \cdot 1 = A$
- 12- $A \cdot A = A$
- 13- $A \cdot \bar{A} = 0$
- 14- $A'' = A$
- 15- $A+AB = A$

Prove:- $A+AB$
 $A(1+B) = A$

16- $A(A+B) = A$
Prove:- $A \cdot A + AB$
 $A + AB$
 $A(1+B) = A$

17- $A+BC = (A+B)(A+C)$
Prove:- Take the left side:-

$$\begin{aligned}
 (A+B)(A+C) &= AA+AC+AB+BC \\
 &= A+AC+AB+BC \\
 &= A(1+C)+AB+BC \\
 &= A+AB+BC \\
 &= A(1+B)+BC \\
 &= A+BC
 \end{aligned}$$

$$18 - A + \bar{A}B = A + B$$

Prove:- $A + \bar{A}B$

$$\underline{(A + \bar{A})} (A + B) = A + B$$

Simplification Using Boolean Algebra:-

Many times in the application of Boolean algebra, you have to reduce a particular expression to its simplest form. A simplified Boolean expression uses the fewest gates possible to implement a given expression.

Ex:- Using Boolean algebra techniques, simplify the following ^{Functions.} expressions:

a) $AB + A(B+C) + B(B+C)$ b) $A\bar{B} + A(\overline{B+C}) + B(\overline{B+C})$

Solution:- a) $AB + A(B+C) + B(B+C)$ c) $[A\bar{B}(C+BD) + A'B']C$

$$F = AB + AB + AC + BB + BC$$

$$F = AB + AC + \underline{B} + \underline{BC}$$

$$F = AB + AC + B(\underline{1+C})$$

$$F = \underline{AB} + AC + \underline{B}$$

$$F = B(\underline{A+1}) + AC$$

$$F = B + AC$$

b) $A\bar{B} + A(\overline{B+C}) + B(\overline{B+C})$

$$F = A\bar{B} + A(\bar{B} \cdot \bar{C}) + B(\bar{B} \cdot \bar{C})$$

$$F = A\bar{B} + A\bar{B} + A\bar{C} + \underline{B\bar{B}} + B\bar{C}$$

$$F = A\bar{B} + A\bar{C} + B\bar{C}$$

c) $[A\bar{B}(C+BD) + A'B']C$

$$F = [A\bar{B}C + A\bar{B}BD + A'B']C$$

$$F = [A\bar{B}C + A'B']C$$

$$F = A\bar{B}C + A'B'C$$

$$F = A\bar{B}C + A'B'C$$

$$F = B'C(\underline{A + A'})$$

$$F = B'C$$

H.w. :- Simplify the following Boolean expressions:-

$$a) \overline{A} \overline{B} C + \overline{(A+B+\overline{C})} + \overline{A} \overline{B} C' D$$

$$b) ABCD + AB(\overline{CD}) + \overline{(AB)} CD$$

- Standard form of Boolean expressions:-

All Boolean expressions, regardless of their form, can be converted into either of two standard forms:-

1. The sum of products (SOP)

2. The product of sum (POS)

Standardization makes the evaluation, simplification, and implementation of Boolean expressions much more systematic and easier.

1. The Sum of Products (SOP):-

SOP is a term consisting of the product of literals (variables) or their complements, when two or more product terms are summed by Boolean addition. A sum of products expression is also known as a minterm expression. It can be obtained from the truth table directly by considering those input combinations that produce a logic 1 at the output.

Ex:- $AB + \overline{A}BC' + AB \rightarrow \text{SOP}$

Ex:- Convert the Boolean expression to SOP form:-

a) $F = (A+B)(B+C+D)$

b) $\overline{(A+B)+c}$

Solution:- a) $F = AB + AC + AD + BB + BC + BD$

$$b) \overline{(A+B)+c} = \overline{AB+c} = (\overline{A+B}) \cdot \overline{c} \\ = \overline{(A+B)} \overline{c} \\ = \overline{A} \overline{c} + \overline{B} \overline{c}$$

Note: ① Canonical or standard form of Boolean expressions is an Expanded form of Boolean expression where each term contains all Boolean variables in their true or complemented form and is obtained by including all possible combinations of missing variables.

② In SOP to convert it to standard SOP form we ANDed it misses one or more variables with an expression such as $(X + \bar{X})$ where X is one of the missing variables.

Ex: - Convert the following Boolean expression in to standard SOP form: -

$$F = A\bar{B}C + \bar{A}\bar{B} + AB\bar{C}D$$

$$F = A\bar{B}C(D + \bar{D}) + \bar{A}\bar{B}(C + \bar{C})(D + \bar{D}) + AB\bar{C}D$$

$$F = A\bar{B}CD + A\bar{B}C\bar{D} + \bar{A}\bar{B}(CD + C\bar{D} + \bar{C}D + \bar{C}\bar{D}) + AB\bar{C}D$$

$$F = A\bar{B}CD + A\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + AB\bar{C}D$$

Ex: - Put F in SOP form and simplify it using Boolean algebra and theorem and then implement this function: -

| | A | B | F | |
|-------|---|---|---|------------------|
| m_0 | 0 | 0 | 1 | $\bar{A}\bar{B}$ |
| m_1 | 0 | 1 | 1 | $\bar{A}B$ |
| m_2 | 1 | 0 | 0 | |
| m_3 | 1 | 1 | 1 | AB |

$$\begin{array}{l} 0 \rightarrow \bar{X} \\ 1 \rightarrow X \end{array} \left] \leftarrow \text{in SOP} \right.$$

$$F = \sum m_0, m_1, m_3$$


$$F = \sum 0, 1, 3$$

$$F = \bar{A}\bar{B} + \bar{A}B + AB$$

$$F = \bar{A}(\bar{B} + B) + AB$$

$$F = \bar{A} + AB$$

$$F = \bar{A} + B$$

 

Ex:- List the truth table of the function, and then implement it using NAND gate only:-

$$F = AB + BC + \bar{A}\bar{B}C$$

Solution:- $F = AB + BC + \bar{A}\bar{B}C$

$$F = AB(C + \bar{C}) + BC(A + \bar{A}) + \bar{A}\bar{B}C$$

$$F = \underline{ABC} + \underline{ABC\bar{C}} + \underline{ABC} + \underline{\bar{A}BC} + \underline{\bar{A}\bar{B}C}$$

$$F = \overset{111}{\underline{ABC}} + \overset{110}{\underline{ABC\bar{C}}} + \overset{011}{\underline{\bar{A}BC}} + \overset{001}{\underline{\bar{A}\bar{B}C}}$$

| ABC | F |
|-----|---|
| 000 | 0 |
| 001 | 1 |
| 010 | 0 |
| 011 | 1 |
| 100 | 0 |
| 101 | 0 |
| 110 | 1 |
| 111 | 1 |

$$F = \sum 1, 3, 6, 7$$


$$F = ABC + ABC\bar{C} + \bar{A}BC + \bar{A}\bar{B}C$$

$$F = AB[C + \bar{C}] + \bar{A}C[B + \bar{B}]$$

$$F = AB + \bar{A}C$$

$$F = \overline{\overline{AB + \bar{A}C}}$$
 
$$F = \overline{\bar{A}B \cdot \bar{A}C}$$



(H.w): Develop a truth table for the following sop expression:-

$$F = \bar{X} + Y\bar{Z} + WZ + X\bar{Y}Z$$

(H.w): Convert the following expressions to standard sop forms:-

a) $AB(\bar{B}\bar{C} + BD)$ b) $A + B[AC + (B + \bar{C})D]$

2- The Product of Sums (POS):-

POS is a term consisting of the sum (Boolean adding) of literal (variable) or their complements, when two or more sum are multiplied. A product of sum is also known as a maxterm expression. It can be obtained from the truth table by considering these input combinations that produce a logic 0 at the output.

Ex:- $F = (\bar{A} + B)(A + \bar{B} + C) \rightarrow \text{POS}$

Ex:- Convert the following Boolean expression to standard POS form:-

$F = (A + \bar{B} + C)(\bar{B} + C + \bar{D})(\bar{A} + \bar{B} + \bar{C} + D)$

Note:- In POS to convert it to standard POS form use ORed it misses one or more variables with an expression such as $(X\bar{X})$ where is one of the missing variables

Solution:- $F = (A + \bar{B} + C + D\bar{D})(\bar{B} + C + \bar{D} + A\bar{A})(\bar{A} + \bar{B} + \bar{C} + D)$

$F = (A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + \bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{C} + D)$

Ex:- Represent F in POS form then simplify using theorem and implement it:-

| | A | B | C | F |
|----------------|---|---|---|---|
| M ₀ | 0 | 0 | 0 | 0 |
| M ₁ | 0 | 0 | 1 | 1 |
| M ₂ | 0 | 1 | 0 | 1 |
| M ₃ | 0 | 1 | 1 | 1 |
| M ₄ | 1 | 0 | 0 | 0 |
| M ₅ | 1 | 0 | 1 | 1 |
| M ₆ | 1 | 1 | 0 | 1 |
| M ₇ | 1 | 1 | 1 | 1 |

0 → X
1 → \bar{X}] in POS

$F = \prod M_{0,4}$

$F = \prod 0,4$

$F = (A + B + C)(\bar{A} + \bar{B} + \bar{C})$

$F = \underline{A}\bar{A} + \underline{A}B + \underline{A}C + \bar{A}\underline{B} + \underline{B}\bar{B} + \underline{B}C + \bar{A}\underline{C} + \underline{B}\bar{C} + \underline{C}\bar{C}$

$F = \underline{A}B + \underline{A}C + \bar{A}\underline{B} + \underline{B}C + \bar{A}\underline{C} + \underline{B}\bar{C} + \underline{C}$

$F = B(A + \bar{A} + 1 + C) + C(A + \bar{A} + C)$

$F = B + C$



Note: - The complement of standard sop minterms equals the sum of minterms missing from the original function which are equal the standard pos maxterms.

$$\text{POS maxterm} = \overline{\text{SOP minterm}}$$

$$\text{SOP minterm} = \overline{\text{POS maxterm}}$$

Ex:- $F = \sum (1, 4, 5, 6, 7)$
 $\bar{F} = \sum 0, 2, 3 = \prod 0, 2, 3$

Ex:- $F = \prod (0, 2, 4, 5)$
 $\bar{F} = \sum (1, 3, 6, 7)$

Ex:- Convert the following sop expression to an equivalent pos expression:-

a) $F = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC$

$$F = \sum 0, 2, 3, 5, 7$$

$$F = \prod 1, 4, 6$$

$$F = (A+B+\bar{C})(\bar{A}+B+C)(\bar{A}+\bar{B}+C)$$

b) $F = w\bar{x}y + \bar{x}y\bar{z} + wx\bar{y}$

$$F = w\bar{x}y(z+\bar{z}) + \bar{x}y\bar{z}(w+\bar{w}) + wx\bar{y}(z+\bar{z})$$

$$F = \begin{matrix} w\bar{x}yZ & w\bar{x}y\bar{Z} & w\bar{x}yZ & \bar{w}\bar{x}y\bar{Z} & w\bar{x}yZ & w\bar{x}y\bar{Z} \\ \begin{matrix} 1011 \\ 1010 \\ 1001 \\ 1000 \end{matrix} & \begin{matrix} 1010 \\ 1000 \end{matrix} & \begin{matrix} 1010 \\ 1000 \end{matrix} & \begin{matrix} 0010 \\ 0000 \end{matrix} & \begin{matrix} 1101 \\ 1100 \end{matrix} & \begin{matrix} 1100 \\ 1100 \end{matrix} \end{matrix}$$

$$F = \sum 2, 10, 11, 12, 13$$

$$F = \prod 1, 3, 4, 5, 6, 7, 8, 9, 14, 15, 0$$

$$F = (w+x+y+\bar{z})(w+\bar{x}+\bar{y}+\bar{z})(w+\bar{x}+y+\bar{z})(w+\bar{x}+\bar{y}+\bar{z})(w+\bar{x}+\bar{y}+\bar{z}) \\ (\bar{w}+\bar{x}+\bar{y}+\bar{z})(\bar{w}+\bar{x}+y+\bar{z})(\bar{w}+\bar{x}+\bar{y}+\bar{z})(\bar{w}+\bar{x}+\bar{y}+\bar{z})(\bar{w}+\bar{x}+\bar{y}+\bar{z}) \\ (\bar{w}+\bar{x}+y+\bar{z})$$

Karnaugh Maps (K-map):

The K-map is simply another form of a truth table and is easiest method for simplifying logical expression and, if properly used, will produce the simplest SOP or POS expression possible. A logic function containing n variables requires 2^n rectangles.

Notes:-

1- The main thing to remember is that only one variable can be change between adjacent rectangles when moving in a horizontal or a vertical direction. This is because that the minterms are not arranged in binary sequence but in sequence similar to Gray code and the characteristic of this sequence is that only one bit changes from $1 \rightarrow 0$ or from $0 \rightarrow 1$ in the listing sequence.

2- The logic expression obtained from K-map must be in the easiest form and cannot be simplified more.

Type of K-map:-

1- Two Variables:-

$$F = (A, B)$$

msB \uparrow \downarrow LSB

$$\begin{aligned} \text{No. of cells} &= 2^n \\ &= 2^2 \\ &= 4 \end{aligned}$$

$$0 \rightarrow 3$$

| | | |
|-----------|-----------|---|
| B/A | \bar{A} | A |
| \bar{B} | 0 | 2 |
| B | 1 | 3 |

2- Three Variables:-

$F = (A, B, C)$
 msB \uparrow \leftarrow LSB
 No. of cells = 2^3
 = 8
 0 \rightarrow 7

| | | | | |
|-----------|-------------------------|-------------------|-------------------|-------------|
| AB | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB |
| C | 00 | 01 | 11 | 10 |
| \bar{C} | $\bar{A}\bar{B}\bar{C}$ | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $\bar{A}BC$ |
| 0 | 0 | 2 | 6 | 4 |
| C | $\bar{A}Bc$ | $\bar{A}B\bar{c}$ | ABc | $AB\bar{c}$ |
| 1 | 1 | 3 | 7 | 5 |

3- Four Variables:-

$F = (A, B, C, D)$
 msB \uparrow \leftarrow LSB
 No. of cells = 2^4
 = 16
 0 \rightarrow 15

| | | | | |
|------------------|--------------------------------|--------------------------|--------------------------|--------------------|
| AB | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB |
| CD | 00 | 01 | 11 | 10 |
| $\bar{C}\bar{D}$ | $\bar{A}\bar{B}\bar{C}\bar{D}$ | $\bar{A}\bar{B}C\bar{D}$ | $\bar{A}B\bar{C}\bar{D}$ | $\bar{A}BC\bar{D}$ |
| 00 | 0 | 4 | 12 | 8 |
| $\bar{C}D$ | $\bar{A}B\bar{C}D$ | $\bar{A}BCD$ | $AB\bar{C}D$ | $ABC\bar{D}$ |
| 01 | 1 | 5 | 13 | 9 |
| $C\bar{D}$ | $\bar{A}BcD$ | $\bar{A}B\bar{c}D$ | $ABcD$ | $AB\bar{c}D$ |
| 11 | 3 | 7 | 15 | 11 |
| $C\bar{D}$ | $\bar{A}BC\bar{D}$ | $\bar{A}Bc\bar{D}$ | $ABc\bar{D}$ | $AB\bar{c}\bar{D}$ |
| 10 | 2 | 6 | 14 | 10 |

4- Five Variables:-

$F = (A, B, C, D, E)$
 msB \uparrow \leftarrow LSB
 No. of cells = 2^5
 = 32
 0 \rightarrow 31

| | | | | | | | | |
|------------------|-------------------------|-------------------|-------------------|-------------|-------------------|-------------|-------------|-------|
| ABC | $\bar{A}\bar{B}\bar{C}$ | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $\bar{A}BC$ | $A\bar{B}\bar{C}$ | $A\bar{B}C$ | $AB\bar{C}$ | ABC |
| DE | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| $\bar{D}\bar{E}$ | 000 | 4 | 12 | 8 | 24 | 28 | 20 | 16 |
| $\bar{D}E$ | 01 | 1 | 5 | 13 | 9 | 25 | 21 | 17 |
| $D\bar{E}$ | 11 | 3 | 7 | 15 | 11 | 27 | 23 | 19 |
| DE | 10 | 2 | 6 | 14 | 10 | 26 | 22 | 18 |

5- Six Variables:-

$F = (A, B, C, D, E, F)$
 msB \uparrow \leftarrow LSB
 No. of cells = 2^6
 = 64
 0 \rightarrow 63

| | | | | | | | | |
|-------------------------|-------------------------|-------------------|-------------------|-------------|-------------------|-------------|-------------|-------|
| ABC | $\bar{A}\bar{B}\bar{C}$ | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $\bar{A}BC$ | $A\bar{B}\bar{C}$ | $A\bar{B}C$ | $AB\bar{C}$ | ABC |
| DEF | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| $\bar{D}\bar{E}\bar{F}$ | 000 | 8 | 24 | 16 | 48 | 56 | 40 | 32 |
| $\bar{D}\bar{E}F$ | 001 | 1 | 9 | 25 | 17 | 49 | 57 | 33 |
| $\bar{D}E\bar{F}$ | 011 | 3 | 11 | 27 | 19 | 51 | 59 | 35 |
| $\bar{D}EF$ | 010 | 2 | 10 | 26 | 18 | 50 | 58 | 34 |
| $D\bar{E}\bar{F}$ | 110 | 6 | 18 | 30 | 22 | 54 | 62 | 38 |
| $D\bar{E}F$ | 111 | 7 | 15 | 31 | 23 | 55 | 63 | 39 |
| $DE\bar{F}$ | 101 | 5 | 13 | 29 | 21 | 53 | 61 | 37 |
| DEF | 100 | 4 | 12 | 28 | 20 | 52 | 60 | 36 |

Ex:- Find the Boolean expression for F by using K-map?

| AB | F |
|----|---|
| 00 | 1 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

$$F = \sum_{0,1,2}$$

| A | \bar{A} | A |
|-----------|-----------|---|
| \bar{B} | 1 | 1 |
| B | 1 | 0 |

$$F = \bar{A} + \bar{B}$$

Ex:- Simplify F using K-map?

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}C\bar{D} + A\bar{B}C\bar{D}$$

Solution:- $F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}C\bar{D}(B + \bar{B}) + A\bar{B}C\bar{D}$

$$F = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D}$$

$$F = \sum_{0,2,3,7,8,10}$$

| CD | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB |
|------------------|------------------|------------|------------|------|
| $\bar{C}\bar{D}$ | 1 | 0 | 0 | 1 |
| $\bar{C}D$ | 0 | 0 | 0 | 0 |
| $C\bar{D}$ | 1 | 1 | 0 | 0 |
| CD | 1 | 0 | 0 | 1 |

$$F = \bar{B}\bar{D} + \bar{A}C\bar{D}$$

Ex:- Simplify F using K-map:-

$$F = ABC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C}$$

$$F = \sum_{0,1,2,3,7}$$

| AB | $\bar{A}\bar{B}$ | $\bar{A}B$ | AB | AB |
|-----------|------------------|------------|------|------|
| \bar{C} | 1 | 1 | 0 | 0 |
| C | 1 | 1 | 1 | 0 |

$$F = \bar{A} + BC$$

Don't Care Conditions:-

The presence of don't care in the design specifications gives us flexibility in selecting the output function that is to be synthesized. When simplifying logic expressions, the Don't Care terms are represented by X and may be used as 1's or 0's.

Ex:- Simplify:- $F = \sum_{d} 0, 2, 4, 8, 10, 13, 15 + \sum_{d} 1, 12, 14$, using k-map

solution:-

| | AB | AB | AB | AB |
|----|----|----|----|----|
| CD | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | X | 1 |
| 01 | X | 0 | 1 | 0 |
| 11 | 0 | 0 | 1 | 0 |
| 10 | 1 | 0 | X | 1 |

$$F = \bar{C}\bar{D} + AB + \bar{B}\bar{D}$$

Ex:- Simplify: $F = \sum_{d} 0, 1, 2, 8, 9, 10 + \sum_{d} 3, 11, 14, 15$ using k-map

solution:-

| | AB | AB | AB | AB |
|----|----|----|----|----|
| CD | 00 | 01 | 11 | 10 |
| 00 | 1 | 0 | 0 | 1 |
| 01 | 1 | 0 | 0 | 1 |
| 11 | X | 0 | X | X |
| 10 | 1 | 0 | X | 1 |

$$F = \bar{B}$$

Ex:- Design a logic ckt using NAND gates only to convert

BCD to EX-3 code:-

BCD count from 0 → 9
10 → 15 Invalid

| ABCD | WXYZ |
|------|---------|
| 0000 | 0011 |
| 0001 | 0100 |
| 0010 | 0101 |
| 0011 | 0110 |
| 0100 | 0111 |
| 0101 | 1000 |
| 0110 | 1001 |
| 0111 | 1010 |
| 1000 | 1011 |
| 1001 | 1100 |
| 1010 | X X X X |
| 1011 | X X X X |
| 1100 | X X X X |
| 1101 | X X X X |
| 1110 | X X X X |
| 1111 | X X X X |

$W = \sum 10, 11, 12, 13, 14, 15$

$X = \sum 5, 6, 7, 8, 9$

$Y = \sum 0, 3, 4, 7, 8$

$Z = \sum 0, 2, 4, 6, 8$

| AB | AB | AB | AB |
|----|----|----|----|
| 00 | 01 | 11 | 10 |
| 0 | 0 | X | 1 |
| 0 | 1 | X | 1 |
| 0 | 1 | X | X |
| 0 | 1 | X | X |

$W = A + BD + BC$

| AB | AB | AB | AB |
|----|----|----|----|
| 00 | 01 | 11 | 10 |
| 0 | 0 | X | 1 |
| 0 | 1 | 0 | X |
| 0 | 1 | 0 | X |
| 0 | 1 | 0 | X |

$X = B\bar{C}\bar{D} + \bar{B}D + \bar{B}C$


| AB | AB | AB | AB |
|----|----|----|----|
| 00 | 01 | 11 | 10 |
| 1 | 1 | X | 1 |
| 1 | 1 | X | X |
| 1 | 1 | X | X |

$Y = \bar{C}\bar{D} + CD$

| AB | AB | AB | AB |
|----|----|----|----|
| 00 | 01 | 11 | 10 |
| 1 | 1 | X | X |
| 1 | 1 | X | X |
| 1 | 1 | X | X |

$Z = \bar{D}$

 $W = A + BD + BC$
 $W = A + \overline{BD \cdot BC}$ ✓
 $X = B\bar{C}\bar{D} + \bar{B}D + \bar{B}C$
 $X = \overline{B\bar{C}\bar{D} \cdot \bar{B}D \cdot \bar{B}C}$ ✓
 $Y = \bar{C}\bar{D} + CD$
 $Y = \overline{\bar{C}\bar{D} \cdot CD}$ ✓
 $Z = \bar{D}$ ✓



Ex:- Use K-map to design a logic circuit to convert from 5421 code to 8421 code using NAND gates only.

| ABCD | WXYZ |
|---------|--------|
| 0 0000 | 0 0000 |
| 1 0001 | 0 0001 |
| 2 0010 | 0 0010 |
| 3 0011 | 0 0011 |
| 4 0100 | 0 1000 |
| 8 1000 | 0 1000 |
| 9 1001 | 0 1100 |
| 10 1010 | 0 1101 |
| 11 1011 | 1 0000 |
| 12 1100 | 1 0001 |

$d = \sum 5, 6, 7, 13, 14, 15$

$w = \sum 11, 12$

$x = \sum 4, 8, 9, 10$

$y = \sum 2, 3, 9, 10$

$z = \sum 1, 3, 8, 10, 12$

| AB/CD | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB |
|------------------|------------------|----------------|-----------------|------|
| $\bar{C}\bar{D}$ | 0 | 0 | 1 | 0 |
| $\bar{C}D$ | 0 | X ₅ | X ₇ | 0 |
| CD | 0 | X ₃ | X ₁₁ | 0 |
| $C\bar{D}$ | 0 | X ₂ | X ₆ | 0 |

$w = \bar{A}B + A\bar{C}D$

| AB/CD | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB |
|------------------|------------------|----------------|-----------------|------|
| $\bar{C}\bar{D}$ | 0 | 1 | 0 | 1 |
| $\bar{C}D$ | 0 | X ₅ | X ₁₃ | 1 |
| CD | 0 | X ₇ | X ₁₅ | 0 |
| $C\bar{D}$ | 0 | X ₂ | X ₁₄ | 1 |

$x = \bar{A}B + \bar{A}\bar{B}\bar{C} + A\bar{C}\bar{D}$

| AB/CD | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB |
|------------------|------------------|----------------|-----------------|------|
| $\bar{C}\bar{D}$ | 0 | 0 | 1 | 1 |
| $\bar{C}D$ | 1 | X ₅ | X ₁₃ | 0 |
| CD | 1 | X ₂ | X ₁₅ | 0 |
| $C\bar{D}$ | 0 | X ₆ | X ₁₄ | 1 |

$z = \bar{A}D + A\bar{D}$

| AB/CD | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB |
|------------------|------------------|----------------|-----------------|------|
| $\bar{C}\bar{D}$ | 0 | 0 | 0 | 0 |
| $\bar{C}D$ | 0 | X ₅ | X ₁₃ | 1 |
| CD | 1 | X ₂ | X ₁₅ | 0 |
| $C\bar{D}$ | 1 | X ₆ | X ₁₄ | 1 |

$y = \bar{C}\bar{D} + \bar{A}C + A\bar{C}D$

$w = \bar{A}B + A\bar{C}D = \overline{\bar{A}\bar{B} \cdot A\bar{C}\bar{D}}$

$x = \bar{A}B + \bar{A}\bar{B}\bar{C} + A\bar{C}\bar{D} = \overline{\bar{A}\bar{B} \cdot A\bar{B}\bar{C} \cdot A\bar{C}\bar{D}}$

$y = \bar{C}\bar{D} + \bar{A}C + A\bar{C}D = \overline{\bar{C}\bar{D} \cdot \bar{A}\bar{C} \cdot A\bar{C}\bar{D}}$

$z = \bar{A}D + A\bar{D} = \overline{\bar{A}\bar{D} \cdot A\bar{D}}$

Draw the cct as H.w

Parity Generators and Checkers:-

Errors can occur as digital codes are being transferred from one point to another within a digital system or while codes are being transmitted from one system to another. The errors take the form of undesired changes in the bits that make up the coded information; that is, a "1" can change to "0", or a "0" to "1", due to component malfunction or electrical noise.

Parity bit Generator Methods:-

Many systems employ a parity bit as a means of detecting a bit error. A word always contains either an even or an odd number of 1's. For this reason digital systems employ some method for detection (sometimes correction) of errors. One of the simplest and most widely used schemes for error detection is "the parity bit method" and the two different methods used are:-

- 1- Even parity Generator method
- 2- Odd parity Generator method.

1- Even Parity Generator method:-

Even parity means attaching an extra bit to a group of bits to produce an even number of 1's as shown in Table 1.

2- Odd parity Generator method:-

Odd parity means attaching an extra bit to a group of bits to produce an odd number of 1's as shown in Table 2.

Table 1- Even parity Generator for three bits

| A B C | Even parity P_e |
|-------|----------------------|
| 0 0 0 | 0 |
| 0 0 1 | 1 |
| 0 1 0 | 1 |
| 0 1 1 | 0 |
| 1 0 0 | 1 |
| 1 0 1 | 0 |
| 1 1 0 | 0 |
| 1 1 1 | 1 |

$$X = \bar{A}\bar{B} + \bar{A}B = A \oplus B$$

$$\bar{X} = \bar{A}\bar{B} + AB = A \oplus \bar{B}$$


$$P_e = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$P_e = C(\bar{A}\bar{B} + AB) + \bar{C}(\bar{A}B + A\bar{B})$$

$$P_e = C\bar{X} + \bar{C}X$$

$$P_e = C \oplus X$$

$$P_e = C \oplus A \oplus B$$

 

Logic diagram of even parity generator.

Table 2- Odd parity Generator for three bits.

| A B C | odd parity P_o |
|-------|---------------------|
| 0 0 0 | 1 |
| 0 0 1 | 0 |
| 0 1 0 | 0 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |
| 1 0 1 | 1 |
| 1 1 0 | 1 |
| 1 1 1 | 0 |

$$X = \bar{A}B + A\bar{B} = A \oplus B$$

$$\bar{X} = \bar{A}\bar{B} + AB = A \oplus \bar{B}$$


$$P_o = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$P_o = C(\bar{A}\bar{B} + A\bar{B}) + \bar{C}(\bar{A}\bar{B} + AB)$$

$$P_o = CX + \bar{C}\bar{X}$$

$$P_o = C \odot X$$

$$P_o = C \odot (A \oplus B)$$

 

Logic diagram for odd parity generator.

Parity checking:-


Ex:- show how to design a parity checker ckt for a 3-bit

data:-
Solution:-

| A B C | even Parity checker C_o |
|-------|---------------------------|
| 0 0 0 | 0 |
| 0 0 1 | 1 ✓ |
| 0 1 0 | 1 ✓ |
| 0 1 1 | 0 |
| 1 0 0 | 1 ✓ |
| 1 0 1 | 0 |
| 1 1 0 | 0 |
| 1 1 1 | 1 ✓ |

$X = A\bar{B} + \bar{A}B = A \oplus B$
 $\bar{X} = AB + \bar{A}\bar{B} = \overline{A \oplus B}$

 $C_o = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$
 $C_o = C(AB + \bar{A}\bar{B}) + \bar{C}(\bar{A}B + A\bar{B})$
 $C_o = C\bar{X} + \bar{C}X$
 $C_o = C \oplus A \oplus B$



Ex:- Design a logic ckt to provide the odd parity bit for BCD code using NAND gates only:-

Solution:-

| ABCD | P_o |
|---------|-------|
| 0 0 0 0 | 1 ✓ |
| 0 0 0 1 | 0 |
| 0 0 1 0 | 0 |
| 0 0 1 1 | 1 ✓ |
| 0 1 0 0 | 0 |
| 0 1 0 1 | 1 ✓ |
| 0 1 1 0 | 1 ✓ |
| 0 1 1 1 | 0 |
| 1 0 0 0 | 0 |
| 1 0 0 1 | 1 |

$d = \sum 10, 11, 12, 13, 14, 15$
 $P_o = \sum 0, 3, 5, 6, 9$

| CD \ AB | 00 | 01 | 10 | 11 |
|---------|----|----|----|----|
| 00 | 1 | 0 | X | 0 |
| 01 | 0 | 1 | X | 1 |
| 10 | 1 | X | 1 | X |
| 11 | 0 | 1 | X | X |

$P_o = \bar{A}D + B\bar{C}D + B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{B}C\bar{D}$

$P_o = \overline{AD \cdot B\bar{C}D \cdot B\bar{C}\bar{D} \cdot \bar{A}B\bar{C}\bar{D} \cdot \bar{B}C\bar{D}}$

H.w:- Draw the ckt using NAND gates only.

- H.w.:-
1. Design an even/odd parity generator for 4-bit data, then implement its cct. diagram.
 2. Design a parity checker cct for a 4-bit data, then implement its cct diagram.

Adders:-

Adders are important not only in computers, but in many type of digital systems in which numerical data are processed. There are two types of adders:-

- 1- Half adder
- 2- Full adder

1- Half Adder (H.A):

It is a digital circuit having two inputs and two outputs. The inputs are the inputs bits of the binary number and outputs are the sum of them and carry of them. The truth table and the block diagram are shown below:-





| AB | SC ₀ |
|----|-----------------|
| 00 | 0 0 |
| 01 | 1 0 |
| 10 | 1 0 |
| 11 | 0 1 |

By means of using gates, we can have different forms of H.A.


$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C_o = AB$$

  

2- Full Adder (F.A)

 Application for the H.A are limited. The H.A is no sufficient for adding more than two one-bit numbers. Full Adder is a logic circuit that can add 3-bit and have two outputs. These outputs are the sum of three bits inputs and the second output is Carry of them. The truth table and the block diagram are shown below:-



| A | B | C _{in} | S | C _o |
|---|---|-----------------|---|----------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

From the truth table:-

$$S = \sum 1, 2, 4, 7$$

$$= \overline{A}\overline{B}C_{in} + \overline{A}B\overline{C}_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

$$= \overline{A}(\overline{B}C_{in} + B\overline{C}_{in}) + A(\overline{B}\overline{C}_{in} + BC_{in})$$

$$= \overline{A}(B \oplus C_{in}) + A(\overline{B} \oplus C_{in})$$

$$= \overline{A}(B \oplus C_{in}) + A(B \oplus C_{in})$$

$$S = A \oplus B \oplus C_{in}$$


$$B \odot C_{in} = \overline{B \oplus C_{in}}$$

$$C_o = \sum 3, 5, 6, 7$$

$$= \overline{A}B\overline{C}_{in} + \overline{A}BC_{in} + A\overline{B}\overline{C}_{in} + ABC_{in}$$

$$= AB(\overline{C}_{in} + C_{in}) + C_{in}(\overline{A}B + A\overline{B})$$


$$= AB + C_{in}(A \oplus B)$$

 

Ex:- Implement Full-Adder circuit diagram by using H.A blocks and any gate:-

Solution:- $S = A \oplus B \oplus C$
 $C_o = AB + C_i(A \oplus B)$] F.A \Rightarrow 2 bits
 الخرجين

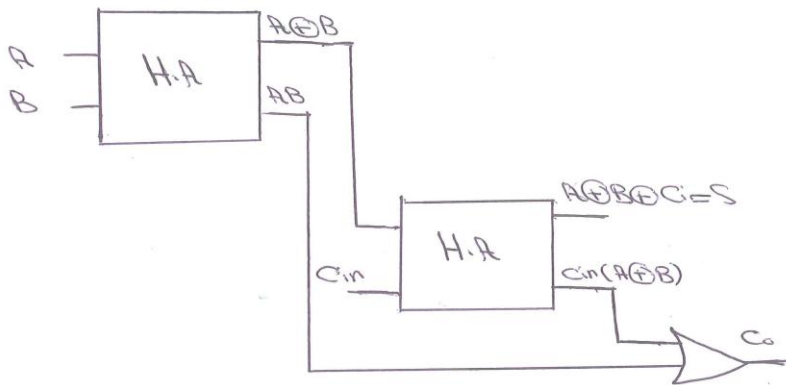
$S = A \oplus B$] HA \Rightarrow 2 bits
 $C_o = AB$ الخرجين



Ex:- Design NAND gate by using H.A's only:-

Solution:- $F = \overline{AB}$] الخرجين
 الخرجين

 $S = A \oplus B$] الخرجين
 $C_o = AB$ الخرجين




Note:- $A \oplus 1 = \overline{A}$
 $A \oplus 0 = A$] Very Important.

Ex:- Design OR gate by using H.A only:-

Solution:- $F = A + B$] $\left. \begin{array}{l} \text{الحاصل} \\ \text{المطلوب} \end{array} \right\}$

$S = A \oplus B$] $\left. \begin{array}{l} \text{المطلوب} \\ \text{المطلوب} \end{array} \right\}$

$C_0 = AB$

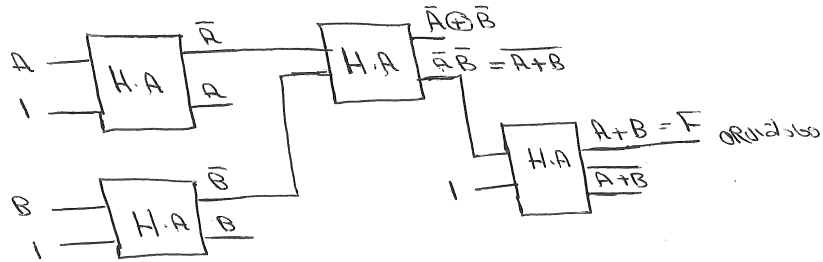

Ex:- Implement the following ^{boolean} functions below, using H.A blocks only:-

blocks only:-

$X = A \oplus B \oplus C$ $Y = \bar{A}Bc + A\bar{B}c$ $Z = AB\bar{C} + C(\bar{A} + \bar{B})$

$W = ABC$

Solution:- $X = A \oplus B \oplus C$

$Y = \bar{A}Bc + A\bar{B}c = c(\bar{A}B + A\bar{B}) = c(A \oplus B)$


$Z = AB\bar{C} + C(\bar{A} + \bar{B}) = AB\bar{C} + C(\overline{A+B}) = AB\bar{C} + C\overline{A+B}$

$= AB \oplus C$

$W = ABC$

$S = A \oplus B$] $\left. \begin{array}{l} \text{الحاصل} \\ \text{المطلوب} \end{array} \right\}$

$C_0 = AB$

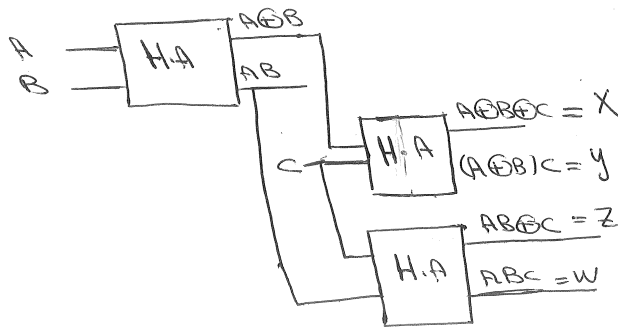


Binary Parallel Adder:-

For two numbers of two bits, two adders are needed and for three bits numbers, three adders are needed and so on. The Carry of each adder is connected to the Carry input of the next higher order adder.


Ex:- The two bit binary parallel adder is shown below.

Solution:- Let $A = A_1 A_0$ (msb to lsb)
 $B = B_1 B_0$ (msb to lsb)
 Result = $S_2 S_1 S_0$
 
$$\begin{array}{r} \textcircled{1} \\ A = 11 \\ B = 01 \\ \hline 100 \end{array} +$$



 Note:- Two bit binary parallel adder 7482 IC



$A_0, B_0 \rightarrow$ (LSB input)


$A_1, B_1 \rightarrow$ (MSB input)

$C_i \rightarrow$ (Carry input to the LSB)

$C_o \rightarrow$ (Carry output to the MSB)


Ex:- The four bit binary parallel adder is shown below:-

 Solution:- Let $R = R_3 R_2 R_1 R_0$ (msB to lsb)
 $B = B_3 B_2 B_1 B_0$ (msB to lsb)



$$\begin{array}{r}
 A = 1001 \\
 B = 0111 \\
 \hline
 10000
 \end{array}$$

 
Note:- Four bit binary parallel adder 7483 IC



Ex:- Show how you can obtain Four bit adder from IC of 7482 only:-

Solution:-
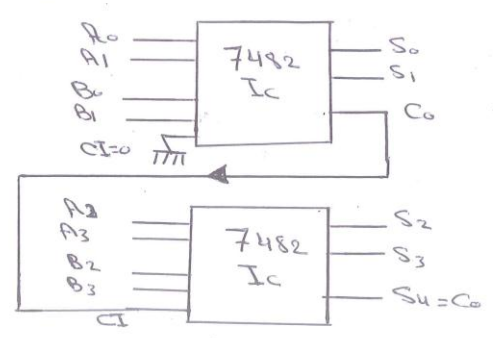
$$\begin{array}{r}
 R = R_3 R_2 R_1 R_0 \\
 B = B_3 B_2 B_1 B_0 \\
 \hline
 S_4 S_3 S_2 S_1 S_0
 \end{array}$$



How:- Design 8-bits adder by using block diagram of IC 7483 (4-bit) adder.


How:- Use Full adder block diagram of IC 7483 to convert BCD to Ex-3 code.

Adder/Subtractor:-

Ex:- Design an Adder/subtractor ckt. using FA's and gates:-

Solution:- $A = A_3 A_2 A_1 A_0$

$B = B_3 B_2 B_1 B_0$

 


$X=0$ in Adding operation and output result = $S_4 S_3 S_2 S_1 S_0$

$X=1$ in subtraction operation and output result equal $S_3 S_2 S_1 S_0$ and S_4 or C_0 will be (discarded) due to 2's Complement operation.

Ex:- Using an Adder/subtractor ckt. to convert from Ex-3 code to BCD code:-

Solution:- Let $R = A_3 A_2 A_1 A_0$ in Ex-3 code

 Then BCD number = $\underline{\underline{0011}}$




H.w:- Using an adder/subtractor ckt. to convert from BCD code to Ex-3 code?

Comparators:-


A magnitude Comparator is a combinational circuit that compares two numbers (A and B), and determines their relative magnitudes. The outputs of the comparison are specified by three binary variables that indicate whether $A=B$ or $A>B$ or $A<B$.

 The block diagram for comparator is shown below:-



- For two binary numbers, each one have one bit, the truth table:-

| A | B | Z_1 | Z_2 | Z_3 |
|---|---|-------|-------|-------|
| 0 | 0 | 0 | 1 ✓ | 0 |
| 0 | 1 | 0 | 0 | 1 ✓ |
| 1 | 0 | 1 ✓ | 0 | 0 |
| 1 | 1 | 0 | 1 ✓ | 0 |

 

$$Z_1(A > B) = A\bar{B}$$

$$Z_2(A = B) = \bar{A}\bar{B} + AB = A \oplus B$$

$$Z_3(A < B) = \bar{A}B$$

- For two binary numbers, each one have two bits (n=2)

$$\begin{matrix} \text{MSB} \rightarrow & & \text{MSB} \rightarrow \\ A = A_1 A_0 & , & B = B_1 B_0 \end{matrix}$$

$$\begin{aligned} A > B &= (A_1 > B_1) \text{ or } (A_1 = B_1) \text{ and } (A_0 > B_0) \\ &= (A_1\bar{B}_1) + (A_1 \odot B_1)(A_0\bar{B}_0) \\ &= (A_1\bar{B}_1) + X_1 \cdot A_0\bar{B}_0 \end{aligned}$$

$$\begin{aligned} A < B &= (A_1 < B_1) \text{ or } (A_1 = B_1) \text{ and } (A_0 < B_0) \\ &= \bar{A}_1 B_1 + (A_1 \odot B_1) \cdot (\bar{A}_0 B_0) \\ &= \bar{A}_1 B_1 + X_1 \cdot \bar{A}_0 B_0 \end{aligned}$$


Note: $X_0 = A_0 \odot B_0$
 $X_1 = A_1 \odot B_1$

* للقيمة ذاتها في أعلى
MSB ↓

 (67)

$$\begin{aligned}
 A = B &= (A_1 = B_1) \text{ and } (A_0 = B_0) \\
 &= (A_1 \odot B_1) \cdot (A_0 \odot B_0) \\
 &= X_1 X_0
 \end{aligned}$$

From the expression we may obtain the digital Comparator circuit as shown below: -



Digital Comparator Circuit for 2-bits

- For two binary numbers, each one have 4-bits ($n=4$).

$$A = A_3 A_2 A_1 A_0, B = B_3 B_2 B_1 B_0$$

Note: $X_0 = A_0 \odot B_0$
 $X_1 = A_1 \odot B_1$
 $X_2 = A_2 \odot B_2$
 $X_3 = A_3 \odot B_3$

$$\begin{aligned}
 A > B (G) &= A_3 > B_3 \text{ or } A_3 = B_3 \text{ and } A_2 > B_2 \text{ or } A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 > B_1 \text{ or } \\
 & \quad A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 = B_1 \text{ and } A_0 > B_0 \\
 &= A_3 \bar{B}_3 + (A_3 \odot B_3) A_2 \bar{B}_2 + (A_3 \odot B_3) (A_2 \odot B_2) A_1 \bar{B}_1 + \\
 & \quad (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \bar{B}_0) \\
 &= A_3 \bar{B}_3 + X_3 A_2 \bar{B}_2 + X_3 X_2 A_1 \bar{B}_1 + X_3 X_2 X_1 A_0 \bar{B}_0 \\
 A < B (L) &= A_3 < B_3 \text{ or } A_3 = B_3 \text{ and } A_2 < B_2 \text{ or } A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 < B_1 \text{ or } \\
 & \quad A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 = B_1 \text{ and } A_0 < B_0
 \end{aligned}$$

$$\begin{aligned}
 &= \bar{A}_3 B_3 + (A_3 \odot B_3)(\bar{A}_2 B_2) + (A_3 \odot B_3)(A_2 \odot B_2) \bar{A}_1 B_1 + \\
 &\quad (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)(\bar{A}_0 B_0) \\
 &= \bar{A}_3 B_3 + X_3 \bar{A}_2 B_2 + X_3 X_2 \bar{A}_1 B_1 + X_3 X_2 X_1 \bar{A}_0 B_0
 \end{aligned}$$

$$\begin{aligned}
 A = B (E) &= (A_3 = B_3) \text{ and } (A_2 = B_2) \text{ and } (A_1 = B_1) \text{ and } (A_0 = B_0) \\
 &= (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)(A_0 \odot B_0) \\
 &= X_3 X_2 X_1 X_0
 \end{aligned}$$

Ex: - Implement a Comparator of two binary numbers each one have four bits, Let $A = 0101$ and $B = 1101$

Solution:-

$$\begin{aligned}
 A &= A_3 A_2 A_1 A_0 \\
 B &= B_3 B_2 B_1 B_0
 \end{aligned}$$

by substitute the values of A and B in the previous equations:-

$$G = 0 + 0 + 0 + 0 = 0$$

$$L = 1 + 0 + 0 + 0 = 1 \quad \therefore A < B$$


$$E = 0 \times 1 \times 1 \times 1 = 0$$

H.w:- For each of the binary numbers, determine the output states for the comparator:-

$$\begin{aligned}
 A) \quad A_3 A_2 A_1 A_0 &= 1100 \\
 B_3 B_2 B_1 B_0 &= 1001
 \end{aligned}$$

$$\begin{aligned}
 B) \quad A_3 A_2 A_1 A_0 &= 0100 \\
 B_3 B_2 B_1 B_0 &= 0100
 \end{aligned}$$

7485 IC:-

 


(Two binary numbers of four bits comparator 7485 Ic)

Ex:- Use 7485 Ic to compare two binary numbers each one have

eight bits:- $A = A_7 A_6 A_5 A_4 A_3 A_2 A_1 A_0$
 $B = B_7 B_6 B_5 B_4 B_3 B_2 B_1 B_0$

Solution:-

 

Ex:- Design H.A. using Comparators only:-

Solution:-

HA
 $S = AB' + \bar{A}B = A \oplus B$
 $C_o = AB$


Note:-
 $A \odot 1 = A$
 $A \odot 0 = \bar{A}$

Comparator

$A > B (G) = A\bar{B}$

$A = B (E) = AB + \bar{A}\bar{B} = A \odot B$

$A < B (L) = \bar{A}B$

 

H.w:- Design F.A, using Comparators only.

H.w:- Design H.A by using Comparators and any gate.

H.w:- Design F.A by using Comparator and one gate.

H.w:- Verify all logic gates using Comparator only.

AND, NOR, OR, EX-OR, EX-NOR, NAND, NOT.

Decoder and Encoder

Decoder:-

A decoder is a combinational logic circuit that converts coded information such as binary, into a recognizable form, such as decimal. There are many type of decoders such as:-


- 1- Binary decoder.
- 2- BCD to Decimal decoder.
- 3- BCD to 7-segment decoder.

Note:- In general form, a decoder has n input lines to handle n bits and form one to 2ⁿ output lines to indicate the presence of one or more n-bit combinations.

1- Binary decoder:- (n × 2ⁿ) (n-to-2ⁿ) decoder.

It converts binary coded information in to a decimal recognizable form. The output lines of this decoder is 2ⁿ where n is the number of bits of the binary input such as 2x4 decoder, 3x8 decoder, 4x16 decoder.

 A 2x4 line decoder cct. is shown below with the Truth table




From the truth table:-
 D₀ = $\bar{A}\bar{B}$; D₂ = $A\bar{B}$
 D₁ = $\bar{A}B$; D₃ = AB

Ex:- Show how you can indicate the No(10)10 for high or low
 Determine the logic required to decode the binary code 1010 with active high or low output.

Solution:- Active High

A NAND gate is used and the output = 1


$$1010 = A\bar{B}C\bar{D}$$

 

Active Low

A NAND gate is used and the output = 0

$$1010 = A\bar{B}C\bar{D}$$

 

Implement Logic Functions Using Decoders:-

Ex:- Implement the following logic function using decoders and Logic gates:-

$$F = \sum_{D_0, D_1, D_4, D_6, D_7}$$

Solution:-

$$D_0 = \bar{A}\bar{B}\bar{C}$$


$$D_1 = \bar{A}\bar{B}C$$

$$D_4 = A\bar{B}\bar{C}$$

$$D_6 = ABC\bar{C}$$

$$D_7 = ABC$$

| ABC | F |
|-----|---|
| 000 | 1 |
| 001 | 1 |
| 010 | 0 |
| 011 | 1 |
| 100 | 1 |
| 101 | 0 |
| 110 | 1 |
| 111 | 1 |

 

$$F = D_0 + D_1 + D_4 + D_6 + D_7$$


Ex:- Implement HA ckt using decoder and logic gates:-

Solution:-

$$S = \sum 1, 2 = \bar{A}\bar{B} + A\bar{B} = D_1 + D_2$$

$$C_o = \sum 3 = AB = D_3$$

| AB | S | C _o |
|----|---|----------------|
| 00 | 0 | 0 |
| 01 | 1 | 0 |
| 10 | 1 | 0 |
| 11 | 0 | 1 |

 

Hw:- By means of decoder and logic gates implement:-


1- FA ckt

2- $F = \sum 0, 2, 5, 6, 7$.

Enable Control Inputs:-

Decoders include one or more enable inputs to control the circuit operation. In general, a decoder may operate with complemented or uncomplemented outputs. The enable inputs may be activated with a 0 or with a 1 signal. Some decoders have two or more enable i/p's that must satisfy a given logic condition in order to enable the ckt.

 A 2x4 line decoder with an enable input constructed with NAND gate is shown below:-



| E | AB | D ₀ | D ₁ | D ₂ | D ₃ |
|---|----|----------------|----------------|----------------|----------------|
| 1 | 00 | 1 | 1 | 1 | 1 |
| 0 | 00 | 0 | 1 | 1 | 1 |
| 0 | 01 | 1 | 0 | 1 | 1 |
| 0 | 10 | 1 | 1 | 0 | 1 |
| 0 | 11 | 1 | 1 | 1 | 0 |

Truth Table


2-to-4 Decoder with Enable input (Active Low)

$$D_0 = \overline{E} \overline{A} \overline{B}$$

$$D_1 = \overline{E} \overline{A} B$$

$$D_2 = \overline{E} A \overline{B}$$

$$D_3 = \overline{E} A B$$

 

VIP

Note: - Decoders with enable inputs can be connected together to form a larger decoder circuit.


Ex: - Design 3x8 decoder using 2x4 decoders with Enable:-

Solution: -

| ABC | D ₀ | D ₁ | D ₂ | ... | D ₇ |
|-----|----------------|----------------|----------------|-----|----------------|
| 000 | 1 | 0 | 0 | ... | 0 |
| 001 | 0 | 1 | 0 | ... | 0 |
| 010 | 0 | 0 | 1 | ... | 0 |
| 011 | 0 | 0 | 0 | ... | 0 |
| 100 | 0 | 0 | 0 | ... | 0 |
| 101 | 0 | 0 | 0 | ... | 0 |
| 110 | 0 | 0 | 0 | ... | 0 |
| 111 | 0 | 0 | 0 | ... | 1 |


1st Dec

2nd Dec

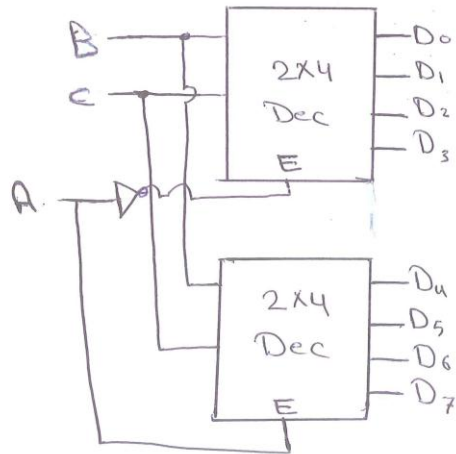

Ex: - Design 4-to-16 Decoder, using 3x8 decoders with enable.

Solution:-

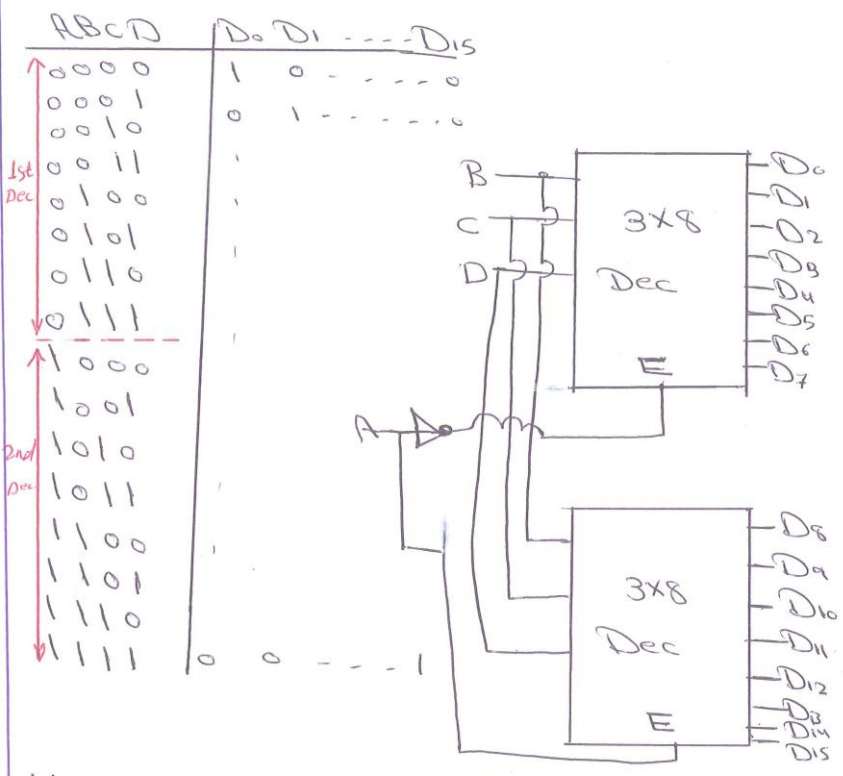

H.w:- Design 4-to-16 Decoder, using 2x4 decoders with enables-

2- BCD to Decimal Decoders, -

The BCD decoder converts each BCD code (8421) into one of the possible decimal digit-indications it is referred to as 4-line-to-10-line decoder or a 4-to-10 decoder.

A list of the ten BCD codes and their corresponding decoding functions is given in Table below:-

| ABCD | D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ | D ₈ | D ₉ |
|------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0000 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0001 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0010 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0011 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0100 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0101 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0110 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0111 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1000 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1001 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1010 | X | X | X | X | X | X | X | X | X | X |
| 1011 | X | X | X | X | X | X | X | X | X | X |
| 1100 | X | X | X | X | X | X | X | X | X | X |
| 1101 | X | X | X | X | X | X | X | X | X | X |
| 1110 | X | X | X | X | X | X | X | X | X | X |
| 1111 | X | X | X | X | X | X | X | X | X | X |

- D₀ = $\overline{A}\overline{B}\overline{C}\overline{D}$
- D₁ = $\overline{A}\overline{B}C\overline{D}$
- D₂ = $\overline{A}B\overline{C}\overline{D}$
- D₃ = $\overline{A}BC\overline{D}$
- D₄ = $B\overline{C}\overline{D}$
- D₅ = $B\overline{C}D$
- D₆ = $BC\overline{D}$
- D₇ = BCD
- D₈ = $A\overline{D}$
- D₉ = AD

dec. care = $\sum 10, 11, 12, 13, 14, 15$


| AB \ CD | $\overline{A}\overline{B}$ | $\overline{A}B$ | $A\overline{B}$ | AB |
|----------------------------|----------------------------|-----------------|-----------------|-----------------|
| $\overline{C}\overline{D}$ | 0 | 4 | X ₁₂ | 5 |
| $\overline{C}D$ | 1 | 5 | X ₁₃ | 9 |
| $C\overline{D}$ | 7 | 7 | X ₁₄ | X ₁₁ |
| CD | 1 | 6 | X ₁₄ | X ₁₅ |

D₂ = $\overline{B}C\overline{D}$


H.w.:- write the K-map for the other D. [D₃ ... D₉]

3- BCD to-7-Segment Decoder:-

 This type of decoder accepts the BCD code on its input and provides outputs to drive 7-segment display in order to produce a decimal digital readout.



| ABCD | a | b | c | d | e | f | g |
|------|---|---|---|---|---|---|---|
| 0000 | 1 | 1 | 1 | 1 | 1 | 0 | |
| 0001 | 0 | 0 | 0 | 0 | 1 | 0 | |
| 0010 | 1 | 1 | 0 | 1 | 0 | 0 | |
| 0011 | 0 | 1 | 1 | 1 | 0 | 0 | |
| 0100 | 0 | 1 | 1 | 0 | 0 | 0 | |
| 0101 | 1 | 0 | 1 | 1 | 0 | 0 | |
| 0110 | 1 | 0 | 1 | 1 | 1 | 0 | |
| 0111 | 1 | 1 | 1 | 0 | 0 | 0 | |
| 1000 | 1 | 1 | 1 | 1 | 1 | 1 | |
| 1001 | 1 | 1 | 1 | 0 | 1 | 1 | |
| 1010 | x | - | - | - | - | - | x |
| 1011 | x | - | - | - | - | - | x |
| 1100 | x | - | - | - | - | - | x |
| 1101 | x | - | - | - | - | - | x |
| 1110 | x | - | - | - | - | - | x |
| 1111 | x | - | - | - | - | - | x |

 

$a = \sum 0, 2, 3, 5, 6, 7, 8, 9$
 $b = \sum 0, 2, 3, 4, 7, 8, 9$
 $c = \sum 0, 3, 4, 5, 6, 7, 8, 9$
 $d = \sum 0, 2, 3, 5, 6, 8, 9$
 $e = \sum 0, 1, 2, 6, 8$
 $f = \sum 0, 1, 4, 5, 6, 8, 9$
 $g = \sum 2, 3, 4, 5, 6, 8, 9$
 don't care = $\sum 10, 11, 12, 13, 14, 15$

Encoder:-

An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has 2^n (or fewer) inputs lines and n output lines. An encoder accepts an active level on one of its inputs representing a digit, such as a decimal or octal digit, and converts it to a coded outputs

Such as BCD or Binary

| D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 | A | B | C |
|-------|-------|-------|-------|-------|-------|-------|-------|---|---|---|
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

Truth Table of octal-to-binary Encoder

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

Truth table of Decimal to BCD Encoder

| D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 | D_8 | D_9 | A | B | C | D |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|---|---|---|---|
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |

MSB


$$A = D_8 + D_9$$

$$B = D_4 + D_5 + D_6 + D_7$$


$$C = D_2 + D_3 + D_6 + D_7$$

$$D = D_1 + D_3 + D_5 + D_7$$


LSB

 

 Logic symbol for octal-to-binary Encoder.



Logic symbol for Decimal to BCD Encoder

 

Basic logic diagram of an octal to Binary Encoder.

H.w. :- Draw the Basic logic diagram of a decimal to BCD Encoder.

Note :- If two inputs are active simultaneously, the output produces an undefined combination. To resolve this ambiguity, encoder circuits must establish an input priority to ensure that only one input is encoded. If we establish a higher priority for i/p's with higher subscript numbers, and if both D_3 and D_6 are 1 at the same time, the output will be 110 because D_6 has higher priority than D_3 .


~~BA~~
2016/10/12

Multiplexer and Demultiplexer: -

Multiplexer :

A multiplexer (Mux) is a device that allows digital information from several sources to be routed onto a single line for transmission over that line to a common destination. The basic multiplexer, then has several data input lines (2^N) and a single o/p line. It also has data selector inputs (N) that permit digital data on any one of the input to be switched to the o/p line.

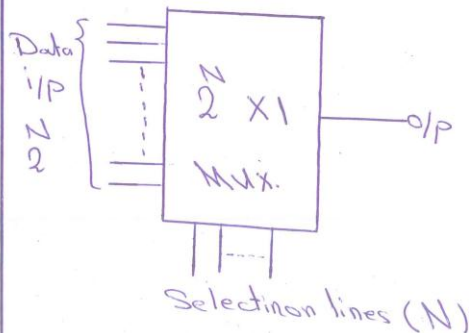
The block diagram for such multiplexer ($2^N \times 1$) is shown below: -



The multiplexer may be considered as a multi-switch.

The block diagram of 4x1 Mux and its truth table is shown below: -


| S_1 | S_0 | F |
|-------|-------|-------|
| 0 | 0 | D_0 |
| 0 | 1 | D_1 |
| 1 | 0 | D_2 |
| 1 | 1 | D_3 |

 


The equation of F is: -

$$F = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

 The circuit diagram of the equation is: -



Ex :- Find the o/p of the following: -

 


Solution:- $S_1 S_0 = \frac{10}{2}$
 $F = D_2 = 0$

Ex:- Implement the following function by means of using the suitable Mux. $F = \sum 0, 1, 3, 5, 7$.


Solution:-

1) By using 8X1 MUX

| ABC | F |
|-----|---|
| 000 | 1 |
| 001 | 0 |
| 010 | 1 |
| 011 | 1 |
| 100 | 0 |
| 101 | 0 |
| 110 | 1 |
| 111 | 1 |


 


2) By using 4x1 MUX.

 

| Select line input | D ₀ B̄c | D ₁ B̄c | D ₂ Bc | D ₃ Bc |
|-------------------|-----------------------|-----------------------|----------------------|----------------------|
| Ā | 0 | 1 | 2 | 3 |
| A | 4 | 5 | 6 | 7 |
| result | Ā | 1 | 0 | 1 |

| Select line input | D ₀ Āc | D ₁ Āc | D ₂ Ac | D ₃ Ac |
|-------------------|-----------------------|-----------------------|----------------------|----------------------|
| B̄ | 0 | 1 | 4 | 5 |
| B | 2 | 3 | 6 | 7 |
| result | B̄ | 1 | 0 | 1 |

  


Ex: - If $F = \sum m(0, 1, 3, 4, 8, 9, 15)$, Implement it using :-

- 1- 16x1 Mux.
- 2- 8x1 Mux.
- 3- 4x1 Mux.
- 4- 2x1 Mux.

Solution: -


1- By using 16x1 Mux

| ABCD | F |
|------|---|
| 0000 | 1 |
| 0001 | 1 |
| 0010 | 0 |
| 0011 | 1 |
| 0100 | 0 |
| 0101 | 0 |
| 0110 | 0 |
| 0111 | 0 |
| 1000 | 1 |
| 1001 | 1 |
| 1010 | 0 |
| 1011 | 0 |
| 1100 | 0 |
| 1101 | 0 |
| 1110 | 0 |
| 1111 | 1 |

 

2- 1x8 Mux.


| Select input | D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 |
|-----------------|-------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------|
| | ABC | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $A\bar{B}\bar{C}$ | $\bar{A}B\bar{C}$ | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $A\bar{B}C$ |
| \bar{D} | 0 | 2 | 4 | 6 | 8 | 10 | 12 | 14 |
| D | 1 | 3 | 5 | 7 | 9 | 11 | 13 | 15 |
| result | 1 | D | \bar{D} | 0 | 1 | 0 | 0 | D |

 

3- 4x1 Mux.


| Select input | D_0 | D_1 | D_2 | D_3 |
|------------------|-------|------------------|------------|------------|
| | AB | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ |
| $\bar{C}\bar{D}$ | 0 | 4 | 8 | 12 |
| $\bar{C}D$ | 1 | 5 | 9 | 13 |
| $C\bar{D}$ | 2 | 6 | 10 | 14 |
| CD | 3 | 7 | 11 | 15 |
| result | | $\bar{C}\bar{D}$ | $\bar{C}D$ | $C\bar{D}$ |

 $\bar{C}\bar{D} + \bar{C}D + C\bar{D} = \bar{C} + D$



4- 2x1 Mux.

| SL input | D ₀ Ā | D ₁ A |
|-------------------------|----------------------|---------------------|
| $\bar{B}\bar{C}\bar{D}$ | 0 | 8 |
| $\bar{B}C\bar{D}$ | 1 | 9 |
| $\bar{B}C\bar{D}$ | 2 | 10 |
| $\bar{B}C\bar{D}$ | 3 | 11 |
| $B\bar{C}\bar{D}$ | 4 | 12 |
| $B\bar{C}\bar{D}$ | 5 | 13 |
| $B\bar{C}\bar{D}$ | 6 | 14 |
| $B\bar{C}\bar{D}$ | 7 | 15 |
| result | | |

 

$$\bar{B}\bar{C}\bar{D} + \bar{B}C\bar{D} + \bar{B}C\bar{D} + \bar{B}C\bar{D}$$

$$\bar{C}\bar{D} [\bar{B} + B] + \bar{B}D[\bar{C} + C]$$

$$\bar{C}\bar{D} + \bar{B}D$$

$$\bar{B}\bar{C}\bar{D} + \bar{B}C\bar{D} + B\bar{C}\bar{D}$$

$$\bar{B}\bar{C}[\bar{D} + D] + B\bar{C}\bar{D}$$

$$\bar{B}\bar{C} + B\bar{C}\bar{D}$$

Ex:- Implement the function $F = \sum m(2, 4, 6, 7) + \sum d(1)$

using :- 1- (4x1) Mux.

2- (2x1) multiplexers. (2x1 Mux) (two 2x1 Muxes)


3- (2x1) MUX (As HW)

Solution:-

1- (4x1) Mux :-

| ABC | F |
|-----|---|
| 000 | 1 |
| 001 | x |
| 010 | 1 |
| 011 | 0 |
| 100 | 1 |
| 101 | 0 |
| 110 | 1 |
| 111 | 1 |

| SL input | D ₀ ĀB | D ₁ ĀB̄ | D ₂ AB | D ₃ AB̄ |
|-------------|-----------------------|------------------------|----------------------|-----------------------|
| \bar{C} | 0 | 2 | 4 | 6 |
| C | 1 | 3 | 5 | 7 |
| result | 1 | \bar{C} | \bar{C} | 1 |

 


V. Imp.

2- (2x1) Multiplexers:-

2x1 mux 5/12/1
الاجابة

| | | | | |
|---|----------------|----------------|----------------|----------------|
| | A=0 | | A=1 | |
| | D ₀ | D ₁ | D ₀ | D ₁ |
| S | AB | AB | AB | AB |
| C | 0 | 2 | 4 | 6 |
| | 1x | 3 | 5 | 7 |
| | 1 | \bar{C} | \bar{C} | 1 |

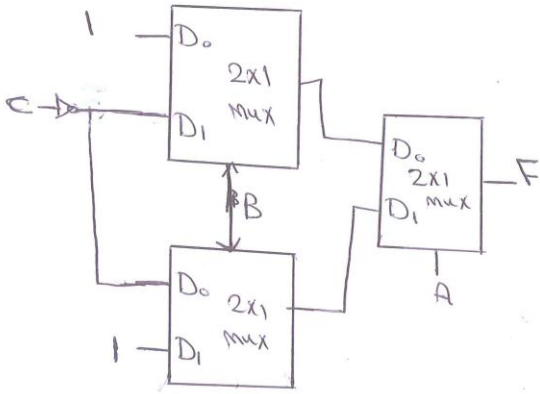

Another way:-

| A/B | \bar{C} | C | Result |
|-----|-----------|----|--------------------------|
| 0/0 | 0 | 1x | 1 D ₀ |
| 0/1 | 2 | 3 | \bar{C} D ₁ |
| 1/0 | 4 | 5 | \bar{C} D ₀ |
| 1/1 | 6 | 7 | 1 D ₁ |


Ex:- Implement HA, using:-

- 1- Proper Mux.
- 2- 2x1 Mux.
- 3- (2x1) multiplexers.

Solution:-

| AB | S | C ₀ |
|----|---|----------------|
| 00 | 0 | 0 |
| 01 | 1 | 0 |
| 10 | 1 | 0 |
| 11 | 0 | 1 |

$S = \sum 1, 2$
 $C_0 = \sum 3$

 


2 (2x1) mux (Sand Co) must have the same select line.

a) for $S = \sum 1, 2$

| input | \bar{B} | B |
|-----------|-----------|-----------|
| \bar{A} | 0 | 1 |
| A | 1 | 0 |
| result | A | \bar{A} |

b) for $C_o = \sum 3$

| input | \bar{B} | B |
|-----------|-----------|-----|
| \bar{A} | 0 | 1 |
| A | 1 | 0 |
| result | 0 | A |

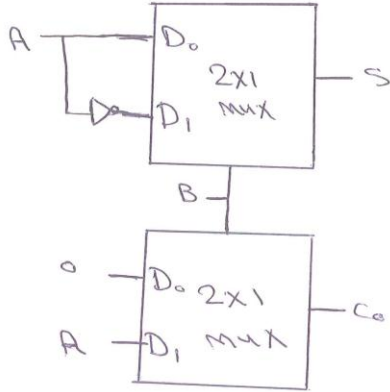


3- (2x1) Multiplexers:-

a) for S

| A | B | S |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

b) for Co

| A | B | Co |
|---|---|----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

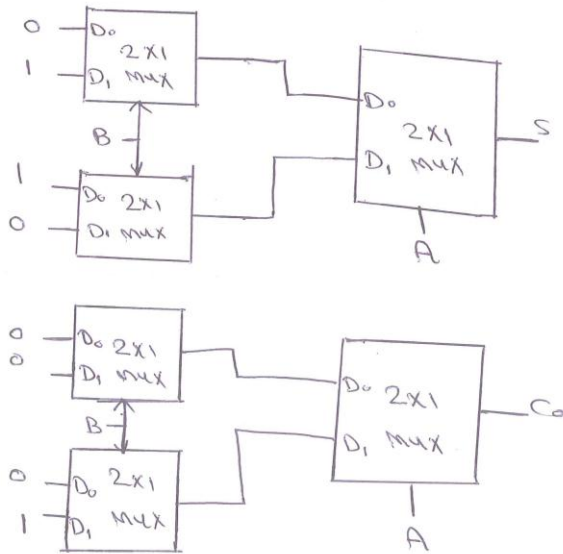

H.w:- Implement FA by using:-

- 1- proper mux
- 2- 4x1 mux
- 3- 2x1 mux
- 4- (2x1) multiplexers.

Ex:- Implement the following function by using

(4x1 Mux) and (2x1 Mux). $F = \sum 0, 1, 3, 4, 8, 9, 15$.

Solution:-


| ABCD | F |
|------|---|
| 0000 | 1 |
| 0001 | 1 |
| 0010 | 0 |
| 0011 | 1 |
| 0100 | 1 |
| 0101 | 0 |
| 0110 | 0 |
| 0111 | 0 |
| 1000 | 1 |
| 1001 | 1 |
| 1010 | 0 |
| 1011 | 0 |
| 1100 | 0 |
| 1101 | 0 |
| 1110 | 0 |
| 1111 | 1 |

4x1 mux Need 2 select line
 2x1 mux Need 1 select line
 ∴ total no. of select line = 2+1=3

A is a select line for 2x1 mux
 Bc are select lines for 4x1 mux
 D is an input.


| SL input | D ₀ BC | D ₁ BC | D ₂ BC | D ₃ BC |
|-----------|----------------------|----------------------|----------------------|----------------------|
| \bar{D} | 0 | 2 | 4 | 6 |
| D | 1 | 3 | 5 | 7 |
| result | 1 | D | \bar{D} | 0 |

| SL input | D ₀ BC | D ₁ BC | D ₂ BC | D ₃ BC |
|-----------|----------------------|----------------------|----------------------|----------------------|
| \bar{D} | 8 | 10 | 12 | 14 |
| D | 9 | 11 | 13 | 15 |
| result | 1 | 0 | 0 | D |

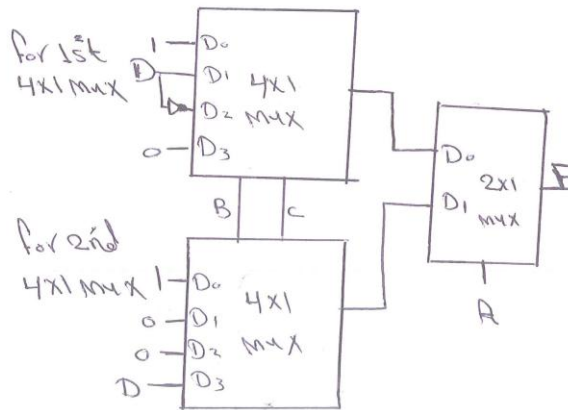


Demultiplexer

 A demultiplexer (DMUX) basically reverses the multiplexing function. It takes data from one line and distributes them to a given number of output lines.



Ex:- $F = \sum 0, 2$


| $S_1 S_0$ | F | D_0 | D_1 | D_2 | D_3 |
|-----------|---|-------|-------|-------|-------|
| 00 | 1 | 1 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 | 0 |
| 10 | 0 | 0 | 0 | 1 | 0 |
| 11 | 0 | 0 | 0 | 0 | 1 |

 

when $S_1 S_0 = 00$

O/p = $D_0 = F = 1$

 Note:- The decoder with enable input can be used as Demultiplexer which is a circuit that receives information in single line and transmit this information on the multi output.




$$D_0 = F \bar{A} \bar{B}$$


$$D_1 = F \bar{A} B$$

$$D_2 = F A \bar{B}$$

$$D_3 = F A B$$

 

 Ex Find the value of y and z for the circuit below:-



| a | b | x | y | z |
|---|---|---|---|---|
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |