

## ② Fixed-bias Circuit: Electronics I

\* The fixed-bias circuit of Fig (4-2.)  
 \* For the dc analysis the network can be isolated from the indicated ac levels by replacing the capacitors with an open-circuit equivalent.

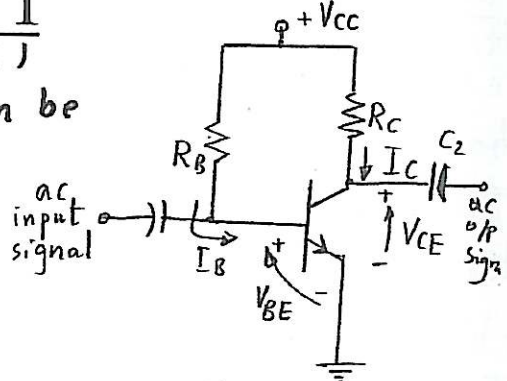


Fig (4-2)  
Fixed-bias Circuit

\* Forward bias of Base-Emmitter writing kirchhoff's voltage equation in the clockwise direction

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$



(4-4)

\* Collector-Emmitter Loop

$$I_C = \beta I_B$$

KVL applied clockwise direction

$$V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

$$V_{CE} = V_C \quad \text{since } V_E = 0$$

$$V_{BE} = V_B - V_E$$

$$V_{BE} = V_B \quad \text{since } V_E = 0$$

\* How the network parameters define the possible range of Q-points and how the actual Q-point is determined.

$$V_{CE} = V_{CC} - I_C R_C$$

on the output c/c/s is to use the fact that a straight line is defined by two points.

$$\text{set } I_C = 0 \quad \text{so } V_{CE} = V_{CC} \quad | \quad I_C = 0$$

$$\text{set } V_{CE} = 0 \quad I_C = \frac{V_{CC}}{R_C} \quad | \quad V_{CE} = 0$$

 


Fig (4-3) load line

### ③ Emitter Bias:

\* It contains an emitter resistor to improve the stability level over that of the fixed-bias.

\* Base - Emitter Loop

KVL around i/p clockwise direction.

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1) I_B$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E} \quad \text{--- (4-10)}$$

$R_E$  reflected by  $(\beta + 1)$  to the i/p resistance

\* Collector - Emitter Loop

using KVL at o/p Loop clockwise direction results:

$$+I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

substituting  $I_E \cong I_C$

$$V_{CE} - V_{CC} + I_C (R_C + R_E) = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E) \quad \text{--- (4-11)}$$

$$V_E = I_E R_E$$

$$V_{CE} = V_C - V_E$$

$$V_C = V_{CE} + V_E$$

$$V_C = V_{CC} - I_C R_C$$

$$\text{also } V_B = V_{CC} - I_B R_B$$

$$V_B = V_{BE} + V_E$$

\* and for d.c load line connected between

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E} \Big|_{V_{CE}=0}$$

$$\text{and } V_{CE} = V_{CC} \Big|_{I_C=0}$$

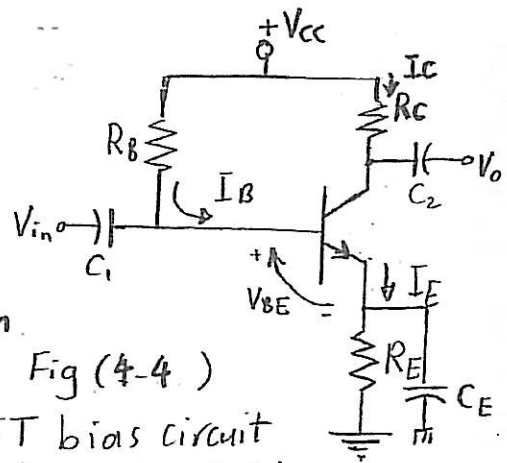


Fig (4-4)  
BJT bias circuit  
with emitter resistor

# Electronics I

\* Set  $R_c = R_L$

slope of ac load line:

$$\text{line} = -\frac{1}{R_L}$$

$$y - y_1 = m(x - x_1)$$

$$i_C - I_{CQ} = -\frac{1}{R_L} (V_{CE} - V_{CEQ})$$

$i_{Cmax}$  when  $V_{CE} = 0$

$$i_{Cmax} = I_{CQ} + \frac{V_{CEQ}}{R_L}$$

to obtain maximum symmetrical swing

$$i_{Cmax} = 2 I_{CQ}$$

$$\frac{V_{CEQ}}{R_L} = I_{CQ}$$

for d.c load line

$$V_{CC} = V_{CEQ} + I_{CQ} (R_L + R_E)$$

$$V_{CC} = I_{CQ} R_L + I_{CQ} (R_L + R_E) = 2 I_{CQ} R_L + I_{CQ} R_E$$

$$\therefore I_{CQ} = \frac{V_{CC}}{2 R_L + R_E} \text{ for max. symmetrical swing}$$

$$R_{ac} = R_c = R_L, \quad R_{dc} = R_E + R_L$$

$$I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}}$$

$$V_{CC} = V_{CEQ} + V_{CEQ} + \frac{V_{CEQ} \cdot R_E}{R_L}$$

$$\therefore V_{CEQ} = \frac{V_{CC}}{2 + \frac{R_E}{R_L}} = \frac{V_{CC}}{1 + \frac{R_L + R_E}{R_L}} = \frac{V_{CC}}{1 + \frac{R_{dc}}{R_{ac}}}$$

$$\therefore V_{CEQ} = I_{CQ} \cdot R_{ac}$$

Ex: For the circuit shown, Find the Q-point for maximum symmetrical swing.

Ans:  $I_{CQ} = 7.5 \text{ mA}$ ,  $V_{CEQ} = 3.75 \text{ V}$


 


Fig (4-5) A

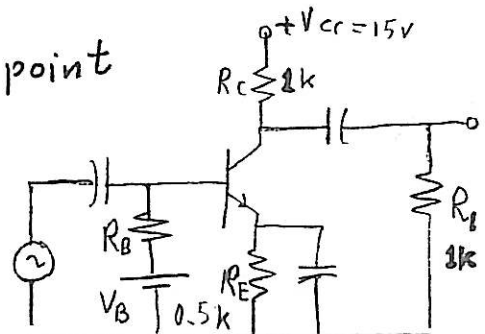

# Electronics I

## ④ DC bias with Voltage feedback:

\* An improved level of stability can be obtained by introducing a feedback path from collector to base as shown.

Base - Emitter Loop:

Writing KVL around clockwise direction

$$V_{CC} - I_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$(I_C = I_C + I_B) \approx I_C = \beta I_B$$

$$V_{CC} - V_{BE} - \beta I_B (R_C + R_E) - I_B R_B = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta (R_C + R_E)} \quad \text{--- (4-12)}$$

 


Fig (4-5)  
DC bias Circuit with voltage feedback.

\* In general, the feedback path results in a reflection of the resistance  $R_C$  back to the input circuit, much like the reflection of  $R_E$ .

Collector - Emitter Loop

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since  $I_C \approx I_C$  and  $I_E \approx I_C$  we have

$$I_C (R_C + R_E) + V_{CE} - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E) \quad \text{--- (4-13)}$$

## ⑤ VOLTAGE-DIVIDER BIAS: ( $\beta$ -independent)

\* It is independent of  $\beta$  such a network

Exact Analysis

The Thévenin equivalent network to the left of the base terminal can be found in following manner:

$$R_{th} = R_1 // R_2$$

$$E_{th} = V_{R_2} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} \quad \{6.7\}$$

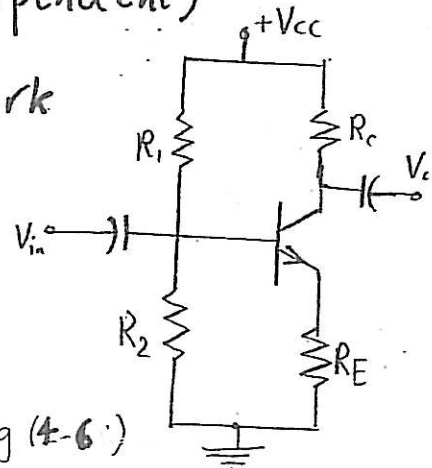


Fig (4-6)  
Voltage divider bias Configuration