

# Electronics I

the coupling capacitors  $C_1$  and  $C_2$  and bypass capacitor  $C_3$  were chosen to have a very small reactance at the frequency of application.

\* It is important to define the ac equivalent parameters of interest such as  $Z_i$ ,  $Z_o$ ,  $I_i$  and  $I_o$

$$\text{voltage gain} = \frac{V_o}{V_i}$$

$$\text{Current gain} = \frac{I_o}{I_i}$$

$$\text{input impedance} = Z_{in}$$

$$\text{output impedance} = Z_o$$

\* Transistor equivalent model will be introduced to complete the ac analysis of the network of Fig (5-3).

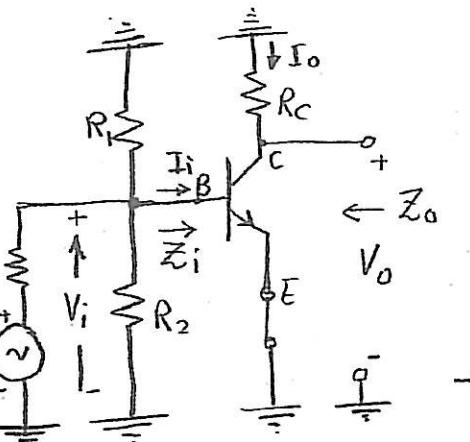


Fig (5-2)

The network of Fig (2-1) following removal of the dc supply and insertion of the short-circuit equivalent for the capacitors

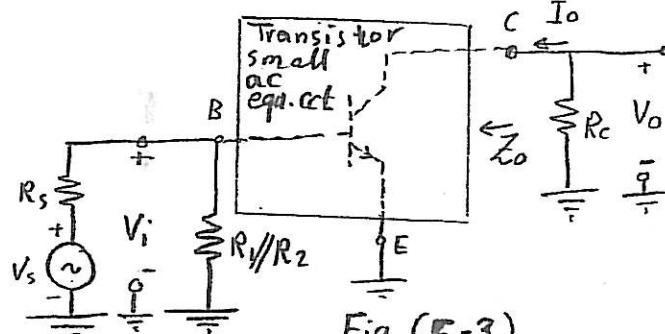


Fig (5-3).

Circuit of Fig (5-3) redrawn for small-signal ac analysis


### (3) The $V_E$ transistor Model:

\* The  $V_E$  model for the CB, CE and CC BJT transistor configurations will now be introduced


#### Common-base Configuration

Fig (5-4)

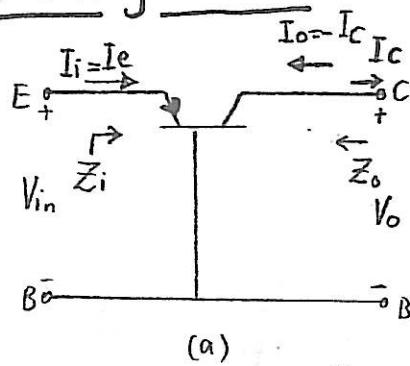Common-base BJT transistor  $V_E$  model for the configuration of (a).



(a)

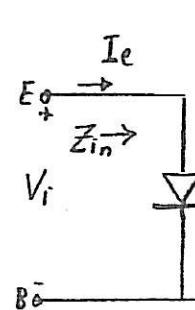

(b)


# Electronics I

- \* The transistor (CB) has been replaced by the  $r_e$  model which replaced by a single diode between emitter and base terminals and controlled current source between base and collector terminals.
- \* For the ac response, the diode can be replaced by its equivalent ac response. Recall ac resistance of a diode can be determined by the equation  $r_{ac} = \frac{26 \text{ mV}}{I_D \text{ mA}}$ , where  $I_D$  is the dc current through the diode.

$$r_e = \frac{26 \text{ mV}}{I_E}$$

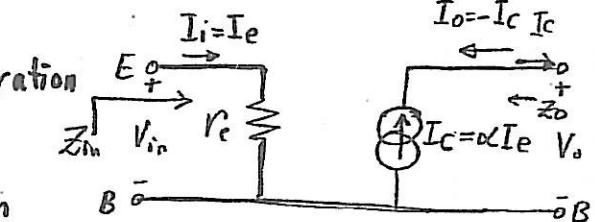--- (5-1)

- \* For the common-base configuration typical values of  $Z_i = r_e$  range from a few ohms to a maximum of about  $50 \Omega$ .



Fig(5-5)  
Common base  $r_e$  equ. circ.

- \* In general, for the Common-base configuration the input impedance is relatively small and the output impedance quite high.

- \* In general, for the Common-base configuration voltage gain will now be determined for the network of Fig 5-6


$$V_o = -I_o R_L = -(-I_c) R_L = \alpha I_e R_L$$

$$V_i = I_i Z_i = I_e Z_i = I_e r_e$$

$$A_V = \frac{V_o}{V_i} = \frac{\alpha I_e R_L}{I_e r_e} = \frac{\alpha R_L}{r_e} \approx \frac{R_L}{r_e}$$

$$A_i = \frac{I_o}{I_i} = \frac{-I_e}{I_e} = -\alpha \approx -1$$

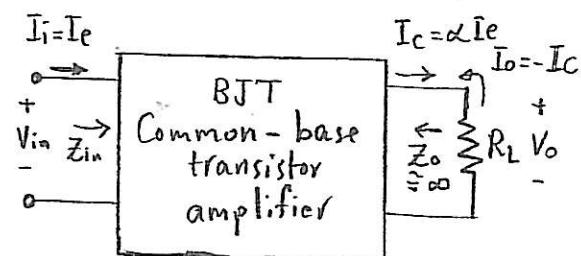$V_i$  and  $V_o$  are inphase for C.B.C {73}



Fig(5-6)  
Defining  $A_V = \frac{V_o}{V_i}$  for C.B.C



## Electronics I

### Common-Emitter Configuration.

\* The emitter terminal is common between the input and output ports of the amplifier.

$$I_C = \beta I_B \quad \dots \quad (5-2)$$

The current through the diode is:

$$I_E = I_C + I_B = \beta I_B + I_B$$

$$I_E = (\beta + 1) I_B \quad \dots \quad (5-3)$$

$$Z_i = \frac{V_i}{I_i} = \frac{V_{BE}}{I_B} = \frac{(\beta + 1) I_B R_E}{I_B} = (\beta + 1) R_E \approx \beta R_E \quad \dots \quad (5-4)$$

\* For C-E-C, typical values of  $Z_i$  defined

by  $\beta R_E$  range from few hundred ohms to the kilohm range, with maxima of about  $6 k\Omega$  to  $7 k\Omega$ .

\* For the output impedance, the

Circuits of interest are the output set of Fig (5-9).

for C-E-C, typical values of  $Z_o$  are in the range of  $40 k\Omega$  to  $50 k\Omega$ .

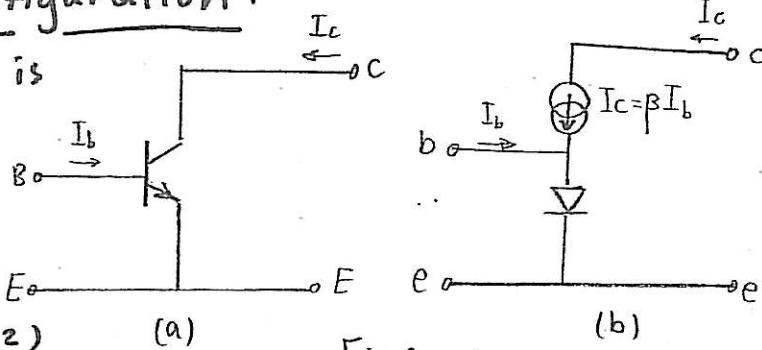


Fig (5-7)

a) C-E BJT transistor

b) approximate model for the configuration of (a)

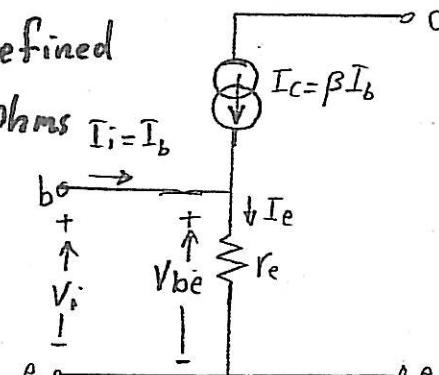


Fig (5-8)

Determining  $Z_i$  using + approximate model

\* For the model of Fig (5-10), if the applied signal is set to zero,

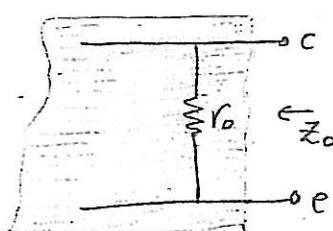


Fig (5-10)

the current  $I_C$  is indicating  $r_o$  in the OA and the transistor equiv. cct. output impedance is

$$Z_o = r_o \quad \text{--- (5-5)}$$

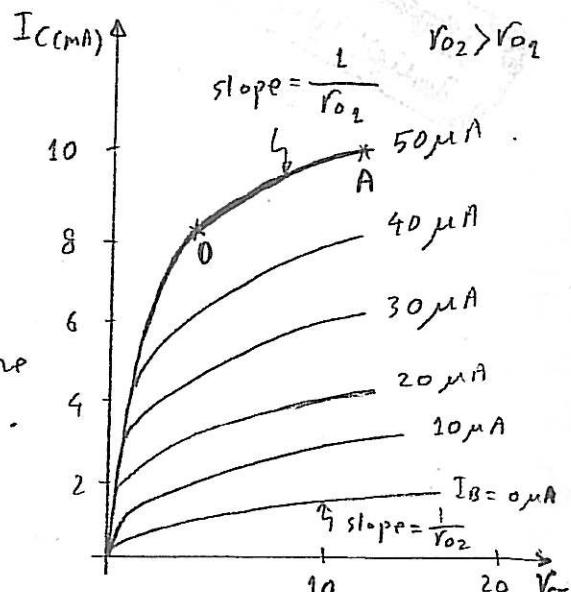


Fig (5-9)

\* For the defined direction of  $I_o$  and polarity of  $V_o$ ,

$$V_o = -I_o R_L = -I_C R_L \\ = -\beta I_b R_L$$

$$V_i = I_i Z_i = I_b \beta r_e$$

$$Av = \frac{V_o}{V_i} = -\frac{\beta I_b R_L}{\beta I_b r_e}$$

$$Av = -\frac{R_L}{r_e} \quad \text{--- (5-6)}$$

$$A_i = \frac{I_o}{I_i} = \frac{I_c}{I_b} = \frac{\beta I_b}{I_b} = \beta$$

$$A_i = \beta \quad \text{--- (5-7)}$$

Defining  $r_o$  for the C-E-C

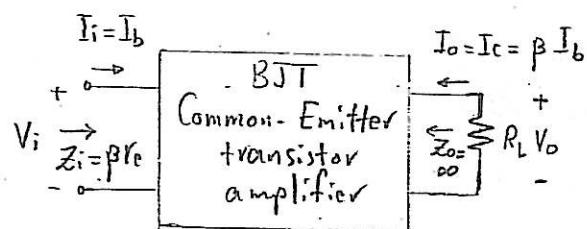


Fig (5-11)

Determining the voltage and current gain for the C-E transistor amplifier

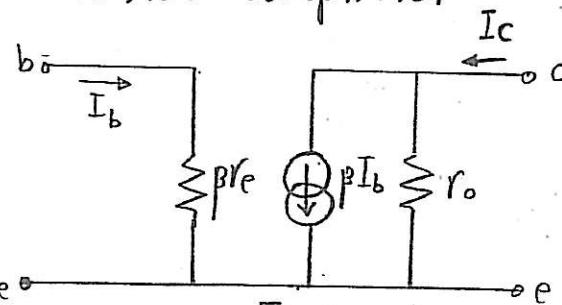


Fig (5-12)

\* So  $Z_i = \beta r_e$ ,  $I_e = \beta I_b$ ,  $Z_o = r_o$   
we find the equivalent model of Fig (5-12)

COMMON-COLLECTOR Configuration:

The model defined for the C-E-C of Fig (5-7) is normally applied rather than defining a model for the C.C.C.