

#### 4) The Hybrid Equivalent Model :

We will begin with the general two-port system of Fig (5-13) which defined as a linear circuit that gives the same response at the o/p and i/p ports.

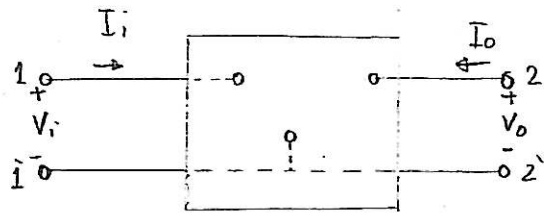


Fig (5-13)  
Two-port system

\* By equating the parameters of a network to the measured parameters of the transistor, a two-port equivalent circuit can be made to act as does the transistor in the circuit

\* We can use :

- 1) Impedance (Z) parameters /  $V_i, V_o$  interms of  $I_i$  and  $I_o$
- 2) Admittance (Y) parameter /  $I_i, I_o$  interms of  $V_i$  and  $V_o$
- 3) Input parameters
- 4) Output parameters
- 5) Hybrid (h) Parameters: which is the most frequently employed in transistor circuit analysis, however, and therefore is discussed in details:

$$V_i = h_{11} I_i + h_{12} V_o \quad \text{----- (5-8)}$$

$$I_o = h_{21} I_i + h_{22} V_o \quad \text{----- (5-9)}$$



\* The term hybrid was chosen because the mixture of variables (V and I) in each equation results in a hybrid set of units of measurement for the h-parameters.

$$h_{11} = \left. \frac{V_i}{I_i} \right|_{V_o=0} \quad \text{ohms (short-circuit input-impedance parameter) ----- (5-10)}$$

$$h_{12} = \left. \frac{V_i}{V_o} \right|_{I_i=0} \quad \text{unitless (open cct. reverse transfer voltage ratio parameter) --- (5-11)}$$

$$h_{22} = \left. \frac{I_o}{V_o} \right|_{I_i=0} \quad \text{siemens (open-circuit output admittance parameter) --- (5-12)}$$

$h_{21} = \frac{I_o}{I_i} \Big|_{V_o=0}$  (short circuit forward transfer current ratio parameter) --- (5-13)

\* apply KVL for equation (5-8) as an input cct.  
 apply KCL for equation (5-9) as an output cct.  
 we get the complete hybrid equivalent cct with a new set of subscripts for the h-parameters.

- $h_{11} \rightarrow$  input resistance  $\rightarrow h_i$
- $h_{12} \rightarrow$  reverse transfer voltage ratio  $\rightarrow h_r$
- $h_{21} \rightarrow$  forward transfer current ratio  $\rightarrow h_f$
- $h_{22} \rightarrow$  output conductance  $\rightarrow h_o$

\* The circuit of Fig (5-14) is applicable to any linear three-terminal electronic device or system.

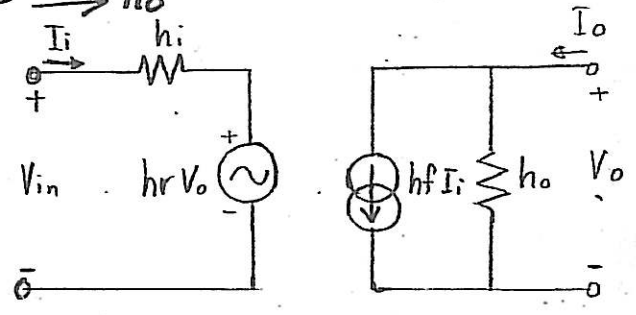


Fig (5-14)

Complete hybrid equivalent circuit

\* Transistor is a three terminal device, even though it has three basic configuration.

\* For C-E, a second subscript (e) has been added to the h-parameter notation.

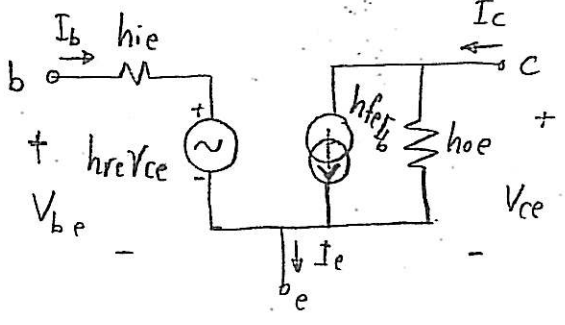
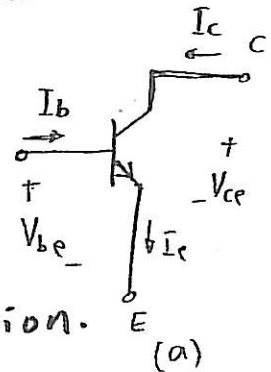


Fig (5-15) (b)

a) graphical symbol  
 b) hybrid equivalent circuit

\* For C.B.C of Fig (5-16) a subscript (b) to h-parameter notation.

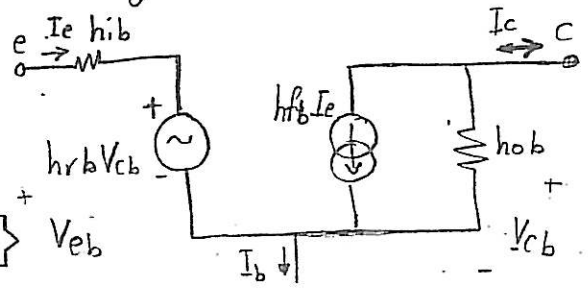
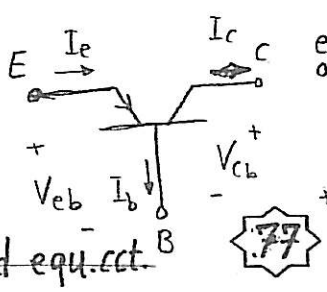


Fig (5-16)  
 a) Symbol  
 b) hybrid equ. cct.

\* For the common-emitter and Common-base configurations the magnitude of  $h_r$  and  $h_o$  is often such that the results obtained for the important parameters such as  $Z_i, Z_o, A_v$  and  $A_i$  are only slightly affected if  $h_r$  and  $h_o$  are not included in the model.

\* set  $h_r \cong 0$  so  $h_r V_o \cong 0$  (S.C equivalent)  
 set resistance  $\frac{1}{h_o}$  large enough to be ignored in comparison to a parallel load (O.C equivalent).

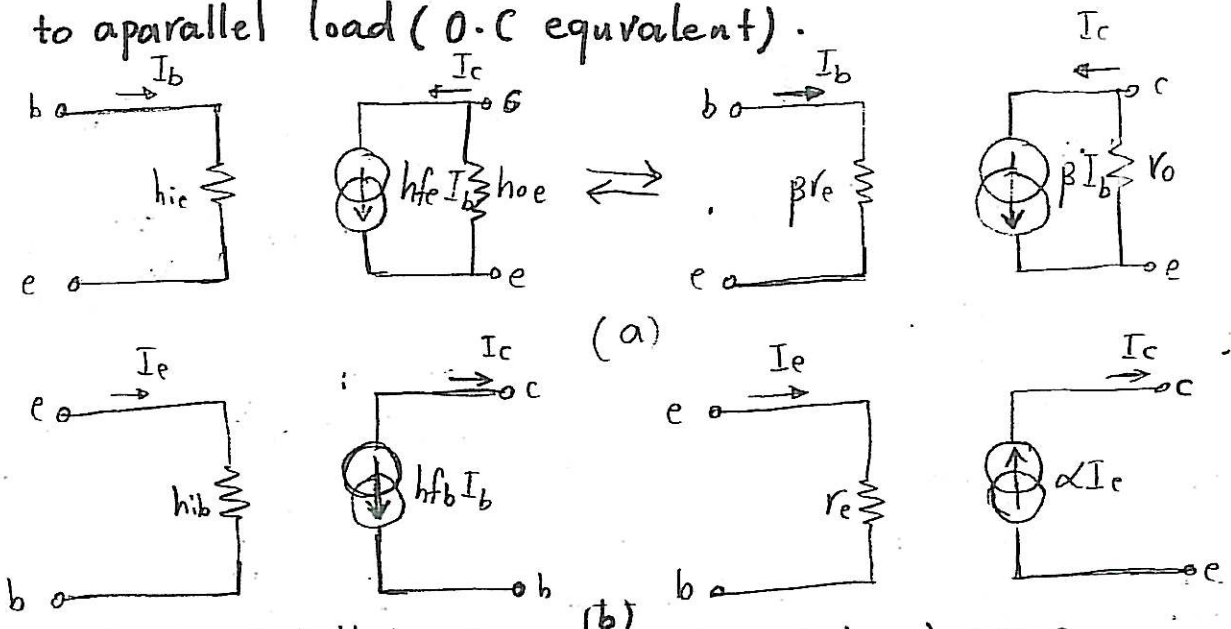


Fig (5-17) Hybrid versus  $r_e$  model a) C.E.C  
 b) C.B.C

\* It should be reasonably clear from Fig (5-17) a that:

$$h_{ie} = \beta r_e \quad \text{--- (5-14)}$$

$$h_{fe} = \beta_{ac} \quad \text{--- (5-15)}$$

From Fig (2-17) b

$$h_{ib} = r_e \quad \text{--- (5-16)}$$

$$h_{fb} = -\alpha \cong -1 \quad \text{--- (5-17)}$$

\* With some approximate conversion equations

$$h_{ie} = \frac{h_{ib}}{1 + h_{fb}} \cong \beta r_e$$

$$h_{oe} \cong \frac{h_{ob}}{1 + h_{fb}}$$

$$h_{ic} \cong \frac{h_{ib}}{h_{fb} + 1} \cong \beta r_e$$

$$h_{re} \cong \frac{h_{ib} h_{ob}}{1 + h_{fb}} - h_{rb}$$

$$h_{ib} \cong \frac{h_{ie}}{h_{fe} + 1} \cong -\frac{h_{ie}}{h_{fe}} \cong r_e$$

$$h_{rc} \cong 1$$

$$h_{fe} \cong \frac{-h_{fb}}{1 + h_{fb}} \cong \beta$$

78

$$h_{fc} \cong \frac{-2}{h_{fb} + 1} \cong -\beta$$

$$h_{fb} \cong \frac{-h_{fe}}{h_{fe} + 1} \cong -1 = -\alpha$$

## 5) Hybrid $\pi$ Model:

\* The hybrid  $\pi$  model appear in Fig (2-18) with all the parameters necessary for a full-frequency analysis.

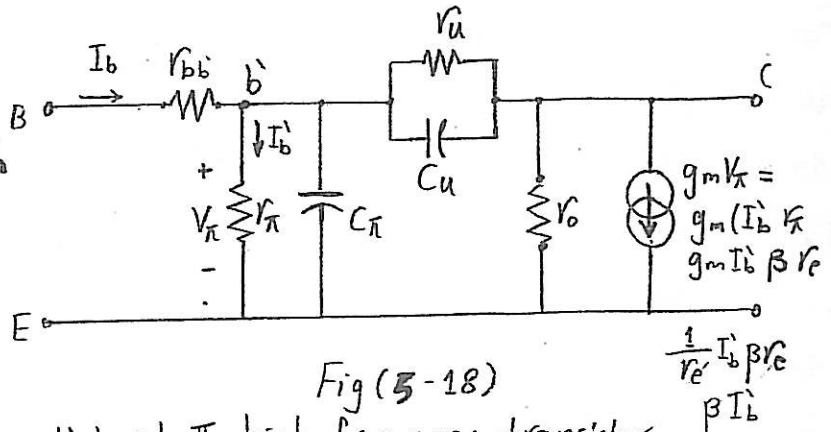


Fig (5-18)  
Hybrid  $\pi$  high frequency transistor small-signal ac equivalent circuit

\* All the capacitors that appear in Fig (5-18)

are stray parasitic capacitors between the various junction of the device, play at high frequencies. For low to mid-frequencies their reactance is very large and can be considered open circuits.  $C_u$ : few picofarads (PF).

\* The resistors  $r_\pi$ ,  $r_u$  and  $r_o$  are the resistances between the indicated terminals of the device

\* The resistance  $r_u$  (the subscript u refers to the union, is very large resistance, and provides a feedback path from output to input circuits.

$$r_\pi = \beta r_e \quad \text{--- (5-18)}$$

$$g_m = \frac{1}{r_e} \quad \text{--- (5-19)}$$

$$r_o = \frac{1}{h_{oe}} \quad \text{--- (5-20)}$$

$$h_{re} = \frac{r_\pi}{r_\pi + r_u} \approx \frac{r_\pi}{r_u} \quad \text{--- (5-21)}$$

## 6) COMMON-EMITTER FIXED-BIAS CONFIGURATION:

\* Circuit of Common-emitter fixed-bias network of Fig (2-19)

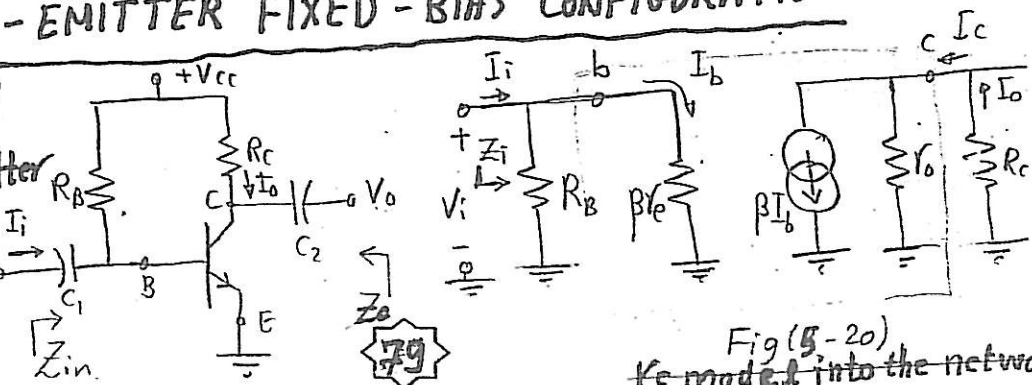


Fig (5-20)  
 $r_e$  model into the network