

If we construct the network defined by Eq. of I_e .

To determine Z_o , V_i is set to zero and $Z_o = R_E // r_e \cong r_e$ (low) if $R_E \gg r_e$

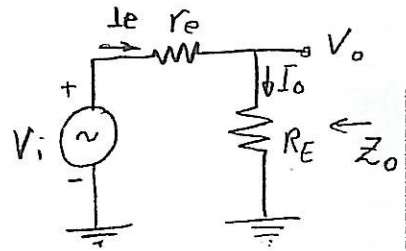


Fig (5-28) Defining the output impedance for emitter-fol

A_v $V_o = V_i * \frac{R_E}{R_E + r_e}$ (voltage divider rule)

$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$

R_E is usually much greater than r_e
 $R_E + r_e \cong R_E$ and:
 V_o and V_i are inphase

$A_v = \frac{V_o}{V_i} \cong 1$

Effect of r_o

Z_i $Z_b = \beta r_e + \frac{(\beta + 1) R_E}{1 + \frac{R_E}{r_o}}$ (high)

if $r_o \gg 10 R_E$

$Z_b = \beta r_e + (\beta + 1) R_E \cong \beta (r_e + R_E)$ $r_o \gg 10 R_E$

Z_o

$Z_o = r_o // R_E // \frac{\beta r_e}{(\beta + 1)}$

using $(\beta + 1) \cong \beta$

$Z_o = r_o // R_E // r_e$

and since $r_o \gg r_e$

$Z_o \cong R_E // r_e \cong r_e$ (very low)



A_v

$A_v = \frac{(\beta + 1) R_E / Z_b}{1 + \frac{R_E}{r_o}}$

for $r_o \gg 10 R_E$
 $\beta + 1 \cong \beta$

$A_v \cong \frac{\beta R_E}{Z_b}$

but $Z_b = \beta (r_e + R_E)$

so that $A_v \cong \frac{\beta R_E}{\beta (r_e + R_E)} \cong \frac{R_E}{r_e + R_E}$

A_i

$A_i = -A_v * \frac{Z_{in}}{R_L} \cong -1 * \frac{\beta R_E}{R_E} \cong -\beta$

10) COMMON-BASE CONFIGURATION:

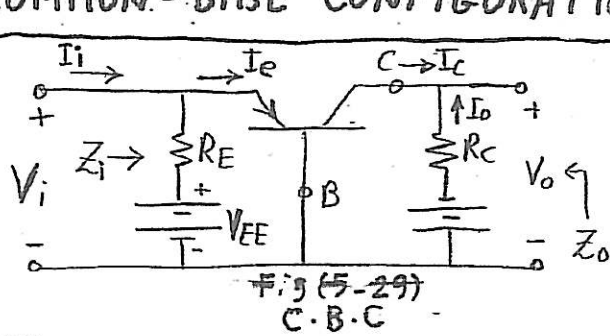


Fig (5-29)
C.B.C

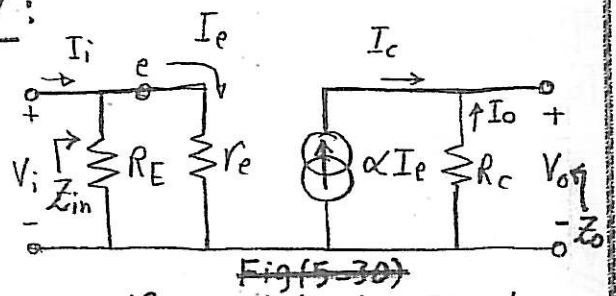


Fig (5-30)

r_e equivalent circuit

* The C.B.C is characterized by low input and high output impedance and a current gain less than 1. The voltage gain, however, can be quite large.

Z_i $Z_i = R_E // r_e \approx r_e$

Z_o $Z_o = R_C$

A_v $V_o = -I_o R_C = -(-I_c) R_C = \alpha I_e R_C$

$$I_e = \frac{V_i}{r_e}$$

$$V_o = \alpha \left(\frac{V_i}{r_e} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} \approx \frac{R_C}{r_e}$$

A_i assume $R_E \gg r_e$ yields

$$I_e \approx I_i$$

$$I_o = -\alpha I_e = -\alpha I_i$$


$$A_i = \frac{I_o}{I_i} = -\alpha \approx -1$$

* For C.B.C, $r_o = \frac{1}{h_{ob}}$ is typically in the megohm range

so $r_o // R_C \approx R_C$

11) COLLECTOR FEEDBACK CONFIGURATION:

* The collector feedback network of Fig (5-31) employs a feedback path from collector to base

* Substituting the equivalent circuit and redrawing the network results in the  configuration of Fig (5-32).

$$Z_i \parallel \dot{I} = \frac{V_o - V_i}{R_F}$$

$$V_o = -I_o R_c$$

$$I_o = \beta I_b + \dot{I}$$

$$\beta I_b \gg \dot{I}$$

$$I_o \approx \beta I_b$$

$$V_o = -(\beta I_b) R_c = -\beta I_b R_c$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) R_c = -\frac{R_c}{r_e} V_i \Rightarrow \underline{\underline{A_v}} = -\frac{R_c}{r_e}$$

$$\dot{I} = \frac{V_o - V_i}{R_F} = \frac{V_o}{R_F} - \frac{V_i}{R_F} = -\frac{R_c V_i}{r_e R_F} - \frac{V_i}{R_F} = -\frac{1}{R_F} \left[1 + \frac{R_c}{r_e} \right] V_i$$

$$V_i = I_b \beta r_e = (I_i + \dot{I}) \beta r_e = I_i \beta r_e + \dot{I} \beta r_e$$

$$V_i = I_i \beta r_e - \frac{1}{R_F} \left[1 + \frac{R_c}{r_e} \right] \beta r_e V_i$$

$$V_i \left[1 + \frac{\beta r_e}{R_F} \left(1 + \frac{R_c}{r_e} \right) \right] = I_i \beta r_e$$

$$Z_i = \frac{V_i}{I_i} = \frac{\beta r_e}{1 + \frac{\beta r_e}{R_F} \left[1 + \frac{R_c}{r_e} \right]}$$

but $R_c \gg r_e$

$$1 + \frac{R_c}{r_e} \approx \frac{R_c}{r_e}$$

$$\text{so that } Z_i = \frac{\beta r_e}{1 + \frac{\beta R_c}{R_F}} = \frac{r_e}{\frac{1}{\beta} + \frac{R_c}{R_F}}$$

Z_o if we set V_i to zero as required to define Z_o , the network will appear as shown in Fig (5-33). The effect of βr_e is removed and R_F appears in parallel with R_c and

$$Z_o \approx R_c \parallel R_F$$

$$\underline{\underline{A_v}} \text{ at node c } \quad I_o = \beta I_b + \dot{I}$$

$$\beta I_b \gg \dot{I} \text{ and } I_o \approx \beta I_b$$

$$V_o = -I_o R_c = -(\beta I_b) R_c$$

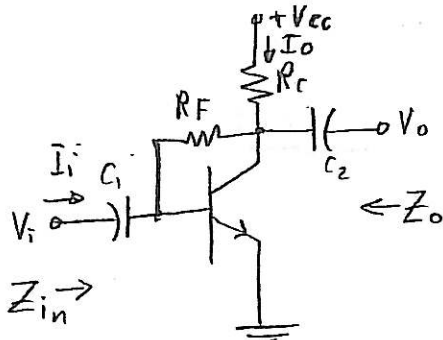


Fig (5-31)

Collector feedback Configuration

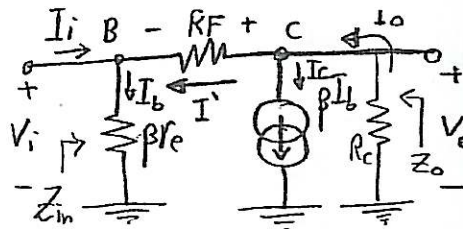


Fig (5-32)
re equivalent circuit

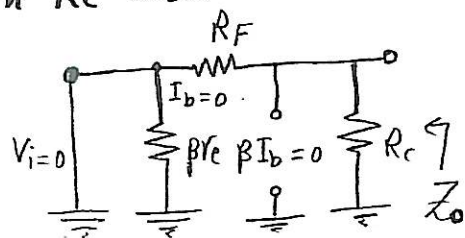


Fig (5-33)