

ELECTRONICS I

Substituting $I_b = V_i / \beta r_e$ gives

$$V_o = -I_o R_c = -\beta \frac{V_{in}}{\beta r_e} R_c$$

$$A_v = \frac{V_o}{V_i} = -\frac{R_c}{r_e}$$

* Or we can use Miller's theorem which states:
if we have an impedance (Z) connected between two different potential points N_1, N_2 can be transferred V_1 in two impedance one into input the other into output side

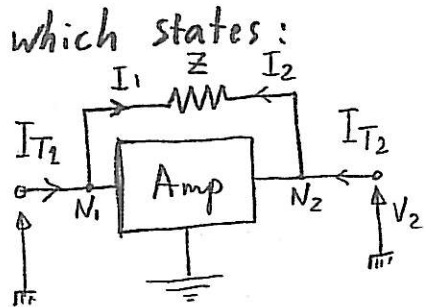


Fig (5-34)

let $\frac{V_2}{V_1} = k = A_v$

so $I_1 = \frac{V_1 - V_2}{Z}$

$I_1 = \frac{V_1(1 - k)}{Z}, \therefore I_2 = \frac{V_1}{Z_1}$

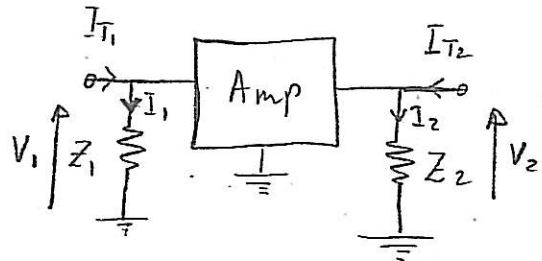


Fig (5-35)

$$\therefore Z_1 = \frac{Z}{1 - k} \quad \text{--- (5-22)}$$

$$I_2 = \frac{V_2 - V_1}{Z} = \frac{V_2 - \frac{V_2}{k}}{Z} = \frac{V_2}{Z} \left(1 - \frac{1}{k}\right)$$

$\therefore I_2 = \frac{V_2}{Z_2}$

$$\therefore Z_2 = \frac{Z}{1 - \frac{1}{k}} \quad \text{--- (5-23)}$$

if $1 \gg \frac{1}{k} \Rightarrow Z_2 \cong Z$

second case :

if $\frac{I_2}{I_1} = A_I$

For Fig (3-36)

$V_1 = (I_1 - I_2)Z$
 $= Z I_1 (1 - A_I)$

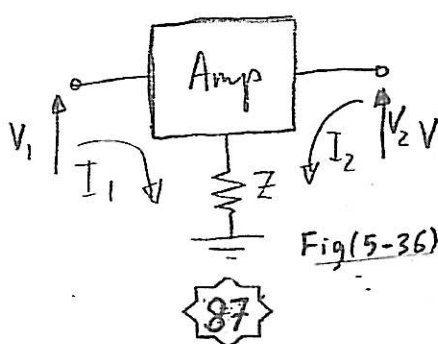


Fig (5-36)

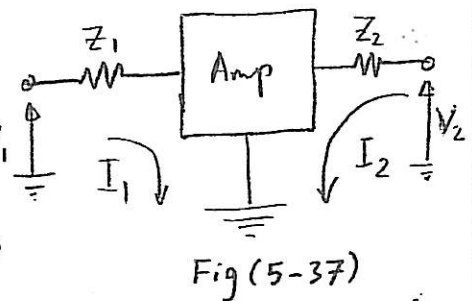


Fig (5-37)

$$V_1 = I_1 Z_1 \quad \text{Fig (5-37)}$$

$$\boxed{Z_1 = Z (1 - A_i)} \quad \text{--- (5-24)}$$

also: $V_2 = Z (I_2 - I_1)$
 $= Z I_2 (1 - \frac{1}{A_i})$
 $V_2 = I_2 Z_2$

$$\boxed{Z_2 = Z (1 - \frac{1}{A_i})}$$

if $A_i \gg 1 \Rightarrow Z_2 = Z$



--- (5-25)

Return to Fig (5-32) applying Miller theorem:

Consider $I_c = 0$ as $\ll \beta I_b$

so $A_v = -\frac{R_c}{r_e}$

$$Z_1 = \frac{R_F}{1 - (-\frac{R_c}{r_e})} = \frac{R_F}{1 + \frac{R_c}{r_e}}$$

$$Z_2 = \frac{R_F}{1 + \frac{r_e}{R_c}} \approx R_F \quad \text{as } \frac{r_e}{R_c} \ll 1$$

$$Z_i = \frac{\beta r_e \left(\frac{R_F}{1 + R_c/r_e} \right)}{\beta r_e + \frac{R_F}{1 + \frac{R_c}{r_e}}} = \frac{\beta r_e R_F}{\beta r_e (1 + \frac{R_c}{r_e}) + R_F} = \frac{\beta r_e}{1 + \frac{\beta r_e}{R_F} (1 + \frac{R_c}{r_e})}$$

$$Z_i = \frac{\beta r_e}{1 + \frac{\beta r_e}{R_F}} = \frac{r_e}{\frac{1}{\beta} + \frac{R_c}{R_F}}$$

$$Z_o \approx R_c \parallel R_F$$

To calculate current gain in general (A_i)

$$A_i = \frac{I_o}{I_i} = \frac{\frac{V_o}{R_L}}{\frac{V_i}{Z_i}} = \frac{V_o}{V_i} \cdot \frac{Z_i}{R_L}$$

$$\boxed{A_i = A_v \frac{Z_i}{R_L}}$$

--- (5-26)

12) Effects of R_L and R_S :

ELECTRONICS

* $A_V = \frac{V_o}{V_i}$ with R_L .

$$A_{V_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = A_V \cdot \frac{V_i}{V_s}$$

* For a particular amplifier, the larger the level of R_L , and the smaller the internal resistance of the signal source, the greater is the overall gain.

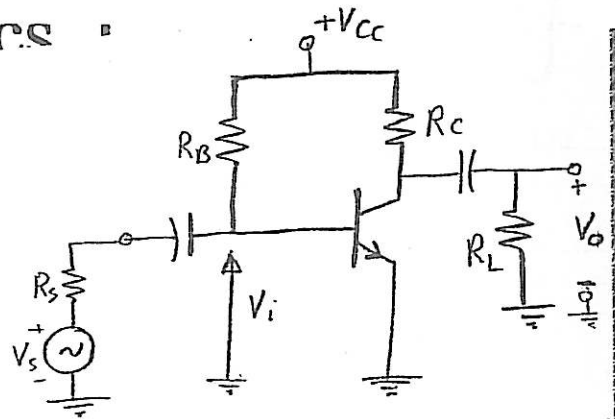


Fig (5-39)

13) CASCADED SYSTEMS :

The two-port systems is particularly useful for cascaded systems such as that appearing in Fig (5-40), where $A_{V_1}, A_{V_2}, A_{V_3}$ and so on, are the voltage gain of each stage under loaded

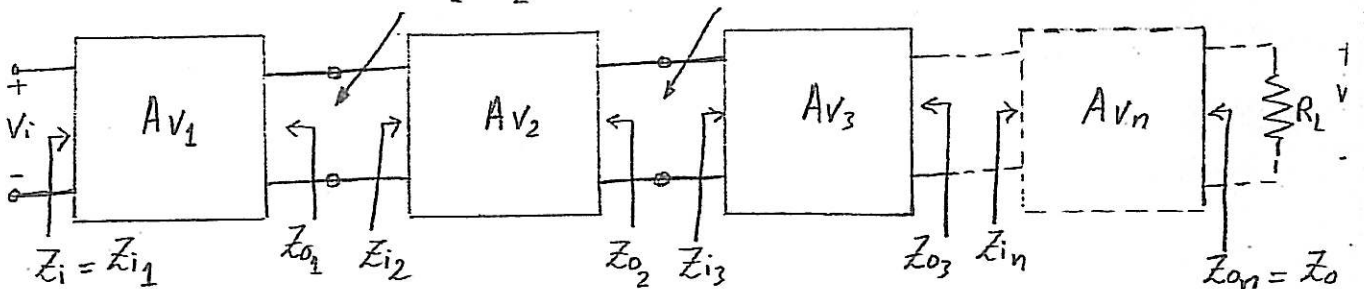


Fig (5-40)

Cascaded System

The total gain of the system is then determined by the product of the individual gains:

$$A_{V_T} = A_{V_1} \cdot A_{V_2} \cdot A_{V_3} \dots$$

(5-27)

and the total current gain is given by

$$A_{i_T} = -A_{V_T} \frac{Z_{i_1}}{R_L}$$

* One popular connection of amplifier stages is the RC-coupled in Fig (5-41)