

- Converting a Flip-Flop:-

- 1- Design A flip-flop from B flip-flop.
- 2- Convert B Flip-flop to A Flip-flop.
- 3- Using B Flip-Flop to Design A Flip flop.

Note:- The third questions above are the same. (i.e. Designing A Flip-Flop using B flip-flop.

- There are 5 steps for flip-flop conversions:-

- 1- Identify available and required flip-flop.
- 2- Make characteristic table for required flip-flop.
- 3- Make excitation table for available flip-flop.
- 4- write boolean expression for available flip-flop.
- 5- Draw the circuit.

Note:- We can summarize the (Excitation Tables) of all flip flops

Q_n	Q_{n+1}	S	R	D	T	J	K
0	0	0	X	0	0	0	X
0	1	1	0	1	1	1	X
1	0	0	1	0	1	X	1
1	1	X	0	1	0	X	0

- Flip-Flop Excitation tables -

Example:- Convert J-K F.F to T F.F:-

Solution:- Available F/F = JK F/F

Required F/F = T F/F

T	Q_n	Q_{n+1}	J	K
0	0	0	0	X
0	1	1	X	0
1	0	1	1	X
1	1	0	X	1


$J = T$

$K = T$

c/s table & Excitation table
for T.F.F. for JK F.F

Q_n/T	\bar{T}	T
Q_n	0	1
\bar{Q}_n	X	X

Q_n/T	\bar{T}	T
Q_n	X	X
\bar{Q}_n	0	1

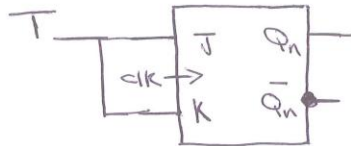

Example:- Convert RS F/F to D Latch

Solution:- Available F/F = RS F/F

Required F/F = D Latch

D	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0


$S = D$

$R = \bar{D}$

c/s table & Excitation table
for D.F.F for SR F.F.

Q_n/D	\bar{D}	D
Q_n	0	1
\bar{Q}_n	0	X

Q_n/D	\bar{D}	D
Q_n	X	0
\bar{Q}_n	1	0

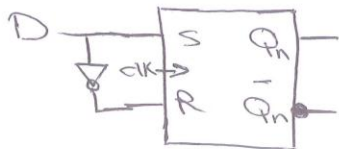

Example:- Design T. f/f, using R.S F/F

Solution:- Available F/F = SR F/F
 Required F/F = T f/f

T	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1


c/c's table & Excitation table
 for T f/f

$$S = T \bar{Q}_n$$

$Q_n \backslash T$	\bar{T}	T
\bar{Q}_n	0	1
Q_n	X	0

$Q_n \backslash T$	\bar{T}	T
\bar{Q}_n	X	0
Q_n	0	1

$$R = T Q_n$$

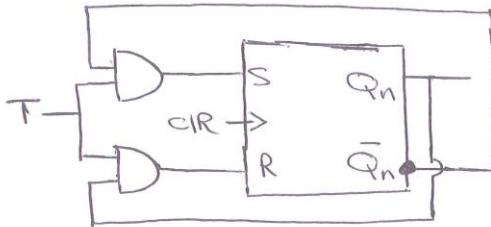

Example:- Using D f/f to design T. f/f

Solution:- Available F/F = D f/f
 Required F/F = T f/f

T	Q_n	Q_{n+1}	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

c/c's table & Excitation table
 for T f/f

$Q_n \backslash T$	\bar{T}	T
\bar{Q}_n	0	1
Q_n	1	0

$$D = T \bar{Q}_n + \bar{T} Q_n$$



Example: Design J-K f/f. using T f/f

Solution: Available F/F = T F/F


Required F/F = JK F/F

J	K	Q_n	Q_{n+1}	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

Q_n \ JK	$\bar{J}\bar{K}$	$\bar{J}K$	$J\bar{K}$	JK
0	0	0	1	1
1	0	1	1	0

$$T = J\bar{Q}_n + KQ_n$$

CKS table & Excitation table for JK F/F

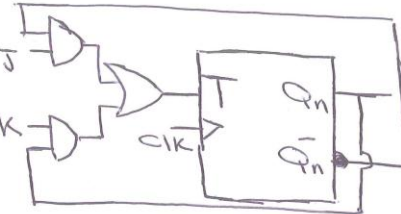

- How:-
- 1- JK to D flip-flop conversion.
 - 2- T flip-flop to D flip-flop conversion.
 - 3- SR flip-flop to JK flip-flop conversion.
 - 4- SR flip-flop to T flip-flop conversion.
 - 5- JK flip-flop to SR flip-flop conversion.

[Signature]
 2017/2/17
 Asst. Lect. Besma Nazir

Difference between Synchronous and Asynchronous SequentialCircuits:-Synchronous Seq. ckt.

- 1- These circuits are easy to design.
- 2- A clocked flip-flops acts as memory element.
- 3- They are slower.
- 4- The status of memory element is affected only at the active edge of clock, if input is changed.

Asynchronous Seq. ckt.

- 1- These circuits are difficult to design.
- 2- An unclocked flip-flops or time delay element is used as memory element.
- 3- Faster as clock is not present.
- 4- The status of memory element will change any time as soon as input is changed.