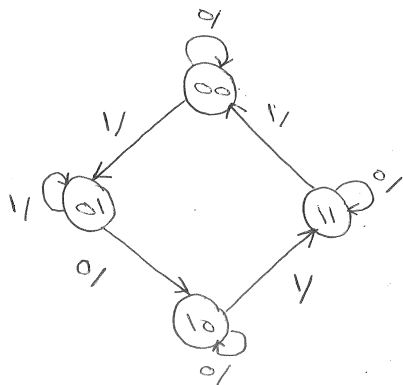


Example:- A sequential circuit has the following state diagram, design the circuit using J-K Flip-Flop:-



(state diagram)

Solution:-

Asst. lect. Besma Nazar

(17)

Present state		input X	Next state		J <sub>A</sub> K <sub>A</sub>		J <sub>B</sub> K <sub>B</sub>	
A <sub>n</sub>	B <sub>n</sub>		A <sub>n+1</sub>	B <sub>n+1</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>
0	0	0	0	0	0	d	0	d
0	0	1	0	1	0	d	1	d
0	1	0	1	0	1	d	d	1
0	1	1	0	1	0	d	d	0
1	0	0	1	0	d	0	0	d
1	0	1	1	1	d	0	1	d
1	1	0	0	0	d	1	d	1
1	1	1	0	0	d	1	d	1

X	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
0	0	1	d	d
1	0	0	d	d

$J_A = B_n \bar{X}$

X	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
0	d	d	0	0
1	d	1	0	0

$K_A = B_n X$


X	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
0	0	d	d	0
1	d	d	d	1

$J_B = X$

X	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
0	1	1	0	d
1	d	0	1	d


$K_B = \bar{A}_n \bar{X} + A_n X$

$K_B = A_n \oplus X$

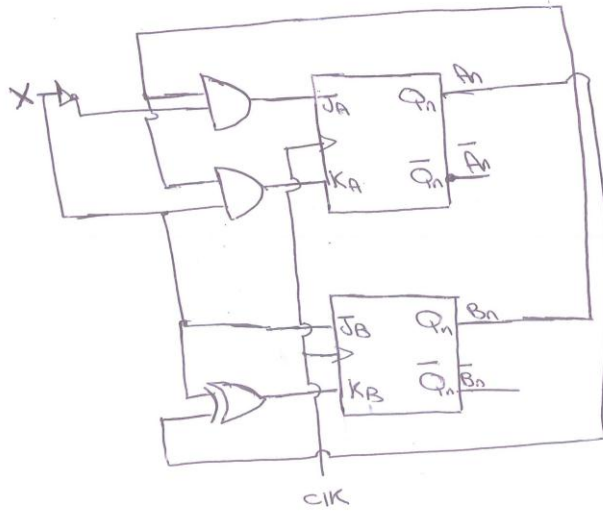

(logic diagram of seq. ckt)

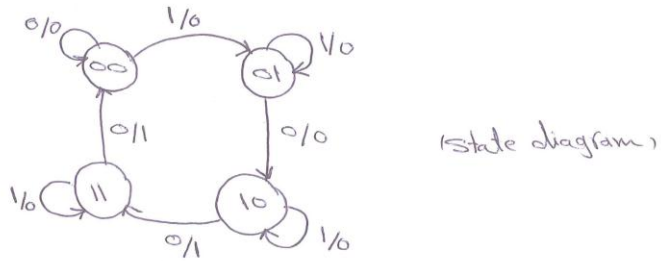Example:- For the state diagram shown below, connect the seq. circuit using T flip-flop:-



present state		input	next state				output
A <sub>n</sub>	B <sub>n</sub>	X	A <sub>n+1</sub>	B <sub>n+1</sub>	T <sub>A</sub>	T <sub>B</sub>	Y
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	1	0
0	1	1	0	1	0	0	0
1	0	0	1	1	0	1	1
1	0	1	1	0	0	0	0
1	1	0	0	0	1	1	1
1	1	1	1	1	0	0	0

X \ A <sub>n</sub> B <sub>n</sub>	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{X}$	0	1	1	0
X	0	0	0	0


X \ A <sub>n</sub> B <sub>n</sub>	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{X}$	0	1	1	1
X	1	0	0	0

X \ A <sub>n</sub> B <sub>n</sub>	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{X}$	0	0	1	1
X	0	0	0	0

$T_A = B_n \bar{X}$

$T_B = B_n \bar{X} + A_n \bar{X} + \bar{A}_n B_n X$


$Y = A_n \bar{X}$

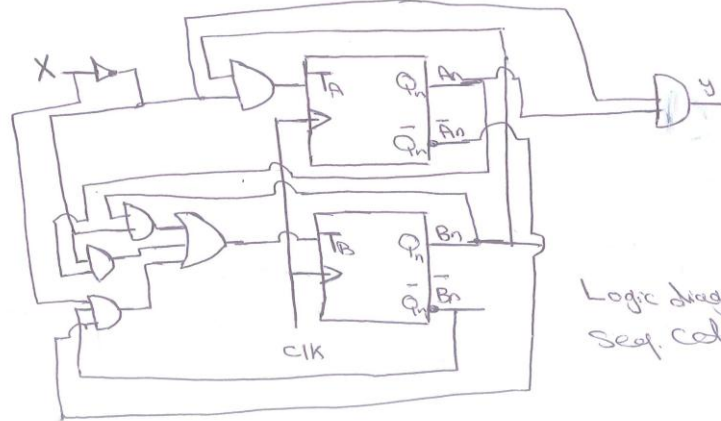

Logic diagram of seq. circ

Hw:- Repeat the previous example by using JK flip flop.

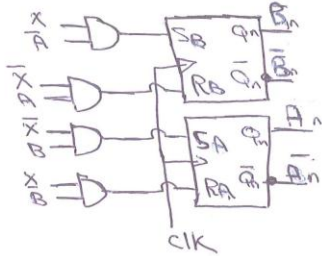Example:- For the circuit shown below, design the circuit using J-K flip flop (one input variable X & one output Y).



Note for SRFF  
 $Q_{n+1} = S + \bar{R}Q_n$   
 $SR = B\bar{X}; RA = \bar{B}X$   
 $A_{n+1} = B_n\bar{X} + (\bar{B}_nX)A_n$   
 $S_B = \bar{A}_nX; R_B = A_n\bar{X}$   
 $B_{n+1} = \bar{A}_nX + (A_n\bar{X})B_n$

Solution:-

Present state input			next state						output
$A_n$	$B_n$	X	$A_{n+1}$	$B_{n+1}$	$J_A$	$K_A$	$J_B$	$K_B$	Y
0	0	0	0	0	0	d	0	d	0
0	0	1	0	1	0	d	1	d	0
0	1	0	1	1	1	d	d	0	0
0	1	1	0	1	0	d	d	0	0
1	0	0	1	0	d	0	0	d	0
1	0	1	0	0	d	1	0	d	1
1	1	0	1	0	d	0	d	1	0
1	1	1	1	1	d	0	d	0	0

$A_n \backslash B_n$	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{X}$	0	1	d	d
X	0	0	d	d

$J_A = B_n\bar{X}$

$A_n \backslash B_n$	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{X}$	d	d	0	0
X	d	d	0	1


$K_A = \bar{B}_nX$

$A_n \backslash B_n$	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{X}$	0	d	d	0
X	1	d	d	0

$J_B = \bar{A}_nX$

$A_n \backslash B_n$	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
$\bar{X}$	d	0	1	d
X	d	0	0	d

$K_B = A_n\bar{X}$

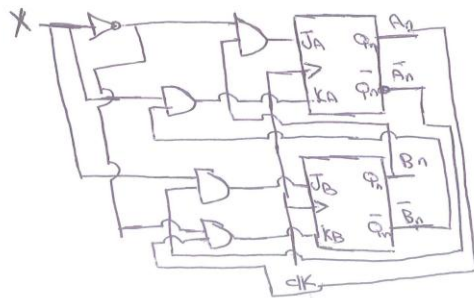

Logic diagram of seq. ckt

Example :- Use (SR) Flip-Flop as a Comparator (or: Design a Comparator using SR Flip-Flop).

Solution :- Available F.F = SR  
Reg. device = comp.

Note :- A or B can be chosen as Q or in the design

A	B	$A \geq B$	$A < B$	$A = B$	$S_Q$	$R_Q$	$S_L$	$R_L$	$S_E$	$R_E$
0	0	0	0	1	0	d	0	d	1	0
0	1	0	1	0	0	1	d	0	0	1
1	0	1	0	0	1	0	0	d	0	d
1	1	0	0	1	0	1	0	1	d	0

$\bar{B}$	A	$S_Q$
1	0	1
0	0	0

$S_Q = A\bar{B}$

B	$\bar{A}$	$R_Q$
1	0	1
1	1	1

$R_Q = B$

$\bar{B}$	$\bar{A}$	$S_L$
1	0	0
1	1	0

$S_L = 0$

B	A	$R_L$
1	0	1
0	1	0


$R_L = A$

$\bar{B}$	$\bar{A}$	$S_E$
1	0	1
0	0	0

$S_E = \bar{A}\bar{B}$

B	A	$R_E$
1	0	1
0	0	0

$R_E = \bar{A}B$

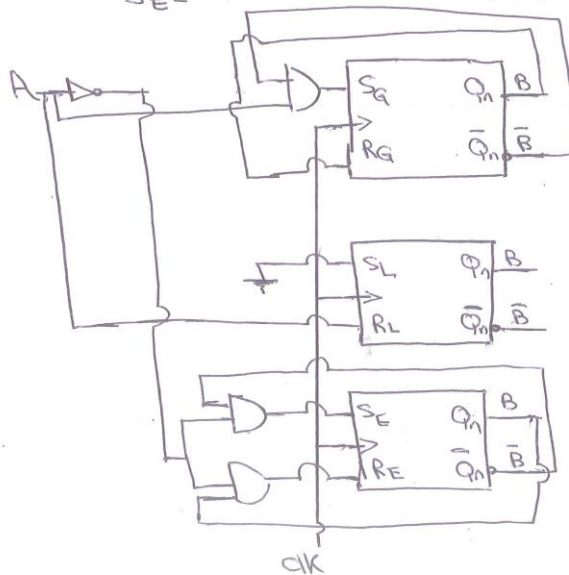

H.w.:- Repeat the Example using J.K Flip-Flop.

Example:- Use JK Flip-Flop as Half Adder:-

Solution:- Available F.F = JK  
Required Device = H.A.

A	B	S	Cout	J <sub>s</sub>	K <sub>s</sub>	J <sub>cout</sub>	K <sub>cout</sub>
0	0	0	0	0	X	0	X
0	1	1	0	X	0	X	1
1	0	1	0	1	X	0	X
1	1	0	1	X	1	X	0

B	$\bar{A}$	A
0	1	0
1	0	1

$J_s = A$

B	$\bar{A}$	A
0	1	0
1	0	1


$K_s = A$

B	$\bar{A}$	A
0	1	0
1	0	1


$J_{cout} = 0$

B	$\bar{A}$	A
0	1	0
1	0	1

$K_{cout} = \bar{A}$

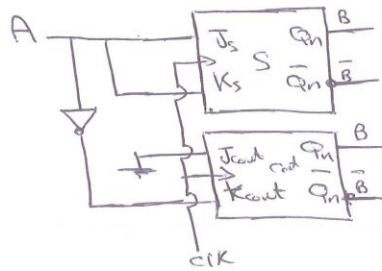

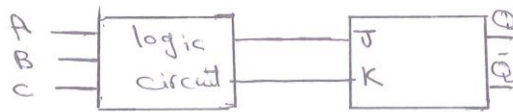Example:- Design a logic circuit shown below. The circuit will set the JK Flip-Flop if the binary number ABC is odd & will reset it otherwise.



Solution:-


A	B	C	J	K
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

$\bar{C}$	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
0	0	0	0	0
1	1	1	1	1


$J = C$

$C$	$\bar{A}\bar{B}$	$\bar{A}B$	$A\bar{B}$	$AB$
0	1	1	1	1
1	0	0	0	0

$K = \bar{C}$

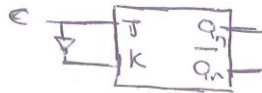

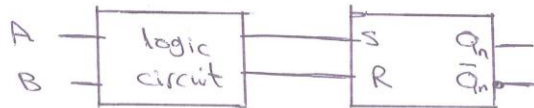Example:- The logic circuit shown below, Design the logic circuit that make the F/F set if  $A=B$  & reset otherwise.



Solution:-

A	B	S	R
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	0

$\bar{B}$	$\bar{A}$	$A$
0	1	0
1	0	1


$S = \bar{A}\bar{B} + AB$   
 $S = A \odot B$

$B$	$\bar{A}$	$A$
0	1	0
1	0	1

$R = \bar{A}B + A\bar{B}$   
 $R = A \oplus B$



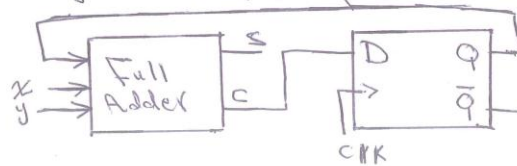Example:- A sequential circuit has one Flip-Flop ( $Q_n$ ), two inputs ( $X$  and  $Y$ ) and one output  $S$ . It consists of a F.A connected to a D F/F as shown below. Derive the state table and state diagram of the sequential ckt.



Solution

Present state	input	next state	output
$Q_n$	$xy$	$Q_{n+1}$	$S$
0	00	0	0
0	01	0	1
0	10	0	1
0	11	1	0
1	00	0	1
1	01	1	0
1	10	1	0
1	11	1	1


Note:-  
For D Flip Flop  
 $Q_{n+1} = D$

For D Flip Flop the c/s equation ( $Q_{n+1}$ ) is

$$Q_{n+1} = D$$

$$Q_{n+1} = xy + Q_n(x+y) \quad D = \text{Out of F.A} \leftarrow \text{From block diagram.}$$
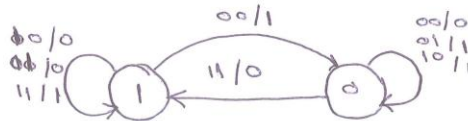
$$S = x \oplus y \oplus y \leftarrow \text{sum of F.A} \leftarrow \text{From block diagram.}$$



How:- ① Use JK as F.A.

② Design the sequential circuit of state diagram shown below using JK Flip-Flop

