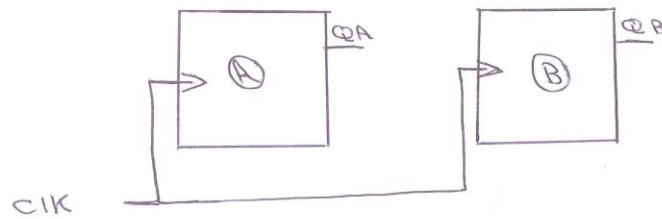



Counters:-

Counters are classified into two broad categories according to the way they are clocked:-


1- Synchronous Counters:- The clock input is connected to all of the Flip-flops; so that they are clocked simultaneously.



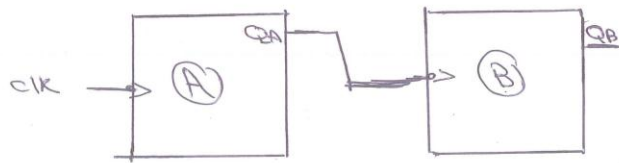2- Asynchronous (Ripple) Counters:- The first Flip-Flop is clocked by external clock pulse and then each successive Flip-Flop is clocked by the output of the preceding Flip-Flop:-



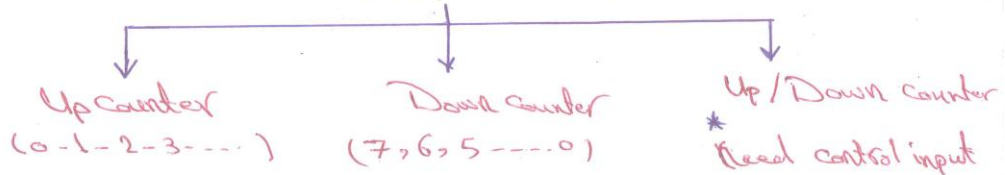Types of Counters (Synchronous, Asynchronous):-



Synchronous Counter operation:-

Design of synchronous counter:-


- 1- Decide the number of flip-flops.
- 2- state diagram.
- 3- Flip-Flop Transition table (Circuit excitation table).
- 4- obtain simplified equations using k-maps.
- 5- Draw the logic Diagram (counter implementation).

Example:- Design mod 4 (0 → 3) synchronous counter using SR Flip-Flop.

Solution:- 0 → 1 → 2 → 3

no. of bits = 2 = no. of flip-flops.

Present state		Next state		S <sub>B</sub> R <sub>B</sub>		S <sub>A</sub> R <sub>A</sub>	
B <sub>n</sub>	A <sub>n</sub>	B <sub>n+1</sub>	A <sub>n+1</sub>	S <sub>B</sub>	R <sub>B</sub>	S <sub>A</sub>	R <sub>A</sub>
0	0	0	1	0	d	1	0
0	1	1	0	1	0	0	1
1	0	1	1	d	0	1	0
1	1	0	0	0	1	0	1

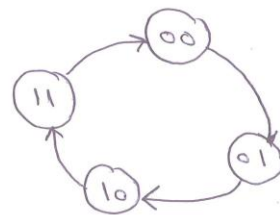

state diagram

$\bar{A}$	B	B
$\bar{A}$	0	d
A	1	0

$S_B = \bar{B}A$

$\bar{A}$	B	B
$\bar{A}$	d	0
A	0	1


$R_B = BA$

$\bar{A}$	B	B
$\bar{A}$	1	1
A	0	0

$S_A = \bar{A}$

$\bar{A}$	B	B
$\bar{A}$	0	0
A	1	1

$R_A = A$

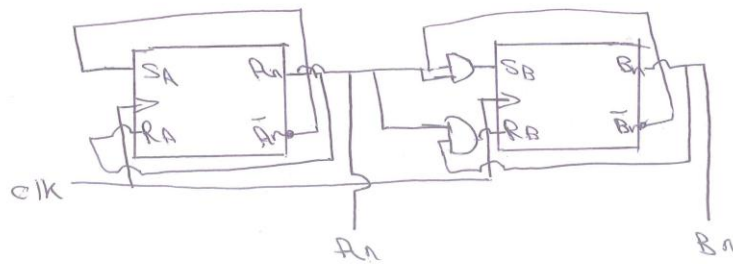


Example:- Design mod 8 (0 → 7) synchronous counter using JK-Flip-Flop.

Note:- (up counter)

Solution:- 0 → 1 → 2 → 3 → 4 → 5 → 6 → 7

no. of bits = 3  
= no. of Flip-flops.

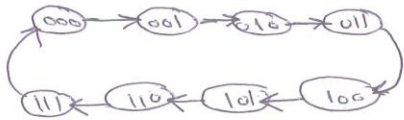

State-diagram.

present state			Next state			Jc	Kc	JB	KB	JA	KA
Cn	Bn	An	Cn	Bn	An						
0	0	0	0	0	1	0	d	0	d	1	d
0	0	1	0	1	0	0	d	1	d	d	1
0	1	0	0	1	1	0	d	d	0	1	d
0	1	1	1	0	0	1	d	d	1	d	1
1	0	0	1	0	1	d	0	0	d	1	d
1	0	1	1	1	0	d	0	1	d	d	1
1	1	0	1	1	1	d	0	d	0	1	d
1	1	1	0	0	0	d	1	d	1	d	1

A/B	C <sup>-</sup> B	C <sup>-</sup> B	CB	CB <sup>-</sup>
A	0	0	d	d
A	0	1	d	d

$Jc = BA$

A/B	C <sup>-</sup> B	CB	CB	CB <sup>-</sup>
A	d	0	0	d
A	d	1	1	d

$KB = A$

A/B	C <sup>-</sup> B	C <sup>-</sup> B	CB	CB <sup>-</sup>
A	d	d	0	0
A	d	d	1	0

$Kc = BA$

A/B	C <sup>-</sup> B	C <sup>-</sup> B	CB	CB <sup>-</sup>
A	1	1	1	1
A	d	d	d	d


$JA = 1$

A/B	C <sup>-</sup> B	C <sup>-</sup> B	CB	CB <sup>-</sup>
A	0	d	d	0
A	1	d	d	1

$JB = A$

A/B	C <sup>-</sup> B	C <sup>-</sup> B	CB	CB <sup>-</sup>
A	d	d	d	d
A	1	1	1	1

$KA = 1$

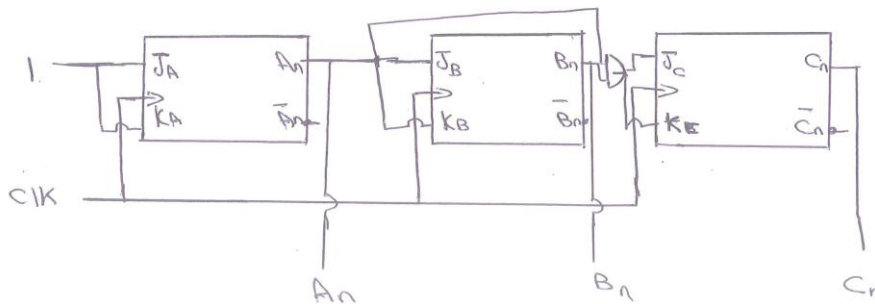

H-w Repeat the previous Example using (SR) - D-T Flip-Flop


Example: Design a counter with the following binary sequence

7 → 6 → 5 → 4 → 3 → 2 → 1 → 0

using D-Flip-Flop:-

\* Note:- Down Counter

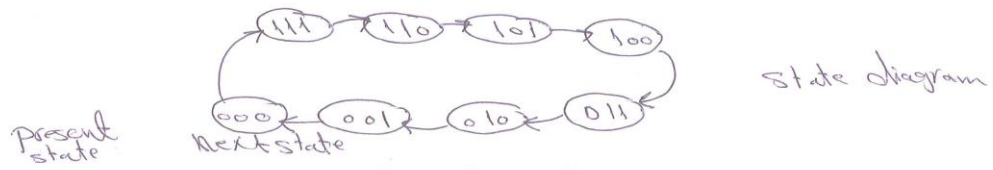
Solution:- No. of bits = 3 = No. of Flip-flops



Present state	Next state	$D_C$	$D_B$	$D_A$
0 0 0	1 1 1	1	1	1
0 0 1	0 0 0	0	0	0
0 1 0	0 0 1	0	0	1
0 1 1	0 1 0	0	1	0
1 0 0	0 1 1	0	1	1
1 0 1	1 0 0	1	0	0
1 1 0	1 0 1	1	0	1
1 1 1	1 1 0	1	1	0

$A_n/B_n$	$\bar{C}_B$	$\bar{C}_B$	$C_B$	$\bar{C}_B$	$A_n/B_n$	$\bar{C}_B$	$\bar{C}_B$	$C_B$	$\bar{C}_B$	$A_n/B_n$	$\bar{C}_B$	$\bar{C}_B$	$C_B$	$\bar{C}_B$
$\bar{A}_n$	1	0	1	0	$\bar{A}_n$	1	0	0	1	$\bar{A}_n$	1	1	1	1
$A_n$	0	0	1	1	$A_n$	0	1	1	0	$A_n$	0	0	0	0

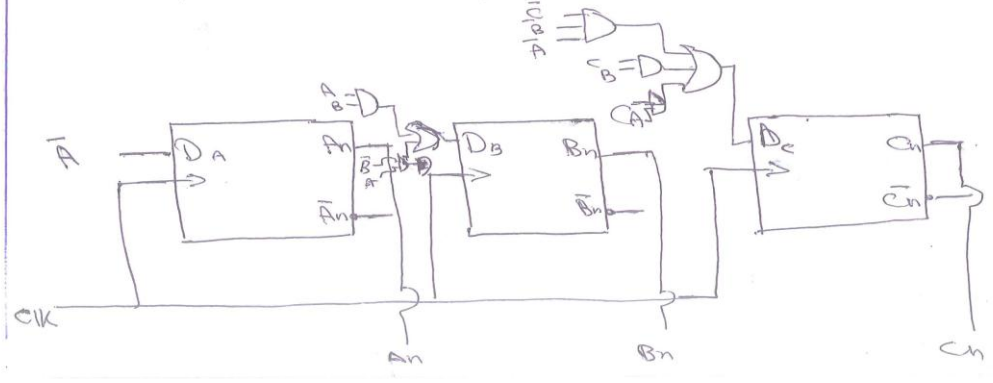
$D_C = \bar{C}_B \bar{A} + C_B + C_A$      $D_B = \bar{B} A + B \bar{A}$      $D_A = \bar{A}$



H.W.: Design a Counter with the following binary Sequence 0, 3, 2, 4, 1, 6, 5, 7 and repeat using D.F.F.

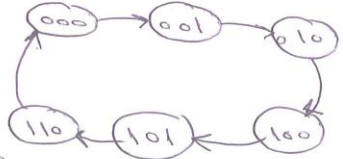Example: - Design a synchronous counter that has a repeated sequences of six states 0, 1, 2, 4, 5, 6, using JK Flip-Flop.

Solution: - no. of bits = 3 = no. of flip-flop.




State diagram

Present state			Next state			J <sub>c</sub>	K <sub>c</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>A</sub>	K <sub>A</sub>
C <sub>n</sub>	B <sub>n</sub>	A <sub>n</sub>	C <sub>n+1</sub>	B <sub>n+1</sub>	A <sub>n+1</sub>						
0	0	0	0	0	1	0	d	0	d	d	d
0	0	1	0	1	0	0	d	1	d	d	1
0	1	0	1	0	0	1	d	d	1	d	d
1	0	0	x	x	x	x	x	x	x	x	x
1	0	1	x	x	x	x	x	x	x	x	x
1	1	0	x	x	x	x	x	x	x	x	x
1	1	1	x	x	x	x	x	x	x	x	x


J <sub>c</sub> = B <sub>n</sub>	K <sub>c</sub> = B	J <sub>B</sub> = A																																				
<table border="1"> <tr><th>A</th><th>B</th><th>C</th><th>D</th></tr> <tr><td>0</td><td>1</td><td>d</td><td>d</td></tr> <tr><td>0</td><td>d</td><td>d</td><td>d</td></tr> </table>	A	B	C	D	0	1	d	d	0	d	d	d	<table border="1"> <tr><th>A</th><th>B</th><th>C</th><th>D</th></tr> <tr><td>d</td><td>d</td><td>1</td><td>0</td></tr> <tr><td>d</td><td>d</td><td>d</td><td>0</td></tr> </table>	A	B	C	D	d	d	1	0	d	d	d	0	<table border="1"> <tr><th>A</th><th>B</th><th>C</th><th>D</th></tr> <tr><td>1</td><td>d</td><td>d</td><td>0</td></tr> <tr><td>1</td><td>d</td><td>d</td><td>1</td></tr> </table>	A	B	C	D	1	d	d	0	1	d	d	1
A	B	C	D																																			
0	1	d	d																																			
0	d	d	d																																			
A	B	C	D																																			
d	d	1	0																																			
d	d	d	0																																			
A	B	C	D																																			
1	d	d	0																																			
1	d	d	1																																			
<table border="1"> <tr><th>A</th><th>B</th><th>C</th><th>D</th></tr> <tr><td>d</td><td>1</td><td>1</td><td>d</td></tr> <tr><td>d</td><td>d</td><td>d</td><td>d</td></tr> </table>	A	B	C	D	d	1	1	d	d	d	d	d	<table border="1"> <tr><th>A</th><th>B</th><th>C</th><th>D</th></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>d</td><td>d</td><td>d</td><td>d</td></tr> </table>	A	B	C	D	1	0	0	1	d	d	d	d	<table border="1"> <tr><th>A</th><th>B</th><th>C</th><th>D</th></tr> <tr><td>d</td><td>d</td><td>d</td><td>d</td></tr> <tr><td>1</td><td>d</td><td>d</td><td>1</td></tr> </table>	A	B	C	D	d	d	d	d	1	d	d	1
A	B	C	D																																			
d	1	1	d																																			
d	d	d	d																																			
A	B	C	D																																			
1	0	0	1																																			
d	d	d	d																																			
A	B	C	D																																			
d	d	d	d																																			
1	d	d	1																																			

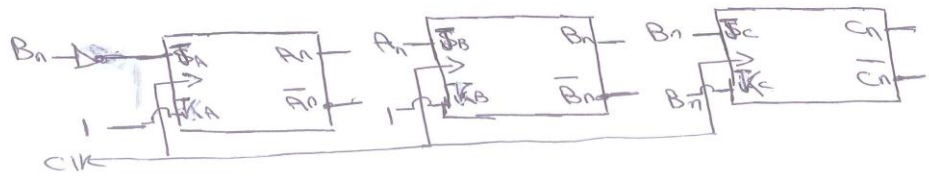$K_B = 1$                        $J_A = \bar{B}$                        $K_A = 1$



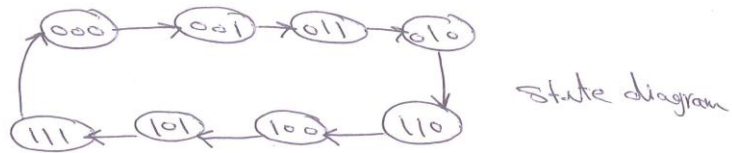Example: - Design a Counter with the following Binary Sequence  
 0, 1, 3, 2, 6, 4, 5, 7 and repeat, using SR  
 Flip-Flop.

Solution: - No. of bits = 3 = No. of Flip-Flops



Cn	Bn	An	Cn-1	Bn-1	An-1	Sc	Rc	Sb	Rb	Sa	Ra
0	0	0	0	0	1	0	d	0	d	1	0
0	0	1	0	1	1	0	d	1	0	d	0
0	1	0	1	1	0	1	0	d	0	d	d
0	1	1	0	1	0	0	d	d	0	0	1
1	0	0	1	0	1	d	0	0	d	1	0
1	0	1	1	1	1	d	0	1	0	d	0
1	1	0	1	0	0	d	0	0	1	0	d
1	1	1	0	0	0	0	1	0	1	0	1

A/B	C <sup>-</sup>	C <sup>-</sup> B	CB	CB <sup>-</sup>
0	0	1	d	d
1	0	0	0	d

A/B	C <sup>-</sup>	C <sup>-</sup> B	CB	CB <sup>-</sup>
0	d	0	1	d
1	0	0	1	0

$R_B = C_B$

A/B	C <sup>-</sup>	C <sup>-</sup> B	CB	CB <sup>-</sup>
0	d	0	0	0
1	d	d	1	0

A/B	C <sup>-</sup>	C <sup>-</sup> B	CB	CB <sup>-</sup>
0	1	0	0	d
1	0	0	0	d

$S_A = \bar{B}$

A/B	C <sup>-</sup>	C <sup>-</sup> B	CB	CB <sup>-</sup>
0	0	d	0	0
1	1	d	0	1

A/B	C <sup>-</sup>	C <sup>-</sup> B	CB	CB <sup>-</sup>
0	0	d	d	d
1	0	1	1	0

$R_A = B$

