


## Shift Register Counters

A shift register counter is basically a shift register with serial o/p is connected to the serial i/p to produce special sequence. Two of the most common types of shift register counters are :-
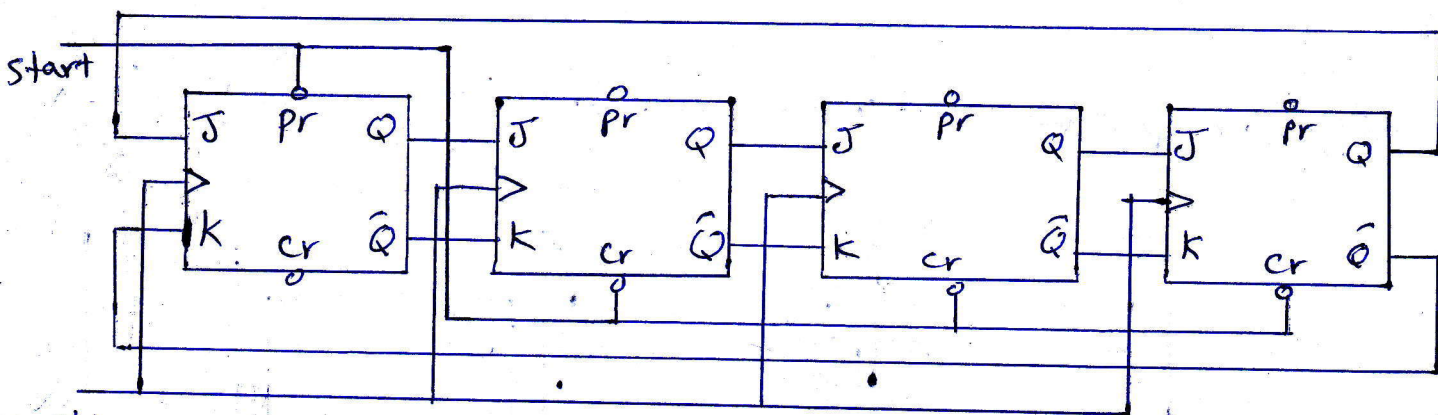
### 1- Ring Counter :-

This type of counter has the characteristic that in most instances only a single 1 is in the register and it is made to circulate around the register as long as clock pulses are applied.

This type of counter is constructed as shown below :-



(4-bit Ring Counter)


<u>D</u>	<u>c</u>	<u>B</u>	<u>A</u>	or	<u>A</u>	<u>B</u>	<u>C</u>	<u>D</u>
0	0	0	1		1	0	0	0
0	0	1	0		0	1	0	0
0	1	0	0		0	0	1	0
1	0	0	0		0	0	0	1

### Notes:-

The maximum length of the code patterns generated by this type of counter is  $N$ , where  $N$  is the number of flip-flop in the ring counter.


EX) If a 6-bit ring counter has the initial state 101000, determine the wave form for each of Q-output?

Sol.)

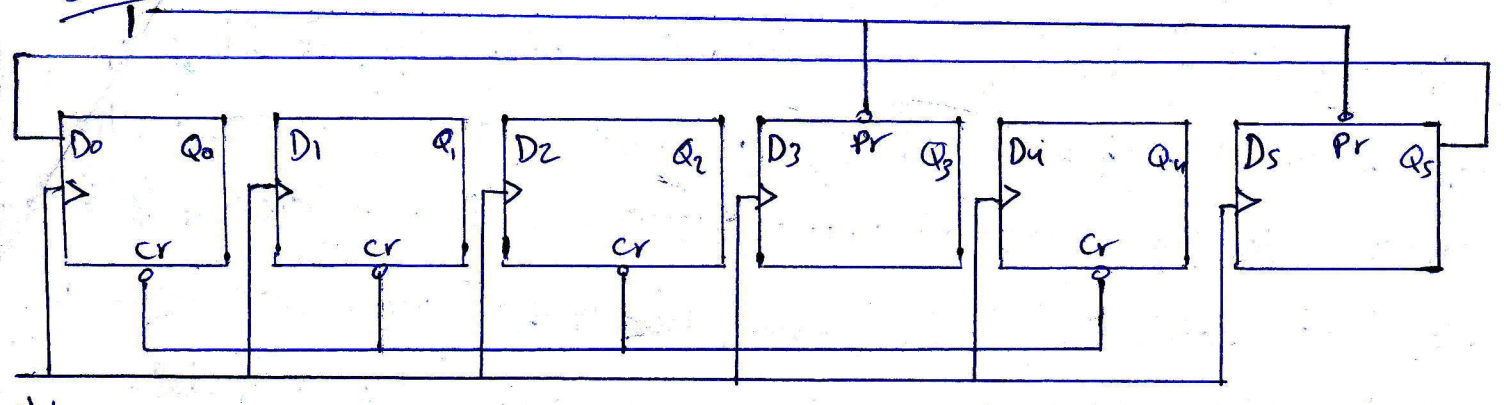


(6-bit ring counter)

$Q_5$	$Q_4$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	or	$Q_0$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$Q_5$
1	0	1	0	0	0		0	0	0	1	0	1
0	1	0	0	0	1		1	0	0	0	1	0
1	0	0	0	1	0		0	1	0	0	0	1
0	0	0	1	0	1		1	0	1	0	0	0
0	0	1	0	1	0		0	1	0	1	0	0
0	1	0	1	0	0		0	0	1	0	1	0
1	0	1	0	0	0		0	0	0	1	0	1

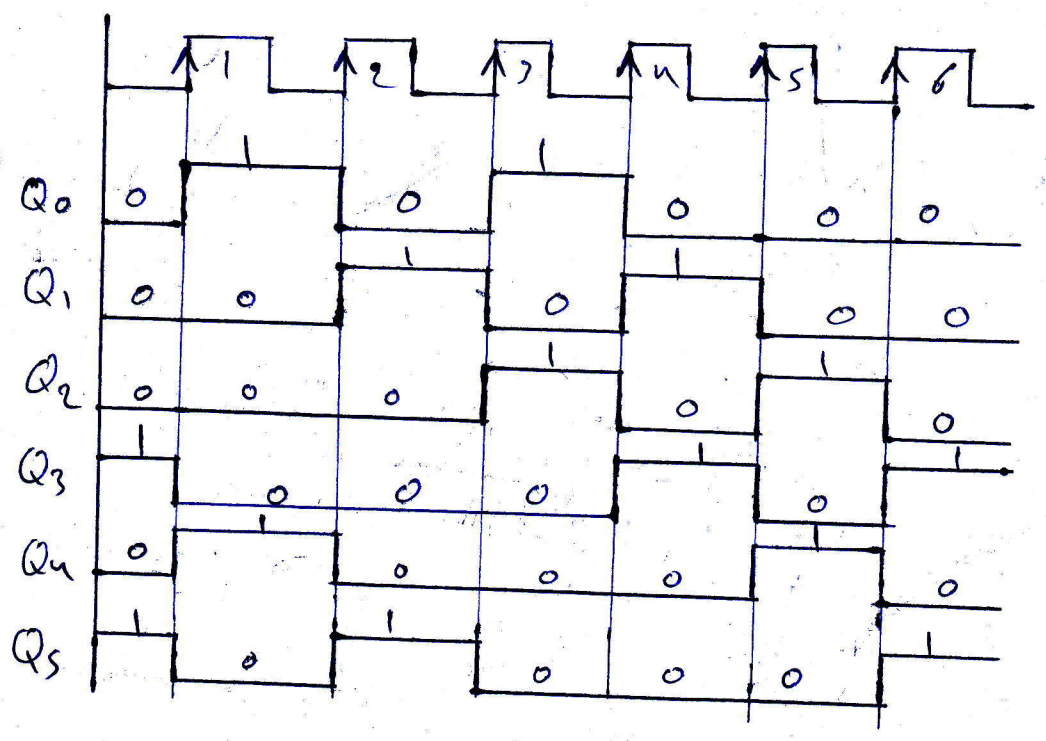
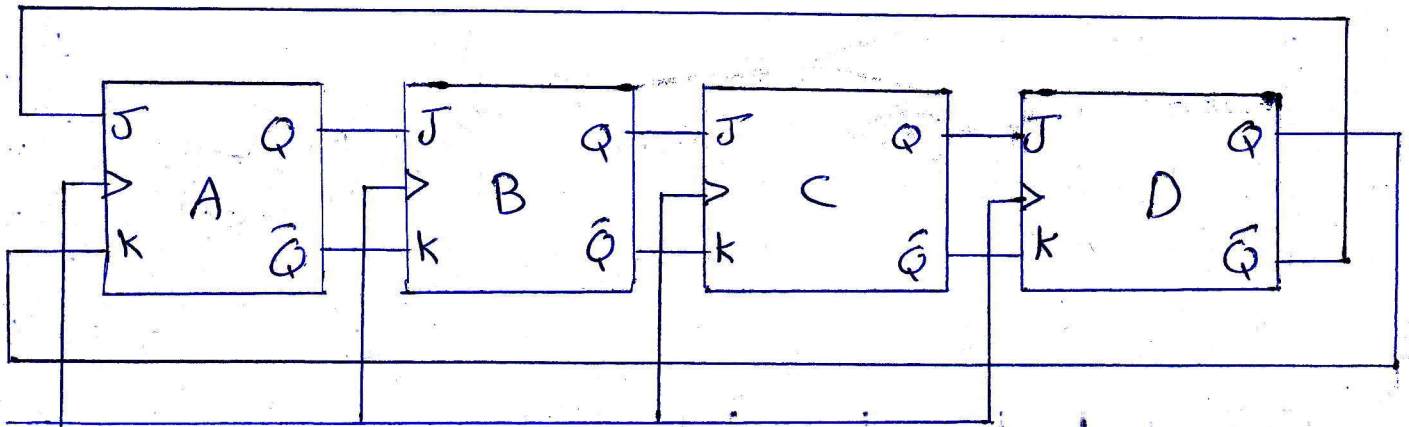
# The Johnson Counters.

In a Johnson Counter the complement of the output of the last flip-flop is connected back to the D input of the first flip-flop (it can be implemented with other types of flip-flops as well). This feedback arrangement produces a characteristic sequence of states as shown in the example below for a 4-bit device. Notice that the 4-bit sequence has a total of eight states, or bit patterns, and the 5-bit sequence has a total of ten states. In general, a Johnson counter will produce a modulus of  $2N$ , when  $N$  is the number of stages (Flip-Flop) in the counter.



CLK

(4-bit Johnson Counter).


A	B	C	D
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
0	0	0	0

or

D	C	B	A
0	0	0	0
0	0	0	1
0	0	1	1
0	1	1	1
1	1	1	1
1	1	1	0
1	1	0	0
1	0	0	0
0	0	0	0

Ex) IF a 4-bit Johnson Gunter has the initial state 1000, determine the wave form for each of Q-output?

Sol.)

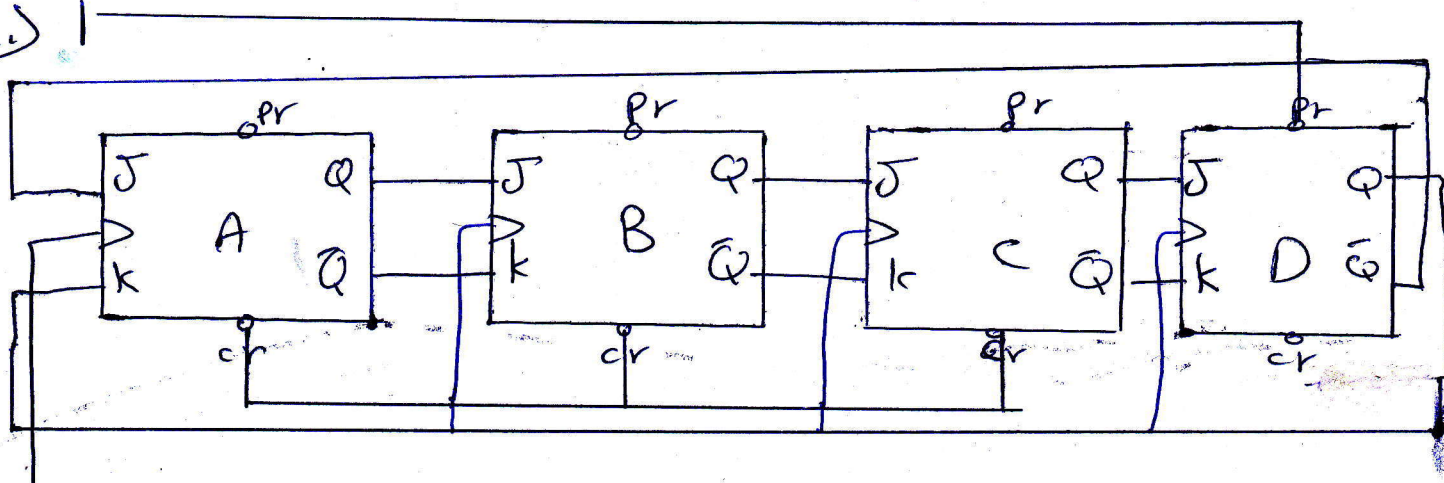

CLK  $\downarrow$

D	C	B	A
1	0	0	0
0	0	0	0
0	0	0	1
0	0	1	1
0	1	1	1
1	1	1	1
1	1	1	0
1	1	0	0
1	0	0	0

Hiw Draw the wave form?