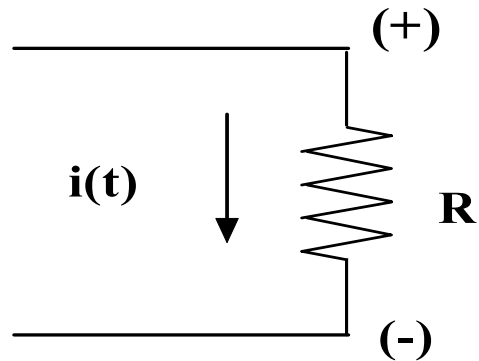


Passive sign convention


Current flow from the positive to the negative terminal.



- Power can be absorbed or supplied by an element.
- Power is absorbed (or dissipated) by an element if the sign of power is $(+)$
- Power is supplied (delivered or generated) by an element if the sign of power is $(-)$

Circuit Active Elements:

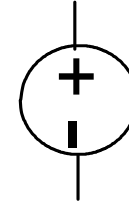There are 4 types of active elements (sources):




1. Independent voltage source:

It is a 2-terminal sources that maintains a specific voltage across its terminals regardless of the current through it

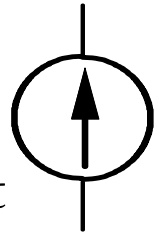
2. Independent current source:

It is a 2-terminal sources that maintains a specific current through it regardless of the voltage across it terminals.



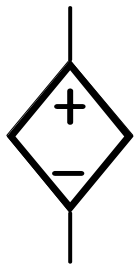3. Dependent voltage source:

It is a 2-terminal sources that generates a voltage that is determined by a voltage or current at a specified location in the circuit.




4. Dependent current source:

It is a 2-terminal sources that generates a current that is determined by voltage or current at a specified location in the circuit.



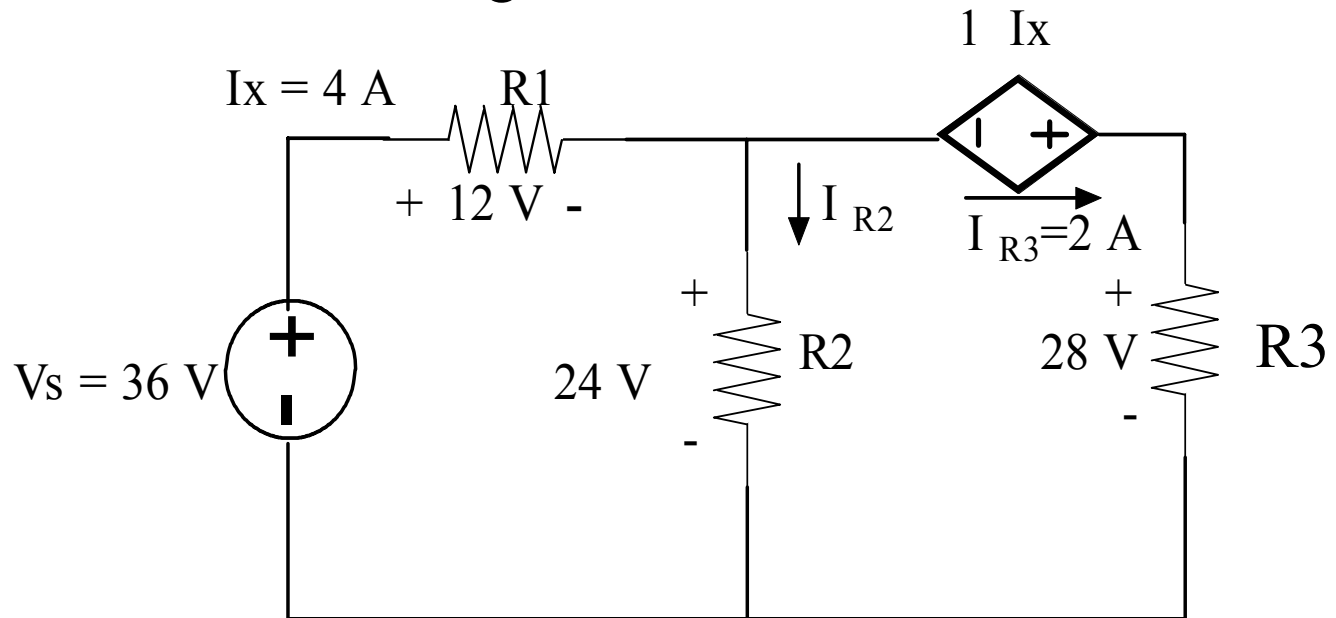Example :

Compute the power that is absorbed or supplied by each of the elements in the following circuit



$$P_{vs} = V_s I_x = (36)(-4) = -144W \quad (\text{supplies})$$

$$P_{R1} = V_{R1} I_x = (12)(4) = 48W \quad (\text{absorbs})$$

$$P_{R2} = V_{R2} I_{R2} = V_{R2} (I_x - I_{R3}) = \\ (24)(4 - 2) = 48W \quad (\text{absorbs})$$

$$P_{Ds} = V_{Ds} I_{R3} = (1I_x)(I_{R3}) = (4)(-2) = -8W \quad (\text{supplies})$$

$$P_{R3} = V_{R3} I_{R3} = (28)(2) = 56W \quad (\text{absorbs})$$

Prefixes For Engineering Notation

POWER OF 10

PREFIX

SYMBOL

10^{12}

tera

T

10^9

giga

G

10^6

mega

M

10^3

kilo

k

10^{-3}

milli

m

10^{-6}

micro

μ

10^{-9}

nano

n

10^{-12}

pico

p