

Chapter 2

Resistive Circuits


Ohm's law :

The voltage across a resistor is directly proportional to the current flowing through it.

$$\mathbf{V(t) = R i(t) \quad R \geq 0}$$

The symbol of ohm is (Ω)
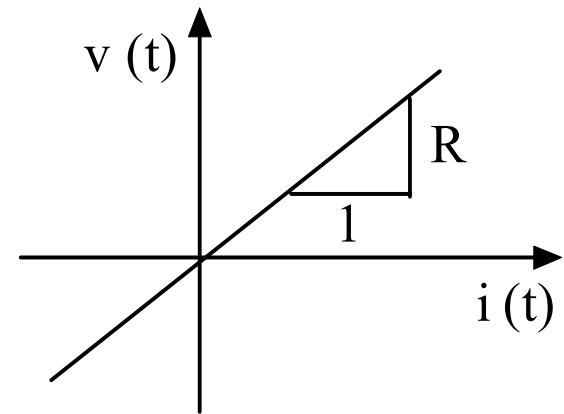
$$1\Omega = \frac{1\text{V}}{1\text{A}}$$



The instantaneous power $P(t)$:

$$P(t) = v(t) i(t) = R i(t) i(t)$$

$$= R i^2(t) = v(t) \frac{v(t)}{R} = \frac{v^2(t)}{R}$$

$$\therefore P(t) = v(t) i(t) = R i^2(t) = \frac{v^2(t)}{R}$$

Note: Last equation says that the power at a resistor is always positive

⇒ Resistors always absorb power.

The inverse of resistance is conductance

$$G = \frac{1}{R}$$

The unit of conductance is Siemens (S)

$$1 \text{ S} = \frac{1 \text{ A}}{1 \text{ V}}$$

The current can be also expressed as

$$i(t) = G V(t)$$

And the instantaneous power is


$$P(t) = v(t)i(t) = \frac{i(t)}{G} i(t) = \frac{i^2(t)}{G}$$

$$P(t) = v(t) i(t) = v(t) G v(t) = G v^2(t)$$

$$\Rightarrow = v(t) i(t) = \frac{i^2(t)}{G} = G v^2(t)$$


Open and short Circuits

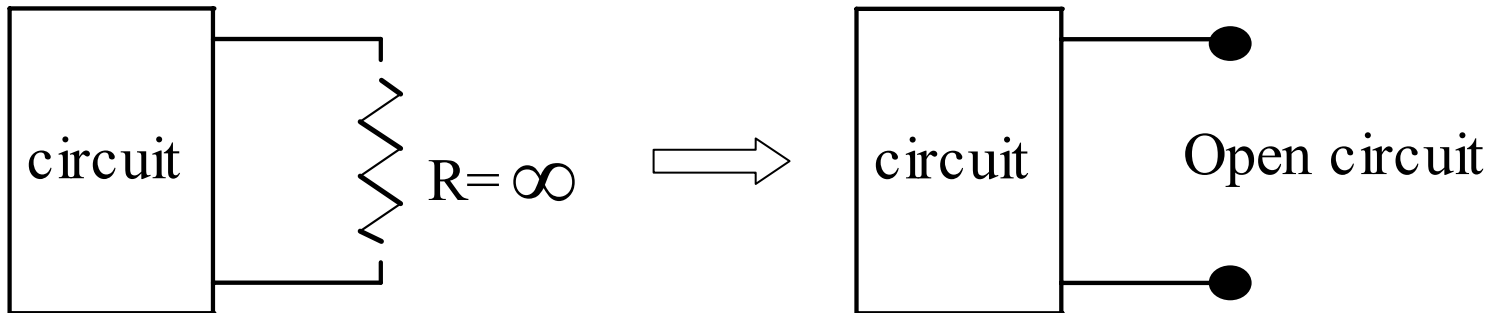Open circuit ($R = \infty$) \Longrightarrow $G = 0$



$$i(t) = \frac{v(t)}{R} = \frac{v(t)}{\infty} = 0$$

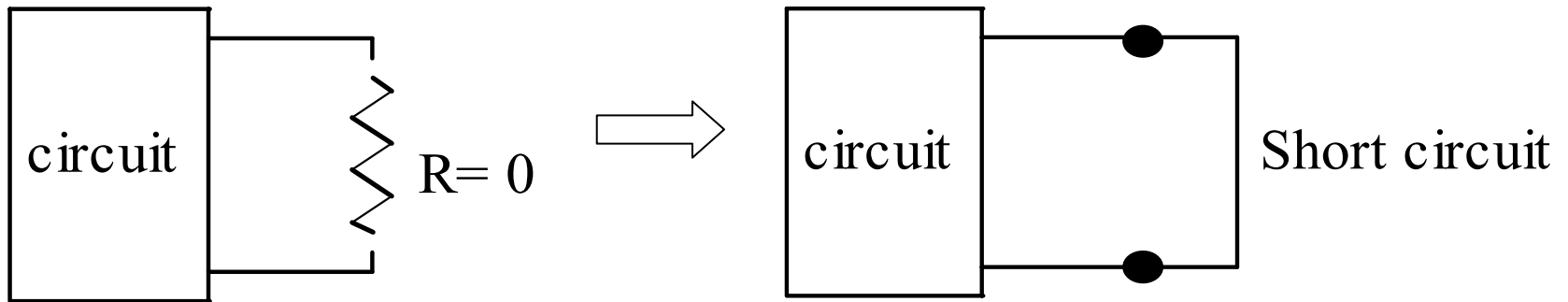
Short circuit ($R = 0$) \Rightarrow $G = \infty$



$$v(t) = Ri(t) = 0 * i(t) = 0$$

Example :

Consider the circuit:

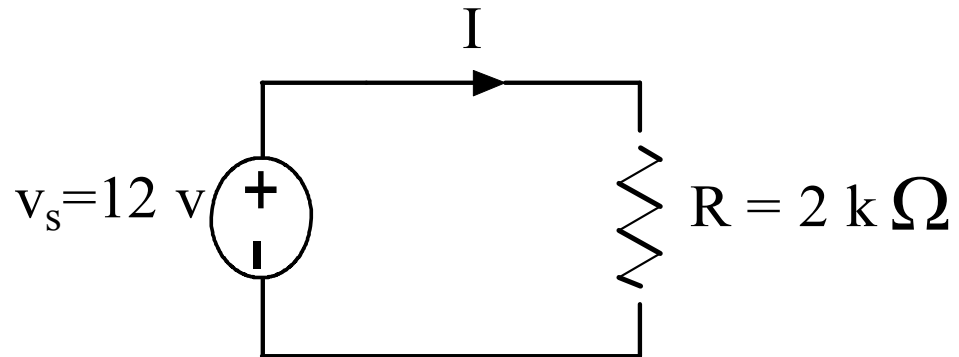

Find the current and power absorbed by the resistor

$$I = \frac{v_s}{R} = \frac{12 \text{ v}}{2 \text{ k} \Omega} = 6 \text{ mA}$$

$$P = v_R I = (12)(6 \text{ mA}) = 72 \text{ mW}$$

Example:

The power absorbed by a $10\text{ k}\Omega$ resistor in the circuit is 3.6 mW .

Find voltage and current in the resistor.

$$P = V_s I = I^2 R$$

$$I^2 = \frac{P}{R}$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{(3.6 * 10^{-3}) / (10 * 10^3)}$$

$$I = \sqrt{3.6 * 10^{-7}} = 0.6\text{ mA}$$

$$V = IR = (0.6\text{ mA})(10\text{ k}\Omega)$$

$$V = 6\text{ V}$$

