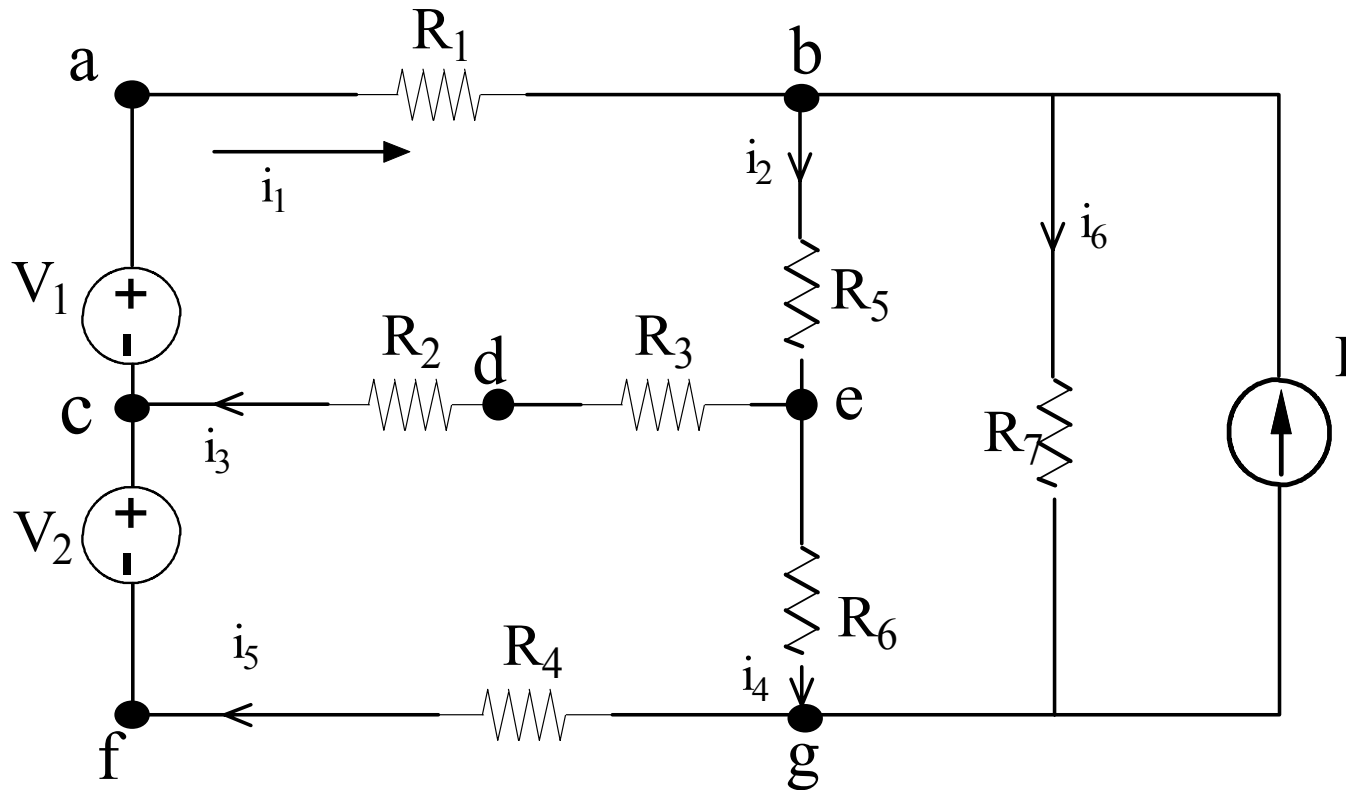


Chapter (3)

Nodal and loop analysis

Consider the following circuit:



Definitions:

Node :

A point where two or more circuit elements join

Ex. a,b,c,d,e,f,g

Essential Node:

A node where three or more circuit element join

Ex. b,c,e,g

Path:

A trace of adjoining elements with no elements included more than once

1. $V_1-R_1-R_5-R_6$
2. $R_5-R_6-R_4-V_2$,etc

Branch:

A path that connects any two nodes.

Ex. R_1 , V_1 , R_1 - R_5 , etc

Essential Branch:

A path that connects two essential nodes without passing through an essential node.

Ex. V_1 - R_1 , R_5 , R_2 - R_3 , V_2 - R_4 , ...

Loop :

A path whose last node is the same as its starting node

Ex. (1) V_1 - R_1 - R_5 - R_3 - R_2

(2) V_1 - R_1 - R_5 - R_6 - R_4 - V_2

Mesh :

A loop that doesn't enclose any other loops.

Ex. $V_1-R_1-R_5-R_3-R_2$

Ex. $V_2-R_2-R_3-R_6-R_4$, ...


- In chapter (2) we studied circuits containing a single loop or a single node-pair
 - Such circuits can be solved easily by one algebraic equation.
 - Here , we will study circuit containing multiple node and multiple loops
 - Hence we will introduce (2) analysis techniques :
1. **Nodal analysis**
 2. **Loop analysis**

(1) Nodal Analysis :

Nodal analysis : is a technique in which KCL is used to determine the nodes' voltages at all essential nodes with respect to the reference node.

• Here , node voltage is defined as the voltage of a given node with respect to a reference node

Example:

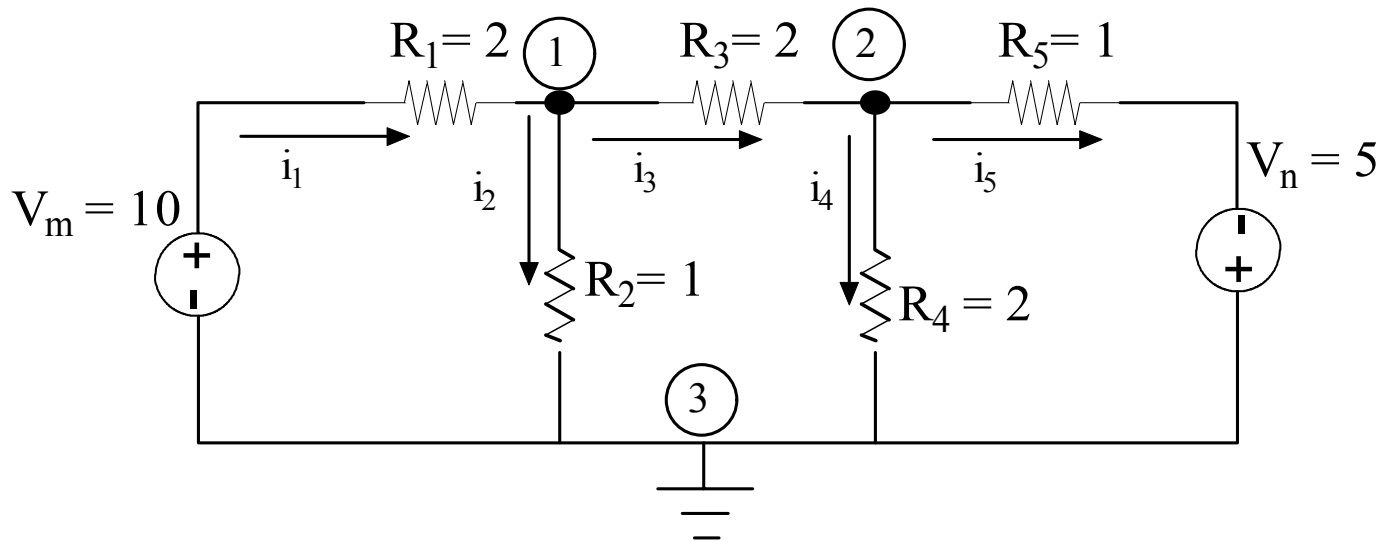

Essential nodes : 1,2,3

Consider (3) to be the reference node (ground)

At (1) apply KCL:

$$i_1 - i_2 - i_3 = 0$$

$$\frac{V_m - V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} = 0$$

$$\frac{10 - V_1}{2} - \frac{V_1}{1} - \frac{V_1 - V_2}{2} = 0$$

$$5 - \frac{V_1}{2} - V_1 - \frac{V_1}{2} + \frac{V_2}{2} = 0$$

$$5 - 2V_1 + \frac{V_2}{2} = 0$$

$$4V_1 - V_2 = 10 \dots\dots (1)$$

At (2), Apply KCL:

$$i_3 - i_4 - i_5 = 0$$

$$\frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} - \frac{V_2 - V_n}{R_5} = 0$$

$$\frac{(V_1 - V_2)}{2} - \frac{V_2}{2} - \frac{(V_2 + 5)}{1} = 0$$

$$\frac{V_1}{2} - 2V_2 - 5 = 0$$

$$V_1 - 4V_2 = 10 \dots\dots (2)$$

$$\begin{bmatrix} 4 & -1 \\ 1 & -4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 10 \end{bmatrix}$$

$$A V = B \Rightarrow V = A^{-1} B \Rightarrow V_1 = 2$$

$$V_2 = -2$$

Note :


Number of equations = $N-1$

Where :

N is the number of essential nodes

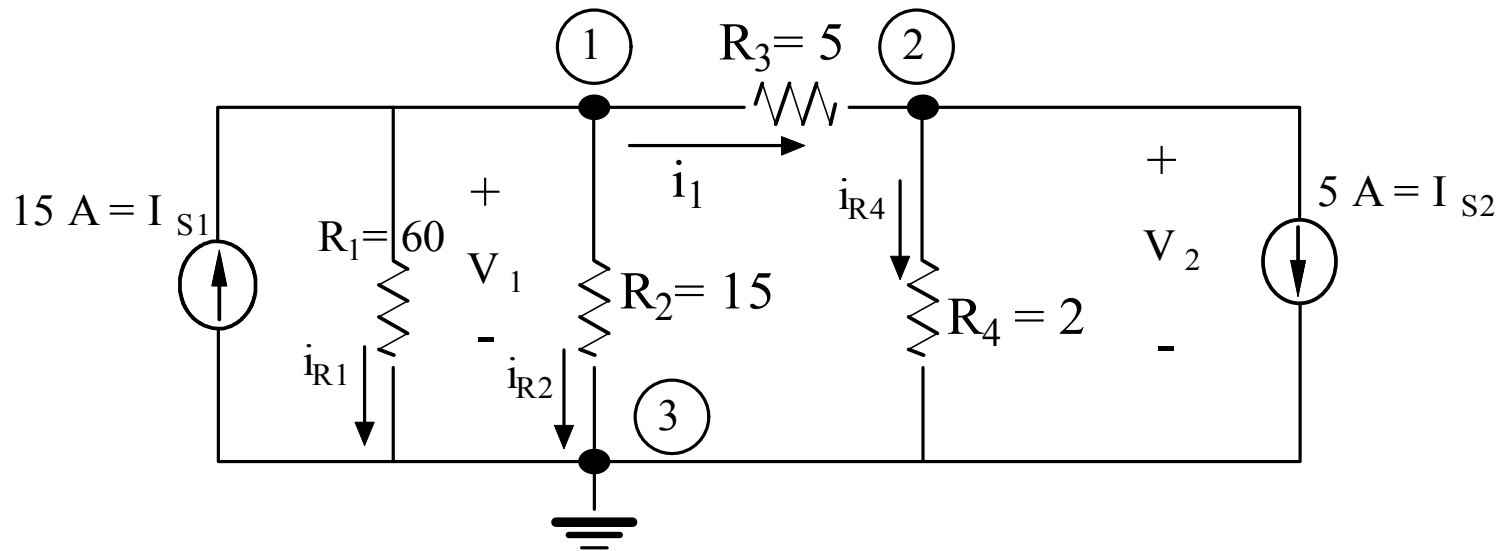Example :

Circuit with only independent current source



Find V_1, V_2 and i

of essential node = $N=3$

Select (3) as ground (reference node)

of KCL equations = $N-1 = 2$

At node (1) apply KCL

$$I_{s1} - i_{R1} - i_{R2} - i_1 = 0$$

$$15 - \frac{V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} = 0$$

$$15 - \frac{V_1}{60} - \frac{V_1}{15} - \frac{V_1}{5} + \frac{V_2}{5} = 0$$

$$\left(\frac{1}{5} + \frac{1}{15} + \frac{1}{60}\right)V_1 - \frac{1}{5}V_2 = 15$$

$$\frac{12 + 4 + 1}{60}V_1 - \frac{1}{5}V_2 = 15$$

$$\frac{17}{60}V_1 - \frac{1}{5}V_2 = 15 \quad \dots\dots(1)$$

At node (2)

$$i_1 - i_{R4} - I_{s2} = 0$$

$$\frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} - 5 = 0$$

$$\frac{V_1 - V_2}{5} - \frac{V_2}{2} - 5 = 0$$

$$2V_1 - 2V_2 - 5V_2 - 50 = 0$$

$$2V_1 - 7V_2 = 50 \quad \dots\dots(2)$$

$$\begin{bmatrix} \frac{17}{60} & \frac{-1}{5} \\ \frac{2}{2} & \frac{-7}{-7} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 15 \\ 50 \end{bmatrix}$$

$$V_1 = 60 \text{ V}$$


$$V_2 = 10 \text{ V}$$

$$i_1 = \frac{V_1 - V_2}{R} = \frac{60 - 10}{5} = 10 \text{ A}$$

Example :

Circuit with dependent current source

Find I_0

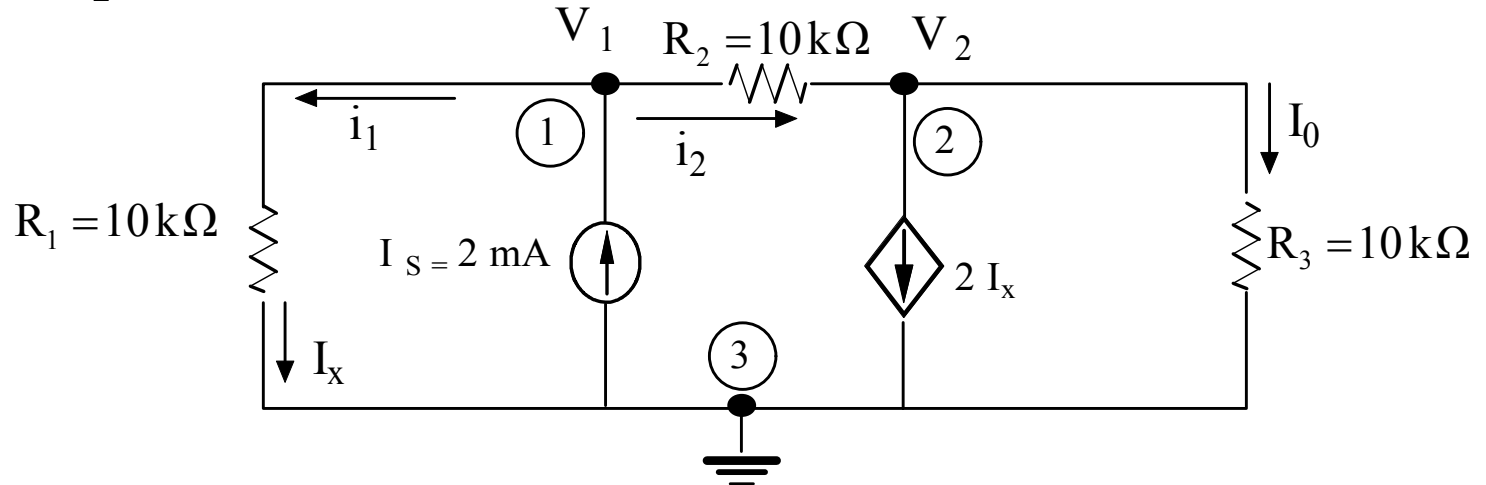

of essential nodes = $N=3$

Choose (3) to be reference node (ground)

We have $N-1 = 2$ KCL equation
at node(1) and(2)

At node (1) , apply KCL

$$I_s - i_1 - i_2 = 0$$

$$2 \text{ m A} - \frac{V_1}{R_1} - \frac{V_1 - V_2}{R_2} = 0$$

$$2 \text{ m A} = \frac{V_1}{10\text{k}} + \frac{V_1 - V_2}{10\text{k}} = \frac{V_1}{5\text{k}} - \frac{V_2}{10\text{k}}$$

$$0.2 V_1 - 0.1 V_2 = 2 \text{ A} \quad \dots\dots(1)$$

At node (2) apply KCL,

$$i_2 - 2I_x - I_0 = 0$$

$$i_2 - 2I_x - I_0 = 0$$

$$\frac{V_1 - V_2}{R_2} - 2I_x - I_0 = 0$$

where $I_x = i_1 = \frac{V_1}{R_1}$

$$I_0 = \frac{V_2}{R_3}$$

$$\Rightarrow \frac{V_1 - V_2}{10k} - 2 \frac{V_1}{10k} - \frac{V_2}{10k} = 0$$

$$1 V_1 + 2 V_2 = 0 \quad \dots\dots(2)$$

$$\begin{bmatrix} 0.2 & -0.1 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

$$V_1 = 8 \text{ V}$$


$$V_2 = -4 \text{ V}$$

$$\Rightarrow I_0 = \frac{V_2}{R_3} = \frac{-4}{10\text{k}} = -0.4 \text{ mA}$$

Example:

(circuit with independent voltage source)

Find i_a, i_b, i_c, i_d, i_e

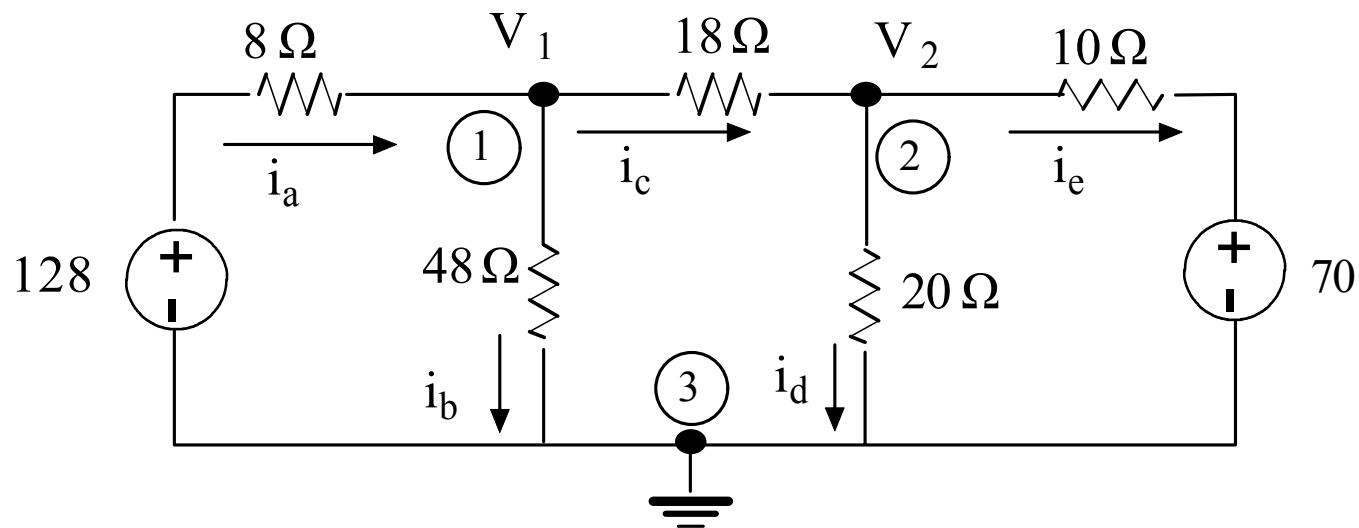

$$N=3 \quad \Longrightarrow \quad N-1 = 2$$

Choose (3) to be ground

KCL at (1)

$$\frac{128 - V_1}{8} - \frac{V_1}{48} - \frac{V_1 - V_2}{18} = 0$$

$$16 - \frac{V_1}{8} - \frac{V_1}{48} - \frac{V_1}{18} + \frac{V_2}{18} = 0$$

$$0.201388 V_1 - \frac{1}{18} V_2 = 16 \quad \dots\dots(1)$$

KCL at (2)

$$\frac{V_1 - V_2}{18} - \frac{V_2}{20} - \frac{V_2 - 70}{10} = 0$$

$$\frac{1}{18} V_1 - 0.20555 V_2 = -7 \quad \dots\dots(2)$$

$$\begin{bmatrix} 0.201338 & \frac{-1}{18} \\ \frac{1}{18} & -0.2055 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 16 \\ -7 \end{bmatrix}$$

$$V_1 = 96 \text{ V}$$

$$V_2 = 60 \text{ V}$$

$$\therefore i_a = \frac{128 - V_1}{8} = \frac{128 - 96}{8} = 4 \text{ A}$$

$$i_b = \frac{V_1}{48} = \frac{96}{48} = 2 \text{ A}$$

$$i_c = \frac{V_1 - V_2}{18} = \frac{96 - 60}{18} = 2 \text{ A}$$

$$i_d = \frac{V_2}{20} = \frac{60}{20} = 3 \text{ A}$$

$$i_e = \frac{V_2 - 70}{10} = -1 \text{ A}$$

$$\therefore i_a = \frac{128 - V_1}{8} = \frac{128 - 96}{8} = 4 \text{ A}$$

$$i_b = \frac{V_1}{48} = \frac{96}{48} = 2 \text{ A}$$

$$i_c = \frac{V_1 - V_2}{18} = \frac{96 - 60}{18} = 2 \text{ A}$$


$$i_d = \frac{V_2}{20} = \frac{60}{20} = 4 \text{ A}$$

$$i_e = \frac{V_2 - 70}{10} = -1 \text{ A}$$

Special case:

What if a branch between two essential non-reference nodes contains a voltage source?

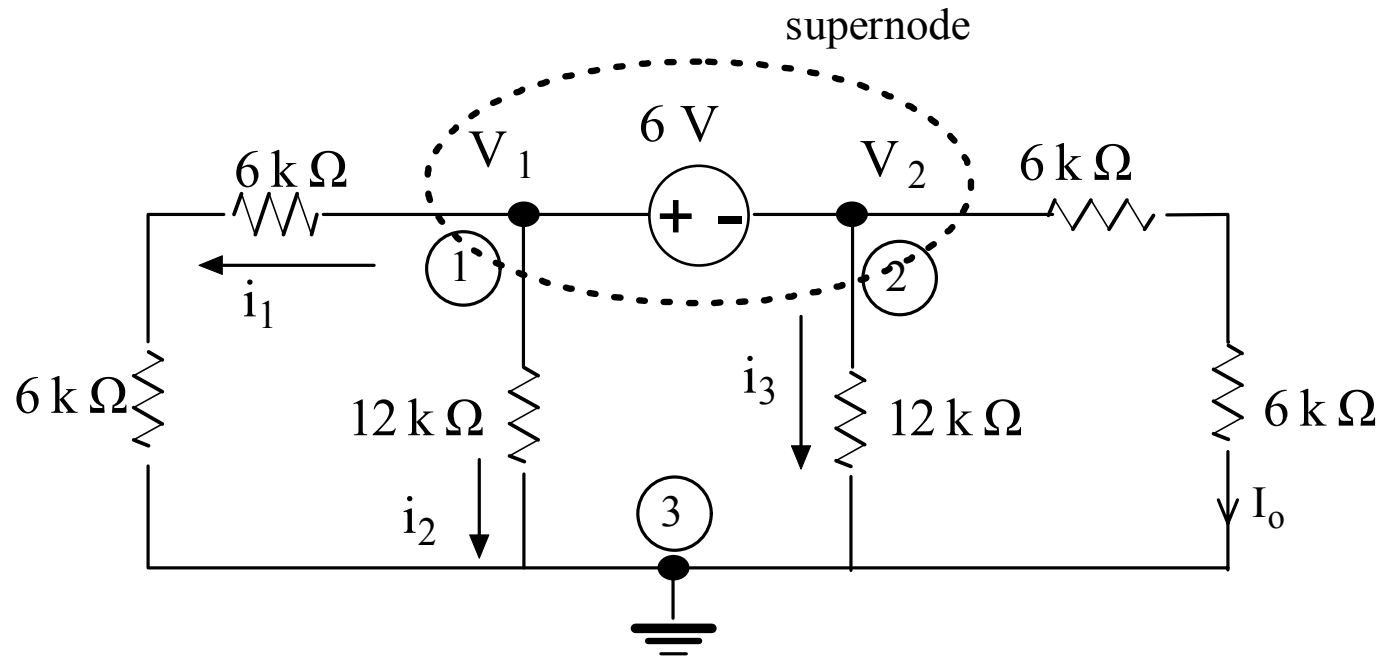This case is called "**super node**" case.




Find I_0

- # of essential nodes = $N = 3$
- “Super node: is the voltage source and the two connecting nodes
- # of equations = $N - 1 - 1 = 3 - 1 - 1 = 1$

Reference node Super node

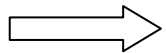But we need (2) equations to find the two unknowns V_1 and V_2



There is an equation that describe the super node.

Apply KCL at the super node :

$$i_1 + i_2 + i_3 + I_0 = 0$$

$$\frac{V_1}{12k} + \frac{V_1}{12k} + \frac{V_2}{12k} + \frac{V_2}{12k} = 0$$

$$\frac{V_1}{6k} + \frac{V_2}{6k} = 0 \quad \dots\dots(1)$$

The super node is described by:

$$V_2 + 6 = V_1 \quad \dots\dots(2)$$

$$\begin{bmatrix} \frac{1}{6k} & \frac{1}{6k} \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 6 \end{bmatrix}$$


$$V_1 = 3 \text{ V}$$

$$V_2 = -3 \text{ V}$$

$$\Rightarrow I_0 = \frac{V_2}{12k} = \frac{-3}{12k} = -0.25 \text{ mA}$$


Example:

Circuits with dependent voltage sources

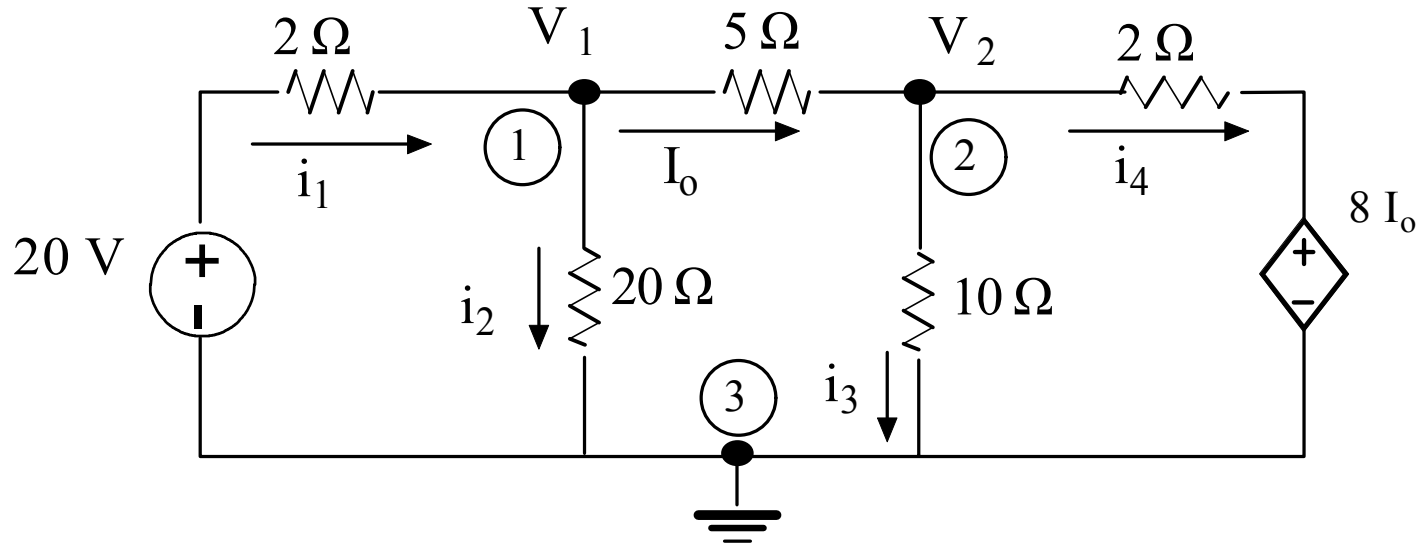

Find I_0 ?

$N = 3$

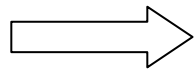

$N-1 = 2$ equations

KCL at node (1):

$$i_1 = i_2 + I_0$$

$$\frac{20 - V_1}{2} = \frac{V_1}{20} + \frac{V_1 - V_2}{5}$$

$$10 - \frac{V_1}{2} = \frac{V_1}{20} + \frac{V_1}{5} - \frac{V_2}{5}$$

$$\left(\frac{1}{2} + \frac{1}{20} + \frac{1}{5} \right) V_1 - \frac{1}{5} V_2 = 10$$

$$\frac{3}{4} V_1 - \frac{1}{5} V_2 = 10 \quad \dots\dots(1)$$

$$I_0 = i_3 + i_4$$

$$\frac{V_1 - V_2}{5} = \frac{V_2}{10} + \frac{V_2 - 8I_0}{2}$$

$$\frac{V_1}{5} - \frac{V_2}{5} = \frac{V_2}{10} + \frac{V_2}{2} - 4 \left(\frac{V_1 - V_2}{5} \right)$$

$$5 \left(\frac{V_1 - V_2}{5} \right) = \frac{V_2}{10} + \frac{V_2}{2}$$

$$V_1 - V_2 = \frac{V_2}{10} + \frac{V_2}{2}$$

$$V_1 - \left(1 + \frac{1}{10} + \frac{1}{2} \right) V_2 = 0$$

$$V_1 - \frac{8}{5} V_2 = 0 \quad \dots\dots(2)$$

$$\begin{bmatrix} 3 & -1 \\ 4 & 5 \\ 1 & -8 \\ & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$V_1 = 16 \text{ V}$$

$$V_2 = 10 \text{ V}$$

$$I_0 = \frac{V_1 - V_2}{5} = \frac{6}{5} = 1.2 \text{ A}$$

Loop Analysis (Mesh)

Mesh analysis : It is a technique in which KVL is used to determine the current in all meshes


of equations needed = # of meshes = $b_e - (n_e - 1)$

Where :

b_e : # of essential branches

n_e : # of essential nodes

Example :

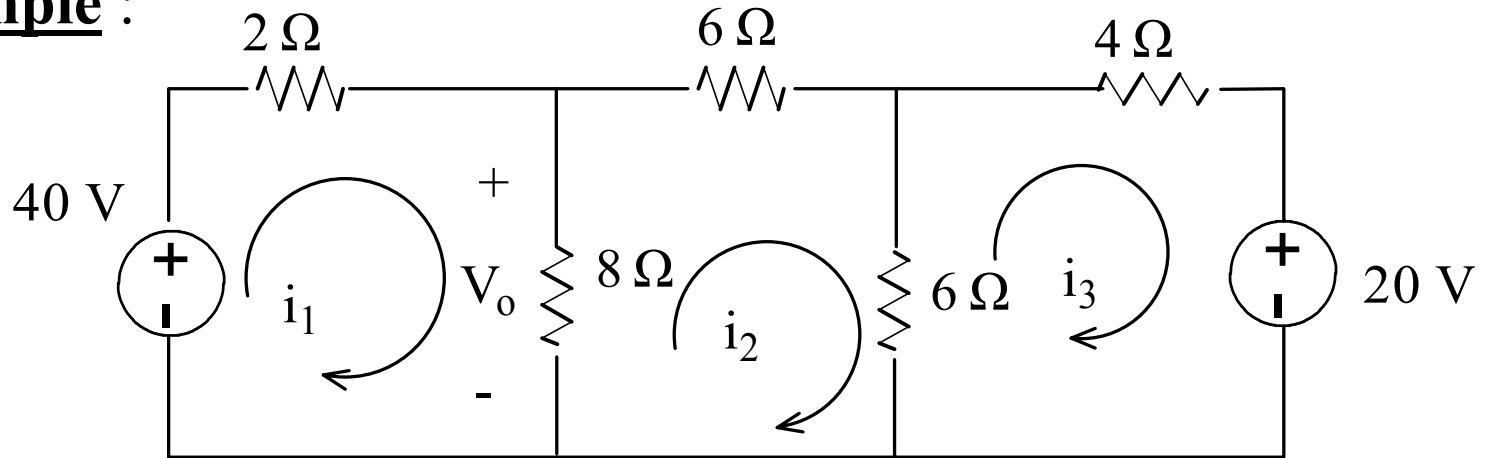

Find V_0 ?

We have (3) meshes

KVL left loop :

$$-40 + 2i_1 + 8(i_1 - i_2) = 0$$
$$10i_1 - 8i_2 + 0i_3 = 40 \quad \dots\dots(1)$$

$$\begin{aligned} \text{KVL middle loop: } & 8(i_2 - i_1) + 6i_2 + 6(i_2 - i_3) = 0 \\ & -8i_1 + 20i_2 - 6i_3 = 0 \end{aligned}$$

$$\begin{aligned} \text{KVL right loop : } & 20 + 6(i_3 - i_2) + 4i_3 = 0 \\ & 0i_1 - 6i_2 + 10i_3 = -20 \end{aligned}$$

$$\begin{bmatrix} 10 & -8 & 0 \\ -8 & 20 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \\ -20 \end{bmatrix}$$


$$i_1 = 5.6 \text{ A} \quad , i_2 = 2 \text{ A} \quad , i_3 = -0.8 \text{ A}$$

$$V_0 = 8(i_1 - i_2) = 8(5.6 - 2) = 8(3.6)$$

$$V_0 = 28.8 \text{ V}$$

Example:

Mesh with dependent source

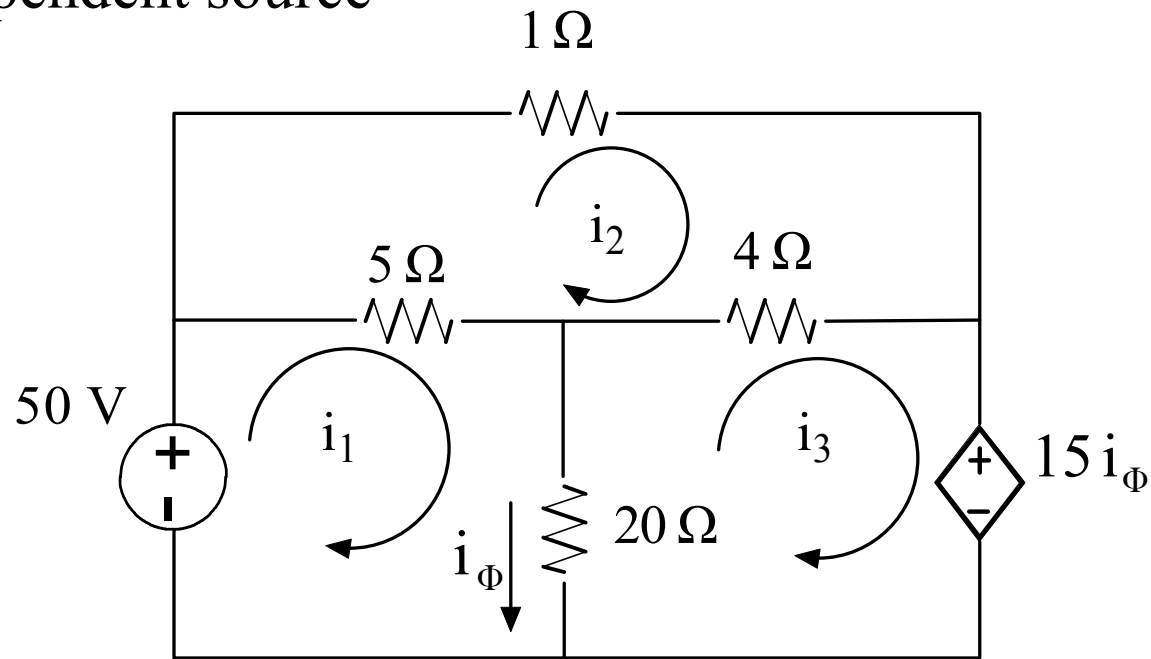

of meshes = 3 so 3 equations are needed

KVL around mesh 1:

$$-50 + 5(i_1 - i_2) + 20(i_1 - i_3)$$
$$25i_1 - 5i_2 - 20i_3 = 50 \quad \dots\dots(1)$$

$$\begin{aligned} \text{KVL around mesh 2: } & 1i_2 + 4(i_2 - i_3) + 5(i_2 - i_1) = 0 \\ & -5i_1 + 10i_2 - 4i_3 = 0 \quad \dots\dots(2) \end{aligned}$$

$$\begin{aligned} \text{KVL around mesh 3: } & 15i_\phi + 20(i_3 - i_1) + 4(i_3 - i_2) = 0 \\ \text{where } & i_\phi = i_1 - i_3 \end{aligned}$$

$$\begin{aligned} \therefore & 15(i_1 - i_3) + 20(i_3 - i_1) + 4(i_3 - i_2) = 0 \\ & -5(i_1 - i_3) + 4(i_3 - i_2) = 0 \\ & -5i_1 - 4i_2 + 9i_3 = 0 \end{aligned}$$


$$\begin{bmatrix} 25 & -5 & -20 \\ -5 & 10 & -4 \\ -5 & -4 & 9 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix}$$

$$i_1 = 29.6 \text{ A}, \quad i_2 = 26 \text{ A}, \quad i_3 = 28 \text{ A}$$

Special Case :


What happens if a current source is located between two meshes

⇒ “Super mesh”

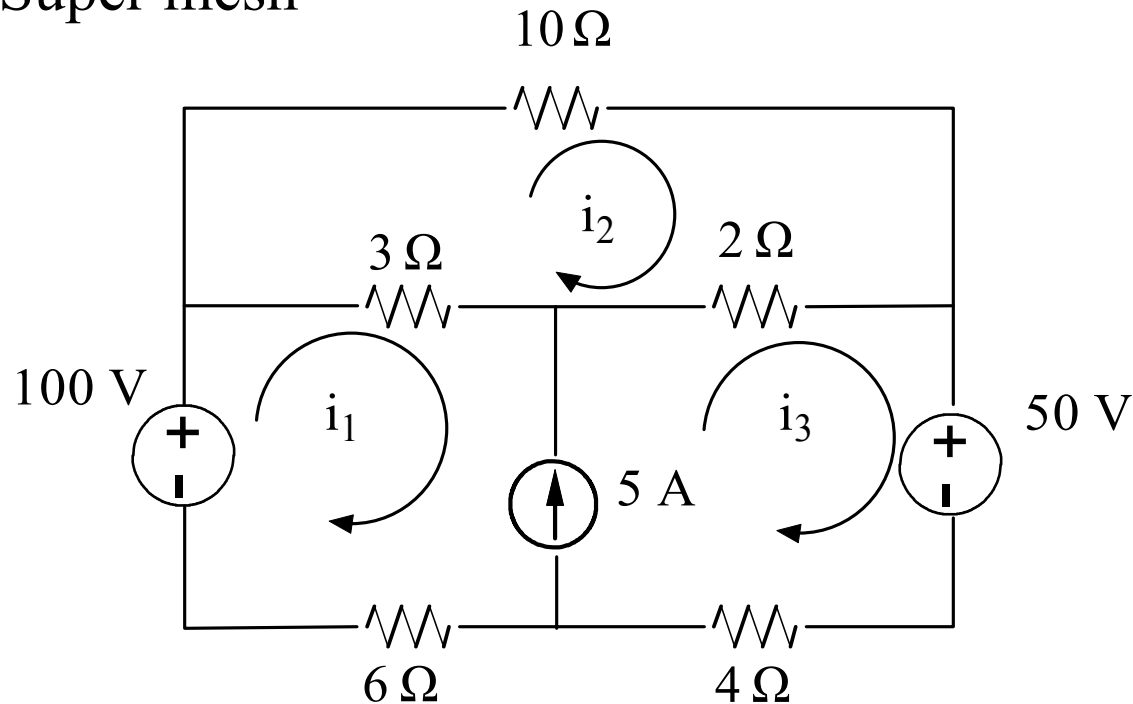

You don't know the voltage across the current source !!

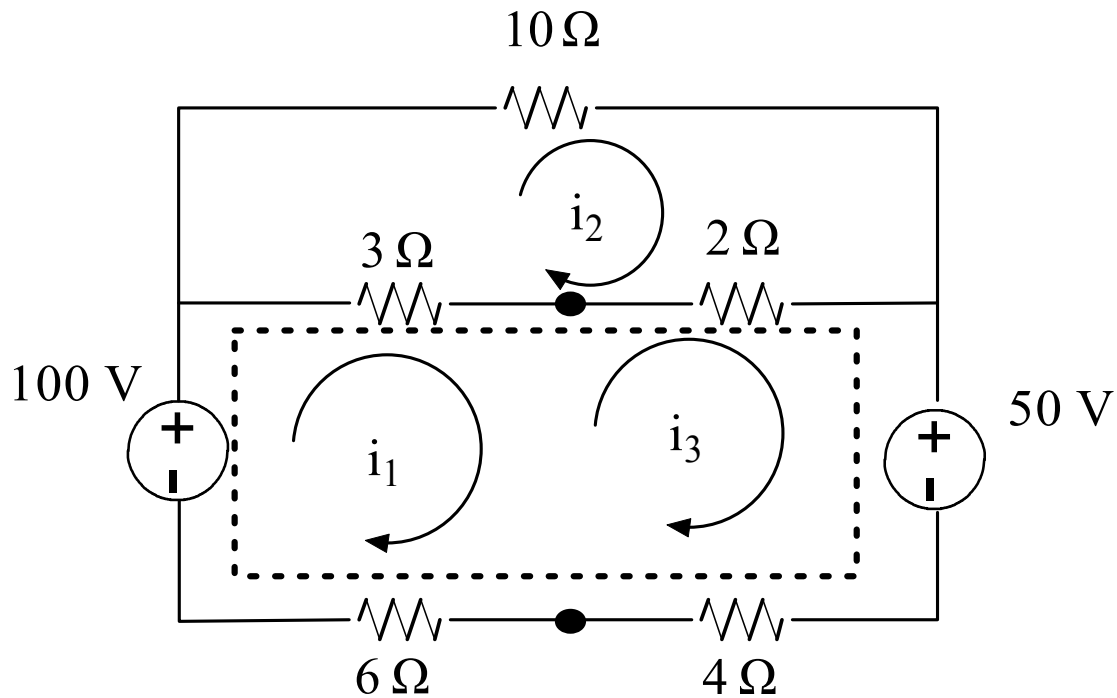⇒ Remove the whole branch that includes the current source



Apply KVL around the super mesh

$$-100 + 3(i_1 - i_2) + 2(i_3 - i_2) + 50 + 4i_3 + 6i_1 = 0$$

$$9i_1 - 5i_2 + 6i_3 = 50 \quad \dots\dots(1)$$

KVL around the upper loop:

$$10i_2 + 2(i_2 - i_3) + 3(i_2 - i_1) = 0$$
$$-3i_1 + 15i_2 - 2i_3 = 0 \quad \dots\dots(2)$$

We also know


$$i_3 - i_1 = 5 \text{ A}$$
$$-i_1 + 0i_2 + i_3 = 5 \quad \dots\dots(3)$$

$$i_1 = 1.75 \text{ A}$$

$$i_2 = 1.25 \text{ A}$$


$$i_3 = 6.75 \text{ A}$$

Example:

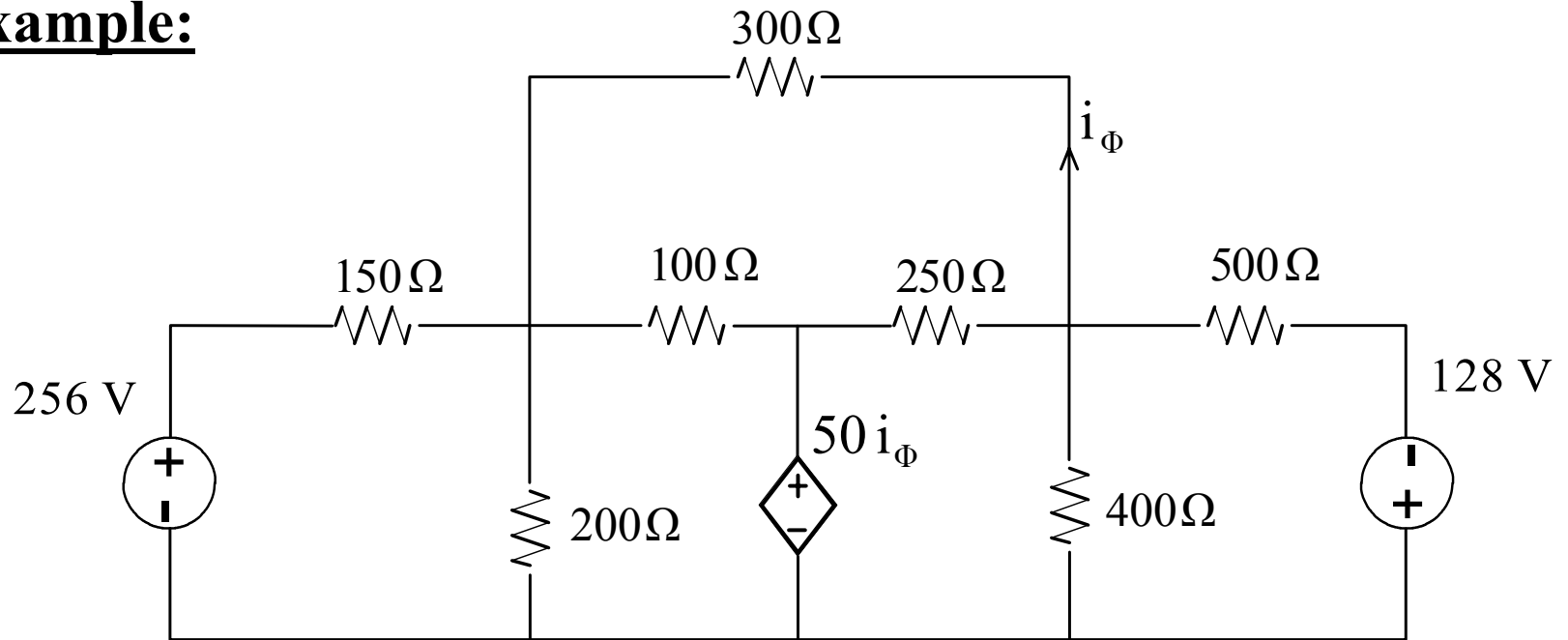

Use nodal analysis and loop analysis to find power in the 300 (Ω) resistor ?

Nodal Analysis :

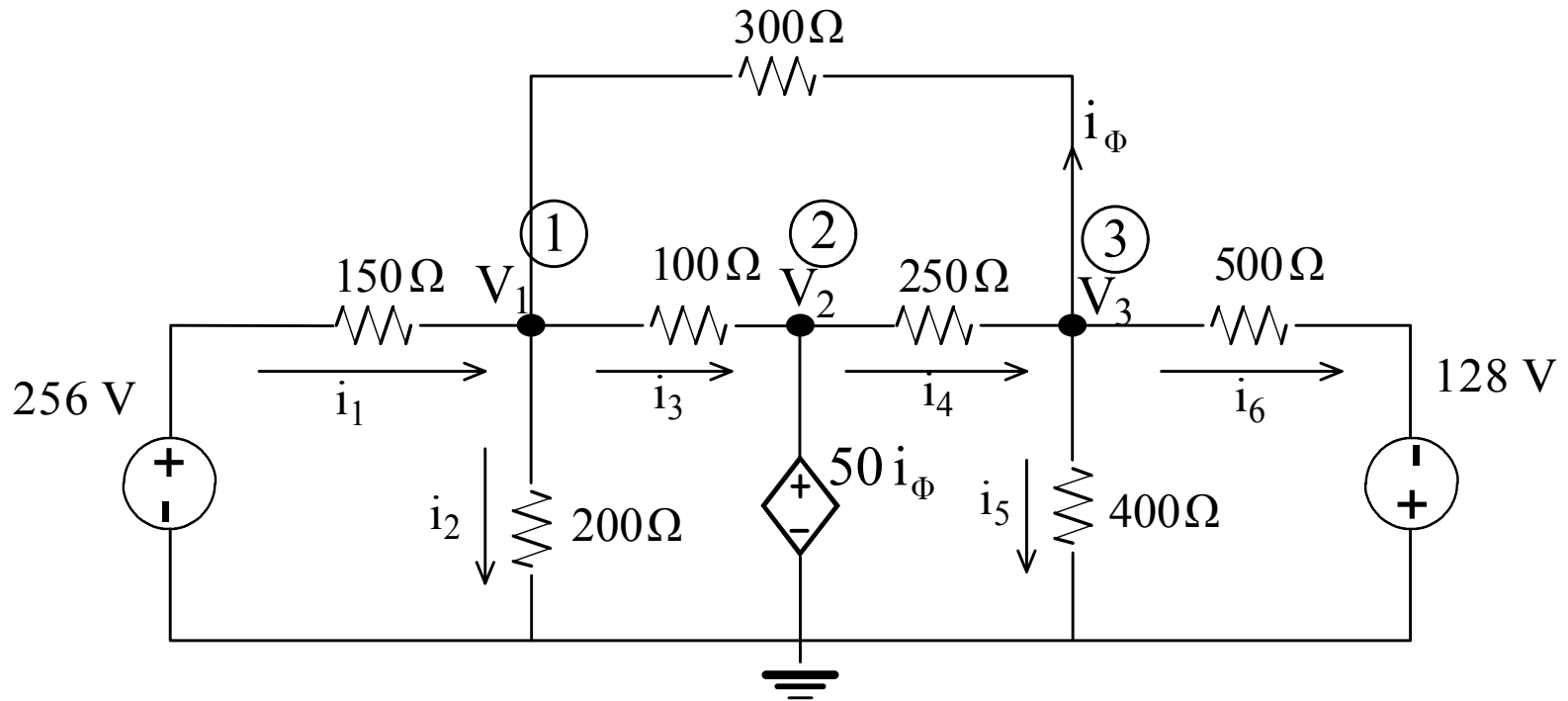

KCL at node (1): $i_1 + i_\phi - i_2 - i_3 = 0$

$$\frac{256 - V_1}{150} + \frac{V_3 - V_1}{300} - \frac{V_1}{200} - \frac{V_1 - V_2}{100} = 0$$

$$V_1 \left(\frac{1}{150} + \frac{1}{300} + \frac{1}{200} + \frac{1}{100} \right) - \left(\frac{1}{100} \right) V_2 - \left(\frac{1}{300} \right) V_3 = \frac{256}{150}$$

$$0.0250 V_1 - 0.01 V_2 - 0.003333 V_3 = 1.7067 \quad \dots\dots(1)$$

KCL at node (3):

$$i_4 - i_5 - i_6 - i_\phi = 0$$

$$\frac{V_2 - V_3}{150} - \frac{V_3}{400} - \frac{V_3 - (-128)}{500} - \frac{V_3 - V_1}{300} = 0$$

$$\frac{V_1}{300} + \frac{V_2}{250} + V_3 \left(\frac{-1}{250} - \frac{1}{400} - \frac{1}{500} - \frac{1}{300} \right) = \frac{128}{500}$$

$$0.0033 V_1 + 0.004 V_2 - 0.0118 V_3 = 0.256 \quad \dots\dots(2)$$

You can notice that

$$V_2 = 50 i_\phi$$

$$V_2 = 50 \left(\frac{V_3 - V_1}{300} \right) = \frac{1}{6} V_3 - \frac{1}{6} V_1$$

$$0.166 V_1 + 1 V_2 - 0.1667 V_3 = 0 \quad \dots\dots(3)$$

$$\begin{bmatrix} 0.0383 & -0.01 & -0.0033 \\ 0.0033 & 0.004 & -0.0118 \\ 0.1667 & 1 & -0.1667 \end{bmatrix} \begin{bmatrix} V1 \\ V2 \\ V3 \end{bmatrix} = \begin{bmatrix} 1.7067 \\ 0.256 \\ 0 \end{bmatrix}$$

$$V_1 = 62.5 \text{ V}$$


$$V_2 = -11.75 \text{ V}$$

$$V_3 = -8 \text{ V}$$


$$i_{\Phi} = \frac{V_2}{50} \Rightarrow i_{\Phi} = -0.235 \text{ A}$$

$$P_{300\Omega} = i_{\Phi}^2 R = (-0.235)^2 (300) = 16.5675 \text{ W}$$

Using loop analysis:

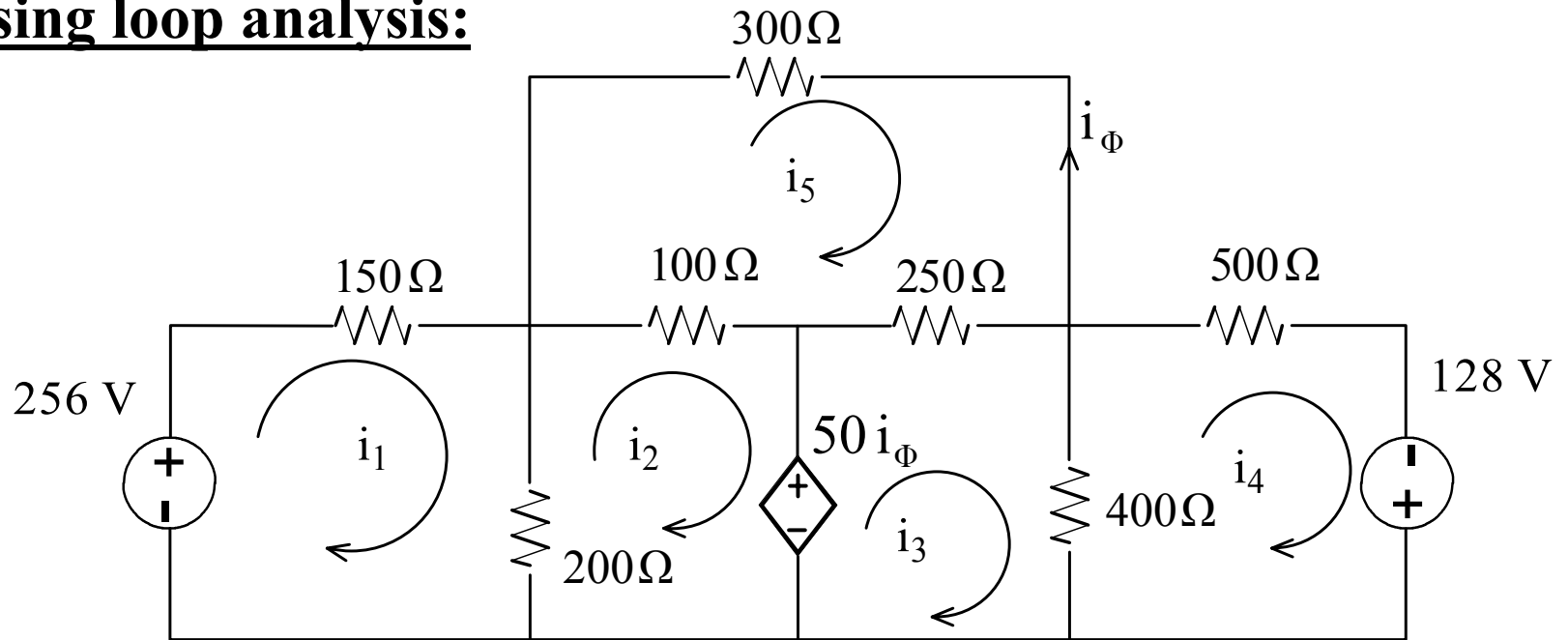

5 meshes

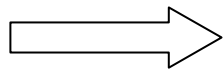

5 equations

KVL around loop (1):

$$150 i_1 + 200 (i_1 - i_2) = 256$$

$$350 i_1 - 200 i_2 = 256 \quad \dots\dots(1)$$

KVL around loop (2):

$$100 (i_2 - i_5) + 50 i_{\Phi} + 200 (i_2 - i_1) = 0$$

$$i_{\Phi} = -i_5$$

$$100 (i_2 - i_5) - 50 i_5 + 200 (i_2 - i_1) = 0$$

$$-200 i_1 + 300 i_2 - 150 i_5 = 0 \quad \dots\dots(2)$$

KVL around loop (3)

$$500 i_4 - 128 + 400 (i_4 - i_3) = 0$$

$$-400 i_3 + 900 i_4 = 128 \quad \dots\dots(4)$$

KVL around loop (4)

$$250 (i_3 - i_5) + 400 (i_3 - i_4) - 50 i_{\Phi} = 0$$

$$650 i_3 - 400 i_4 - 200 i_5 = 0 \quad \dots\dots(3)$$

since $i_{\Phi} = -i_5$

KVL around loop (5)

$$\begin{aligned} 300 i_5 + 250 (i_5 - i_3) + 100 (i_5 - i_2) &= 0 \\ -100 i_2 - 250 i_3 + 650 i_5 &= 0 \quad \dots\dots(5) \end{aligned}$$

$$\begin{bmatrix} 350 & -200 & 0 & 0 & 0 \\ -200 & 300 & 0 & 0 & -150 \\ 0 & 0 & 650 & -400 & -200 \\ 0 & 0 & -400 & 900 & 0 \\ 0 & -100 & -250 & 0 & 650 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 256 \\ 0 \\ 0 \\ 128 \\ 0 \end{bmatrix}$$

$$i_1 = 1.29 \text{ A}$$

$$i_2 = 0.9775 \text{ A}$$

$$i_3 = 0.22 \text{ A}$$


$$i_4 = 0.24 \text{ A}$$

$$i_5 = 0.235 \text{ A}$$

$$\begin{aligned} P_{300\Omega} &= (i_5)^2 R = (0.235)^2 (300) \\ &= 16.5675 \text{ W} \end{aligned}$$

Example:

Use the loop analysis to find V_{Φ}

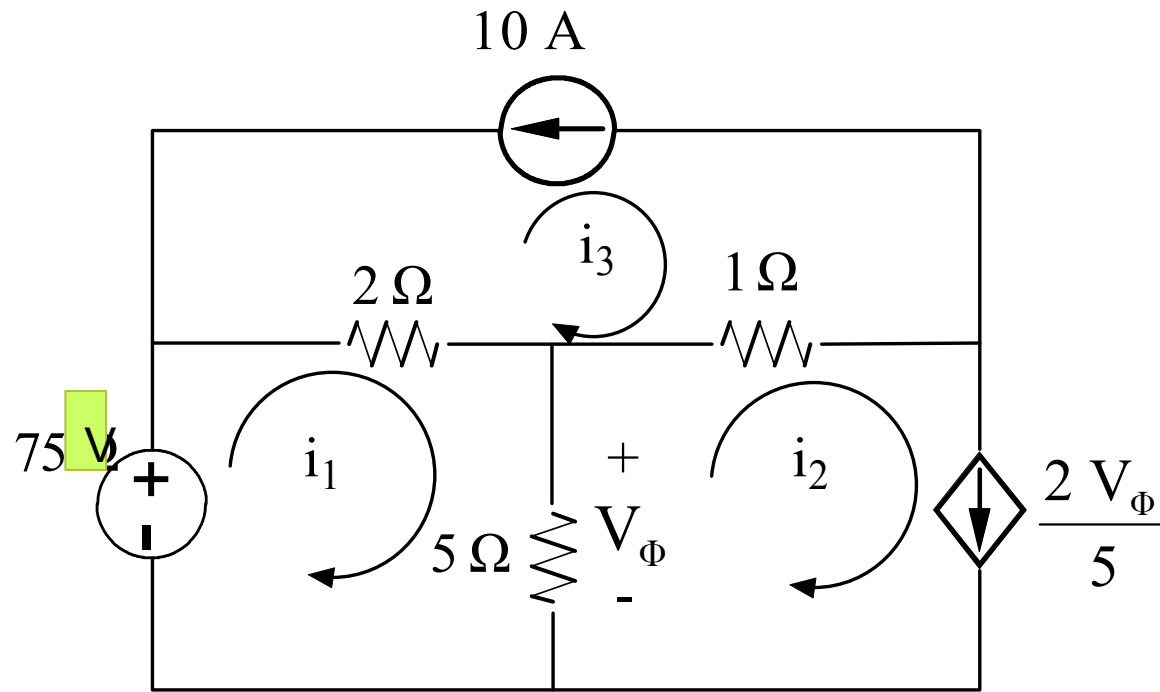

(3) Meshes \Rightarrow (3) equations

$$i_3 = -10\text{ A}$$

KVL around loop (1):

$$2 (i_1 - i_3) + 5 (i_1 - i_2) - 75 = 0$$

$$7 i_1 - 5 i_2 + 20 - 75 = 0$$

$$7 i_1 - 5 i_2 = 55 \quad \dots\dots (1)$$

Equation of dependent source:

$$i_2 = \frac{2 V_\Phi}{5}$$

$$V_\Phi = 5 (i_1 - i_2)$$

$$i_2 = \left(\frac{2}{5} \right) (5) (i_1 - i_2) = 2 i_1 - 2 i_2$$

$$2 i_1 - 3 i_2 = 0 \quad \dots\dots (2)$$

$$\begin{bmatrix} 7 & -5 \\ 2 & -3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 55 \\ 0 \end{bmatrix}$$

$$i_1 = 15 \text{ A}$$

$$i_2 = 10 \text{ A}$$

$$\begin{aligned} V_{\Phi} &= 5 (i_1 - i_2) \\ &= 5 (15 - 10) = 25 \text{ V} \end{aligned}$$

$$V_{\Phi} = 25 \text{ V}$$