
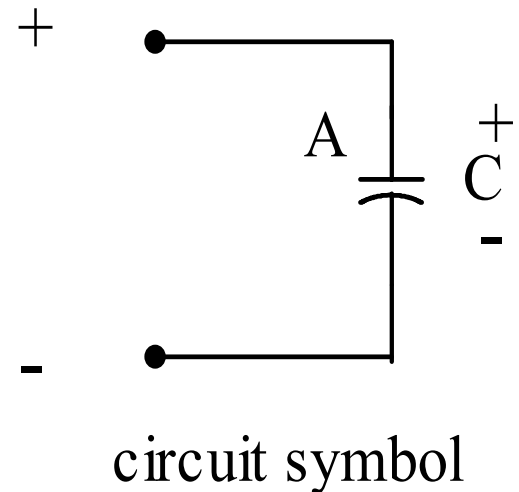


# Chapter (5)

## Capacitors and Inductors
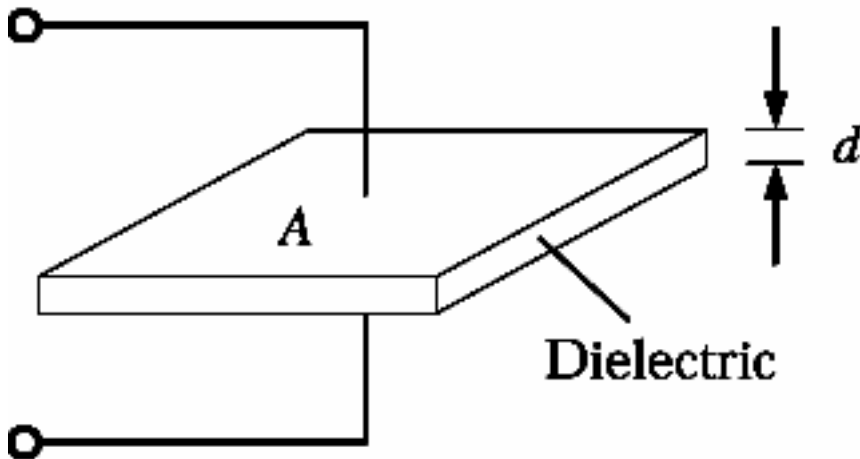
### Capacitors :

A circuit element that is composed of two conducting plates or surfaces separated by a dielectric (non conducting) materials



Let  $A$  : surface area of each plate  
 $d$  : distance between the two plates

Capacitance  $\uparrow$  As Area  $\uparrow$   
Capacitance  $\downarrow$  As distance  $\uparrow$

$$\therefore C \propto \frac{A}{d}$$

It is found that  $C = \frac{\epsilon_0 A}{d}$

Where :

$\epsilon_0 \equiv$  Permittivity of free space

$$\epsilon_0 \equiv 8.85 * 10^{-12} \text{ F/m}$$

- If a voltage source ( $v$ ) is connected to the capacitor, +ve charge will be transferred to one plate while -ve charge will be transferred to the other plate.

Let the charge stored at the capacitor  $\equiv q$

$$\text{If } v \uparrow, q \uparrow$$

$$\therefore v \propto q$$

It has been found that

$$q = c v$$

C is the capacitance

$$\Rightarrow c = \frac{q}{v}$$

Current in capacitor :

We know that

$$i(t) = \frac{dq(t)}{dt}$$

$$\therefore i_c(t) = \frac{d}{dt} (c v_c(t))$$

$$\Rightarrow i_c(t) = C \frac{dv_c(t)}{dt}$$

## Voltage of capacitors

$$\therefore i_c(t) = C \frac{dv_c(t)}{dt}$$

$$\therefore i_c(t) dt = C dv_c(t)$$

$$\Rightarrow dv_c(t) = \frac{1}{C} i_c(t) dt$$


$$v_c(t) = v_c(t_0) + \frac{1}{C} \int_{\tau=t_0}^{\tau=t} i_c(\tau) d\tau$$

Where  $t_0$  : initial time

Note:


Capacitors only store and release ELECTROSTATIC energy. They do not "create"

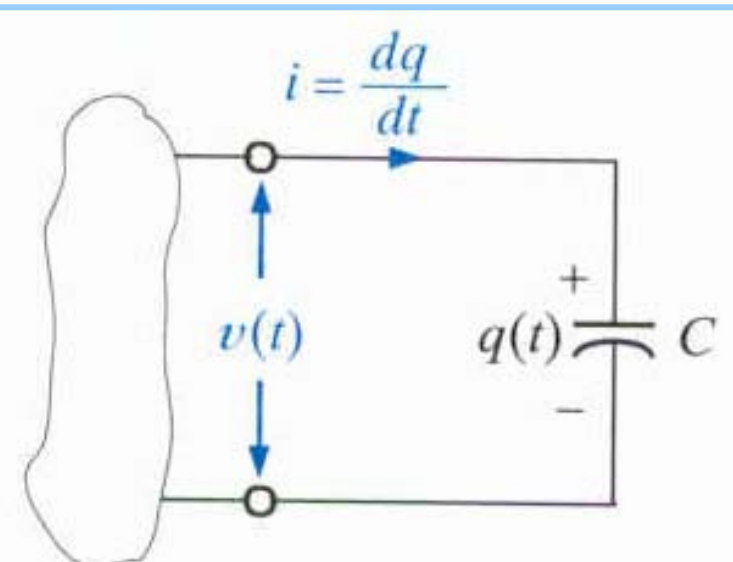The capacitor is a passive element and follows the passive sign convention




Linear capacitor circuit representation

$$i(t) = C \frac{dv}{dt}(t)$$

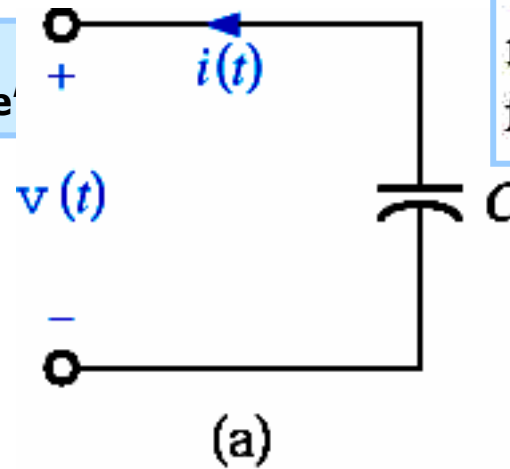

Write the  $i$ - $v$  relationship for the following capacitors.

$$i(t) = -C \frac{dv(t)}{dt}$$

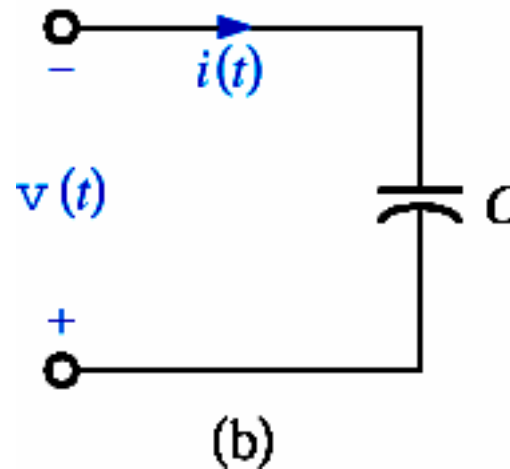

$$i(t) = -C \frac{dv(t)}{dt}$$

## Power of the capacitors :

$$P_c(t) = v_c(t) i_c(t)$$

$$P_c(t) = v_c(t) C \frac{dv_c(t)}{dt} = C v_c(t) \frac{dv_c(t)}{dt}$$

or

$$P_c(t) = i_c(t) \left[ v_c(t_0) + \frac{1}{C} \int_{\tau=t_0}^{\tau=t} i_c(\tau) d\tau \right]$$

## Energy of capacitor

$$\begin{aligned}w_c(t) &= \int_{\tau=-\infty}^{\tau=t} P_c(\tau) d\tau \\&= \int_{\tau=-\infty}^{\tau=t} \left( C v_c(\tau) \frac{dv_c(\tau)}{d\tau} \right) d\tau \\&= \int_{v_c(-\infty)}^{v_c(t)} C v_c(\tau) dv_c(\tau) \\&= \frac{1}{2} C v_c^2(\tau) \Big|_{v_c(-\infty)}^{v_c(t)} \\&= \frac{1}{2} C v_c^2(t) - \frac{1}{2} C v_c^2(-\infty)\end{aligned}$$



Assuming

$$v_c(-\infty) = 0$$

$$\therefore w_c(t) = \frac{1}{2} C v_c^2(t)$$

$$v_c(t) = \frac{q(t)}{C}$$


$$\therefore w_c(t) = \frac{1}{2} C \frac{q^2(t)}{C^2}$$

$$w_c(t) = \frac{1}{2C} q^2(t)$$
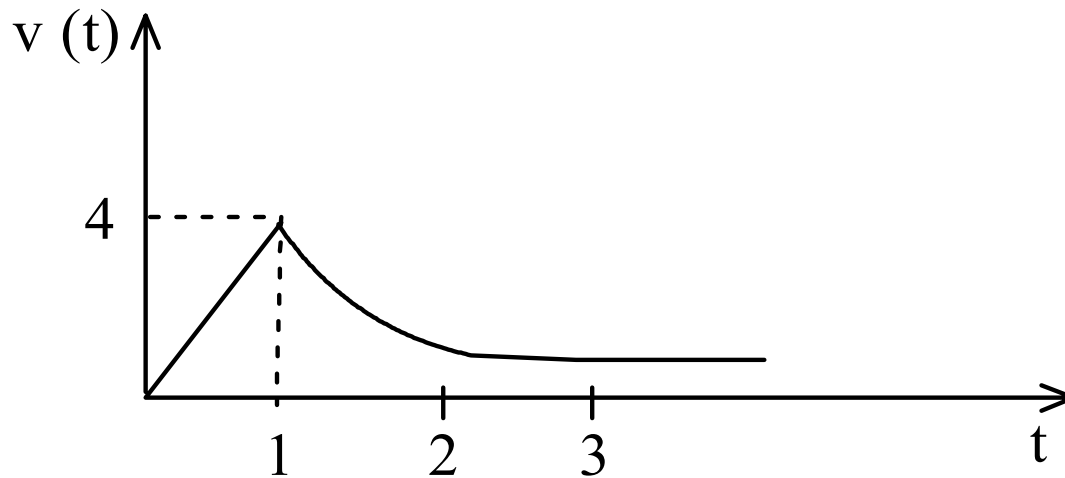
### Example:

The following voltage is imposed across the terminals of a  $0.5 \mu\text{F}$  capacitor.

$$v_c(t) = \begin{cases} 0 \text{ V} & , \quad t \leq 0 \\ 4t \text{ V} & , \quad 0 \leq t \leq 1 \\ 4e^{-(t-1)} \text{ V} & , \quad 1 \leq t < \infty \end{cases}$$




Find the following:

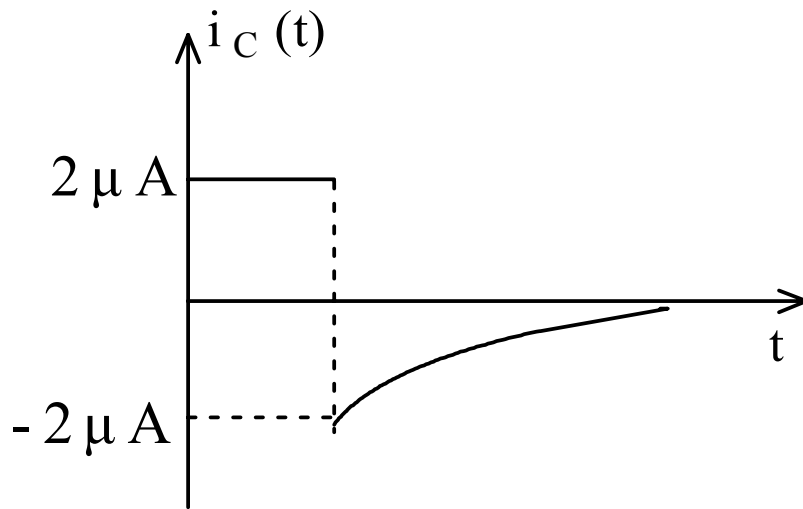
1.  $i_c(t)$
2.  $P_c(t)$
3.  $w_c(t)$

$$(1) \quad i_c(t) = C \frac{dv_c(t)}{dt}$$

$$\therefore i_c(t) = \begin{cases} 0 & t < 0 \\ C \frac{d}{dt}(4t) = 4C = 2 \mu A & 0 < t < 1 \\ C \frac{d}{dt}[4e^{-(t-1)}] = (4C)(-1)e^{-(t-1)} = -2e^{-(t-1)} \mu A & 1 < t < \infty \end{cases}$$



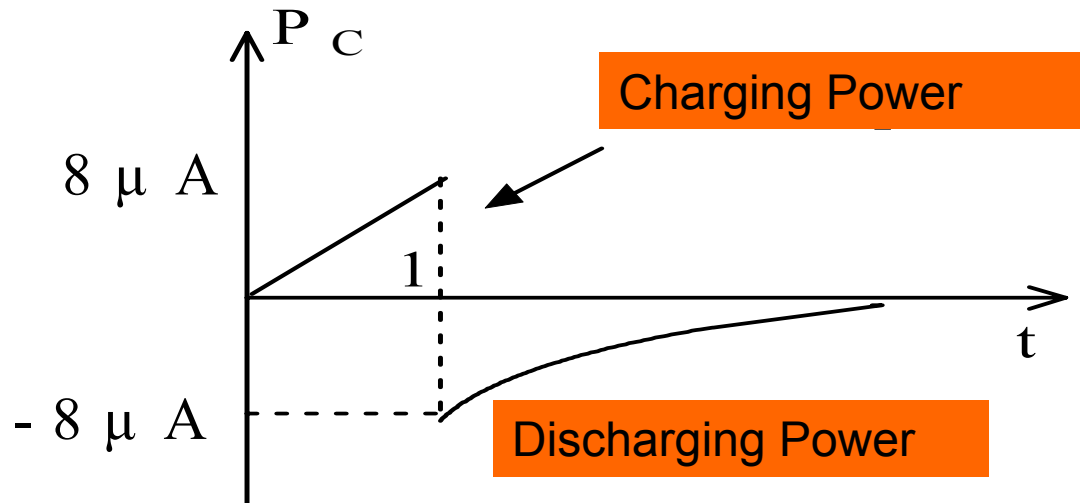
$$\begin{aligned}
 (2) \quad P_c(t) &= C v_c(t) \frac{dv_c(t)}{dt} \\
 &= \begin{cases} (0.5 \mu\text{F})(0) \frac{dv_c(t)}{dt} = 0 & \text{W} & t \leq 0 \\ (0.5 \mu\text{F})(4t)(4) = 8t & \mu\text{W} & 0 \leq t < 1 \\ (0.5 \mu\text{F})(4e^{-(t-1)})(-4)e^{-(t-1)} = -8e^{-2(t-1)} & \mu\text{W} & 1 < t < \infty \end{cases}
 \end{aligned}$$



$$(3) \quad w_c(t) = \frac{1}{2} C v_c^2(t)$$
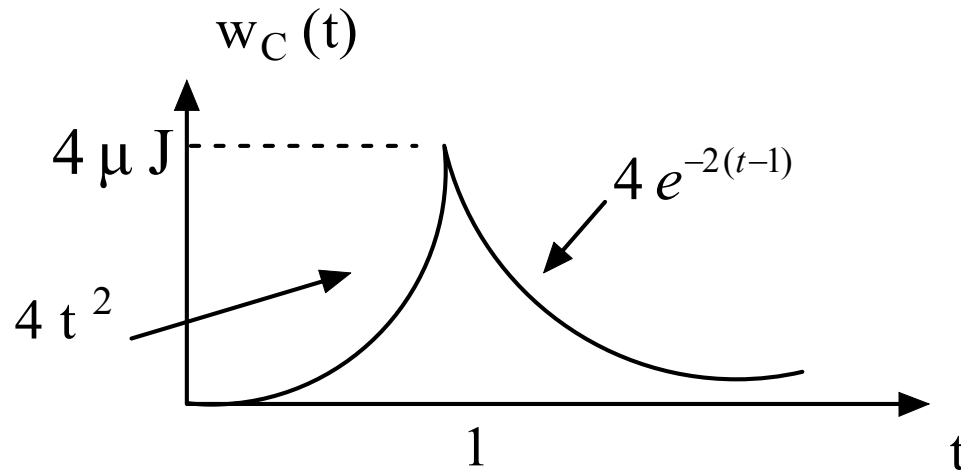
$$w_c(t) = \begin{cases} 0 & t \leq 0 \\ \frac{1}{2} (0.5 \mu\text{F})(4t)^2 = 4t^2 \quad \mu\text{J} & 0 \leq t \leq 1 \\ \frac{1}{2} (0.5 \mu\text{F})[4e^{-(t-1)}]^2 = 4e^{-2(t-1)} \quad \mu\text{J} & 1 \leq t < \infty \end{cases}$$




**Example :**

The voltage at the terminals of a  $0.5 \mu\text{F}$  capacitor is

$$v_c(t) = \begin{cases} 0 & t \leq 0 \\ 100 e^{-20000t} \sin(40000 t) \text{ V} & t \geq 0 \end{cases}$$

Find:

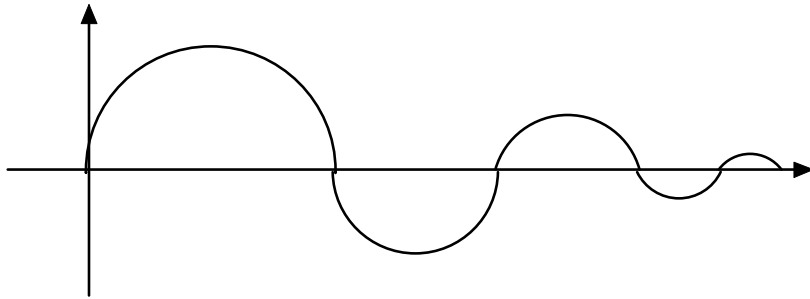1.  $i(0)$
2. Power delivered to the capacitors at  $t = \Pi/80$  m S.
3. Energy stored in the capacitor at  $t = \Pi/80$  m S



$$i(t) = C \frac{dv_c(t)}{dt}$$

$$= C \frac{d}{dt} \left[ 100 e^{-20,000t} \sin(40,000t) \right]$$

$$= C \left[ 100 e^{-20,000t} \cos(40,000t)(40,000) + \sin(40,000t) (-2 * 10^6 e^{-20,000t}) \right]$$

$$i_c(0) = 0.5 * 10^{-6} \left[ 100 (1) (1) (40,000) + 0 \right]$$

$$i_c(0) = 2 \text{ A}$$

(2) Find  $P_c \left( \frac{\pi}{80} \text{ m} \right)$  ?

$$P_c(t) = C v_c(t) \frac{dv_c(t)}{dt}, t \geq 0$$

$$= (0.5 \mu\text{F}) (100 e^{-20,000t} \sin(40,000t))$$

$$* \left[ 100 e^{-20,000t} \cos(40,000t)(40,000) + \sin(40,000t) (-2 * 10^6 e^{-20,000t}) \right]$$



$$P_C \left( \frac{\Pi}{80} \text{ m} \right) = -20.79 \text{ W} \quad (\text{discharging})$$


$$(3) \text{ Find } W_C \left( \frac{\Pi}{80} \text{ m} \right) \quad ?$$

$$W_C(t) = \frac{1}{2} C v_C^2(t) = \frac{1}{2} C \left[ 100e^{-20,000t} \sin(40,000t) \right]^2$$

$$W_C \left( \frac{\Pi}{80} \text{ m} \right) = 519.2 \mu\text{J}$$
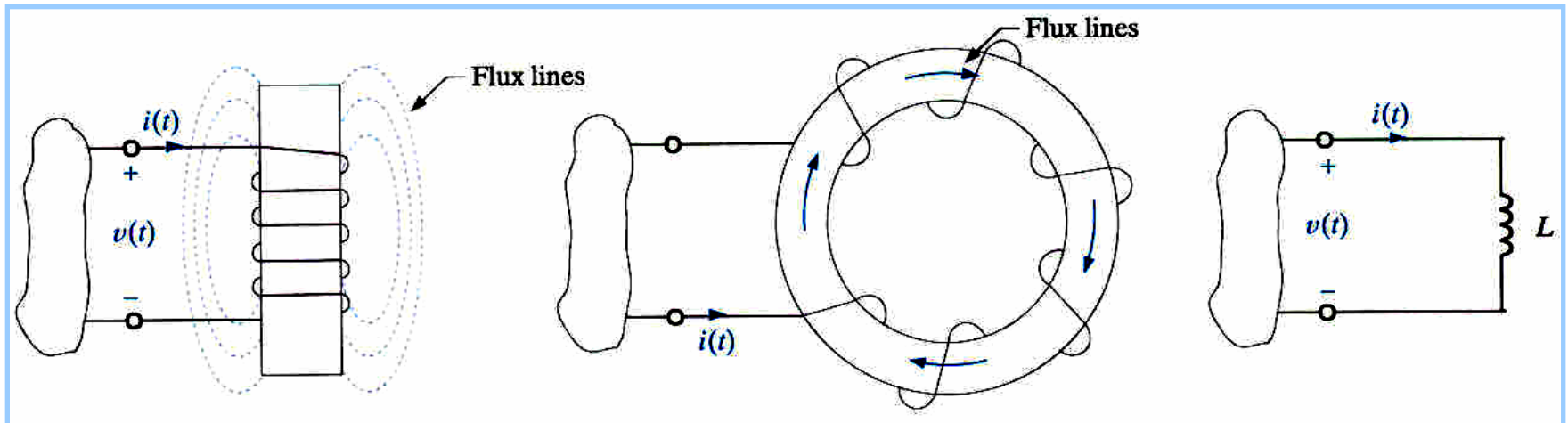
# Inductors :

Inductors are circuit elements that consist of a conducting wire in the shape of a coil



**Circuit representation  
for an inductor**

- If a current is flowing in the inductor, it produce a magnetic field  $\Phi$ .

$$\Phi(t) = Li(t)$$

Where L is the inductance and measured in Henry [H]

- The direction of ( $\Phi$ ) depends on the right-hand rule.
- As the current increases or decreases, the magnetic field spreads or collapse
- The change in magnetic field induces a voltage across the inductor.

$$V_L(t) = \frac{d\Phi(t)}{dt}$$

$$\therefore V_L(t) = L \frac{di_L(t)}{dt}$$

## Current in inductors :


$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$di_L(t) = \frac{1}{L} v_L(t) dt$$


Integrate both sides as before

$$i_L(t) = i_L(t_0) + \frac{1}{L} \int_{\tau=t_0}^{\tau=t} v(\tau) d\tau$$

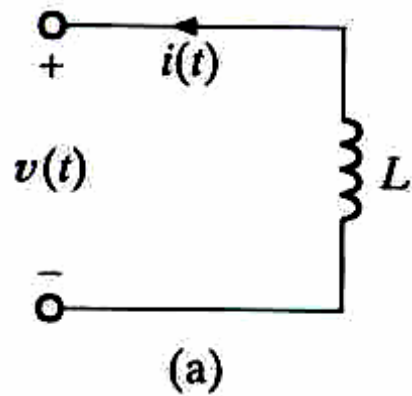Write the  $i$ - $v$  relationship for the following inductors.



$$v(t) = -L \frac{di(t)}{dt}$$

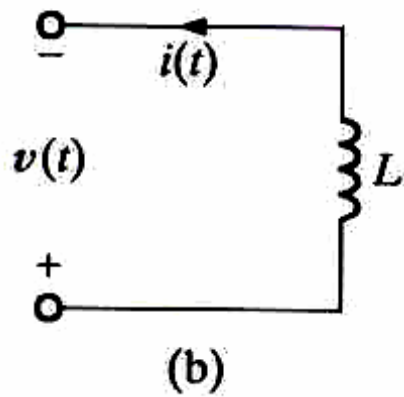

$$v(t) = L \frac{di(t)}{dt}$$

## Power in inductor :

$$P_L(t) = v_L(t) i_L(t)$$

$$= i_L(t) \left[ L \frac{di_L(t)}{dt} \right]$$

$$P_L(t) = L i_L(t) \frac{di_L(t)}{dt}$$

$$P_L(t) = v_L(t) \left[ i_L(t_0) + \frac{1}{L} \int_{\tau=t_0}^{\tau=t} v(\tau) d\tau \right]$$

## Energy in inductors:

$$\begin{aligned}w_L(t) &= \int_{\tau=-\infty}^{\tau=t} P_L(\tau) d\tau \\ &= \int_{\tau=-\infty}^{\tau=t} L i_L(\tau) \frac{di_L(\tau)}{d\tau} d\tau\end{aligned}$$

As before

$$w_L(t) = \frac{1}{2} L i_L^2(t)$$

## Example :

The current flow through an 100 m H inductor

$$i_L(t) = \begin{cases} 0 \text{ A} & t \leq 0 \\ 10 t e^{-5t} \text{ A} & t \geq 0 \end{cases}$$

Find :

- (1) Maximum value of current.
- (2)  $v_L(t)$  , (3)  $P_L(t)$  , (4)  $w_L(t)$


First, find  $t_{\max}$

$$\text{let } \frac{di_L(t)}{dt} = 0$$

$$(10t)(-5e^{-5t}) + e^{-5t}(10) = 0$$

$$\therefore e^{-5t} [-50t + 10] = 0$$

$$t_{\max} = 0.2 \text{ sec}$$

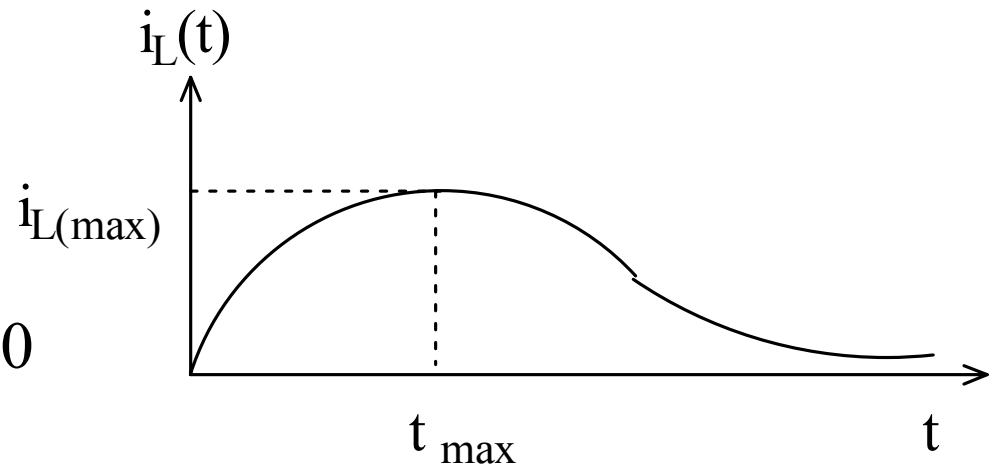



$$\begin{aligned} \dot{i}_{L\max} &= \dot{i}_L (0.2) = 10 (0.2) e^{-5(0.2)} \\ &= 2 e^{-1} = 0.736 \text{ A} \end{aligned}$$

$$\begin{aligned} (2) \quad v_L(t) &= L \frac{di_L(t)}{dt} \\ &= (0.1 \text{ H}) \frac{d}{dt} [10 t e^{-5t}] \\ &= (0.1) e^{-5t} (-50 t + 10) \\ &= e^{-5t} (1 - 5 t) \end{aligned}$$

$$v_L(t) = \begin{cases} 0 & , t < 0 \\ e^{-5t} (1 - 5 t) & , t > 0 \end{cases}$$

(3)  $P_L(t)$  ?

$$P_L(t) = L i_L(t) \frac{di_L(t)}{dt}$$

$$P_L(t) = 0, \quad t \leq 0$$

$$P_L(t) = (0.1) (10 t e^{-5t}) [e^{-5t} (-50 t + 10)] \quad , \quad t \geq 0$$

$$P_L(t) = t e^{-10t} (10 - 50 t)$$

$$P_L(t) = \begin{cases} 0 & , \quad t \leq 0 \\ 10 t e^{-10t} (1 - 5 t) & , \quad t \geq 0 \end{cases}$$

$$(4) \quad w_L(t) \quad ?$$

$$w_L(t) = \frac{1}{2} L i_L^2(t)$$

$$= \begin{cases} 0 & , t \leq 0 \\ \frac{1}{2} (0.1) (10 t e^{-5t})^2 = 5 t^2 e^{-10t} & , t \geq 0 \end{cases}$$

## Summary of results :

	<b>Capacitor</b>	<b>Inductor</b>
<b>v (t)</b>	$v_C(t_0) + \frac{1}{C} \int_{\tau=t_0}^{\tau=t} i_C(\tau) d\tau$	$L \frac{di_L(t)}{dt}$
<b>i (t)</b>	$C \frac{dv_C(t)}{dt}$	$i_L(t_0) + \frac{1}{L} \int_{\tau=t_0}^{\tau=t} v_L(\tau) d\tau$
<b>P (t)</b>	$C v_C(t) \frac{dv_C(t)}{dt}$	$L i_L(t) \frac{di_L(t)}{dt}$
<b>w (t)</b>	$\frac{1}{2} C v_C^2(t)$	$\frac{1}{2} L i_L^2(t)$

## Notes on capacitor :

1. If  $v_C(t) = \text{constant}$  ,  $i_C(t) = 0$

⇒ Capacitor will be open circuit

2.  $v_C(t)$  cannot change instantaneously ( no sudden change)

because 
$$\int_{\tau=t_0}^{\tau=t} i_C(\tau) d\tau = 0$$

3. Capacitors can store energy

$$w_C(t) = \frac{1}{2} C v_C^2(t)$$

## Notes on inductors :

1. If  $i_L(t) = \text{constant}$  ,  $v_L(t) = 0$

⇒ Inductor will be short circuit

2.  $i_L(t)$  cannot change instantaneously ( no sudden change)




because 
$$\int_{\tau=t_0}^{\tau=t} v_L(\tau) d\tau = 0$$

3. Inductors can store energy

$$w_L(t) = \frac{1}{2} L i_L^2(t)$$

# Capacitors and Inductors combinations :

## 1. Series capacitors :

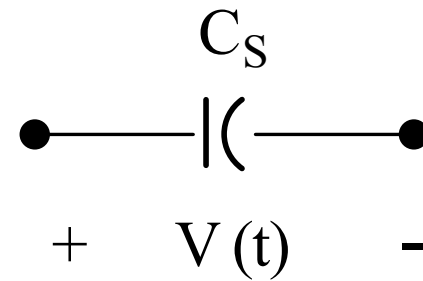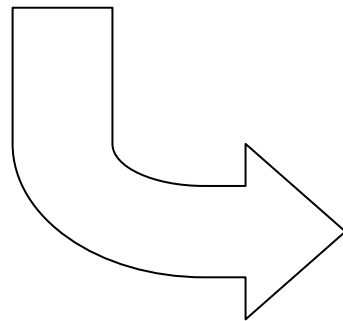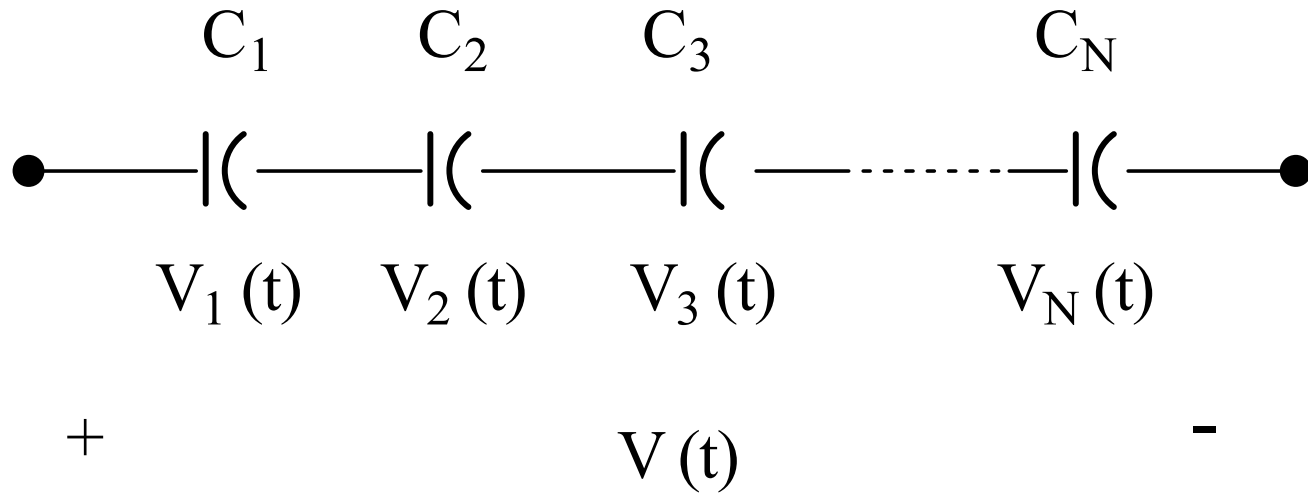

$$v(t) = v_1(t) + v_2(t) + v_3(t) + \cdots + v_N(t)$$

For each capacitor ,

$$v_k(t) = v_k(t_0) + \frac{1}{c_k} \int_{\tau=t_0}^{\tau=t} i(\tau) d\tau$$

$$v(t) = v_1 + v_2 + \cdots + v_N$$


$$v(t) = \left[ \sum_{k=1}^N v_k(t_0) \right] + \left( \sum_{k=1}^N \frac{1}{c_k} \right) \int_{\tau=t_0}^{\tau=t} i(\tau) d\tau$$

The equivalent capacitance  $C_S$  is

$$\frac{1}{C_S} = \sum_{k=1}^N \frac{1}{C_k} = \frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_N}$$



## Parallel capacitors :

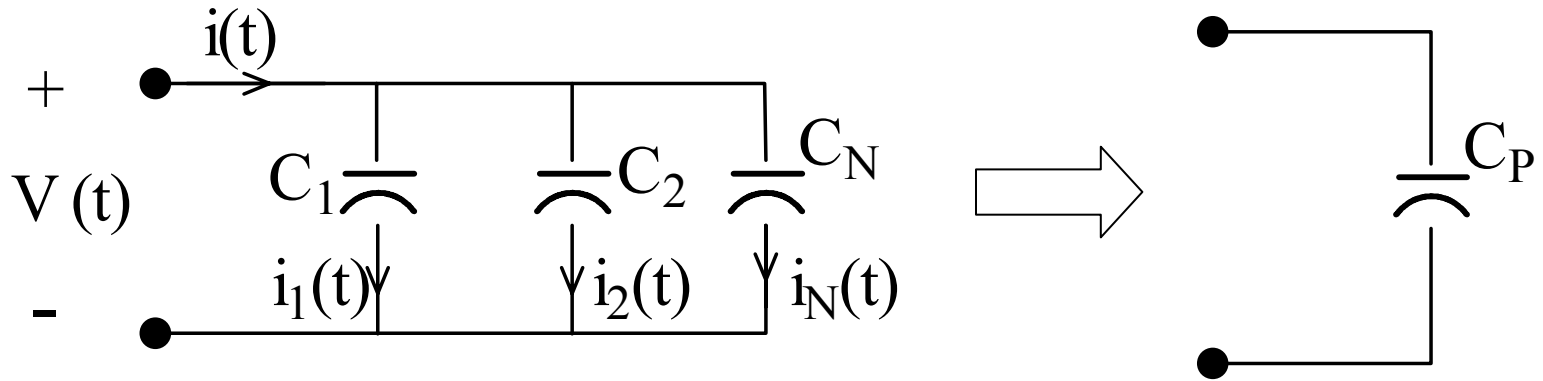

$$i(t) = i_1(t) + i_2(t) + \dots + i_N(t)$$


$$= C_1 \frac{dv(t)}{dt} + C_2 \frac{dv(t)}{dt} + \dots + C_N \frac{dv(t)}{dt}$$

$$i(t) = \frac{dv(t)}{dt} \left[ \sum_{k=1}^N C_k \right] = C_P \frac{dv(t)}{dt}$$

The equivalent capacitance,  $C_P$

$$C_P = C_1 + C_2 + C_3 + \dots + C_N$$

## Series Inductors :

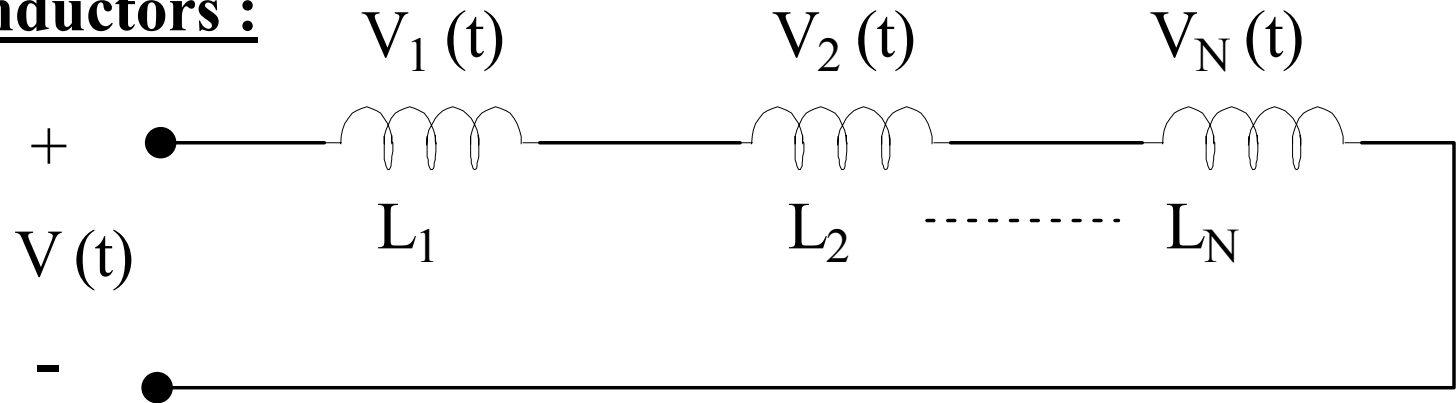


$$v(t) = v_1(t) + v_2(t) + \cdots + v_N(t)$$

$$= L_1 \frac{di(t)}{dt} + L_2 \frac{di(t)}{dt} + \cdots + L_N \frac{di(t)}{dt}$$

$$v(t) = \left( \sum_{k=1}^N L_k \right) \frac{di(t)}{dt} = L_s \frac{di(t)}{dt}$$

$$L_s = L_1 + L_2 + L_3 + \cdots + L_N$$

## Parallel Inductors :

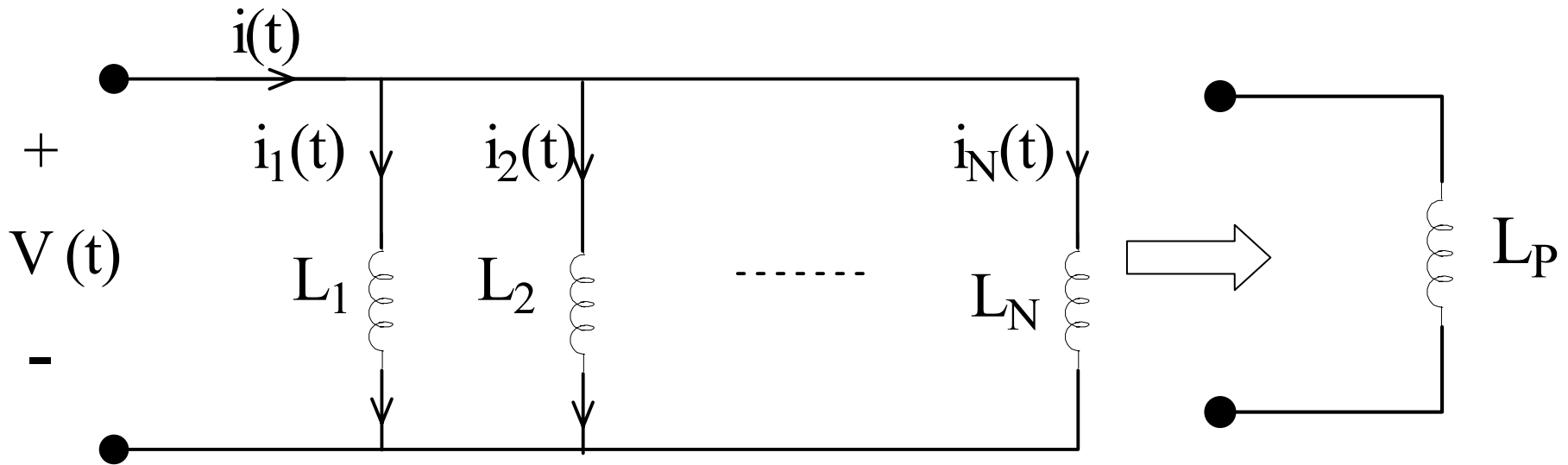

$$i(t) = i_1(t) + i_2(t) + \dots + i_N(t)$$

where

$$i_k(t) = i_k(t_0) + \frac{1}{L_k} \int_{\tau=t_0}^{\tau=t} v(\tau) d\tau$$

$$\mathbf{i}(t) = \left[ \sum_{k=1}^N \mathbf{i}_k(t_0) \right] + \left[ \sum_{k=1}^N \frac{1}{L_k} \right] \int_{\tau=t_0}^{\tau=t} v(\tau) d\tau$$


$$\mathbf{i}(t) = \mathbf{i}(t_0) + \frac{1}{L_P} \int_{\tau=t_0}^{\tau=t} v(\tau) d\tau$$

The equivalent inductance ,  $L_P$

$$\frac{1}{L_P} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$
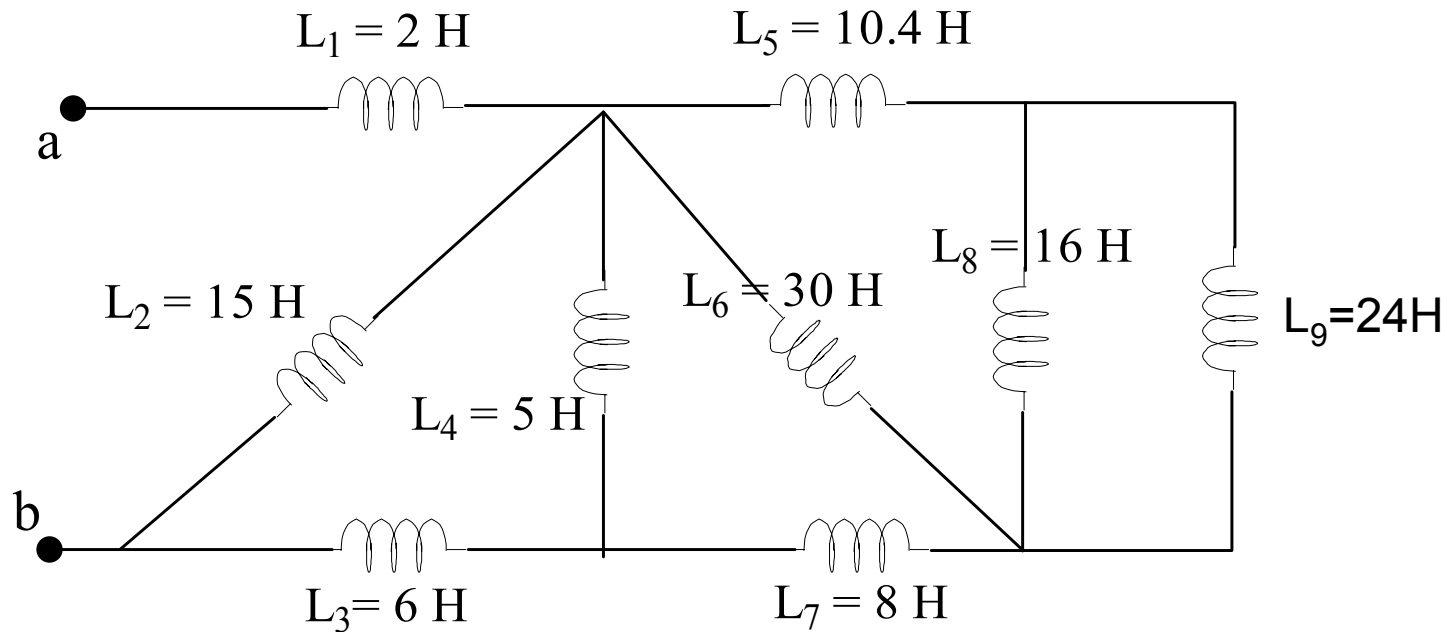
## Example:

Find the equivalent inductance with respect to the terminals a, b?



- $L_8$  and  $L_9$  are in parallel

$$\therefore L_{89} = \frac{L_8 L_9}{L_8 + L_9} = 9.6\text{ H}$$

- $L_{589} = L_5$  in series with  $L_{89}$

$$L_{589} = L_5 + L_{89} = 10.4 + 9.6 = 20 \text{ H}$$

- $L_{6589} = L_6$  in parallel with  $L_{589}$

$$L_{6589} = \frac{L_6 L_{589}}{L_6 + L_{589}} = 12 \text{ H}$$

- $L_{76589} = L_7$  in series with  $L_{6589}$

$$L_{76589} = L_7 + L_{6589} = 8 + 12 = 20 \text{ H}$$

- $L_{476589} = L_4$  in parallel with  $L_{76589}$

$$L_{476589} = \frac{L_4 L_{76589}}{L_4 + L_{76589}} = 4 \text{ H}$$

- $L_{3476589} = L_3$  in series with  $L_{476589}$

$$L_{3476589} = L_3 + L_{476589} = 6 + 4 = 10 \text{ H}$$

- $L_{23476589} = L_2$  in parallel with  $L_{3476589}$


$$L_{23476589} = \frac{L_2 L_{3476589}}{L_2 + L_{3476589}} = 6 \text{ H}$$

- $L_{ab} = L_1$  in series with  $L_{23476589}$

$$L_{ab} = L_1 + L_{23476589} = 2 + 6 = 8 \text{ H}$$
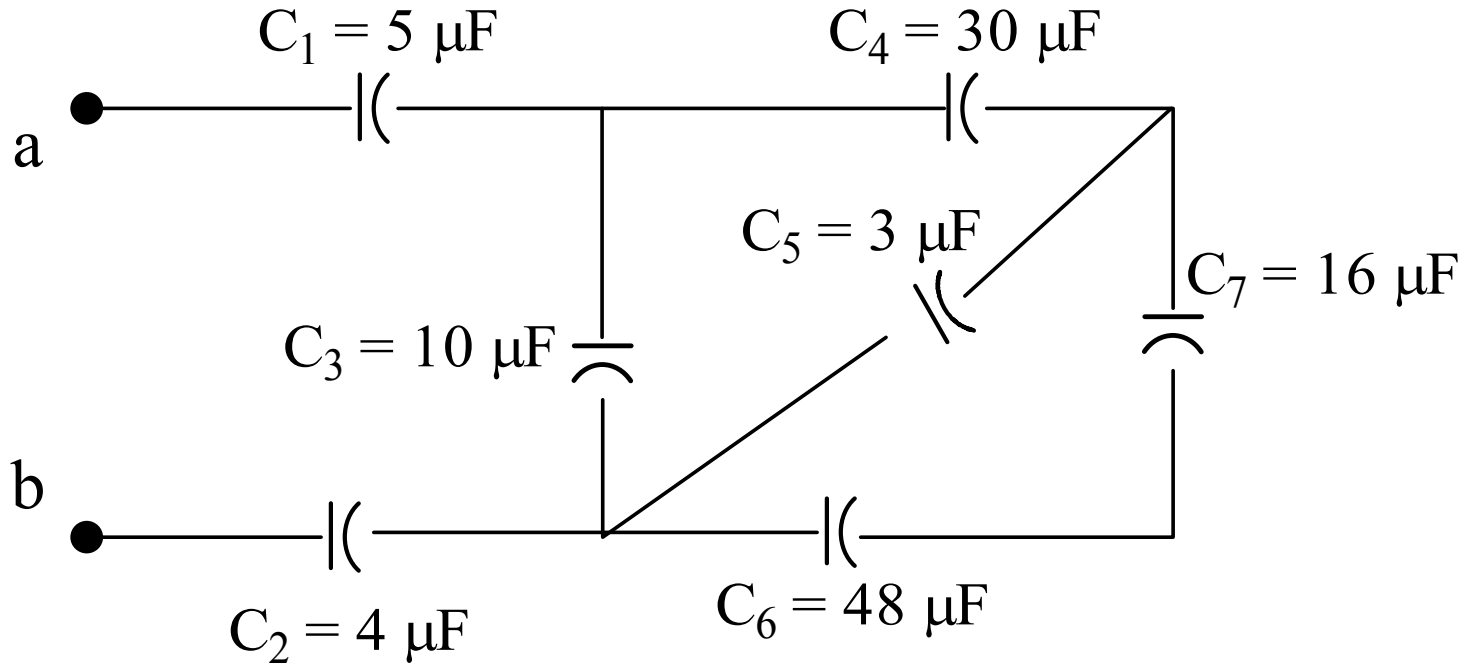
### Example :

Find the equivalent capacitance at the terminals a and b ?



- $C_{67} = C_6$  in series with  $C_7$

$$C_{67} = \frac{C_6 C_7}{C_6 + C_7} = 12 \mu\text{F}$$



- $C_{567} = C_5$  in parallel with  $C_{67}$

$$C_{567} = C_5 + C_{67} = (3 + 12) \mu F = 15 \mu F$$

- $C_{4567} = C_4$  in series with  $C_{567}$

$$C_{4567} = \frac{C_4 C_{567}}{C_4 + C_{567}} = 10 \mu F$$

- $C_{34567} = C_3$  in parallel with  $C_{4567}$

$$C_{34567} = C_3 + C_{4567} = (10 + 10) \mu F = 20 \mu F$$

- $C_{ab} = C_1$  in series with  $C_{34567}$  in series with  $C_2$


$$\frac{1}{C_{ab}} = \frac{1}{C_1} + \frac{1}{C_{34567}} + \frac{1}{C_2} = \frac{1}{5\mu} + \frac{1}{20\mu} + \frac{1}{4\mu}$$

$$\Rightarrow C_{ab} = 2 \mu F$$

## Example :



Find the equivalent inductance at a,b

in all inductors  
are 4 mH

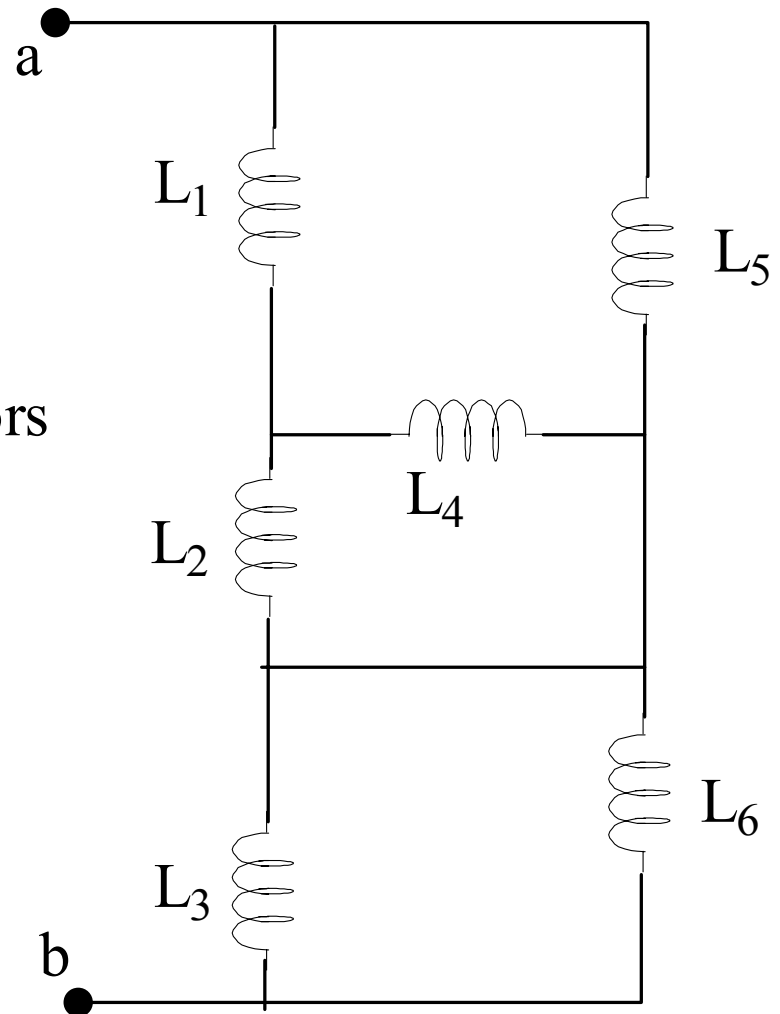

- $L_{36} = L_3$  in parallel with  $L_6$
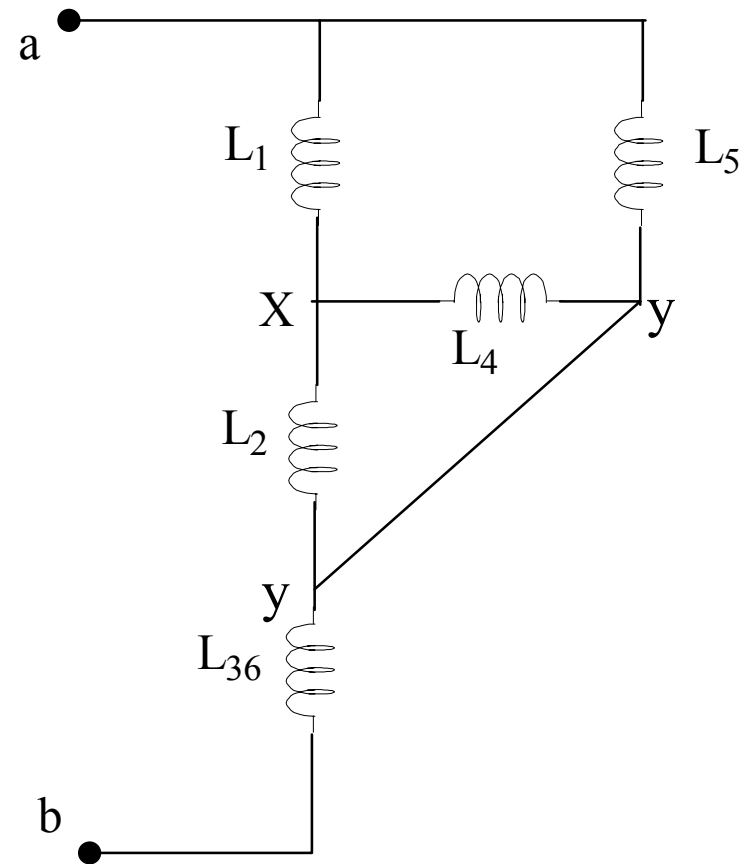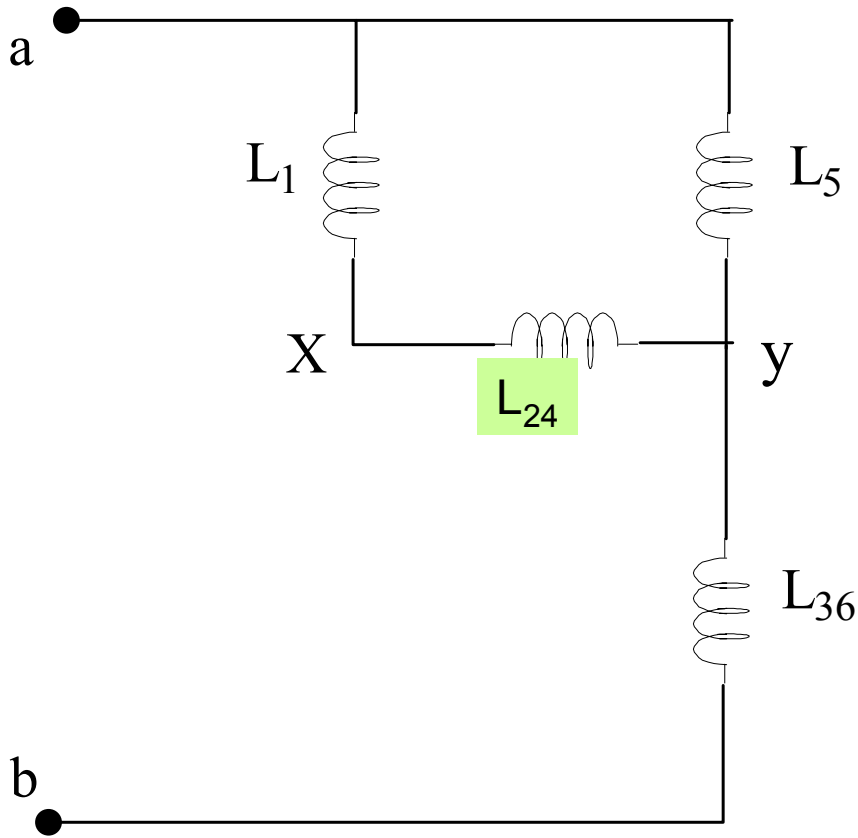
$$L_{36} = \frac{L_3 L_6}{L_3 + L_6} = 2 \text{ m H}$$



- $L_{24} = L_2$  in parallel with  $L_4$

$$L_{24} = \frac{L_2 L_4}{L_2 + L_4} = 2 \text{ m H}$$

- $L_{124} = L_1$  in series with  $L_{24}$

$$L_{124} = L_1 + L_{24} = (4 + 2) \text{ m H} = 6 \text{ m H}$$

- $L_{1245} = L_{124}$  in parallel with  $L_5$

$$L_{1245} = \frac{L_{124} L_5}{L_{124} + L_5} = 2.4 \text{ m H}$$


- $L_{124536} = L_{1245}$  in series with  $L_{36}$

$$L_{124536} = L_{1245} + L_{36} = (2.4 + 2) \text{ m H}$$

$$L_{124536} = 4.4 \text{ m H}$$

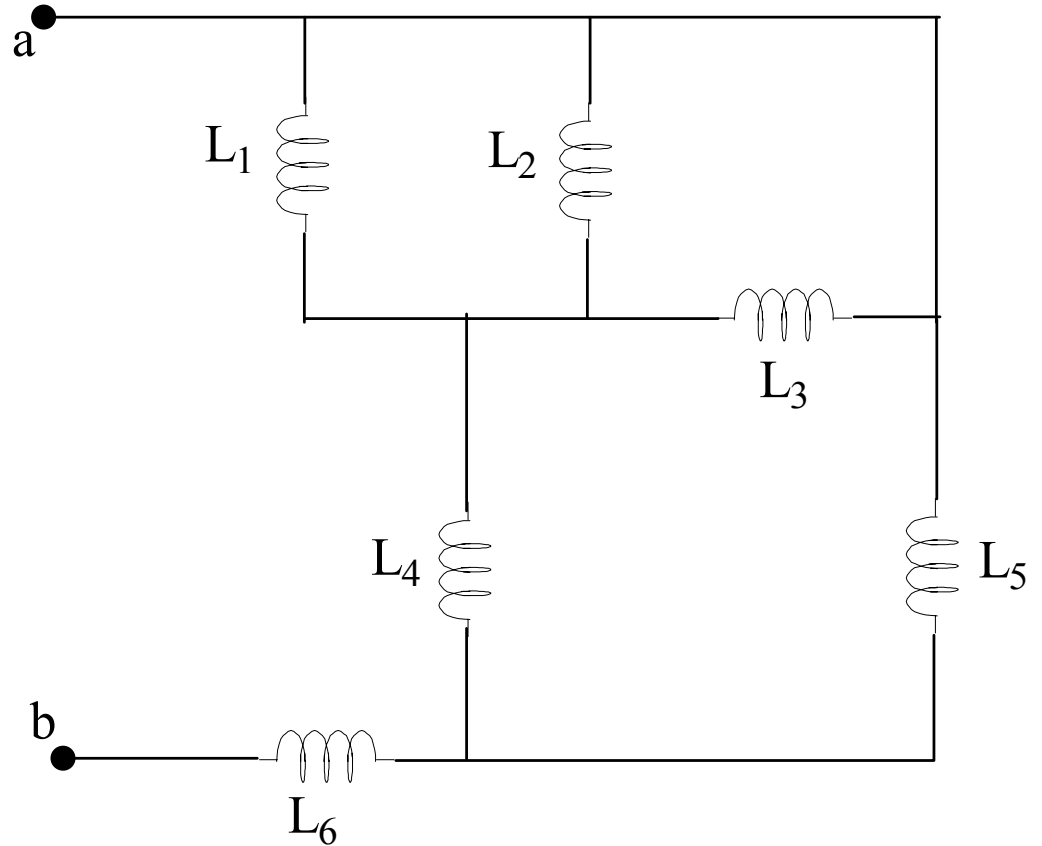
### Example :

Find the equivalent inductance at a , b if all L are 6 m H




$L_{12} = L_1$  in parallel with  $L_2$
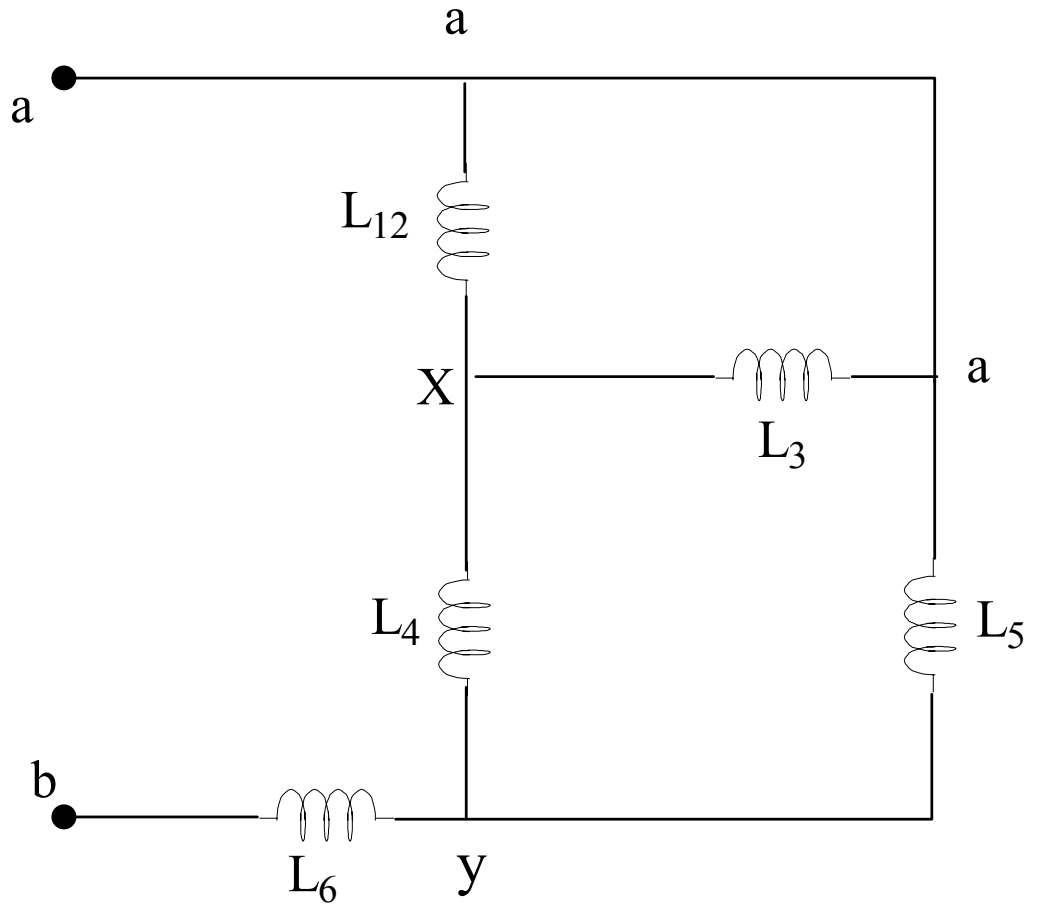
$$L_{12} = \frac{L_1 L_2}{L_1 + L_2} = 3 \text{ m H}$$



$L_{123} = L_{12}$  in parallel with  $L_3$
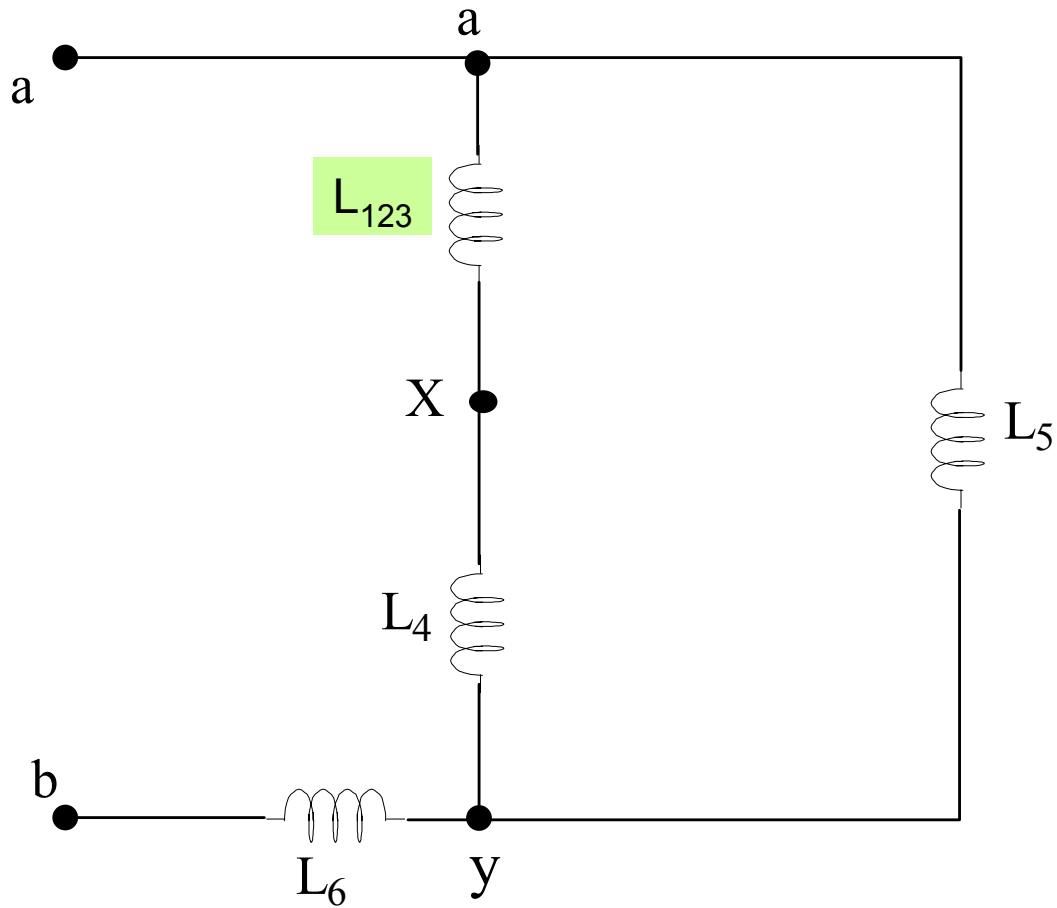
$$L_{123} = \frac{L_{12} L_3}{L_{12} + L_3} = \frac{(3)(6)}{(3) + (6)} \text{ m H} = 2 \text{ m H}$$



$L_{1234} = L_{123}$  in series with  $L_4$

$$L_{1234} = L_{123} + L_4 = 2 + 6 = 8 \text{ m H}$$

$L_{12345} = L_{1234}$  in parallel with  $L_5$

$$L_{12345} = \frac{L_{1234} L_5}{L_{1234} + L_5} = \frac{(8)(6)}{(8) + (6)} \text{ m H} = 3.42 \text{ m H}$$


$L_{ab} = L_6$  in series with  $L_{12345}$

$$\begin{aligned} L_{ab} &= L_6 + L_{12345} \\ &= 6 + 3.429 \text{ m H} = 9.429 \text{ m H} \end{aligned}$$




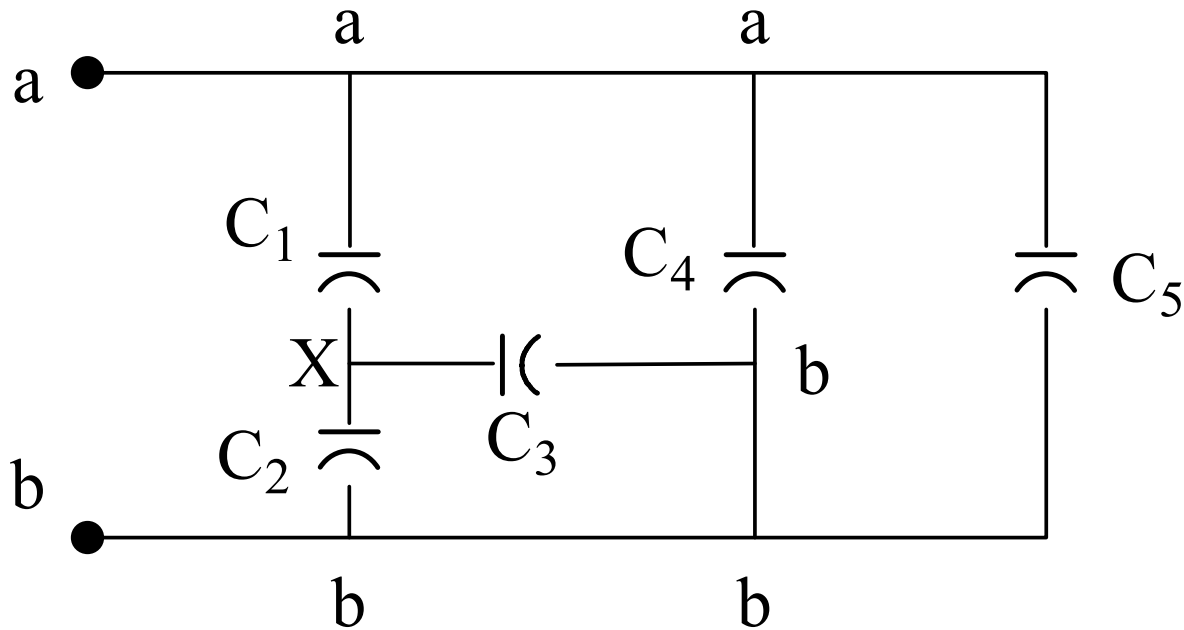**Example:**


Find the equivalent capacitance w.r.t. a, b if all C's are  $4 \mu\text{F}$


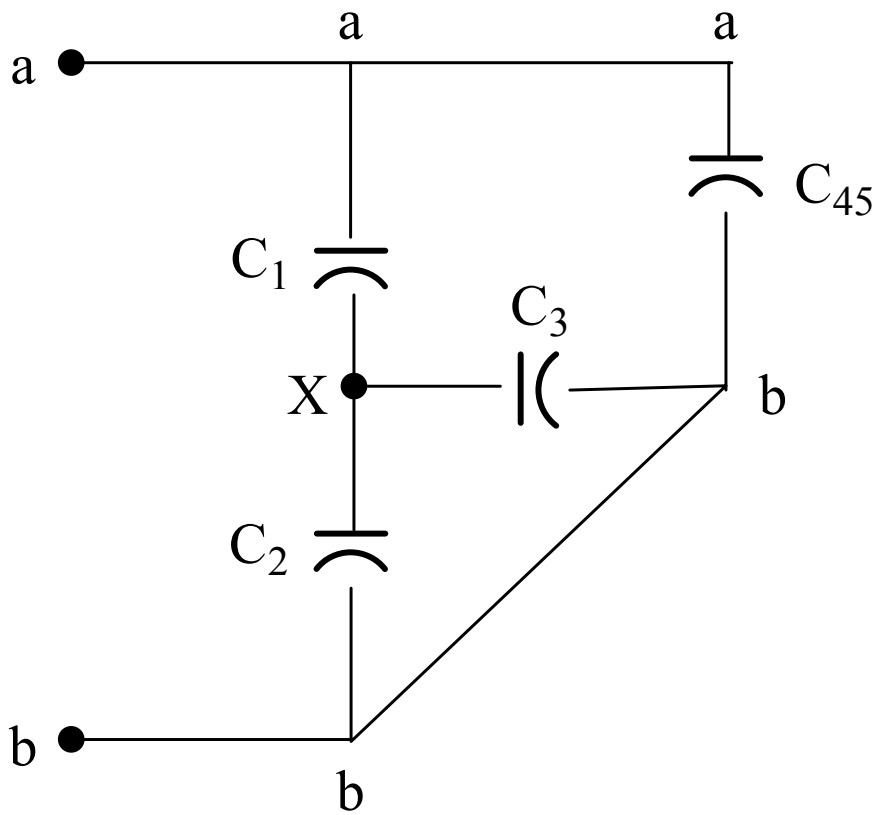
$$\begin{aligned} C_{45} &= C_4 \text{ in parallel with } C_5 \\ &= C_4 + C_5 = 8 \mu\text{F} \end{aligned}$$


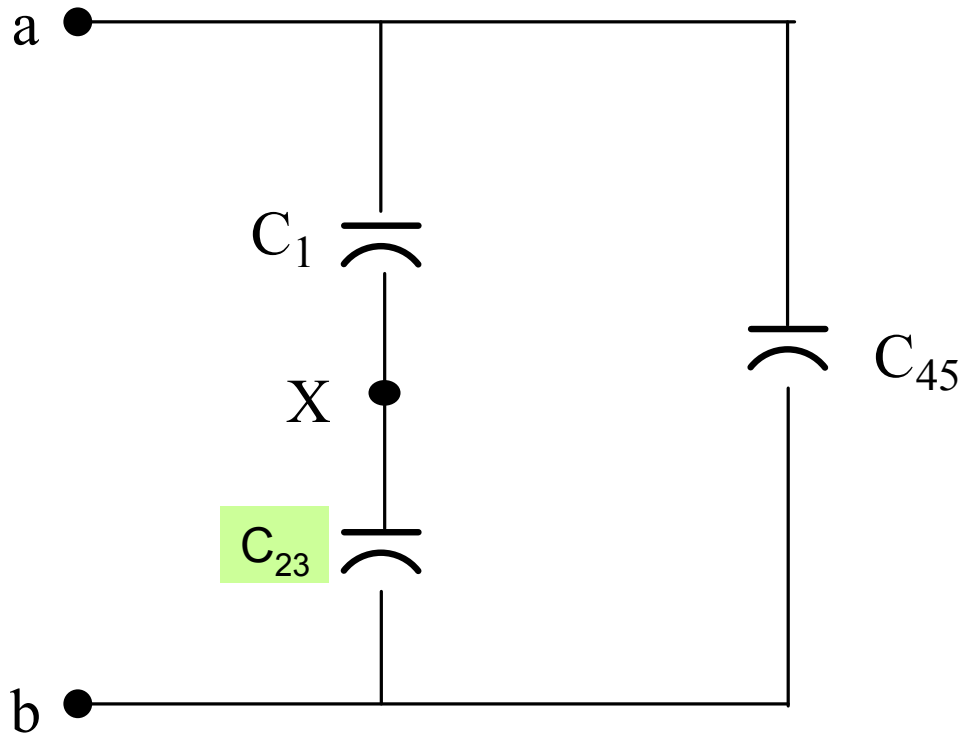
$$\begin{aligned}
 C_{23} &= C_2 \text{ in parallel with } C_3 \\
 &= C_2 + C_3 = 8 \mu F
 \end{aligned}$$



$C_{123} = C_1$  in series with  $C_{23}$


$$C_{123} = \frac{C_1 C_{23}}{C_1 + C_{23}} = \frac{(4)(8)}{4 + 8} \mu\text{F} = \frac{32}{12} \mu\text{F} = \frac{8}{3} \mu\text{F}$$

$C_{ab} = C_{123}$  in parallel with  $C_{45}$

$$\begin{aligned} C_{ab} &= C_{123} + C_{45} = \frac{8}{3} \mu F + 8 \mu F = \frac{8 + 24}{3} \mu F \\ &= \frac{32}{3} \mu F \end{aligned}$$

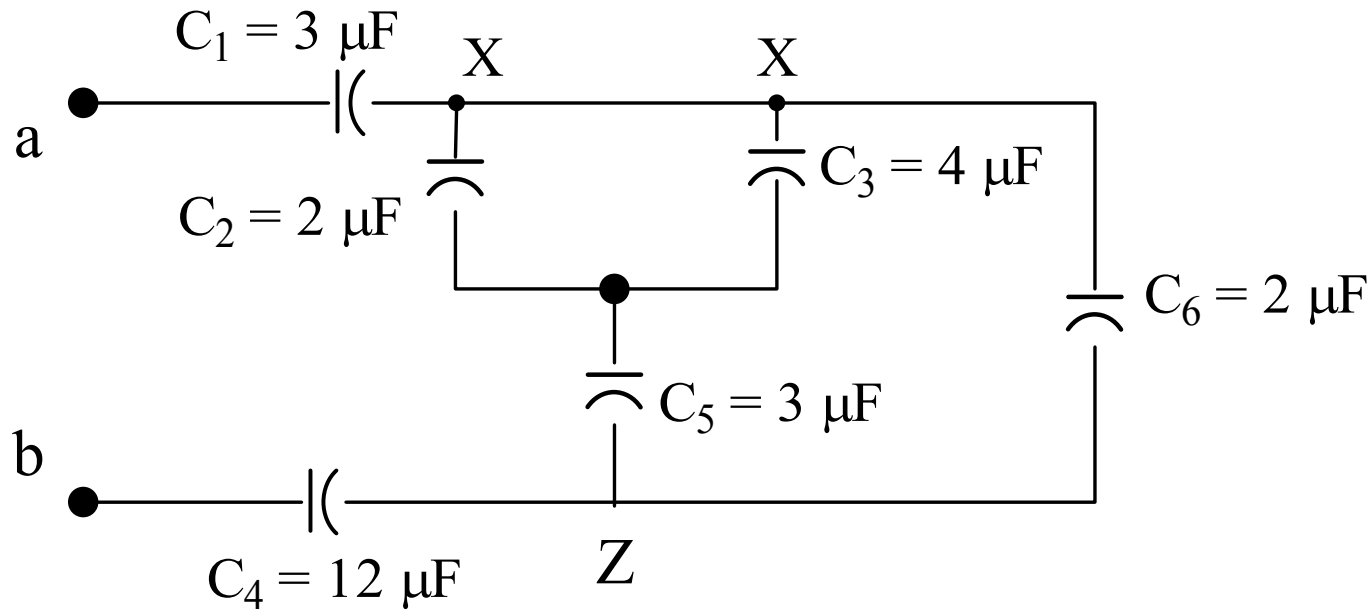**Example :**

Find the equivalent capacitance w.r.t a, b ?



$$\begin{aligned} C_{23} &= C_2 \text{ in parallel with } C_3 \\ &= C_2 + C_3 = 6 \mu\text{F} \end{aligned}$$

$C_{235} = C_{23}$  in series with  $C_5$

$$C_{235} = \frac{C_{23} C_5}{C_{23} + C_5} = \frac{(6)(3)}{6 + 3} \mu F = 2 \mu F$$

$C_{2356} = C_{235}$  in parallel with  $C_6$

$$= C_{235} + C_6 = (2+2) \mu F = 4 \mu F$$

$C_{ab} = C_1$  in series with  $C_{2356}$  in series with  $C_4$

$$\frac{1}{C_{ab}} = \frac{1}{C_1} + \frac{1}{C_{2356}} + \frac{1}{C_4} = \frac{1}{3\mu} + \frac{1}{4\mu} + \frac{1}{12\mu}$$

$$C_{ab} = 1.5 \mu F$$