

Logic Gates:-



Circuits used to process digital signals are called (logic gates).

Logic symbols are used to identify these ccts. The seven gates that are the fundamental logic elements in digital system are shown below:-

Logic Function	Logic gate symbol	Truth table	Boolean Expression												
1- Inverter or NOT		<table border="1"> <tr><td colspan="2">input</td><td>output</td></tr> <tr><td>A</td><td></td><td>F = \bar{A}</td></tr> <tr><td>0</td><td></td><td>1</td></tr> <tr><td>1</td><td></td><td>0</td></tr> </table>	input		output	A		F = \bar{A}	0		1	1		0	$F = \bar{A}$
input		output													
A		F = \bar{A}													
0		1													
1		0													
2- AND		<table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>0</td></tr> <tr><td>01</td><td>0</td></tr> <tr><td>10</td><td>0</td></tr> <tr><td>11</td><td>1</td></tr> </table>	AB	F	00	0	01	0	10	0	11	1	$F = A \cdot B$ <i>(AND is)</i>		
AB	F														
00	0														
01	0														
10	0														
11	1														
3- NAND (AND-NOT)		<table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>1</td></tr> <tr><td>01</td><td>1</td></tr> <tr><td>10</td><td>1</td></tr> <tr><td>11</td><td>0</td></tr> </table>	AB	F	00	1	01	1	10	1	11	0	$F = \overline{A \cdot B}$		
AB	F														
00	1														
01	1														
10	1														
11	0														
4- OR		<table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>0</td></tr> <tr><td>01</td><td>1</td></tr> <tr><td>10</td><td>1</td></tr> <tr><td>11</td><td>1</td></tr> </table>	AB	F	00	0	01	1	10	1	11	1	$F = A + B$ <i>(OR is)</i>		
AB	F														
00	0														
01	1														
10	1														
11	1														
5- NOR (OR-NOT)		<table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>1</td></tr> <tr><td>01</td><td>0</td></tr> <tr><td>10</td><td>0</td></tr> <tr><td>11</td><td>0</td></tr> </table>	AB	F	00	1	01	0	10	0	11	0	$F = \overline{A + B}$		
AB	F														
00	1														
01	0														
10	0														
11	0														
6- Exclusive OR Ex-OR (XOR)		<table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>0</td></tr> <tr><td>01</td><td>1</td></tr> <tr><td>10</td><td>1</td></tr> <tr><td>11</td><td>0</td></tr> </table>	AB	F	00	0	01	1	10	1	11	0	$F = A \oplus B$ $= AB' + A'B$ <i>(Ex-OR is)</i>		
AB	F														
00	0														
01	1														
10	1														
11	0														
7- Exclusive NOR Ex-NOR (Ex-OR-NOT) (XNOR)		<table border="1"> <tr><td>AB</td><td>F</td></tr> <tr><td>00</td><td>1</td></tr> <tr><td>01</td><td>0</td></tr> <tr><td>10</td><td>0</td></tr> <tr><td>11</td><td>1</td></tr> </table>	AB	F	00	1	01	0	10	0	11	1	$F = A \odot B$ $= AB + A'B'$ <i>(Ex-NOR is)</i>		
AB	F														
00	1														
01	0														
10	0														
11	1														







Note:- $A \oplus B = \overline{A \odot B}$
 $A \odot B = \overline{A \oplus B}$

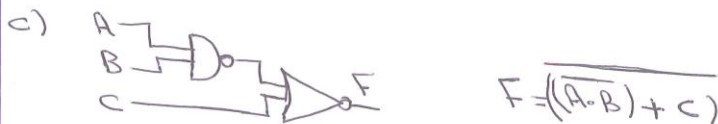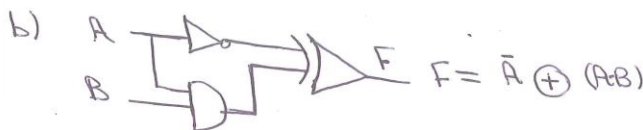Ex:- Write the boolean algebra expression of the following ccts:-



Universal Gates:-

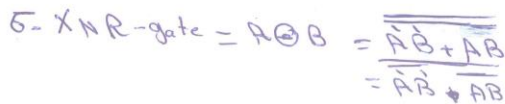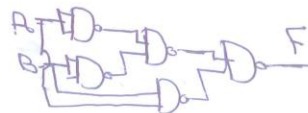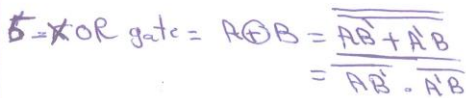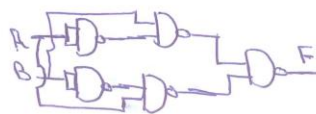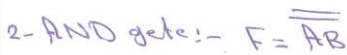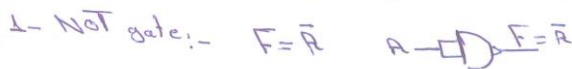NAND and NOR gates have the property that they individually can be used to hardware-implement a logic circuit corresponding to any given Boolean expression. That is, it is possible to use either only NAND gates or only NOR gates to implement any Boolean expression.



Ex: - Implement the following Functions by using NAND gates only:-


a) $F_1 = A\bar{B} + \bar{A}B\bar{C}$

b) $F_2 = AB + C\bar{D}$

Solution:- Mixed gates

a)


$F_1 = A\bar{B} + \bar{A}B\bar{C}$

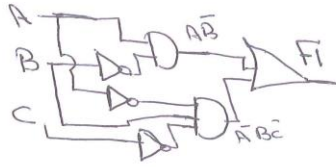

Mixed gates


NAND gates

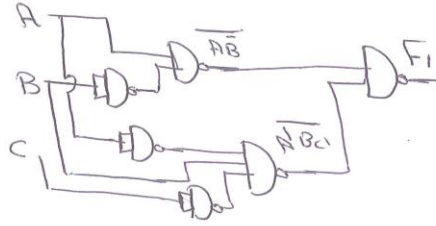$F_1 = \overline{\overline{A\bar{B} + \bar{A}B\bar{C}}}$
 $F_1 = \overline{A\bar{B}} \cdot \overline{\bar{A}B\bar{C}}$




NAND gates

b) $F_2 = AB + C\bar{D}$

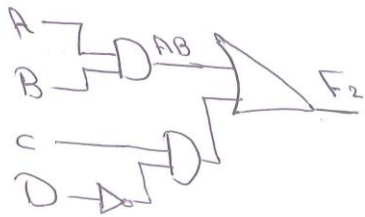

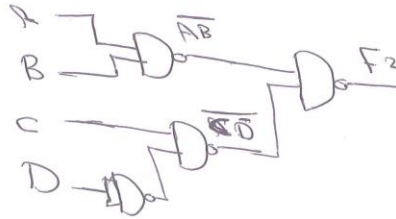$F_2 = \overline{\overline{AB + C\bar{D}}}$
 $F_2 = \overline{AB} \cdot \overline{C\bar{D}}$



1- NOT gate $F_1 = \overline{A}$

2- AND gate $F_2 = \overline{\overline{A} \cdot \overline{B}}$

3- NAND gate $F_3 = \overline{AB} = \overline{A} + \overline{B}$

4- OR gate $F_4 = \overline{\overline{A} \cdot \overline{B}}$

5- EX-OR :- $F_5 = \overline{\overline{A\bar{B} + \bar{A}B}}$
 $= \overline{\overline{A\bar{B}} \cdot \overline{\bar{A}B}}$
 $= \overline{\overline{A} + B} \cdot \overline{A + \overline{B}}$

6- EX-NOR = $\overline{F_5}$




Ex: - Implement following function by using NOR gates only:-

$$F = (A + \bar{B}) \cdot (\bar{A} + c)$$

Solution:-

Mixed gates

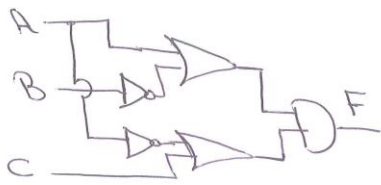
$$F = (A + \bar{B}) \cdot (\bar{A} + c)$$



NOR gates

$$F = \overline{\overline{(A + \bar{B})} \cdot \overline{(\bar{A} + c)}}$$
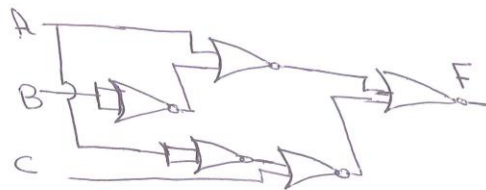
$$F = \overline{(A + \bar{B}) + (\bar{A} + c)}$$



Combinational logic circuits:-

Digital systems are composed of combinations of logic gates described by a truth table and Boolean expression or logic symbol diagram. In combination logic, the output of the circuit depends only on the inputs to the circuit.

- De Morgan's Theorem:-

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$