


Binary Parallel Adder:-

For two numbers of two bits, two adders are needed and for three bits numbers, three adders are needed and so on. The carry of each adder is connected to the carry input of the next higher order adder.


Ex:- The two bit binary parallel adder is shown below.

Solution:- Let $A = A_1 A_0$ (msb to lsb)
 $B = B_1 B_0$ (msb to lsb)
 Result = $S_2 S_1 S_0$
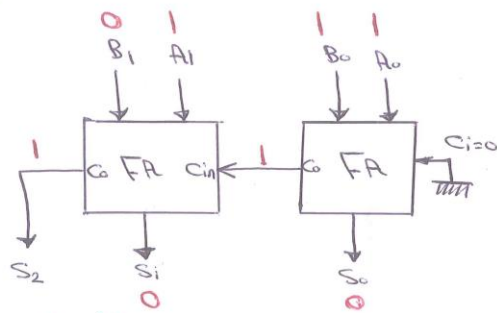
$$\begin{array}{r} \textcircled{1} \\ A = 11 \\ B = 01 \\ \hline 100 \end{array}$$



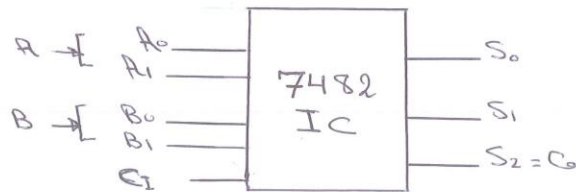Note:- Two bit binary parallel adder 7482 IC



$A_0, B_0 \rightarrow$ (LSB input)


$A_1, B_1 \rightarrow$ (MSB input)

$C_I \rightarrow$ (Carry input to the LSB)

$C_o \rightarrow$ (Carry output to the MSB).


Ex:- The four bit binary parallel adder is shown below:-

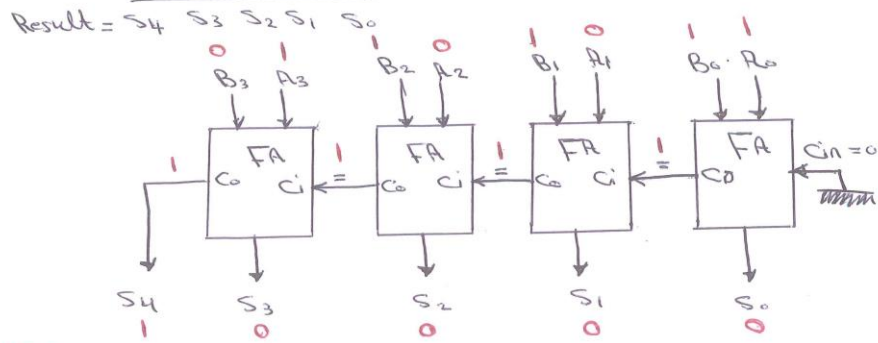Solution:- Let $A = A_3 A_2 A_1 A_0$ (msb to lsb)
 $B = B_3 B_2 B_1 B_0$ (msb to lsb)



$$A = \begin{array}{r} 0001 \\ B = 0111 \\ \hline 1000 \end{array}$$

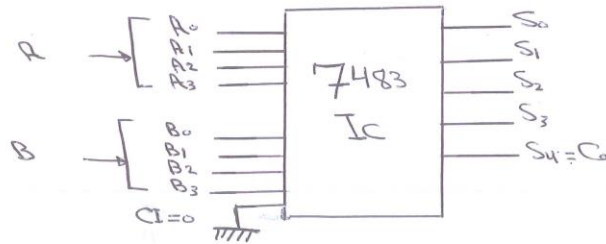Note:- Four bit binary parallel adder 7483 IC




Ex:- Show how you can obtain Four bit adder from IC of 7482 only:-

Solution:-

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

$$S_4 S_3 S_2 S_1 S_0$$

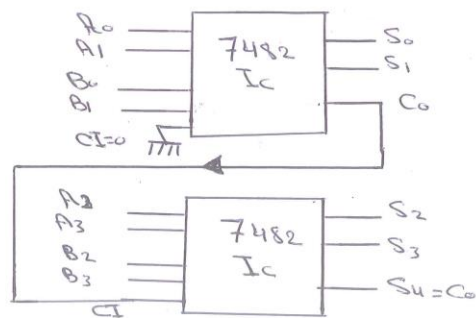

H.W.:- Design 8-bits adder by using block diagram of IC 7483 (4-bit) adder.


H.W.:- Use Full adder block diagram of IC 7483 to convert BCD to Ex-3 code.

Adder/Subtractor:-

Ex:- Design an Adder/subtractor ckt. using FA's and gates:-

Solution:- $A = A_3 A_2 A_1 A_0$

$B = B_3 B_2 B_1 B_0$

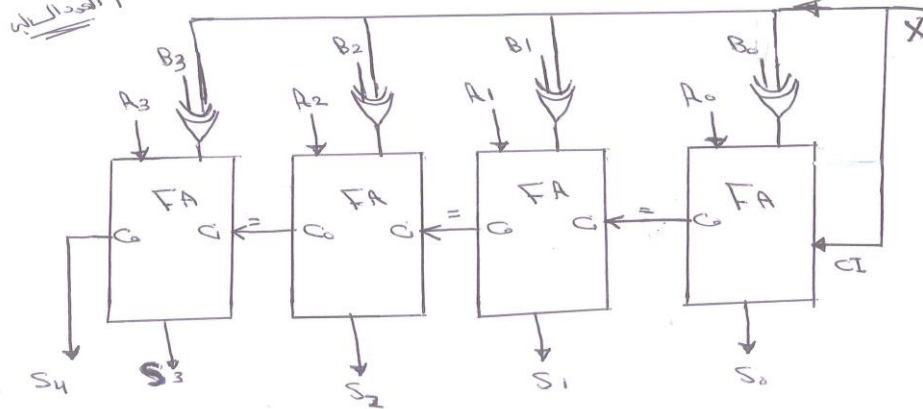


$X=0$ in Adding operation and output result = $S_4 S_3 S_2 S_1 S_0$

$X=1$ in subtraction operation and output result equal $S_3 S_2 S_1 S_0$ and S_4 or C_0 will be (discarded) due to 2's Complement operation.

Ex:- Using an Adder/subtractor ckt. to convert from Ex-3 code to BCD code:-

Solution:- Let $R = A_3 A_2 A_1 A_0$ in Ex-3 code

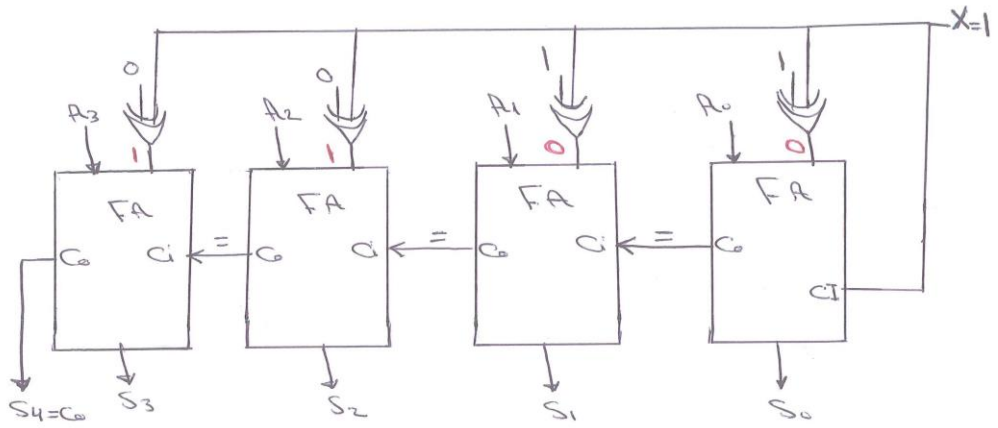Then BCD number = $\begin{matrix} A_3 & A_2 & A_1 & A_0 \\ 0 & 0 & 1 & 1 \end{matrix}$



H.w:- Using an adder/subtractor ckt. to convert from BCD code to Ex-3 code?