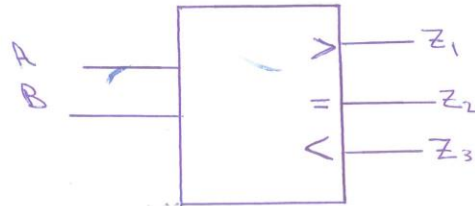


Comparators:-


A magnitude Comparator is a combinational circuit that compares two numbers (A and B), and determines their relative magnitudes. The outputs of the comparison are specified by three binary variables that indicate whether $A=B$ or $A>B$ or $A<B$.

The block diagram for comparator is shown below:-



- For two binary numbers, each one have one bit, the truth table:-

| A | B | Z_1 | Z_2 | Z_3 |
|---|---|-------|-------|-------|
| 0 | 0 | 0 | 1 ✓ | 0 |
| 0 | 1 | 0 | 0 | 1 ✓ |
| 1 | 0 | 1 ✓ | 0 | 0 |
| 1 | 1 | 0 | 1 ✓ | 0 |

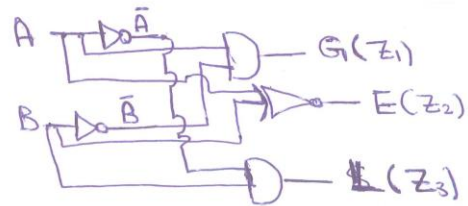

$$Z_1 (A > B) = A\bar{B}$$

$$Z_2 (A = B) = \bar{A}\bar{B} + AB = A \oplus B$$

$$Z_3 (A < B) = \bar{A}B$$

- For two binary numbers, each one have two bits ($n=2$)

msb \downarrow msb \downarrow
 $A = A_1 A_0$, $B = B_1 B_0$

$$\begin{aligned} A > B &= (A_1 > B_1) \text{ or } (A_1 = B_1) \text{ and } (A_0 > B_0) \\ &= (A_1\bar{B}_1) + (A_1 \odot B_1)(A_0 > B_0) \\ &= (A_1\bar{B}_1) + X_1 \cdot A_0\bar{B}_0 \end{aligned}$$

$$\begin{aligned} A < B &= (A_1 < B_1) \text{ or } (A_1 = B_1) \text{ and } (A_0 < B_0) \\ &= \bar{A}_1 B_1 + (A_1 \odot B_1) \cdot (\bar{A}_0 B_0) \\ &= \bar{A}_1 B_1 + X_1 \cdot \bar{A}_0 B_0 \end{aligned}$$


Note: $X_0 = A_0 \odot B_0$
 $X_1 = A_1 \odot B_1$

* للقيمة ذاتها في أعلى
 MSB

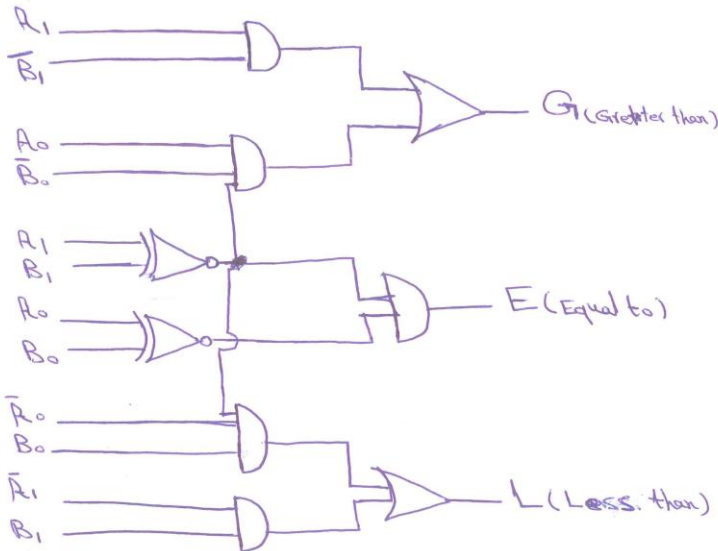(67)

$$\begin{aligned}
 A = B &= (A_1 = B_1) \text{ and } (A_0 = B_0) \\
 &= (A_1 \oplus B_1) \cdot (A_0 \oplus B_0) \\
 &= X_1 X_0
 \end{aligned}$$

From the expression we may obtain the digital Comparator circuit as shown below: -



Digital Comparator Circuit for 2-bits

- For two binary numbers, each one have 4-bits ($n=4$).

$$A = A_3 A_2 A_1 A_0, B = B_3 B_2 B_1 B_0$$

Note: $X_0 = A_0 \oplus B_0$
 $X_1 = A_1 \oplus B_1$
 $X_2 = A_2 \oplus B_2$
 $X_3 = A_3 \oplus B_3$

$$\begin{aligned}
 A > B (G) &= A_3 > B_3 \text{ or } A_3 = B_3 \text{ and } A_2 > B_2 \text{ or } A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 > B_1 \text{ or } \\
 &A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 = B_1 \text{ and } A_0 > B_0
 \end{aligned}$$

$$\begin{aligned}
 &= A_3 \bar{B}_3 + (A_3 \oplus B_3) A_2 \bar{B}_2 + (A_3 \oplus B_3) (A_2 \oplus B_2) A_1 \bar{B}_1 + \\
 &(A_3 \oplus B_3) (A_2 \oplus B_2) (A_1 \oplus B_1) (A_0 \bar{B}_0) \\
 &= A_3 \bar{B}_3 + X_3 A_2 \bar{B}_2 + X_3 X_2 A_1 \bar{B}_1 + X_3 X_2 X_1 A_0 \bar{B}_0
 \end{aligned}$$

$$\begin{aligned}
 A < B (L) &= A_3 < B_3 \text{ or } A_3 = B_3 \text{ and } A_2 < B_2 \text{ or } A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 < B_1 \text{ or } \\
 &A_3 = B_3 \text{ and } A_2 = B_2 \text{ and } A_1 = B_1 \text{ and } A_0 < B_0
 \end{aligned}$$

$$\begin{aligned}
 &= \bar{A}_3 B_3 + (A_3 \odot B_3)(\bar{A}_2 B_2) + (A_3 \odot B_3)(A_2 \odot B_2) \bar{A}_1 B_1 + \textcircled{88} \\
 &\quad (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)(\bar{A}_0 B_0) \\
 &= \bar{A}_3 B_3 + X_3 \bar{A}_2 B_2 + X_3 X_2 \bar{A}_1 B_1 + X_3 X_2 X_1 \bar{A}_0 B_0
 \end{aligned}$$

$$\begin{aligned}
 A = B (E) &= (A_3 = B_3) \text{ and } (A_2 = B_2) \text{ and } (A_1 = B_1) \text{ and } (A_0 = B_0) \\
 &= (A_3 \odot B_3)(A_2 \odot B_2)(A_1 \odot B_1)(A_0 \odot B_0) \\
 &= X_3 X_2 X_1 X_0
 \end{aligned}$$

Ex: - Implement a comparator of two binary numbers each one have four bits, Let $A = 0101$ and $B = 1101$

Solution:- $A = A_3 A_2 A_1 A_0$
 $B = B_3 B_2 B_1 B_0$

by substitute the values of A and B in the previous equations:-

$$G = 0 + 0 + 0 + 0 = 0$$

$$L = 1 + 0 + 0 + 0 = 1 \quad \therefore A < B$$


$$E = 0 \times 1 \times 1 \times 1 = 0$$

H.w:- For each of the binary numbers, determine the output states for the comparator:-

A) $A_3 A_2 A_1 A_0 = 1100$
 $B_3 B_2 B_1 B_0 = 1001$

B) $A_3 A_2 A_1 A_0 = 0100$
 $B_3 B_2 B_1 B_0 = 0100$

7485 IC:-

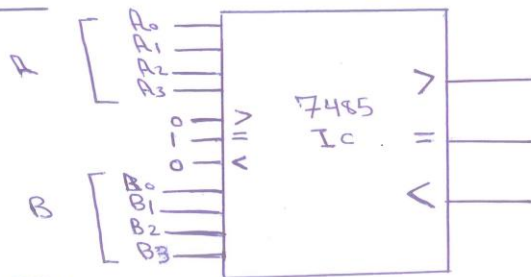


Two binary numbers of four bits comparator 7485 Ic

Ex:- Use 7485 Ic to compare two binary numbers each one have

eight bits:- $A = A_7 A_6 A_5 A_4 A_3 A_2 A_1 A_0$
 $B = B_7 B_6 B_5 B_4 B_3 B_2 B_1 B_0$

Solution:-

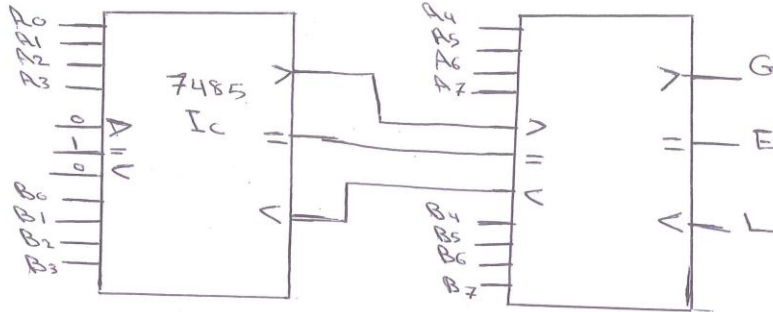

Ex:- Design H.A. using Comparators only:-

Solution:- HA

$$S = AB + \bar{A}\bar{B} = A \oplus B$$

→ 2, 6, 6
→ 2, 6, 6

$$C_0 = AB$$

Note:-
 $AO1 = A$
 $AO0 = \bar{A}$


Comparator

$$A > B (G) = A\bar{B}$$

$$A = B (E) = AB + \bar{A}\bar{B} = A \odot B$$

$$A < B (L) = \bar{A}B$$

→ 2, 6, 6
→ 2, 6, 6

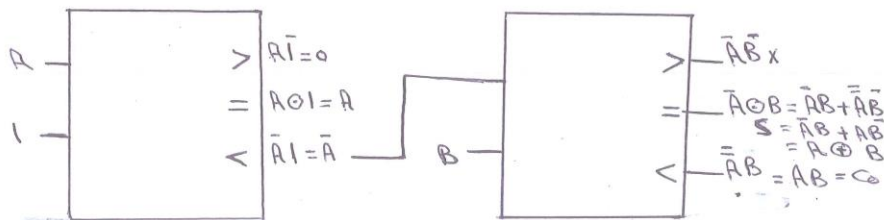

H.w:- Design F.A. using Comparators only.

H.w:- Design H.A by using Comparators and any gate.

H.w:- Design F.A by using Comparator and one gate.

H.w:- Verify all logic gates using Comparator only.

AND, NOR, OR, EX-OR, EX-NOR, NAND, NOT.