

# Contents

Contents	1
The pn Junction	3
Zero applied bias	5
Electric Field	7
Space charge width	8
Problems	10
pn junction current	11
Depletion Width and Electric Field	17
Junction Capacitance	18
Problems	20
Metal-Semiconductor Contact	21
Metal-semiconductor rectifying contact (Schottky barrier diode)	21
Forward and reverse bias	24
Current vs. Voltage Relation	26
Metal-semiconductor ohmic contact	27
Heterojunctions	28
Problems	29
Metal-Oxide-Semiconductor The two-terminal MOS structure	30
Diode Characteristics	40
Resistance level of the diode	40
AC (Dynamic Resistance)	41
Diode equivalent circuit	44
Approximate equivalent model	45
Series Diode Configurations with DC Inputs	46
Parallel and Series-Parallel Diode Configurations	51
Problems	54
Diode Circuit Applications	57
Half wave rectifier	57
PIV	61
Full-wave rectifier	61
Bridge rectifier	61

PIV	63
Center tapped transformer (CT)	64
PIV	65
Problems	67
Clippers	69
Series clipper	69
Clippers with square wave	74
Parallel:	75
Problems	79
Clampers	80
Reverse Bias Operation. Zener Diode	87
Zener Diodes	87
Optical Devices	98
Solar Cells	100
Photodetector	101
Luminescence	103
Luminescence Mechanism	103
Light Emitting Diode (LED)	105
Laser diode	105
The Tunnel Diode	106
Degenerate and Nondegenerate Semiconductors	106
The Tunnel Diode	106
Varactor Diode	108
Problems	109