

Clampers

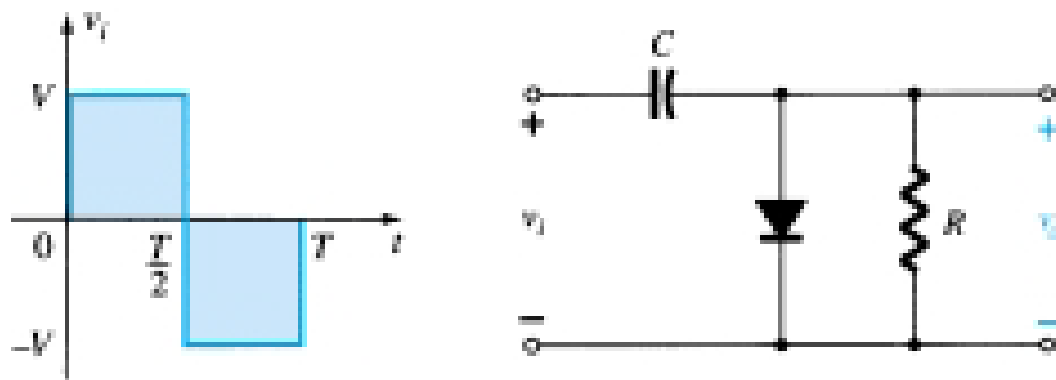


Fig. 12.1 Clamper.

The clamping network is one that will clamp a signal to a different dc level. It must have a capacitor a diode and resistance but it can also employ dc supply to introduce additional shift.

The magnitude of R and C must be chosen because the time constant τ ,

$$\tau = RC$$

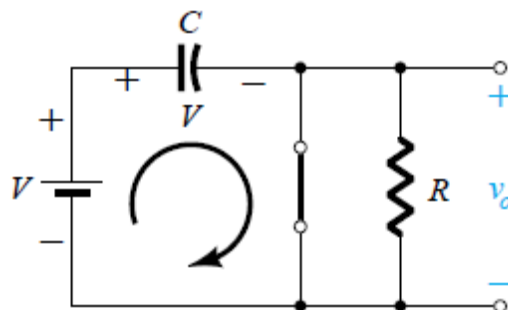


Fig. 12.2 not Diode "on" and the capacitor charging to V volts.

And the capacitor will fully charge or discharge in 5τ , τ must be large enough to ensure that the voltage across capacitor does not discharge significantly during the interval the diode is off.

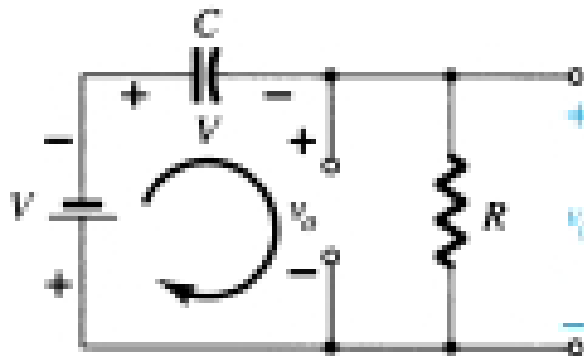


Fig.12.3 Determining v_o with the diode "off."

During the positive half cycle the network will appear as shown with the diode in on state, τ is very small that the capacitor will charge very quickly $v_o=0$.

During the negative half cycle the network will appear as shown, diode off, τ is large, the capacitor holds during the period

$$-V - V - v_o = 0$$

$$v_o = -2V$$

The following steps may be helpful to analysis clampers.

- Start analysis by the part of input signal that will forward bias the diode
- During the period assume that the capacitor will charge to voltage level determined by the network (v_c , v_o)
- Assume that during the diode **OFF** the capacitor will hold to its established voltage level.
- Keep in mind the general rule that the total swing of the output must match the swing of input signal.

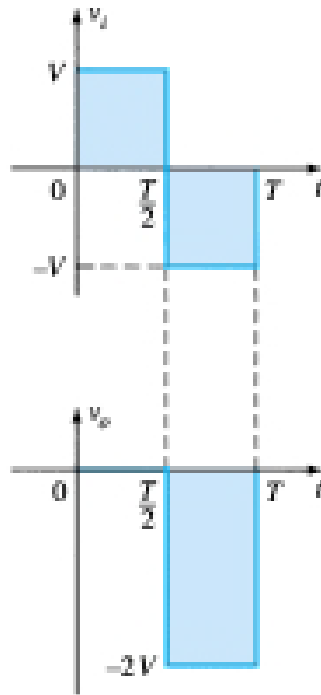
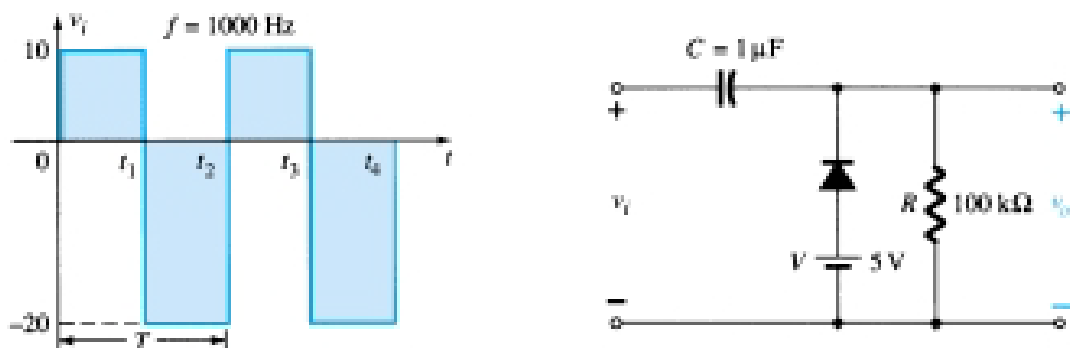
Fig. 12.4 Sketching v_o **Example**Determine v_o 

Fig 12.5 Applied signal and network for Example 12.1.

Solution

$$T = \frac{1}{f} = \frac{1}{1000} = 10^{-3} \text{ s} \quad \text{Half time-period} = \frac{T}{2} = 0.5 \times 10^{-3} \text{ s}$$

-Begin with forward bias, 2nd half Period, the network will appear as shown

$$v_o = 5V$$

$$20 + 5 - v_C = 0$$

$$v_C = 25V$$

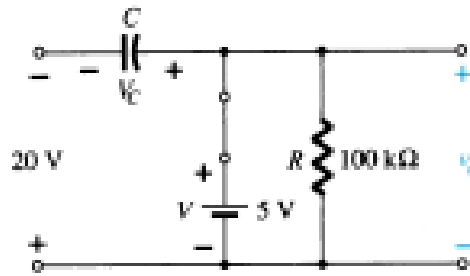


Fig 12.6 Determining v_o and v_C with the diode in the "on" state.

-During the positive half cycle Diode reverse bias

$$10 + 25 - v_o = 0$$

$$v_o = 35V$$

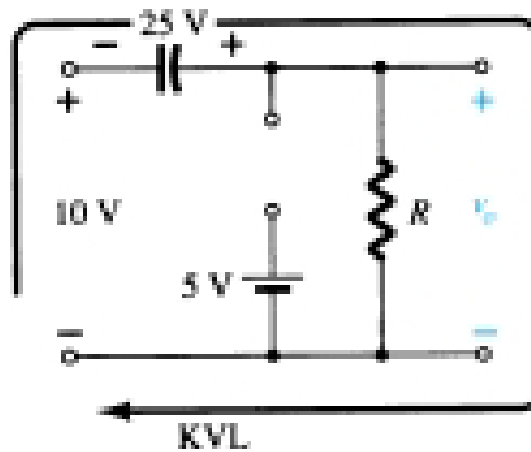


Fig 12.7 Determining v_o with the diode in the "off" state

The output swing of 30V match the swing of input signal.

Time constant of the discharge network

$$\tau = RC = (100k)(0.1\mu) = 0.01s = 10ms$$

The total discharge times

$$5\tau = 50ms$$

Half time-period = $T/2 = 0.5 \times 10^{-3}s$

It's a good approximation that the capacitor will hold its voltage during the discharge period.

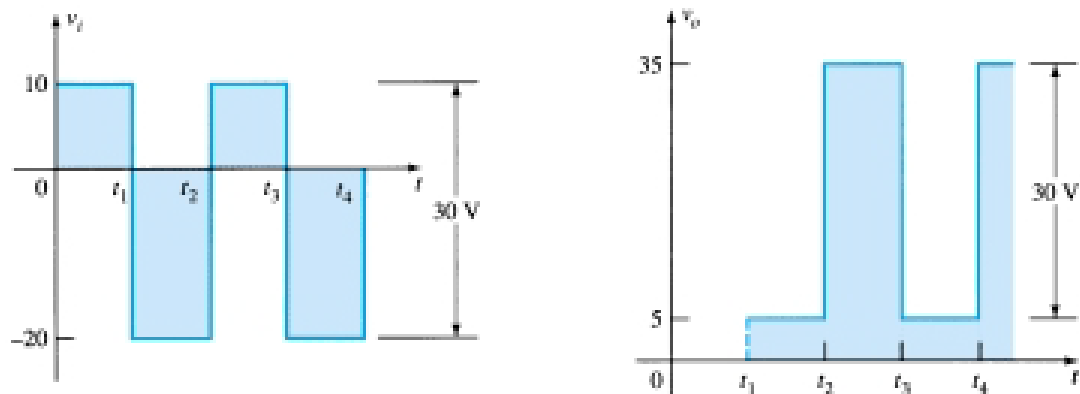


Fig 12.8 v_i and v_o for the clamper

Example

Repeat example using a silicon diode

Solution

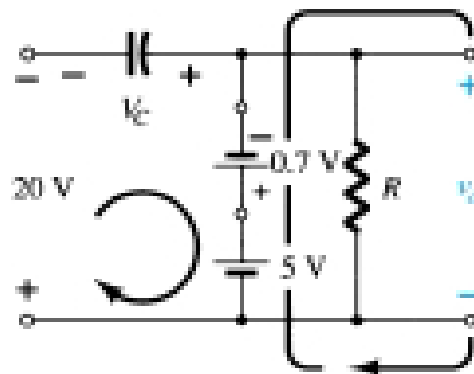


Fig 12.9 Determining v_o and V_C with the diode in the "on" state.

For short circuit state

$$5 - 0.7 - v_o = 0$$

$$v_o = 4.3V$$

for input section

$$-20 - v_C + 0.7 - 5 = 0 \quad v_C = 24.3V$$

-For open circuit state Diode reverse bias

$$10 - 24.3 - v_o = 0 \qquad v_o = 34.3V$$

The output swing of 30V match the swing of input signal.

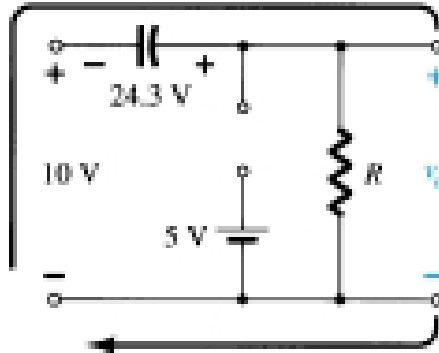


Fig 12.10 Determining v_o with the diode in the “off” state.

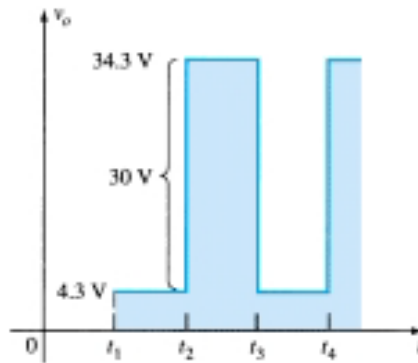


Fig 12.11 v_o for the clamper

Note: -

For sinusoidal signal one approach to the analysis of clamping networks is to replace the sinusoidal signal by a square wave of the same peak value.


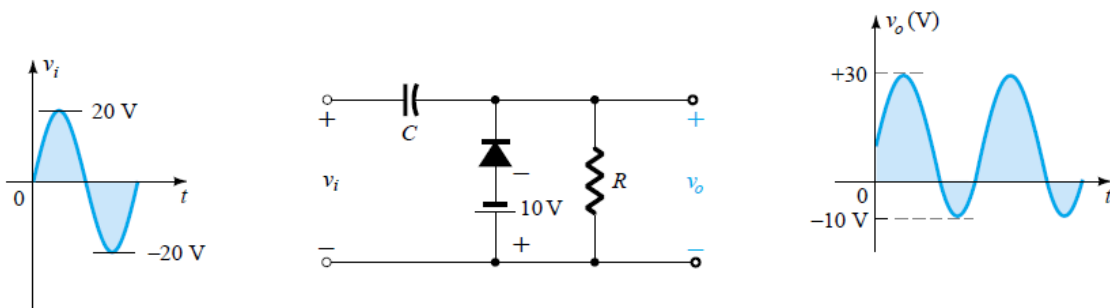



Fig 12.12 Clamping network with a sinusoidal input.

Problems

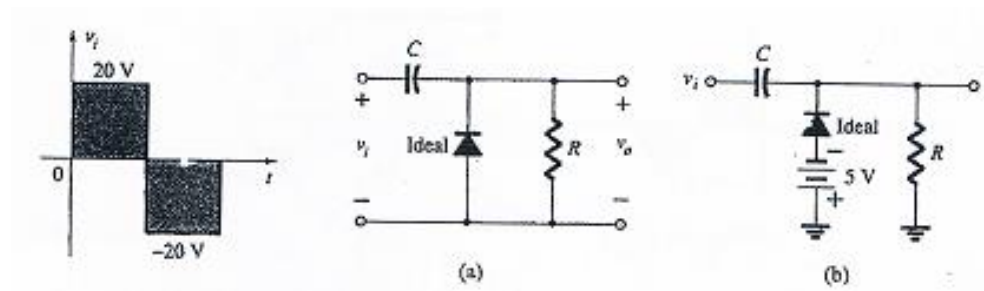Q1: Sketch and determine v_o for configurations shown.



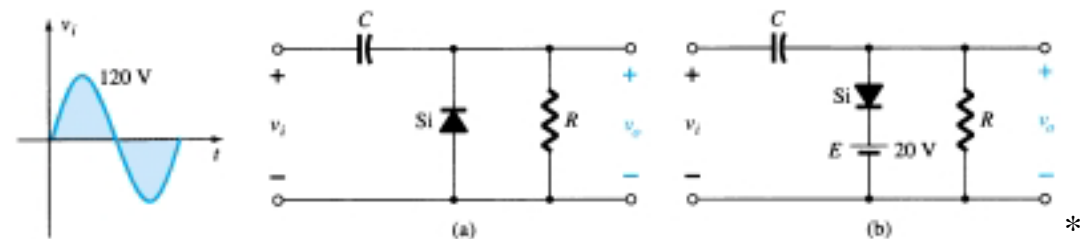Q2: Sketch v_o for each network of Figure for the input shown. Would it be a good approximation to consider the diode to be ideal for both configurations? Why?



Q3. For the network of Figure:

- (a) Calculate τ .
- (b) Compare τ to half the period of the applied signal.
- (c) Sketch v_o .

