



*Digital Techniques II*

**Q1)** Design a synchronous counter by means of T flip-flops and any necessary logic gates to count the sequence (0, 1, 2, 4, 5, 6). Assuming the counter has the property of self-starting, self-stopping and self-correcting to the initial state.

(5 marks)

**Q2)** For a special X-Y Flip Flop of the following characteristic table; X and Y are inputs and  $Q_n$  is the present state.

X	Y	$Q_n$	$Q_{n+1}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

1. Derive the excitation table of this flip flop.
2. Design a synchronous counter which counts the repeated sequence: {0, 1, 3}; using X-Y flip flops.

(5 marks)

**Q3)** Answer (A) or (B):

(A) Design a BCD ripple counter using J-K flip-flops of asynchronous clear and pre-set and any necessary logic gates.

(B) Explain briefly the main differences between synchronous and asynchronous counters. Give an example for each type.


(5 marks)

حل مسألة امتحان نظرية المنطق الرقمي  
المرحلة الثانية.

Q1:- 0 → 1 → 2 → 4 → 5 → 6

Self correction xxx → 000

Self stopping 110 → 110

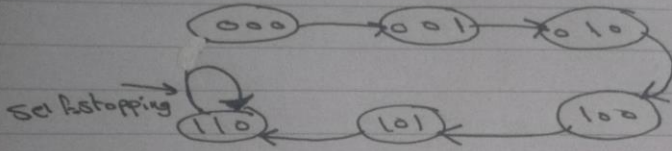

State diagram

Present state			Next state			Tc	Tb	Ta
Cn	Bn	An	Cn+1	Bn+1	An+1			
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	1	0	0	1	1	0
0	1	1	0	0	0	0	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	0	0	0	0
1	1	1	1	1	1	1	1	1

State table

A/B	CB	C $\bar{B}$	CB	C $\bar{B}$
$\bar{A}$	0	1	0	0
A	0	0	1	0

A/B	C $\bar{B}$	CB	CB	C $\bar{B}$
$\bar{A}$	0	1	0	0
A	1	1	1	1


  

A/B	C $\bar{B}$	CB	CB	C $\bar{B}$
$\bar{A}$	1	0	0	1
A	1	1	1	1

$$T_c = (\bar{A}B\bar{C} + ABC) = B(A\bar{C})$$

$$T_b = (B\bar{C} + A)$$

$$T_a = (A + \bar{B})$$

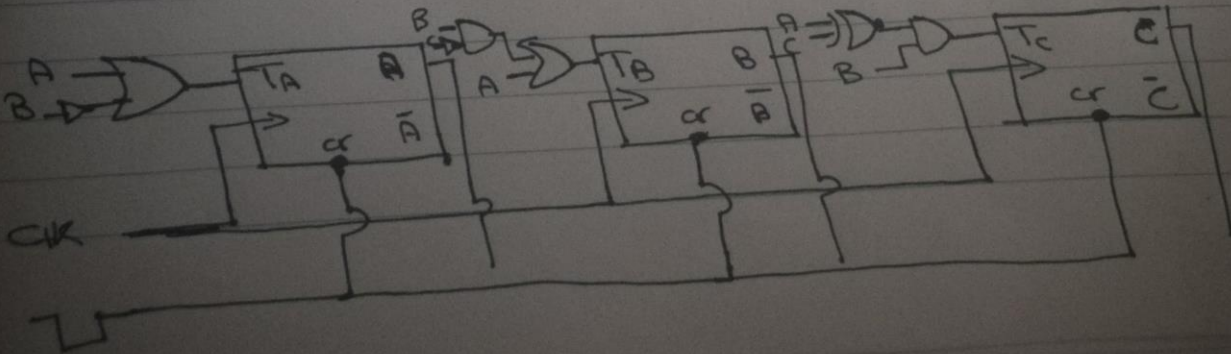


Q2:-

$Q_n$	$Q_{n+1}$	X	Y
0	0	1	X
0	1	0	X
1	0	X	1
1	1	X	0

① Excitation table

②

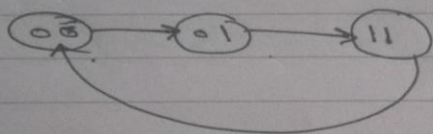

State diagram

Present state		Next state		$X_B$	$Y_B$	$X_A$	$Y_A$
$B_n$	$A_n$	$B_{n+1}$	$A_{n+1}$				
0	0	0	1	1	X	0	X
0	1	1	1	0	X	X	0
1	0	X	X	X	X	X	X
1	1	0	0	X	1	X	1

A/B	$\bar{B}$	B
$\bar{A}$	1	X
A	0	X

$X_B = \bar{A}$

A/B	$\bar{B}$	B
$\bar{A}$	X	X
A	X	1


$Y_B = 1$

A/B	$\bar{B}$	B
$\bar{A}$	0	X
A	X	X

$X_A = 0$


A/B	$\bar{B}$	B
$\bar{A}$	X	X
A	0	1

$Y_A = B$

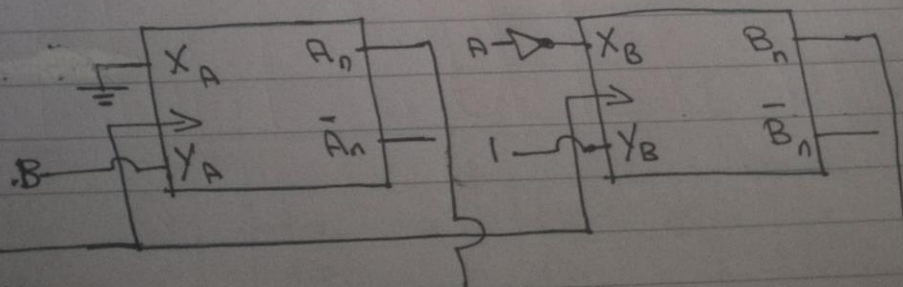

CIK

Q3A:- BCD ripple counter (mod 10)

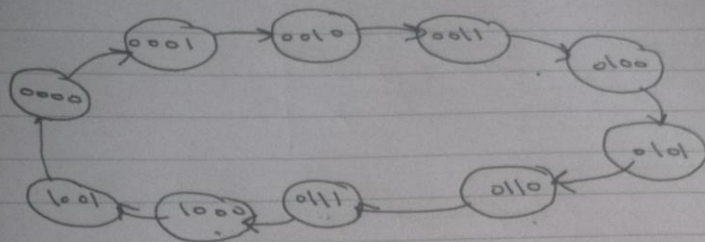


10, 11, 12, 13, 14, 15


$\frac{B}{A} \backslash \frac{D}{C}$	$\bar{D}\bar{C}$	$\bar{D}C$	$DC$	$D\bar{C}$
$\bar{B}\bar{A}$	0	1	1	0
$\bar{B}A$	1	0	0	1
$B\bar{A}$	0	1	0	1
$BA$	1	0	1	0

$$F = DC + DB$$

$$F = \bar{D}\bar{C} \cdot DB$$


CLK	States
	$D_n C_n B_n A_n$
Initially	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1

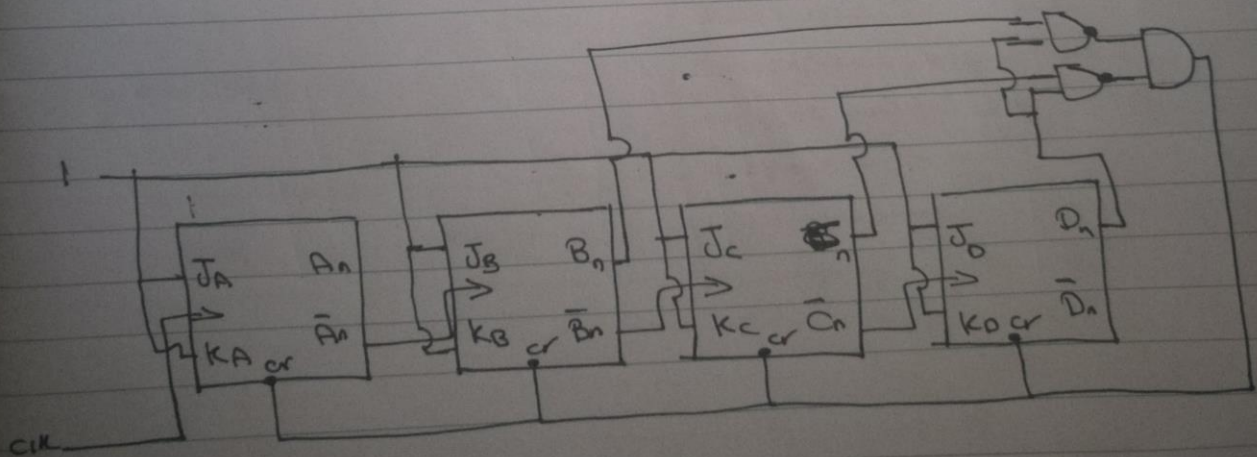

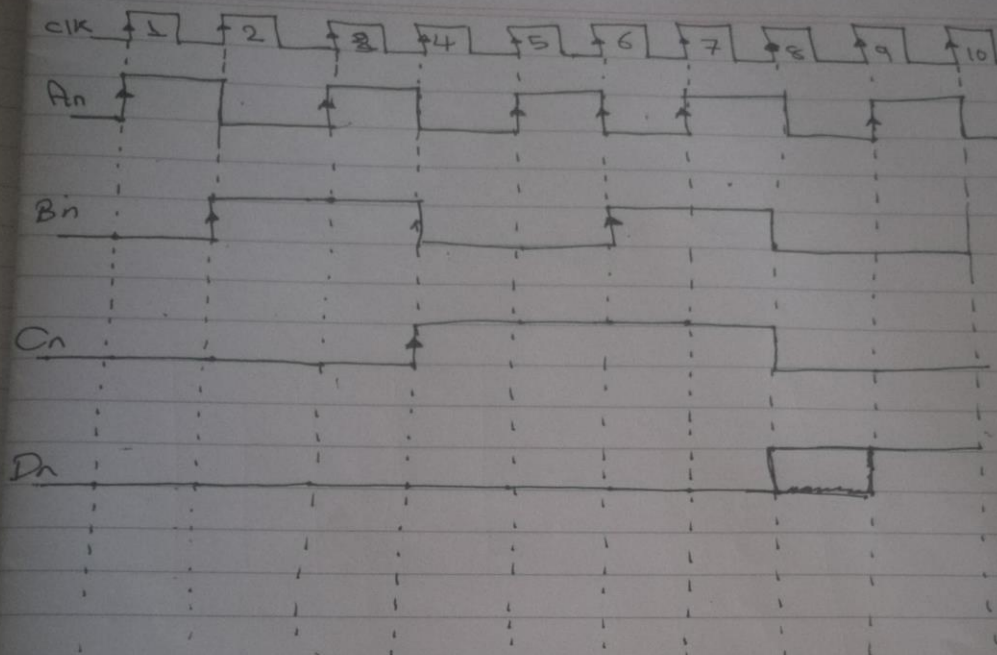

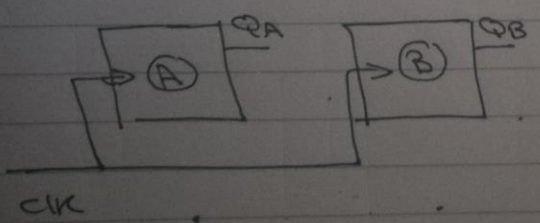Q3B/ Synchron. Counter

The clock input is connected to all of the Flip-Flops; so that they are clocked simultaneously



Asynch. Counter

The first Flip-Flop is clocked by external clock pulse and then each successive Flip-Flop is clocked by the output of the preceding Flip-Flop.

