

Chapter One

Per unit System

The solution of an interconnected power system having several different voltage levels requires the cumbersome transformation of all impedance to a single voltage level. However, power system engineers have devised the per-unit system such that the various physical quantities such as power, voltage, current and impedance are expressed as a decimal fraction or multiples of base quantities.

In this system, the different voltage levels disappear, and a power network involving generators, transformers, and lines (of different voltage levels) reduces a system of simple impedance. The per unit value of any quantity is defined as

$$\text{Quantity in per unit} = \frac{\text{actual quantity}}{\text{base value quantity}} \quad \text{--- (1)}$$

$$\text{For example: } S_{pu} = \frac{S}{S_B} \quad ; \quad V_{pu} = \frac{V}{V_B}$$

$$I_{pu} = \frac{I}{I_B} \quad ; \quad Z_{pu} = \frac{Z}{Z_B}$$

where S_{pu} : per unit apparent power

S : actual apparent power

S_B : Base " "

V_{pu} : per unit voltage

V : actual voltage

V_B : Base voltage

I_{pu} : per unit current

I : actual current

I_B : Base current

Z_{pu} : per unit impedance

Z : actual impedance

Z_B : Base impedance

where the numerator (actual values) are phasor quantities or complex values and the denominators (base values) are always real number.

A minimum of four base quantities are required to completely define a per unit system: volt-ampere, voltage, current and impedance.

Usually, the 3- ϕ base volt-ampere S_B or MVA_B and the line-to-line base voltage V_B or kV_B are selected.

(1-3)

Base current and base impedance are then dependent on S_B and V_B and must obey the circuit law.

These are given by:

$$I_B = \frac{S_B}{\sqrt{3} V_{B \text{ Line}}}$$

$$Z_B = \frac{V_B / \sqrt{3}}{I_B} \Rightarrow Z_B = \frac{V_B / \sqrt{3}}{\frac{S_B}{\sqrt{3} V_B}}$$

$$Z_B = \frac{V_B^2}{S_B} = \frac{kV_B^2}{MVA_B}$$

Then $S_{pu} = V_{pu} I_{pu}^*$

$$V_{pu} = Z_{pu} I_{pu}$$

The complex Load power $S_{L(3\phi)}$ can be defined as

$$S_{L(3\phi)} = 3 V_P I_P^*$$

(Load)

I_P : Load current per phase
 V_P : Load voltage per phase

$$I_P = \frac{V_P}{Z_P}$$

(per phase)

$$Z_P = \frac{V_P}{I_P} = \frac{V_P}{\left(\frac{S_{L(3\phi)}}{3 V_P} \right)^*}$$

$S_{L(3\phi)}$: 3 ϕ Load apparent power

Impedance are calculate per phase

(1-4)

$$Z_P = \frac{V_P}{\frac{S_L(3\phi)^*}{3V_P^*}} = \frac{3V_P^* \times V_P^*}{S_L(3\phi)^*}$$

$$Z_P = \frac{3|V_P|^2}{S_L^*(3\phi)} = \frac{V_{Line}^2}{S_L^*(3\phi)} = \frac{V_{LL}^2}{S_L^*(3\phi)}$$

$$Z_P = \frac{V_{LL}^2}{S_L^*(3-\phi)}$$

$$Z_P = \frac{Z_P}{Z_B} = \frac{\frac{V_{LL}^2}{S_L^*(3-\phi)}}{\frac{V_B^2}{S_B}} = \frac{\text{actual}}{\text{Base}}$$

$$Z_{pu} = \frac{V_{L-L}^2}{V_B^2} \times \frac{S_B}{S_L^*(3-\phi)}$$

$$Z_{pu} = \frac{V_{pu}^2}{S_L^*(pu)}$$

} S_L : load apparent power (per unit)

(1-4)

$$S_{pu} = V_{pu} \times I_{pu}^* \quad (\text{per unit})$$

$$S_B = \sqrt{3} V_B \text{ Line } I_B \quad (\text{Base Value})$$

$$S_{L_{3\phi}} = 3 V_p I_p^* \quad (\text{actual value}) \\ \text{per phase}$$

$$S_{L_{3\phi}} = \sqrt{3} V_{\text{Line}} I_{\text{Line}}^* \quad (\text{actual value}) \\ \text{per line}$$

$$Z_{pu} = \frac{V_{pu}}{I_{pu}}$$

$$Z_B = \frac{V_B}{I_B} = \frac{V_B^2}{S_B}$$

$$Z_{\text{actual}} = \frac{V_p}{I_p} \quad \text{per phase}$$

$$Z_{\text{Load actual}} = \frac{V_{\text{Line}}^2}{S_{\text{Line}}^*_{3\phi}}$$

* Change of Base

(1-5)

For power system analysis, all impedances must be expressed in per unit on a common system base. To accomplish this, an arbitrary base for apparent power is selected; for example, 100 MVA.

Then the voltage base must be selected.

Once a voltage base has been selected for a point in a system, the remaining voltage bases are no longer independent; they are determined by the various transformer turns ratios.

For example, if on a low-voltage side of $\frac{34.5 \text{ kV}}{115 \text{ kV}}$ transformer the base voltage of 36 kV is selected.

The base voltage on the high-voltage side must be

$$36 \times \frac{115}{34.5} = 120 \text{ kV}$$

where $\frac{N_2}{N_1} = \frac{V_{B2}}{V_{B1}}$

Normally we try to select the voltage bases that are the same as the nominal values.

(1-6)

Let Z_{pu}^{old} be the per-unit impedance on the power base S_B^{old} and the voltage V_B^{old}

$$Z_{pu}^{old} = \frac{Z_{\Omega}}{Z_B^{old}} = Z_{\Omega} \frac{S_B^{old}}{(V_B^{old})^2}$$

Expressing Z_{Ω} to a new power base and a new voltage base, results in the new per unit impedance

$$Z_{pu}^{new} = \frac{Z_{\Omega}}{Z_B^{new}} = Z_{\Omega} \frac{S_B^{new}}{(V_B^{new})^2}$$


$$Z_{pu}^{new} = \frac{Z_{pu}^{old}}{\frac{S_B^{old}}{(V_B^{old})^2}} \times \frac{S_B^{new}}{(V_B^{new})^2} =$$

$$Z_{pu}^{new} = Z_{pu}^{old} \cdot \left(\frac{S_B^{new}}{S_B^{old}} \right) \left(\frac{V_B^{old}}{V_B^{new}} \right)^2$$

* The advantage of per-unit system. (1-7)

- 1- The per-unit system gives us a clear idea of relative magnitudes of various quantities, such as voltage, current, power and impedance.
- 2- The per-unit impedance of equipment of the same general type based on their own ratings fall in a narrow range regardless of rating of the equipment. Whereas their impedance in ohms vary greatly with the rating.
- 3- The per-unit values of impedance, voltage and current of a transformer are the same regardless of whether they are referred to the primary or the secondary side. This is a great advantage since the different voltage levels disappear and the entire system reduces to a system of simple impedance.
- 4- The perunit system are ideal for the computerized analysis and simulation of complex power system problem.
- 5- The ckt law are valid in per unit system and the power and the voltage equations are simplified since the factor $\sqrt{3}$ and 3 are eliminated in per unit system.

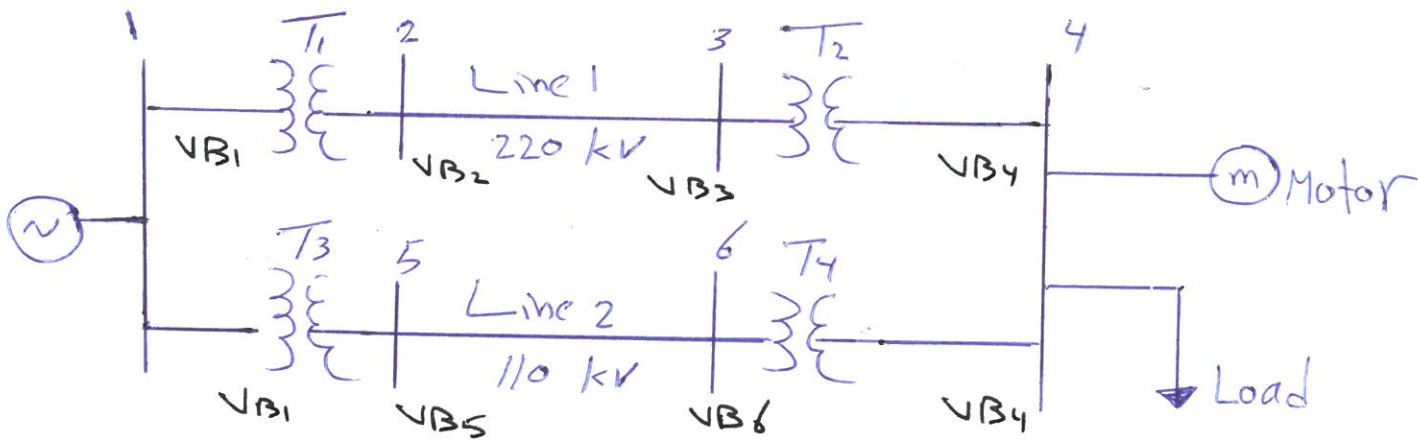ex1) The one-line diagram of a 3-φ power system is shown in the fig. below :-



select a Common base of 100 MVA and 22 kV on the generator side.

Draw an impedance diagram in perunit.

The data for each device is given below:-

G :	90 MVA	22 kV	X = 18 %
T ₁ :	50 MVA	22/220 kV	X = 10 %
T ₂ :	40 MVA	220/11 kV	X = 6 %
T ₃ :	40 MVA	22/110 kV	X = 6.4 %
T ₄ :	40 MVA	110/11 kV	X = 8 %
Motor :	66.5 MVA	10.45 kV	X = 18.5 % 0.8 Lag. P.f

The 3-φ load at bus 4 absorbs 57 MVA, 0.6 P.f Lag. at 10.45 kV. Line 1 and Line 2 have a reactance of 48.4 and 65.43 Ω respectively.

Sol.
- The voltage bases must be determined for all sections of the network. (1-9)

- The generator rated voltage is given at the base voltage at bus 1

$$V_{B1} = V_{G1} = 22 \text{ kV}$$

$$V_{B2} = 22 * \left(\frac{220}{22} \right) = 220 \text{ kV}$$

where

$$\frac{N_2}{N_1} = \frac{V_{B2}}{V_{B1}}$$

$$\frac{220}{22} = \frac{V_{B2}}{22} \Rightarrow V_{B2} = 22 * \left(\frac{220}{22} \right) = 220 \text{ kV}$$

$$V_{B2} = V_{B3} = 220 \text{ kV}$$

$$V_{B4} = 220 \left(\frac{11}{220} \right) = 11 \text{ kV}$$

$$V_{B5} = 22 \left(\frac{110}{22} \right) = 110 \text{ kV}$$

$$V_{B6} = V_{B5} = 110 \text{ kV}$$

$$V_{B4} = 110 * \left(\frac{11}{110} \right) = 11 \text{ kV}$$

$$X_{\text{new}} = X_{\text{old}} \left(\frac{S_{B \text{ new}}}{S_{B \text{ old}}} \right) \left(\frac{V_{B \text{ old}}}{V_{B \text{ new}}} \right)^2$$

$$X_{G1} = 0.18 \left(\frac{100}{90} \right) \left(\frac{22}{22} \right)^2 = 0.2 \text{ pu}$$

$$X_{T1} = 0.1 \times \left(\frac{100}{50}\right) \left(\frac{22}{22}\right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary side} \\ \text{of Transformer 1} \\ \text{i.e.: Low voltage} \\ \text{side.} \end{array} \right.$$

OR

$$X_{T1} = 0.1 \times \left(\frac{100}{50}\right) \left(\frac{220}{220}\right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 1} \\ \text{i.e.: High voltage} \\ \text{side.} \end{array} \right.$$

$$X_{T2} = 0.06 \times \left(\frac{100}{40}\right) \left(\frac{220}{220}\right)^2 = 0.15 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary} \\ \text{side of} \\ \text{Transformer 2} \\ \text{i.e.: High voltage} \\ \text{side.} \end{array} \right.$$

OR

$$X_{T2} = 0.6 \times \left(\frac{100}{40}\right) \left(\frac{11}{11}\right)^2 = 0.15 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 2} \\ \text{i.e.: Low} \\ \text{voltage side.} \end{array} \right.$$

$$X_{T3} = 0.064 \times \left(\frac{100}{40}\right) \left(\frac{22}{22}\right)^2 = 0.16 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary} \\ \text{side of} \\ \text{Transformer 3} \\ \text{i.e.: Low} \\ \text{voltage side} \end{array} \right.$$

OR

$$X_{T3} = 0.064 \times \left(\frac{100}{40}\right) \left(\frac{110}{110}\right)^2 = 0.16 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 3} \\ \text{i.e.: High voltage} \\ \text{side.} \end{array} \right.$$

$$X_{T4} = 0.08 \left(\frac{100}{40} \right) \left(\frac{110}{110} \right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on primary side} \\ \text{of Transformer 4} \\ \text{i.e.: High Voltage} \\ \text{side.} \end{array} \right. \quad (1-11)$$

OR

$$X_{T4} = 0.08 \left(\frac{100}{40} \right) \left(\frac{11}{11} \right)^2 = 0.2 \text{ pu} \quad \left\{ \begin{array}{l} \text{on secondary} \\ \text{side of} \\ \text{Transformer 4} \\ \text{i.e.: Low Voltage} \\ \text{side.} \end{array} \right.$$

$$X_{\text{motor}} = 0.185 \left(\frac{100}{65.5} \right) \left(\frac{10.45}{11} \right)^2 = 0.2 \text{ pu}$$

$$Z_{\text{Line 1}}^B = \frac{V_{B \text{ Line 1}}^2}{S_B} = \frac{(V_{B2} \text{ or } V_{B3})^2}{S_B} = \frac{220^2}{100} = 484 \Omega$$

$$Z_{\text{Line 2}}^B = \frac{V_{B \text{ Line 2}}^2}{S_B} = \frac{(V_{B5} \text{ or } V_{B6})^2}{S_B} = \frac{110^2}{100} = 121 \Omega$$

$$X_{\text{Line 1}}^{\text{pu}} = \frac{\text{actual}}{\text{Base}} = \frac{48.4}{484} = 0.1 \text{ pu} = j0.1 \text{ pu}$$


$$X_{\text{Line 2}}^{\text{pu}} = \frac{\text{actual}}{\text{Base}} = \frac{65.43}{121} = 0.54 \text{ pu} = j0.54 \text{ pu}$$

$$S_{\text{Load}} = 57 \angle 53.13 \text{ MVA} \quad \left\{ \begin{array}{l} 0.6 \text{ Lag. P.F} \end{array} \right.$$

where :-

Lag. P.F. { inductive Load }

(1-12)

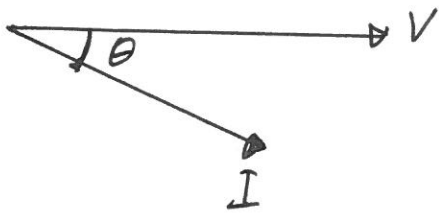

$$V = VL \angle 0 \quad ; \quad I = IL \angle -\theta$$

$$S_{3\phi} = \sqrt{3} V_{line} I_{line}^* \quad \text{or} \quad 3 V_p I_p^*$$

$$S_{3\phi} = \sqrt{3} V (IL \angle -\theta)^*$$

$$= \sqrt{3} V IL \angle \theta = \sqrt{3} (VI \angle \theta)$$


$$= \sqrt{3} (VI \cos \theta + j VI \sin \theta)$$

$$= \sqrt{3} VI \cos \theta + j \sqrt{3} VI \sin \theta$$

$$= P + jQ$$

where $P = \sqrt{3} VI \cos \theta$

$Q = \sqrt{3} VI \sin \theta$

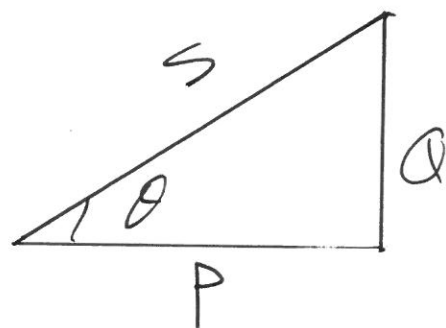

Lag. P.F.

$$S = |S| \angle +\theta$$

Lag p.f. \Rightarrow

(1-13)


$$S_{Load} = 57 \angle +53.13^\circ \text{ MVA}$$

$$Z_{Load}^{actual} = \frac{V_{L-L}^2}{S_{Load}^*} = \frac{10.45^2 \text{ kV}}{57 \angle -53.13 \text{ MVA}} = 1.1495 + j1.1532 \Omega$$

$$Z_{B_{Load}} = \frac{V_{B_{Load}}^2}{S_B} = \frac{11^2 \text{ kV}}{100 \text{ MVA}} = 1.21 \Omega$$

$$Z_{Load}^{pu} = \frac{actual}{Base} = \frac{1.1495 + j1.1532}{1.21} = 0.95 + j1.2667 \text{ pu}$$

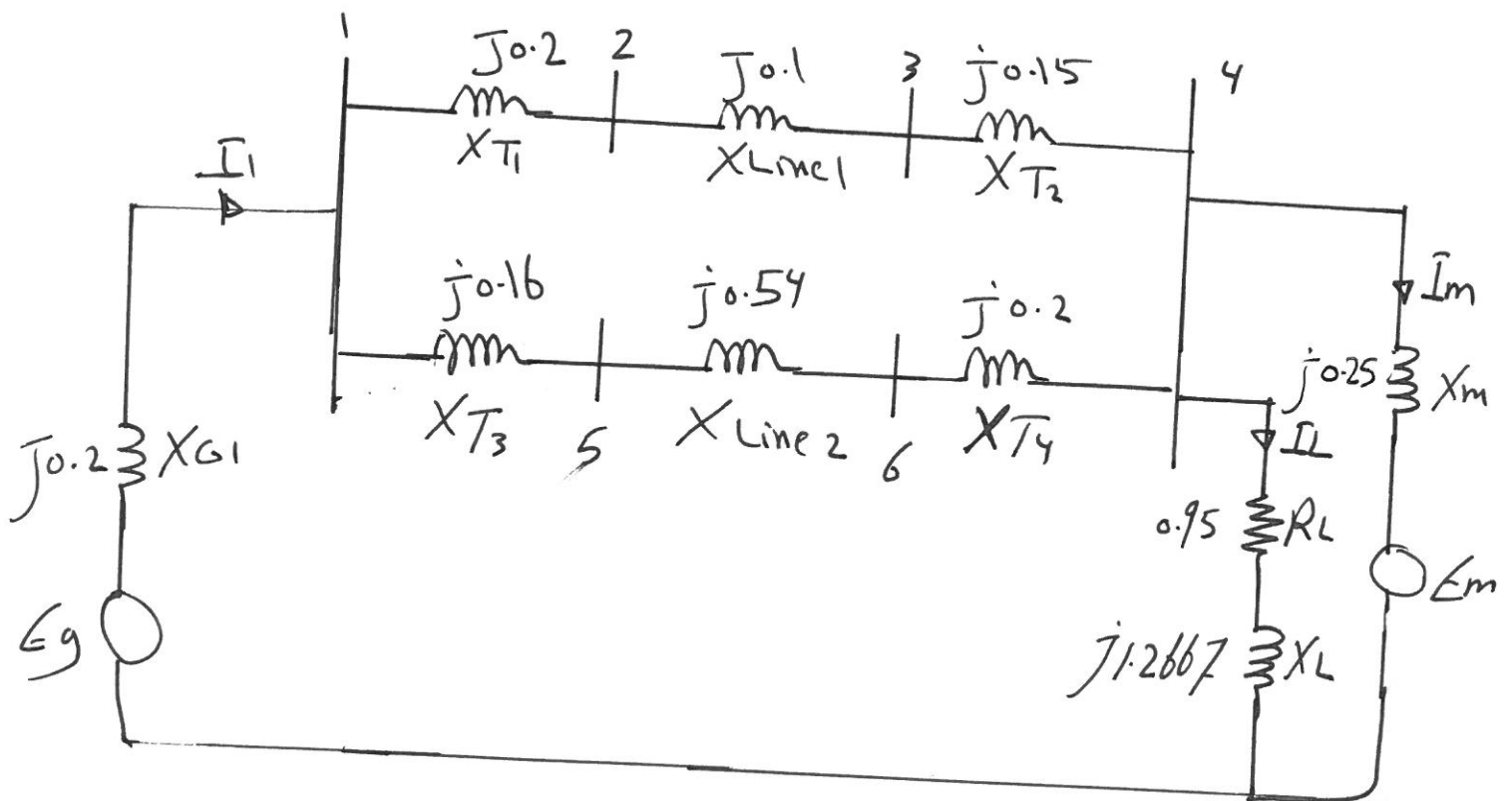The per unit equivalent ckt is shown in Fig. below



ex) If the motor in ex1 operate at Full-Load
0.8 P.f leading at terminal voltage
of 10.45 kV.

- 1- Determine the voltage at the generator busbar (bus 1)
- 2- Determine the generator and the motor internal emfs.


Sol)

The per-unit voltage at bus 4, taken as reference is

$$V_4 = \frac{\text{actual}}{\text{Base}} = \frac{10.45}{11} = 0.95 \angle 0 \text{ pu}$$


The apparent power of motor at 0.8 lead p.f
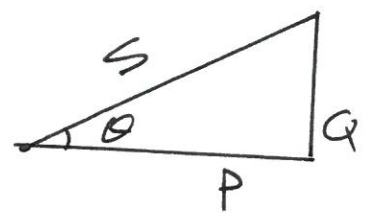
$$S_m = \frac{\text{actual}}{\text{Base}} = \frac{66.5 \angle -36.8}{100} = 0.665 \angle -36.87 \text{ pu}$$



Lag P.f

$$S = S \angle +\theta$$

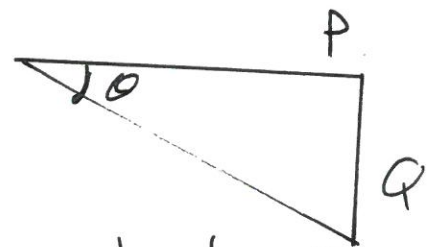

lead P.f

$$S = S \angle -\theta$$

$$S_{pu} = V_{pu} I_{pu}^*$$

The current drawn by the motor is

$$I_m = \frac{S_m^*}{V_m^*} \quad \left\{ \text{where } S_m = V_m I_m^* \right.$$

$$I_m = \frac{0.665 \angle +36.87}{0.95 \angle 0} = 0.56 + j0.42 \text{ pu}$$

The current drawn by the Load is

$$I_L = \frac{V_4}{Z_L} = \frac{0.95 \angle 0}{0.95 + j1.2667} = 0.36 - j0.48 \text{ pu}$$

The current drawn from bus 4

$$I = I_m + I_L = I_1 \quad \left\{ \text{current of } G \right\}$$

$$= (0.56 + j0.42) + (0.36 - j0.48) = 0.92 - j0.06 \text{ pu}$$

The equivalent reactance of the parallel branches is

$$X = \frac{0.45 * 0.9}{0.45 + 0.9} = 0.3 \text{ pu}$$

The generator terminal voltage

$$V_1 = V_4 + Z I$$

$$= 0.95 \angle 0 + j0.3(0.92 - j0.06) = 0.968 + j0.276$$

$$= 1 \angle 15.91^\circ \text{ pu}$$

actual Value = 1 * 22 kV = 22 kV = 22 \angle 15.91^\circ kV =

(1-16)

$$\begin{aligned}
 E_g &= V_t + I_1 X_g \quad \text{pu} \\
 &= 1 \angle 15.91^\circ + (0.92 - j0.06) * (j0.2) \\
 &= 0.961 + j0.274 + j0.184 + 0.012 \\
 &= 0.973 + j0.458 = 1.075 \angle 25.17^\circ
 \end{aligned}$$

$$E_{g \text{ actual}} = 1.075 * V_B \quad [V_B \text{ at the generator side}]$$

$$\frac{E_g}{\text{actual}} = 1.075 * 22 = \underline{23.65 \text{ kV}}$$

$$E_m = V_4 - I_m Z_m \quad [V_4 \text{ is terminal voltage at the motor}]$$

$$\begin{aligned}
 E_m &= 0.95 \angle 0 - (0.56 + j0.42) * j0.25 \\
 &= 0.95 - j0.14 + 0.105 = 1.055 \angle 0.14
 \end{aligned}$$


$$E_m = 1.0642 \angle -7.559^\circ$$

$$\begin{aligned}
 E_{m \text{ actual}} &= 1.0642 * V_B \\
 &= 1.0642 * 11 = \underline{11.7062 \text{ kV}}
 \end{aligned}$$

ex3)

(1-17)

(1-1)

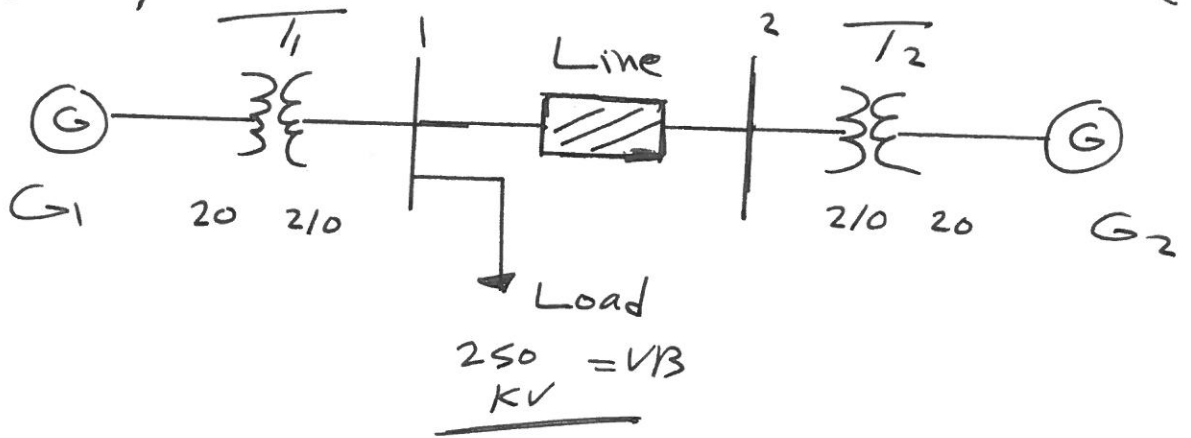

G_1	90 MVA	20 kV	$X = 0.09 \text{ pu}$
T_1	80 MVA	20/210	$X = 0.16 \text{ pu}$
T_2	80 MVA	210/20	$X = 0.2 \text{ pu}$
G_2	90 MVA	18 kV	$X = 0.06 \text{ pu}$
Line	210 kV		$X = 120 \Omega$
Load	210 kV		$S = 48 + j64$

Choose base MVA as 100 MVA and base voltage of 250 kV at the Load bus

Sol) The base voltage = 250 kV at the Load bus bar

$$V_{B \text{ Load}} = 250 \text{ kV}$$

$$V_{B2} \text{ at bus } \underline{2} = 250 \text{ kV}$$

$$V_{BG_2} = 250 * \left(\frac{20}{210} \right) = 23.8 \text{ kV}$$

$$V_{BG1} = 250 \times \left(\frac{20}{210} \right) = 23.8 \text{ kV}$$

$$X_{G1} = X_{old} \left(\frac{S_B^{new}}{S_B^{old}} \right) \left(\frac{V_B^{old}}{V_B^{new}} \right)^2$$

$$X_{G1} = 0.09 \left(\frac{100}{90} \right) \left(\frac{20}{23.8} \right)^2 = 0.0706 \text{ pu}$$

$$X_{G2} = 0.06 \left(\frac{100}{90} \right) \left(\frac{18}{23.8} \right)^2 = 0.038 \text{ pu}$$

$$X_{T1} = 0.16 \left(\frac{100}{80} \right) \left(\frac{20}{23.8} \right)^2 = 0.141 \text{ pu} \left\{ \begin{array}{l} \text{on primary} \\ \text{side} \end{array} \right.$$

OR

$$X_{T1} = 0.16 \left(\frac{100}{80} \right) \left(\frac{210}{250} \right)^2 = 0.141 \text{ pu} \left\{ \begin{array}{l} \text{on secondary} \\ \text{side} \end{array} \right.$$

$$X_{T2} = 0.2 \times \left(\frac{100}{80} \right) \left(\frac{210}{250} \right)^2 = 0.176 \text{ pu} \left\{ \begin{array}{l} \text{on primary} \\ \text{side} \end{array} \right.$$

OR

$$X_{T2} = 0.2 \times \left(\frac{100}{80} \right) \left(\frac{20}{23.8} \right)^2 = 0.176 \text{ pu} \left\{ \begin{array}{l} \text{on} \\ \text{secondary} \\ \text{side} \end{array} \right.$$


$$X_{B \text{ Line}} = \frac{V_B^2 \text{ Line}}{S_B} = \frac{250^2}{100} = 625 \Omega$$

$$X_{pu \text{ Line}} = \frac{\text{actual}}{\text{base}} = \frac{120}{625} = 0.192 \text{ pu}$$


$$Z_{\text{Load actual}} = \frac{V_{LL}^2}{S_{3\phi}^*} = \frac{210^2}{48 - j64} = 378 + j504 \quad \Omega \quad (1-19)$$

$$Z_B = \frac{V_{B \text{ Load}}^2}{S_B} = \frac{250^2}{100} = 625$$

$$Z_{\text{pu Load}} = \frac{\text{actual}}{\text{Base}} = \frac{378 + j504}{625} = 0.6048 + j0.806 \text{ pu}$$

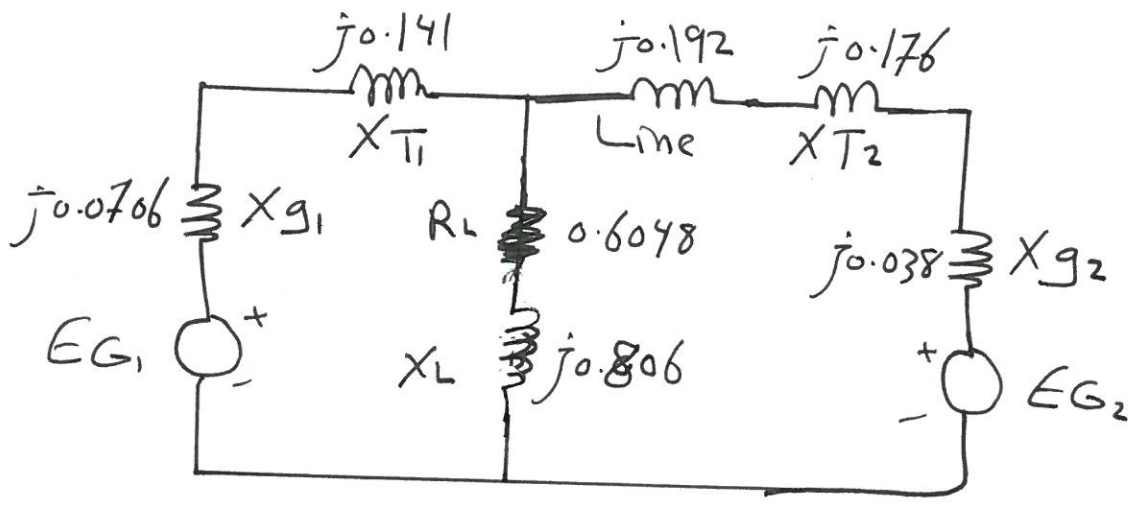

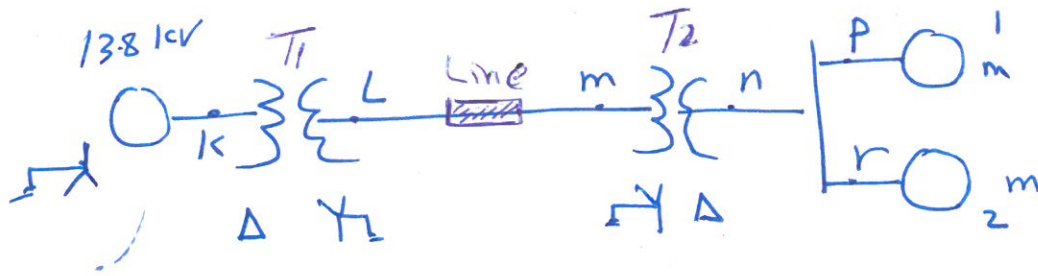ex 4) The system in the fig. below have :-



30,000 kVA, 13.8 kV, 3 ϕ generator has subtransient reactance of 15%. The generator supplies two motors over a transmission line having transformers at both ends as shown in the fig. above.

The motors have rated inputs of 20,000 and 10,000 kVA, both 12.5 kV with $X = 20\%$.

The 3- ϕ transformer T_1 is rated 35,000 kVA, 13.2 Δ -115 Y kV with leakage reactance of 10%.

Transformer T_2 is composed of three single phase transformers each rated 10,000 kVA, 12.5-67 kV with leakage reactance of 10%. Δ -Y

Series reactance of the transmission line is 80Ω .

- Draw the reactance diagram with all reactances marked in per unit.

Select the generator rating as base in the generator circuit.

(1-21)

Sol) - The 3- ϕ rating of T_2

$$3 \times 10,000 = 30,000 \text{ kVA} = 30 \text{ MVA}$$

- The line-to-line voltage ratio $\frac{V_2}{N_1} = \frac{V_2}{V_1} =$

$$\frac{12.5}{\sqrt{3} \times 67} = \frac{12.5}{116} \left\{ \begin{array}{l} \text{secondary} \\ \text{primary} \end{array} = \frac{\Delta}{\text{Y}} \right\}$$

* The base of 30,000 kVA = 30 MVA
13.8 kV in the generator ckt

$$\therefore \text{Base MVA} = 100 \text{ MVA}$$

Base voltage :-
 $V_k = 13.8 \text{ kV}$

$$V_L = 13.8 \times \left(\frac{N_2}{N_1} = \frac{V_2}{V_1} = \text{turns ratio of } T_1 \right)$$

Line to line 3- ϕ

$$V_L = 13.8 \times \frac{115}{13.2} = 120 \text{ kV}$$

= voltage of Transmission Line

$$V_m = V_L = 120 \text{ kV}$$

$$V_n = 120 \times \frac{12.5}{116} = 12.9 \text{ kV}$$

$$V_p = V_r = 12.9 \text{ kV}$$

$$X_{\text{new}} = X_{\text{old}} \cdot \left(\frac{S_{B \text{ new}}}{S_{B \text{ old}}} \right) \left(\frac{V_{B \text{ old}}}{V_{B \text{ new}}} \right)^2$$

Low side



$$X_{T1} = 0.1 \left(\frac{30}{35} \right) \left(\frac{13.2}{13.8} \right)^2 = 0.0784 \text{ pu} \left\{ \begin{array}{l} \text{on L.S. of } T_1 \\ \text{i.e. primary of } T_1 \end{array} \right.$$

OR

$$X_{T1} = 0.1 \left(\frac{30}{35} \right) \left(\frac{115}{120} \right)^2 = 0.078 \text{ pu} \left\{ \begin{array}{l} \text{High side} \\ \text{on H.S. of } T_1 \\ \text{i.e. secondary} \\ \text{of } T_1 \end{array} \right.$$

$$X_{T2} = 0.1 \left(\frac{30}{30} \right) \left(\frac{115}{120} \right)^2 = 0.094 \text{ pu} \left\{ \begin{array}{l} \text{on H.S. of } T_2 \\ \text{i.e. primary of } T_2 \end{array} \right.$$

OR

$$X_{T2} = 0.1 \left(\frac{30}{30} \right) \left(\frac{12.5}{12.9} \right)^2 = 0.094 \text{ pu} \left\{ \begin{array}{l} \text{on L.S. of } T_2 \\ \text{i.e. secondary} \\ \text{of } T_1 \end{array} \right.$$


$$Z_{B \text{ Line}} = \frac{V_B^2}{S_B} = \frac{120^2}{30} = 480 \Omega$$

$$Z_{\text{Line}} = \frac{\text{actual}}{\text{Base}} = \frac{80}{480} = 0.167 \text{ pu}$$


$$X_{m1} = 0.2 \left(\frac{30}{20} \right) \left(\frac{12.5}{12.9} \right)^2 = 0.282 \text{ pu}$$

$$X_{m2} = 0.2 \left(\frac{30}{10} \right) \left(\frac{12.5}{12.9} \right)^2 = 0.563 \text{ pu}$$

$$X_G = 0.15 \left(\frac{30}{30} \right) \left(\frac{13.8}{13.8} \right)^2 = 0.15 \text{ pu}$$

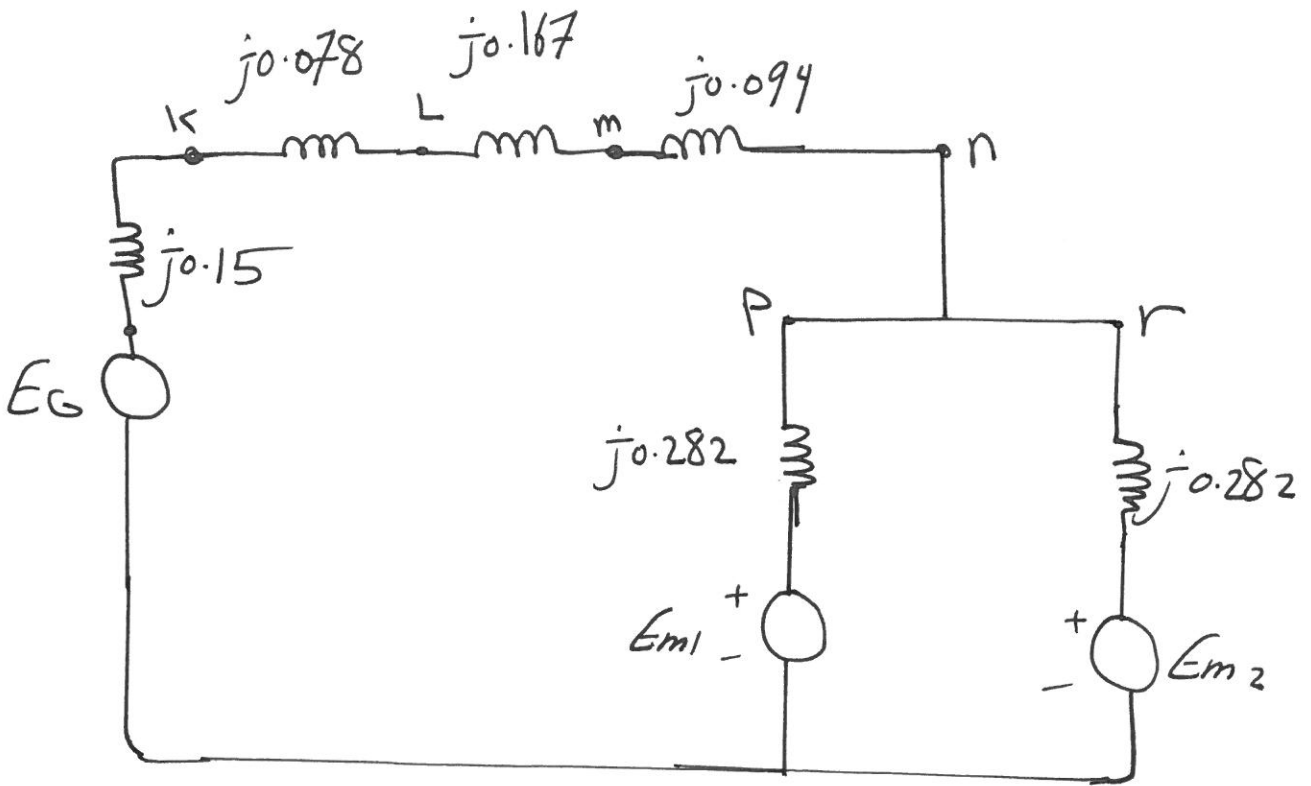

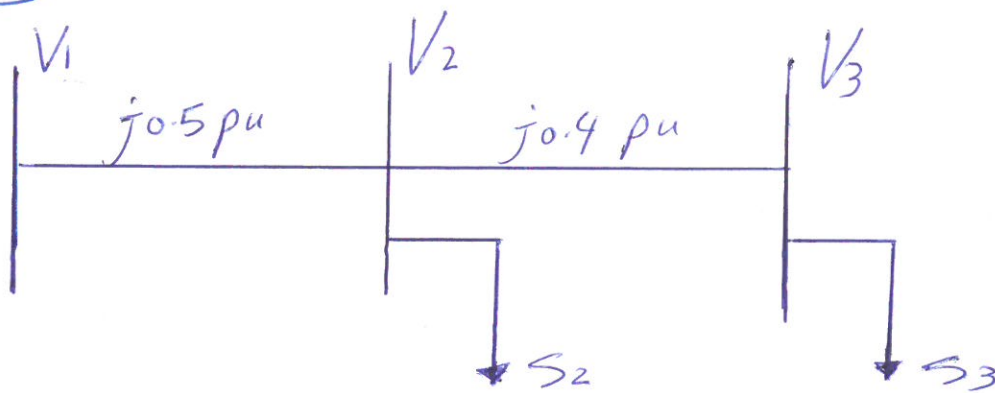ex 9) The one-line diagram of a 3- ϕ system in the ⁽¹⁻²⁴⁾ fig. below



(1-24)

Impedance are marked in per unit on 100 MVA, 400 kV base. The load at bus 2 is

$$S_2 = 15.93 \text{ MW} + j 33.4 \text{ Mvar} \text{ and at bus 3}$$

$$S_3 = 77 \text{ MW} + j 14 \text{ Mvar} \text{ . It is required to hold the voltage at bus 3 at } 400 \angle 0 \text{ kV}$$

working in per unit, determine the voltage at bus 2 and 1

Sol) $V_B = 400$ (in all point because there is no Transformer)
 $S_B = 100 \text{ MVA}$

$$S_2 = \frac{15.9 - j 33.4}{100} = 0.159 - j 0.334 \text{ pu}$$

$$S_3 = \frac{77 + j 14}{100} = 0.77 + j 0.14 \text{ pu}$$

$$S_3 \text{ pu} = V_3 \text{ pu} I_3^* \text{ pu}$$

$$I_3 = \frac{S_3}{V_3^*}$$

$$V_3 \text{ pu} = \frac{\text{actual}}{\text{Base}} = \frac{400}{400}$$

$$V_3 \text{ pu} = 1 \angle 0 \text{ pu}$$

$$\frac{I_3}{pu} = \frac{S_3^*}{V_3^*} = \frac{0.77 - j0.14}{1 \angle 0} = 0.77 - j0.14 \text{ pu}$$

$$V_2 = V_3 + I_3(j0.4)$$

$$= 1 \angle 0 + (0.77 - j0.14) * (j0.4)$$

$$= 1 + j0.308 + 0.056 = 1.056 + j0.308 \text{ pu}$$

$$= 1.11 \angle 16.26^\circ$$

$$V_2 = 1.1 \text{ pu} * 400 \text{ kV Base} = \underline{440 \text{ kV}} \text{ Line to Line}$$

actual

$$\frac{I_2}{pu} = \frac{S_2^*}{V_2^*} = \frac{0.1593 + j0.334}{1.11 \angle -16.26^\circ} = 0.054 + j0.332 \text{ pu}$$

$$I_1 = I_2 + I_3$$

$$= (0.054 + j0.332) + (0.77 - j0.14)$$

$$I_1 = 0.824 + j0.192 \text{ pu}$$


$$V_1 = V_2 + I_1(j0.5)$$

$$= 1.11 \angle 16.26^\circ + (0.824 + j0.192)(j0.5)$$

$$= 1.2 \angle 36.87^\circ$$

$$V_1 = 400 * 1.2 = \underline{480 \text{ kV}} \text{ Line to Line}$$

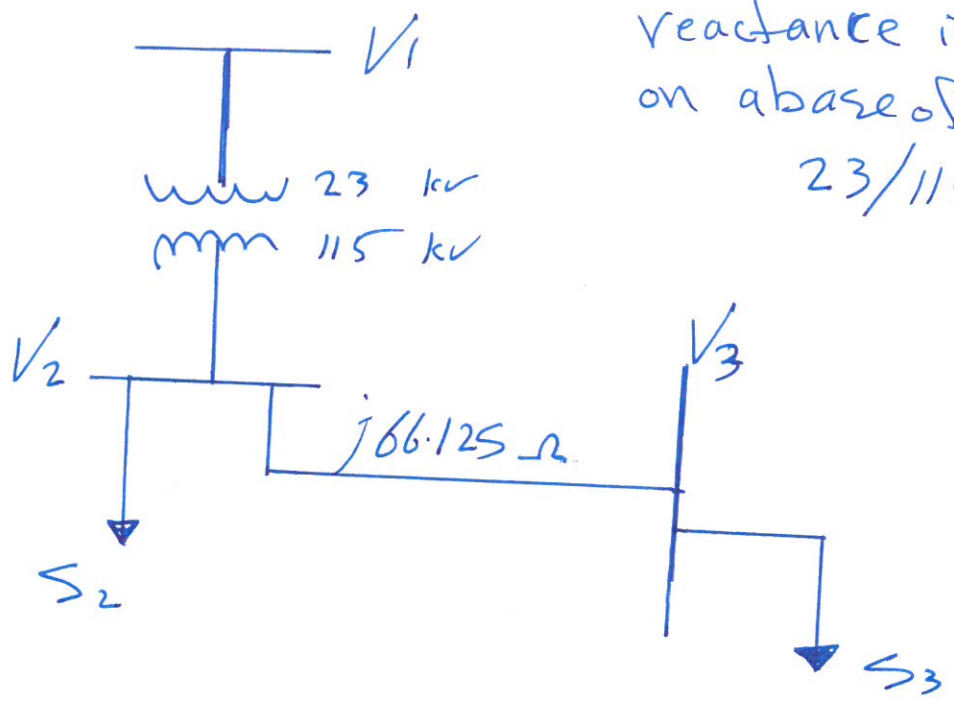Ex 10) The one-line diagram of a 3-φ power system is shown in the fig. below. The transformer



reactance is 20 percent on a base of 100 MVA, 23/115 kV.

The line impedance $Z = j66.125 \Omega$.

The load $S_2 = 184.8 \text{ MW} + j6.6 \text{ MVar}$

$S_3 = 0 \text{ MW} + j20 \text{ MVar}$

It is required to hold the voltage at bus 3 at 115 kV. Working in per unit, find the voltage V_2, V_1

Sol

$S_B = 100 \text{ MVA}$

$V_{B1} = 23 \text{ kV}$

$V_{B2} = 115 \text{ kV}$

$$S_2 = \frac{184.8 + j6.6}{100} = 1.848 + j0.066 \text{ pu}$$

$$S_3 = \frac{0 + j20}{100} = 0 + j0.2 \text{ pu}$$

$$V_3 = \frac{\text{actual}}{\text{Base}} = \frac{115 \text{ kV}}{115} = 1.0 \text{ pu}$$

$$V_2 = V_3 + I_3 Z$$

$$I_3 \text{ pu} = \frac{S_3^*}{V_3^*} = \frac{-j0.2}{1.0} = -j0.2 \text{ pu}$$

$$Z \text{ pu} = \frac{\text{actual}}{\text{Base}} \quad \left| \quad Z_B = \frac{V_B^2}{S_B} = \frac{115^2}{100}$$

$$Z_B = 132.25 \Omega$$

$$Z = \frac{66.125}{132.25} = j0.5 \text{ pu}$$

$$V_2 = 1.0 + (-j0.2)(j0.5)$$

$$= 1 + 0.1 = 1.1 \text{ pu} \quad \neq$$

$$V_2 = 1.1 \times 115 = 126.5 \text{ kV} \quad \text{line to line}$$

$$I_2 = \frac{S_2^*}{V_2^*} = \frac{1.848 - j0.066}{1.1} = 1.68 - j0.26$$

$$I_1 = \hat{I}_3 + I_2$$

$$\hat{I}_1 = (-j0.2) + (1.68 - j0.06) = 1.68 - j0.26 \text{ pu}$$


$$V_1 = \hat{I}_1 X_{\text{Trans}} + V_2$$

$$= (1.68 - j0.26) * (j0.2) + 1.1 \angle 0^\circ$$

$$= 1.2 \angle 16.26^\circ$$

$$V_1 = 1.2 * 23 = 27.6 \text{ kV}$$

Line to Line

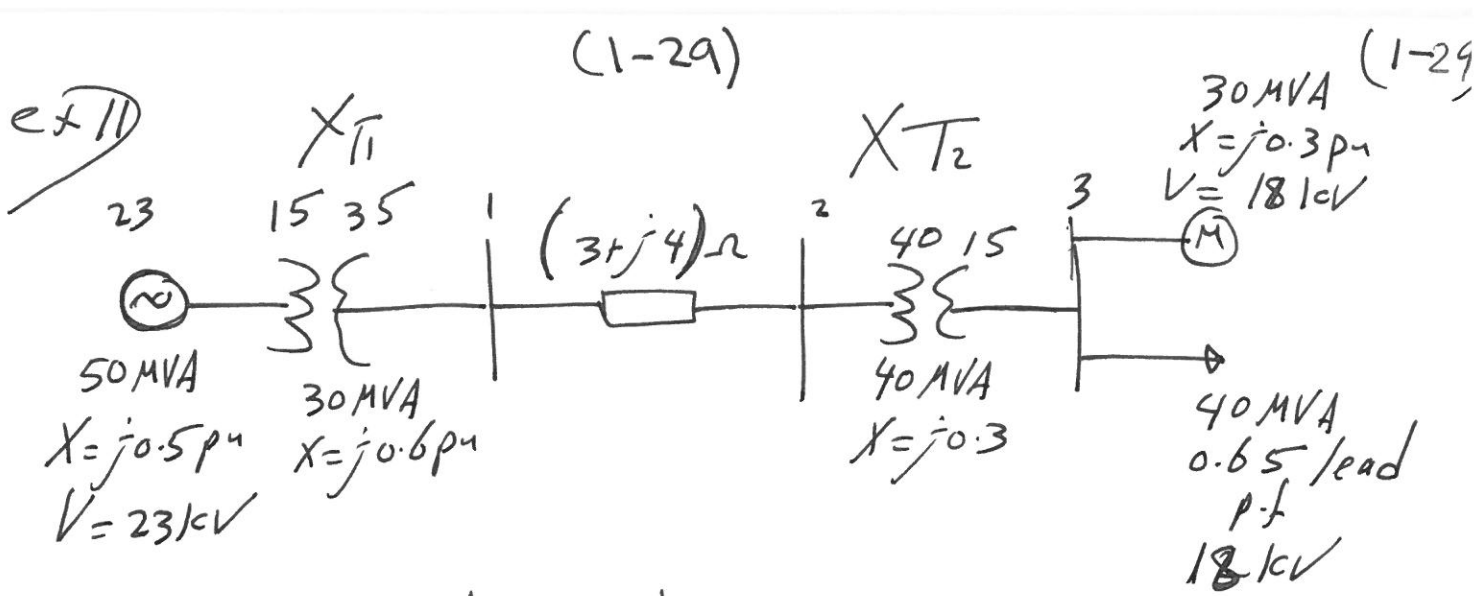

- ① Find per unit impedance
- ② Find E_m of the motor

Take $V_B = 22 \text{ kV}$ at bus bar 1
 $S_B = 100 \text{ MVA}$

Sol

$$V_B = 22 \times \frac{15}{35} = 9.4 \text{ kV (base)}$$

$$V_{m_B} = 22 \times \frac{15}{40} = 8.25 \text{ kV (base)}$$

V_{Load}

$$X_{G1} = 0.5 \left(\frac{100}{50} \right) \left(\frac{23}{9.4} \right)^2 = j5.98 \text{ pu}$$

$$X_{T1} = 0.6 \left(\frac{100}{30} \right) \left(\frac{35}{22} \right)^2 = j5.0619 \text{ pu}$$

Secondary

$$X_{T2} = 0.3 \left(\frac{100}{40} \right) \left(\frac{40}{22} \right)^2 = j2.47 \text{ pu}$$

primary

$$X_m = 0.3 \left(\frac{100}{30} \right) \left(\frac{18}{8.25} \right)^2 = j4.76 \text{ pu}$$

$$Z_{B \text{ Line}} = \frac{V_B^2}{S_B} = \frac{22^2}{100} = 4.84 \Omega$$

$$Z_{\text{Line pu}} = \frac{\text{actual}}{\text{Base}} = \frac{3+j4}{4.84} = 0.62 + j0.826 \text{ pu}$$


$$Z_{\text{Load}} = \frac{V_{LL}^2}{S_{LL}} \implies S_L = 40 \angle -\cos^{-1} 0.65$$

$$= 40 \angle -49.45$$

$$Z_{\text{Load}} = \frac{18^2}{40 \angle 49.45} = 8.1 \angle -49.45$$


$$Z_{\text{Load}} = (5.265 - j6.154) \Omega$$
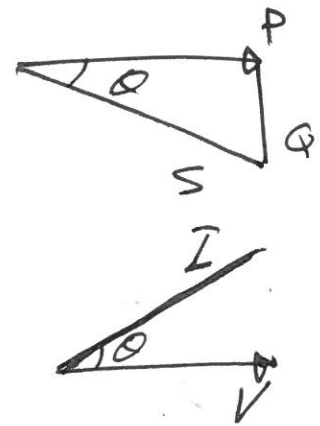
$$Z_{B \text{ Load}} = \frac{V_B^2}{S_B} = \frac{18^2}{100} = 3.24 \Omega$$



leading p.f
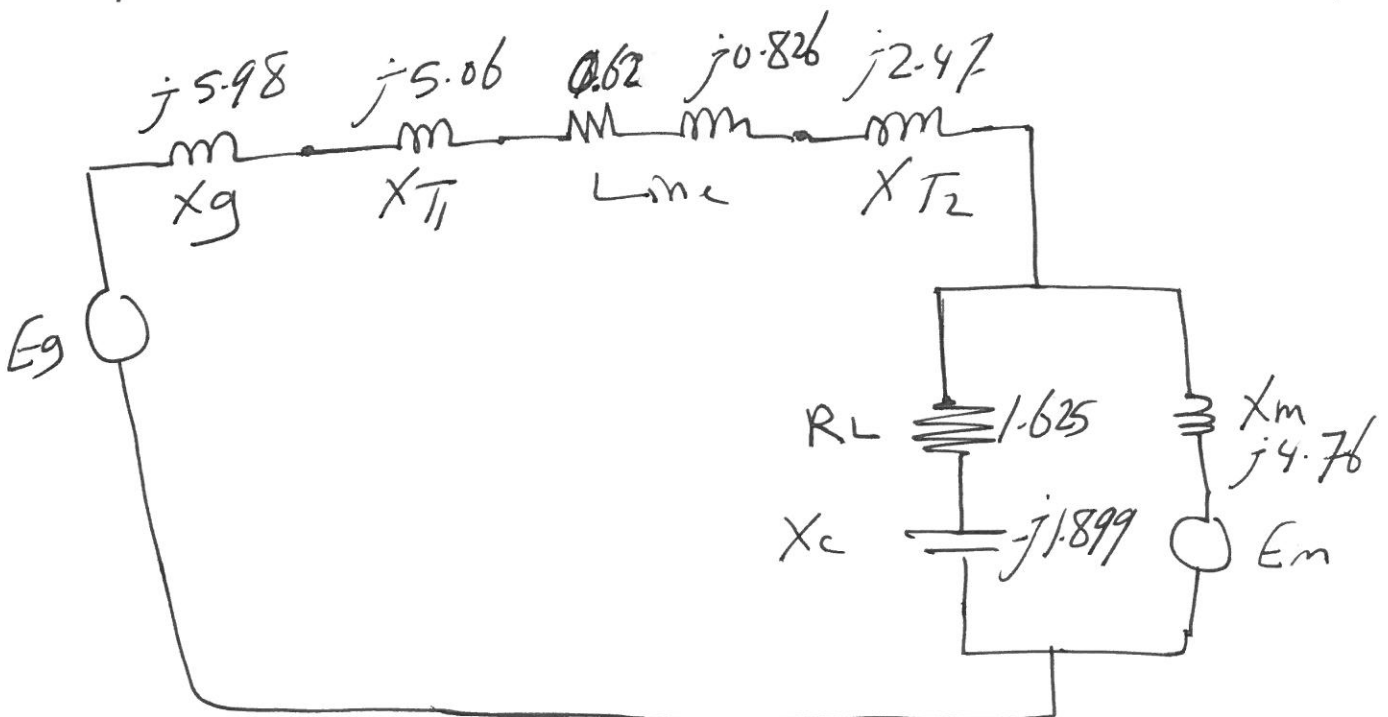
$$Z_{\text{Load pu}} = \frac{\text{actual}}{\text{Base}} = \frac{5.265 - j6.154}{3.24} = 1.625 - j1.899 \text{ pu}$$



$$E_m = V_m - \hat{I}_m X_m \quad (1-31)$$

(1-31)

$$V_m = \frac{\text{actual}}{\text{Base}} = \frac{18}{8.25} = 2.18 \text{ pu} = \sqrt{3}$$

$$S_m = V_m \hat{I}_m^* \Rightarrow \hat{I}_m = \frac{S_m^*}{V_m^*}$$

$$\hat{I}_m = \frac{S_m^*}{V_m^*}$$

$$S_m = 30 \angle -90$$

because it has only
reactance $X_m = j0.476$
(leading P.F)

$$S_m = \frac{30 \angle 90}{100}$$

$$= 0.3 \angle 90 = j0.3 \text{ pu}$$

$$\hat{I}_m = \frac{S_m^*}{V_m^*} = \frac{-j0.3}{2.18} = -j0.1376 \text{ pu}$$

$$E_m = V_m - \hat{I}_m X_m$$



$$= 2.18 \angle 0 - (-j0.1376)^* (j4.76)$$

$$= 2.18 - 0.654$$

$$= 1.526 \text{ pu}$$

OR
$$E_m = V_2 - (\hat{I}_m + \hat{I}_L) X_{T_2} - \hat{I}_m X_m$$
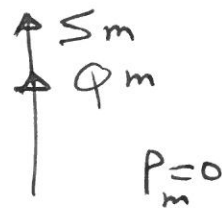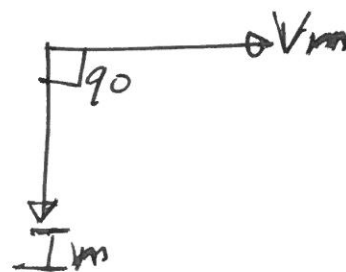
$$V_2 = V_m + (\hat{I}_m + \hat{I}_L) X_{T_2}$$



$$E_m = V_2 - (\hat{I}_m + \hat{I}_L) X_T - \hat{I}_m X_m$$

(1-32)

$$V_2 = (\hat{I}_m + \hat{I}_L) X_T + V_m$$

$$E_m = (\hat{I}_m + \hat{I}_L) X_T + V_m - (\hat{I}_m + \hat{I}_L) X_T - \hat{I}_m X_m$$


$$E_m = V_m - \hat{I}_m X_m$$

$$E_G = V_m + (\hat{I}_m + \hat{I}_L) * (Z + X_G)$$

$$Z = X_{T2} + X_{Line} + X_{T1}$$

Q)

In the Fig. below

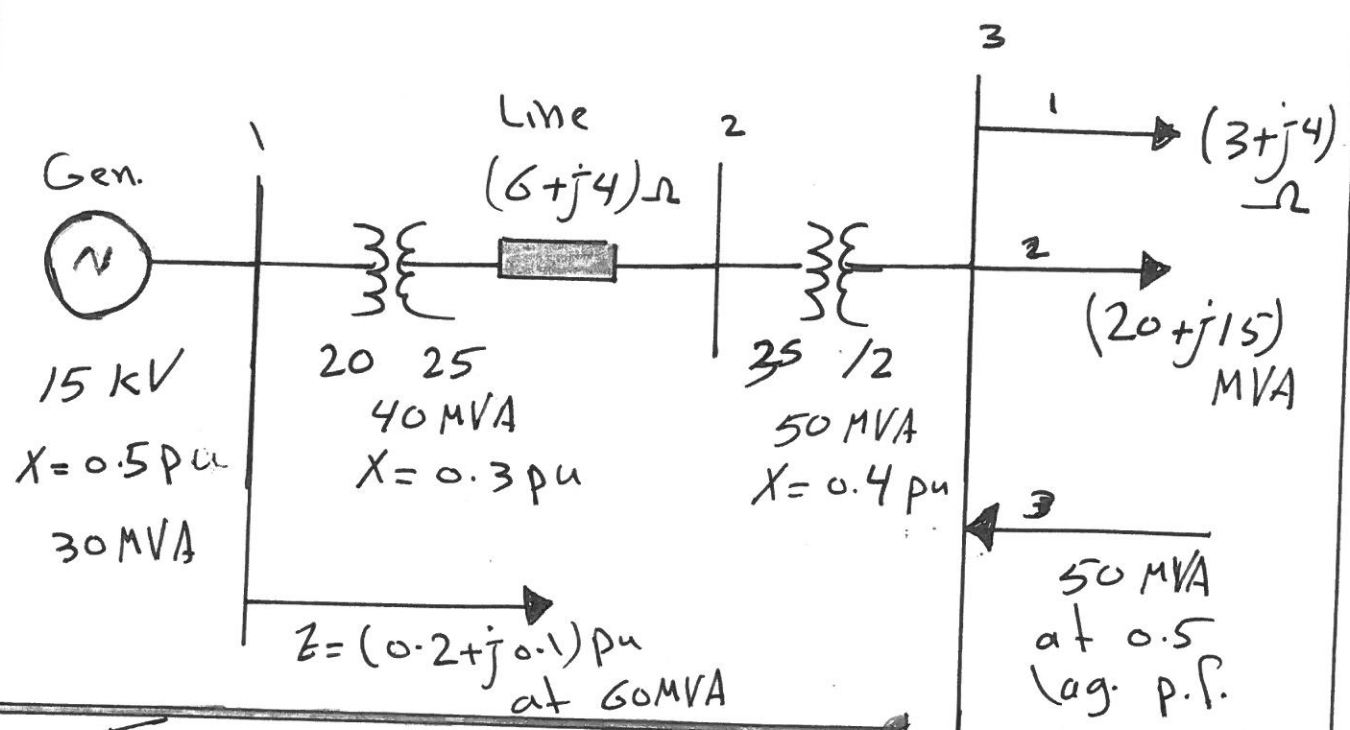

The base MVA is 100 MVA
 and the base voltage is at
 the line circuit is 40 kV
 The terminal voltage at
 bus bar 3 is 15 kV

Find

- 1- The perunit impedance
- 2- The line current (perunit and actual)
- 3- The actual generator current
- 4- The emf of the generator and motor
- 5- Draw the perunit ckt.

Sol)

$$V_{B1} = V_{B2} = 40 \times \frac{20}{25} = 32 \text{ kV}$$

$$V_{B3} = 40 \times \frac{12}{35} = 13.71 \text{ kV}$$

$$X_{G_{\text{new}}} = X_{\text{old}} \left(\frac{S_{B_{\text{new}}}}{S_{B_{\text{old}}}} \right) \left(\frac{V_{B_{\text{old}}}}{V_{B_{\text{new}}}} \right)^2$$

$$\begin{aligned} X_G &= 0.5 \left(\frac{100}{30} \right) \left(\frac{15}{32} \right)^2 \\ &= j 0.3662 \text{ pu} \end{aligned}$$

$$\begin{aligned} X_{T1_{\text{pri}}} &= 0.3 \left(\frac{100}{40} \right) \left(\frac{20}{32} \right)^2 \\ &= j 0.293 \text{ pu} \end{aligned}$$

$$\begin{aligned} X_{T2_{\text{pri}}} &= 0.4 \left(\frac{100}{50} \right) \left(\frac{35}{40} \right)^2 \\ &= j 0.6125 \text{ pu} \end{aligned}$$

$$Z_{B_{\text{line}}} = \frac{V_B^2}{S_B} = \frac{40^2}{100} = 16 \Omega$$

$$Z_{Line pu} = \frac{\text{actual}}{Base} = \frac{(6+j4)}{16} = 0.375 + j0.25 pu$$

$$Z_{Load 3-1} = (3+j4) \Omega$$

$$Z_B = \frac{V_B^2}{S_B} = \frac{13.71^2}{100} = 1.879 \Omega$$

$$Z_{Load pu 3-1} = \frac{\text{actual}}{Base} = \frac{3+j4}{1.879} = 1.596 + j2.128 pu$$

$$Z_{Load 3-2} = \frac{V_L^2}{S_L^*} = \frac{15^2}{(20+j15)^*} = \frac{15^2}{20-j15} = 7.2 + j5.4 \Omega$$

$$Z_{Load 3-2 Base} = \frac{V_B^2}{S_B} = \frac{13.71^2}{100} = 1.879 \Omega$$

$$Z_{Load pu 3-2} = \frac{\text{actual}}{Base} = \frac{7.2+j5.4}{1.879} = 3.83 + j2.87 pu$$

$$Z_{\text{Load } 3-3}^{\text{actual}} = \frac{VL^2}{\sum_{3\phi}^*} = \frac{15^2}{(50 \angle \cos^{-1} 0.5)^*}$$

$$= \frac{15^2}{(50 \angle 60^\circ)^*} = \frac{15^2}{50 \angle -60^\circ}$$

$$= 4.5 \angle 60^\circ \Omega$$

$$Z_{\text{Load } 3-3}^{\text{pu}} = \frac{\text{actual}}{\text{Base}} = \frac{4.5 \angle 60^\circ}{1.879}$$

$$= 2.395 \angle 60^\circ$$

$$= 1.197 + j2.074 \text{ pu}$$

$$Z_{\text{Load } 3-4}^{\text{pu}} = j0.4 \left(\frac{100}{25} \right) \left(\frac{15}{13.71} \right)^2$$

$$= j1.915 \text{ pu}$$

$$X_m = 0.3 \left(\frac{100}{15} \right) \left(\frac{15}{13.71} \right)^2 =$$

$$= \underline{\underline{j2.3941 \text{ pu}}}$$

$$I_G = \underset{\text{pu}}{I_{\text{Line}}} = \underset{\text{pu}}{I_{L3-1}} + \underset{\text{pu}}{I_{L3-2}} + \underset{\text{pu}}{I_{L3-3}} + \underset{\text{pu}}{I_{L3-4}} + \underset{\text{pu}}{I_m}$$

$$\underset{\text{pu}}{I_{L3-1}} = \frac{V_L \text{ pu}}{Z_{L3-1} \text{ pu}}$$

$$\underset{\text{pu}}{V_L} = \frac{V_{L \text{ actual}}}{V_{L \text{ Base}}}$$

$$= \frac{15}{13.71} = 1.094 \angle 0^\circ$$

$$\underset{\text{pu}}{I_{L3-1}} = \frac{1.094}{1.596 + j2.128}$$

$$\begin{aligned} \underset{\text{pu}}{I_{L3-1}} &= 0.246 - j0.329 \quad (\text{lagging}) \\ &= 0.4113 \angle -53.13^\circ \text{ pu} \end{aligned}$$

$$\underset{\text{pu}}{I_{L3-2}} = \frac{V_L}{Z_{L3-2}} = \frac{1.094 \angle 0^\circ}{7.2 + j5.4} =$$

$$= 0.0972 - j0.0729 \text{ pu}$$

$$\underset{\text{pu}}{I_{L3-3}} = \frac{V_L}{Z_{L3-3}} = \frac{1.094 \angle 0^\circ}{1.197 + j2.074}$$

$$= 0.2284 - j0.3957 \text{ pu}$$

$$\begin{aligned} \hat{I}_{L_{3-4}} \text{ pu} &= \frac{VL}{Z_{3-4}} = \frac{1.094 L_0}{j1.915} = \\ &= -j0.5713 \text{ pu} \end{aligned}$$


$$\hat{I}_m = \frac{\sum S_m^*}{V_m^*} \quad \text{where} \quad S_m = V_m \hat{I}_m^*$$

$$\sum S_m \text{ pu} = \frac{S_m \text{ actual}}{S_m \text{ Base}} = \frac{15}{100} = 0.15 \text{ pu}$$

$$\hat{I}_m = \frac{(0.15 \angle +90^\circ)^*}{1.094 L_0} = 0.1371 \angle -90^\circ$$

where $X_m = j2.394$

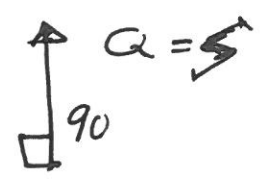means that this motor have an inductive effect (lagging p.f) pure inductive in this case.



$$\begin{aligned} I_G = \hat{I}_{Lme} = & (0.246 - j0.329) + (0.0972 - j0.0729) \\ & - (0.2284 - j0.3957) + (-j0.5713) \\ & + (-j0.1371) = \end{aligned}$$

$$I_G = I_{Line} = 0.1148 - j0.7146 \text{ pu}$$

$$V_1 = V_3 + I_{Line} \times \underbrace{(X_{T2} + Z_{Line} + X_{T1})}_Z$$

$$V_3 = 1.094 \angle 0$$

$$I_{Line} = 0.1148 - j0.7146$$

$$Z = (j0.6125) + (0.375 + j0.25) + (j0.293)$$

$$Z = 0.375 + j1.155 \text{ pu}$$

$$V_1 = 1.094 + (0.1148 - j0.7146) \times (0.375 + j1.155)$$

$$= \underline{1.9628 - j0.135} \text{ pu} = 1.967 \angle -3.93^\circ \text{ pu}$$

$$= 1.967 \times 32 = \underline{62.95} \text{ kV}$$

$$Z_{L1-1} = (0.2 + j0.1) \times \left(\frac{100}{60}\right) \left(\frac{62.95}{32}\right)^2$$

$$= \underline{1.289 + j0.645} \text{ pu}$$

$$E_g = V_1 + I_G X_G$$

$$= (1.9628 - j0.135) + (0.1148 - j0.7146) \times j0.3662$$

$$E_g = 2.2245 - j0.093 \text{ p.u.}$$

$$2.2264 \angle -2.393^\circ \text{ p.u.}$$

$$E_{g \text{ actual}} = 2.264 \times 32$$

$$= 71.244 \text{ kV}$$

$$I_G = (1.9628 - j0.135) \times I_B$$

$$I_B = \frac{S_B}{\sqrt{3} V_B \text{ gen.}} = \frac{100 \times 10^6}{\sqrt{3} \times 32 \times 10^3} \text{ at the generator ckt.}$$

$$I_B = 1.80427 \times 10^3 \text{ A} = 1804.27 \text{ A}$$

$$I_G = (1.9628 - j0.135) \times 1804.27 = 3541.4 - j243.57 \text{ A}$$

1-41

$$\hat{I}_{\text{Line actual}} = (1.9628 - j0.135) * \hat{I}_B$$

$$\hat{I}_{\text{actual}} = I_{\text{pu}} * \hat{I}_B$$

$$\frac{\hat{I}_B}{\text{Line}} = \frac{S_B}{\sqrt{3} V_B \text{Line}} = \frac{100 * 10^6}{\sqrt{3} * 40 * 10^3}$$

$$= 1443.41 \text{ A}$$

$$\hat{I}_{\text{Line actual}} = 1443.41 * (1.9628 - j0.135)$$

$$= 2833.1 - j194.86 \text{ A}$$

$$\text{emf}_{\text{motor pu}} = E_m = V_m - I_m X_m$$

$$= 1.094 \text{ pu} - (-j0.1371) * (j2.394)$$

$$= 0.7657 \text{ pu}$$

$$\text{emf}_m \text{ actual} = 0.7657 * 13.71 \text{ kV}$$

$$= 10.498 \text{ kV}$$

