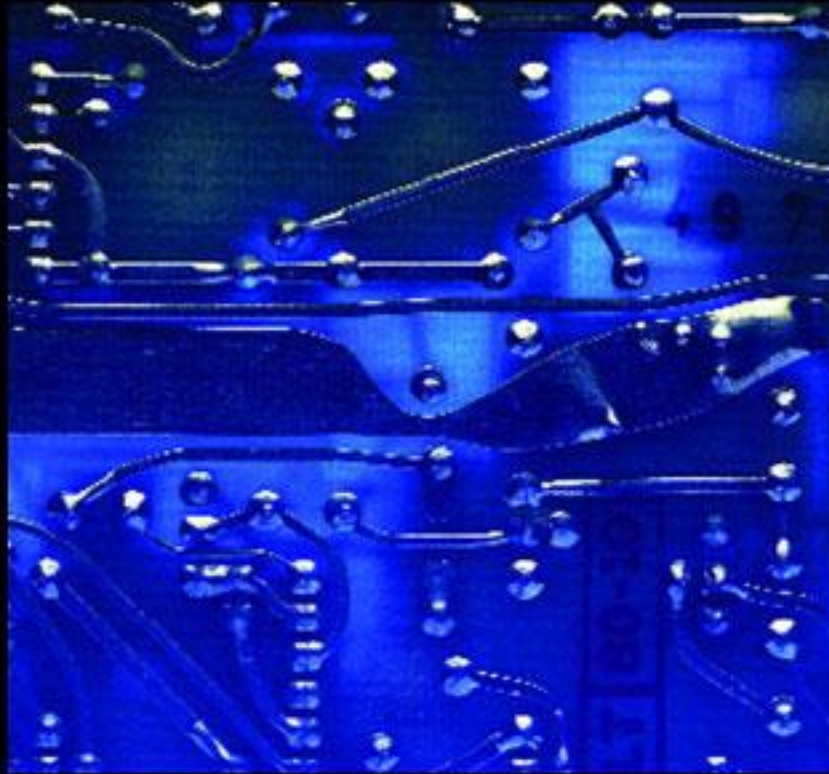


ELECTRONIC DEVICES AND CIRCUIT THEORY

TENTH EDITION



BOYLESTAD

PEARSON

Chapter 5: BJT AC Analysis

Islamic University of Gaza


Dr. Talal Skaik

BJT Transistor Modeling


- A model is an equivalent circuit that represents the AC characteristics of the transistor.
- A model uses circuit elements that approximate the behavior of the transistor.
- There are two models commonly used in small signal AC analysis of a transistor:
 - **r_e model**
 - **Hybrid equivalent model**

BJT Transistor Modeling

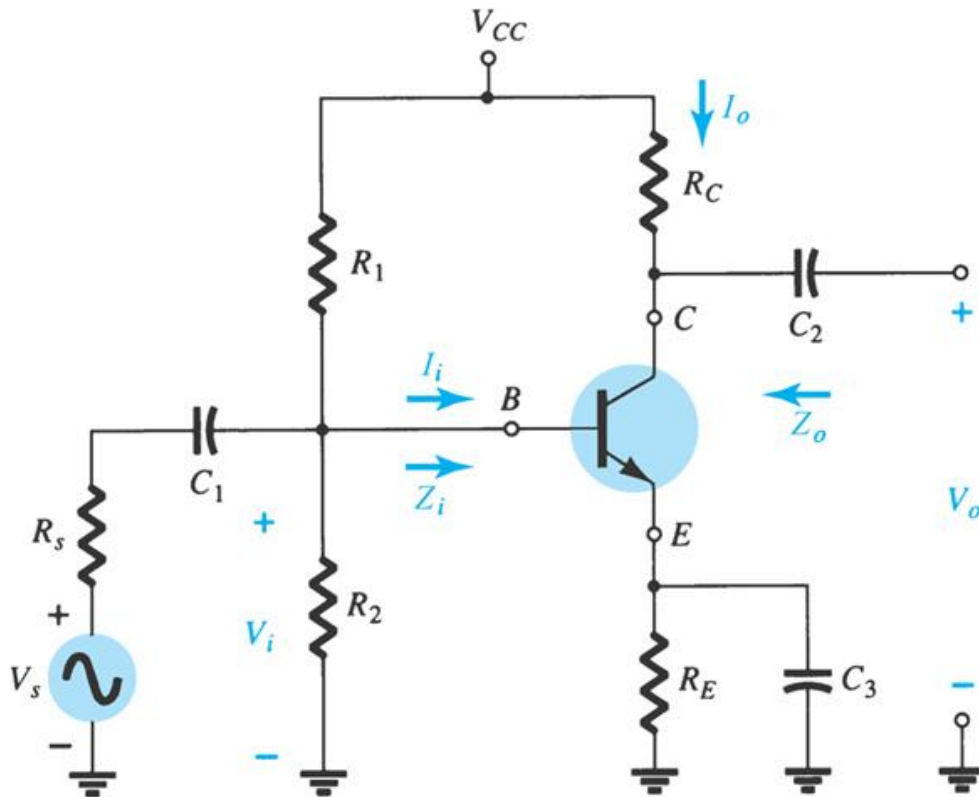Capacitors chosen with very small reactance at the frequency of application \rightarrow replaced by low-resistance or short circuit.





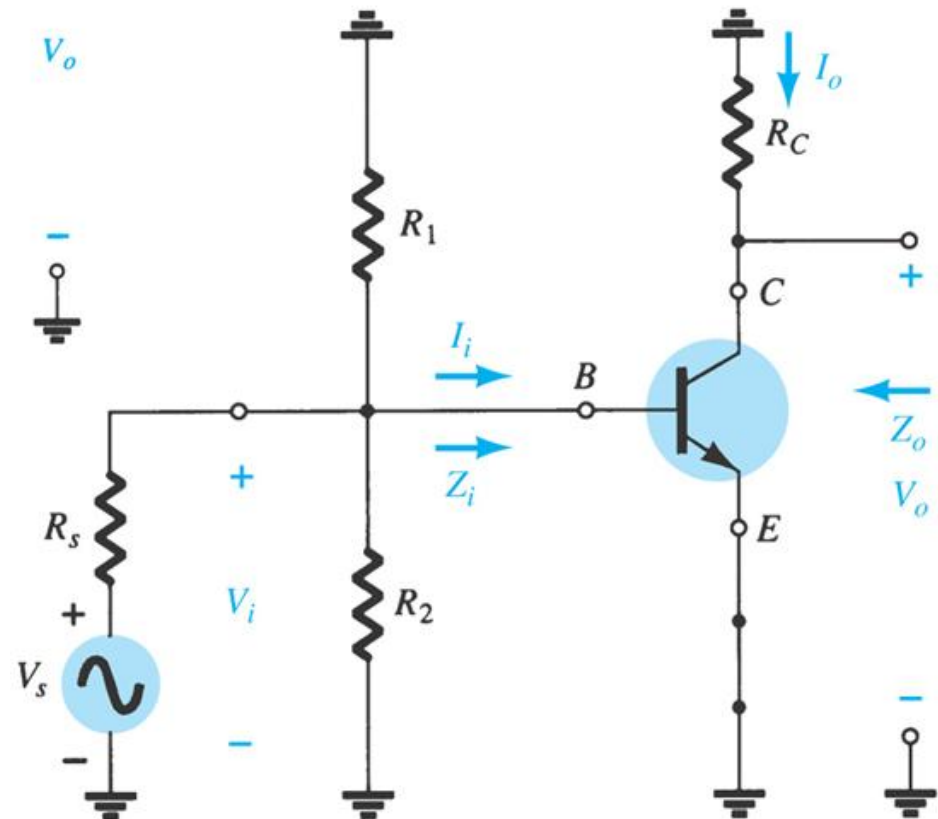Removal of the dc supply and insertion of the short-circuit equivalent for the capacitors.




BJT Transistor Modeling

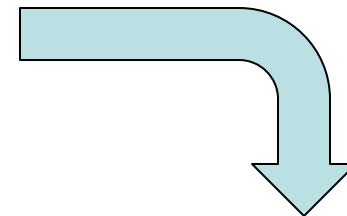
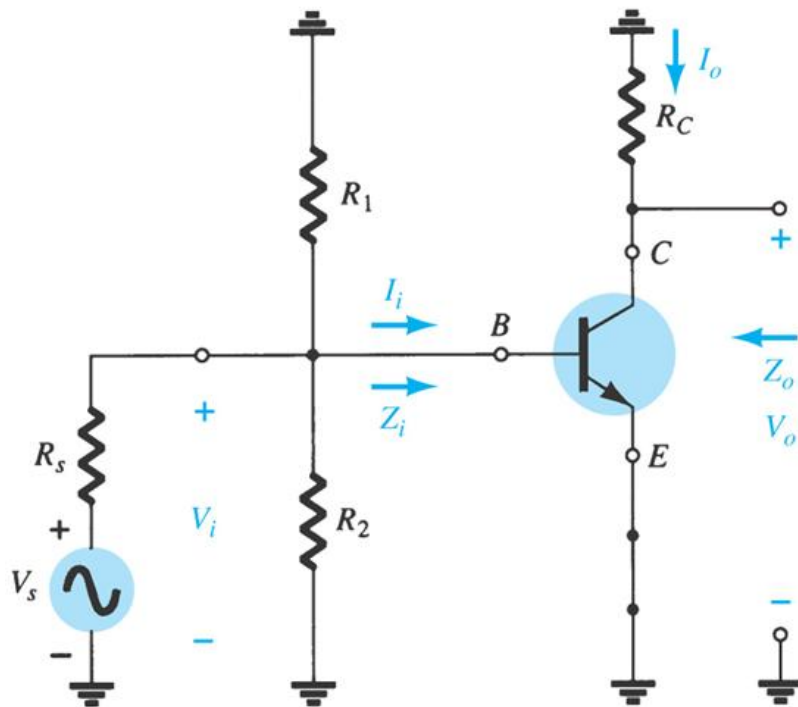
Circuit redrawn for small-signal ac analysis



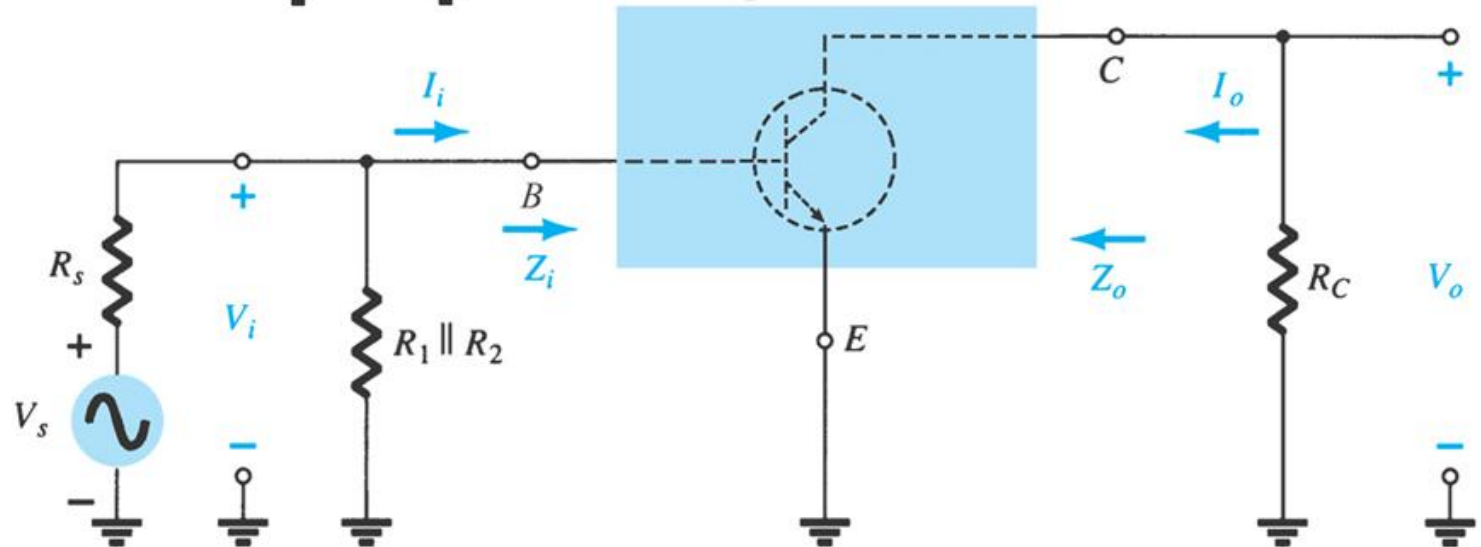Transistor small-signal ac equivalent circuit



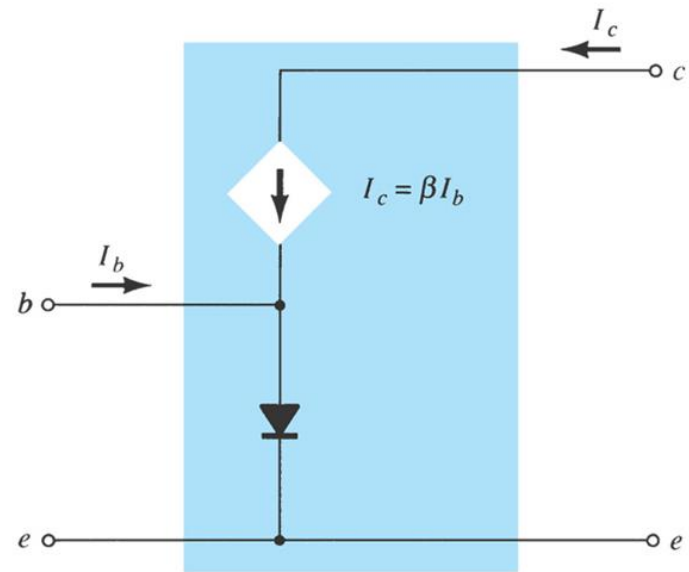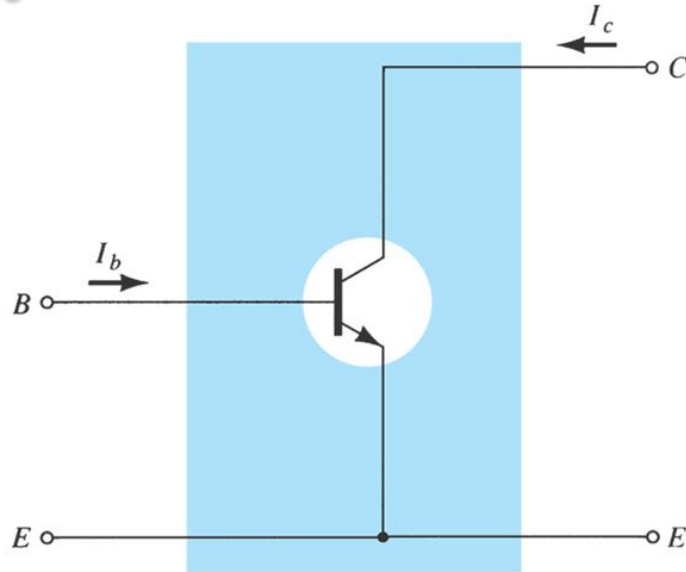
The r_e Transistor Model Common Emitter Configuration



$$Z_i = \frac{V_i}{I_b} = \frac{V_{be}}{I_b}$$



$$V_{be} = I_e r_e = (I_c + I_b) r_e = (\beta I_b + I_b) r_e \\ = (\beta + 1) I_b r_e$$
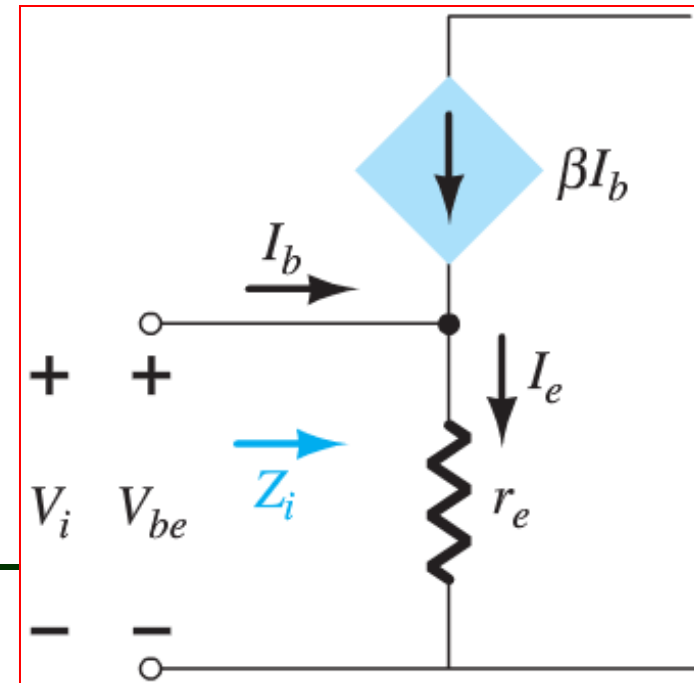
$$Z_i = \frac{V_{be}}{I_b} = \frac{(\beta + 1) I_b r_e}{I_b} = (\beta + 1) r_e \approx \beta r_e$$



The r_e Transistor Model Common Emitter Configuration

$$r_e = \frac{26 \text{ mV}}{I_E}$$

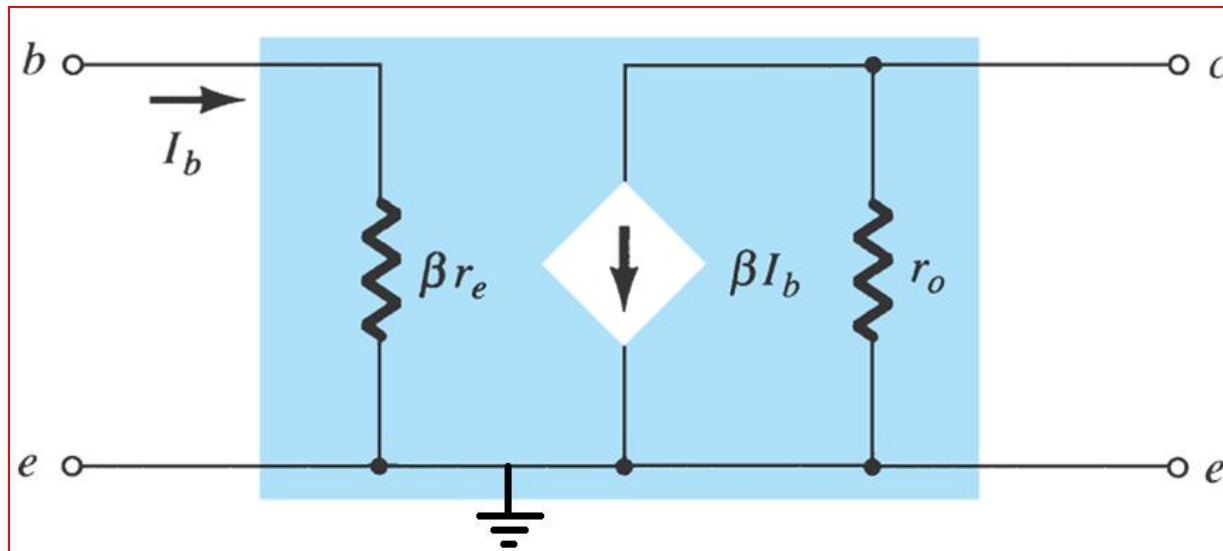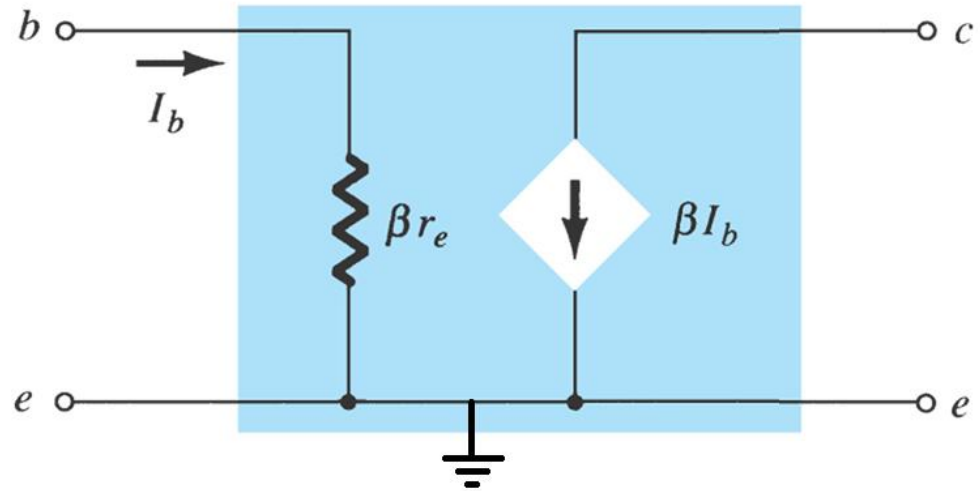


The r_e Transistor Model

Common Emitter Configuration



$$\text{slope} = \frac{\Delta I_C}{\Delta V_{CE}} = \frac{1}{r_0}$$

$$r_0 = \frac{\Delta V_{CE}}{\Delta I_C}$$


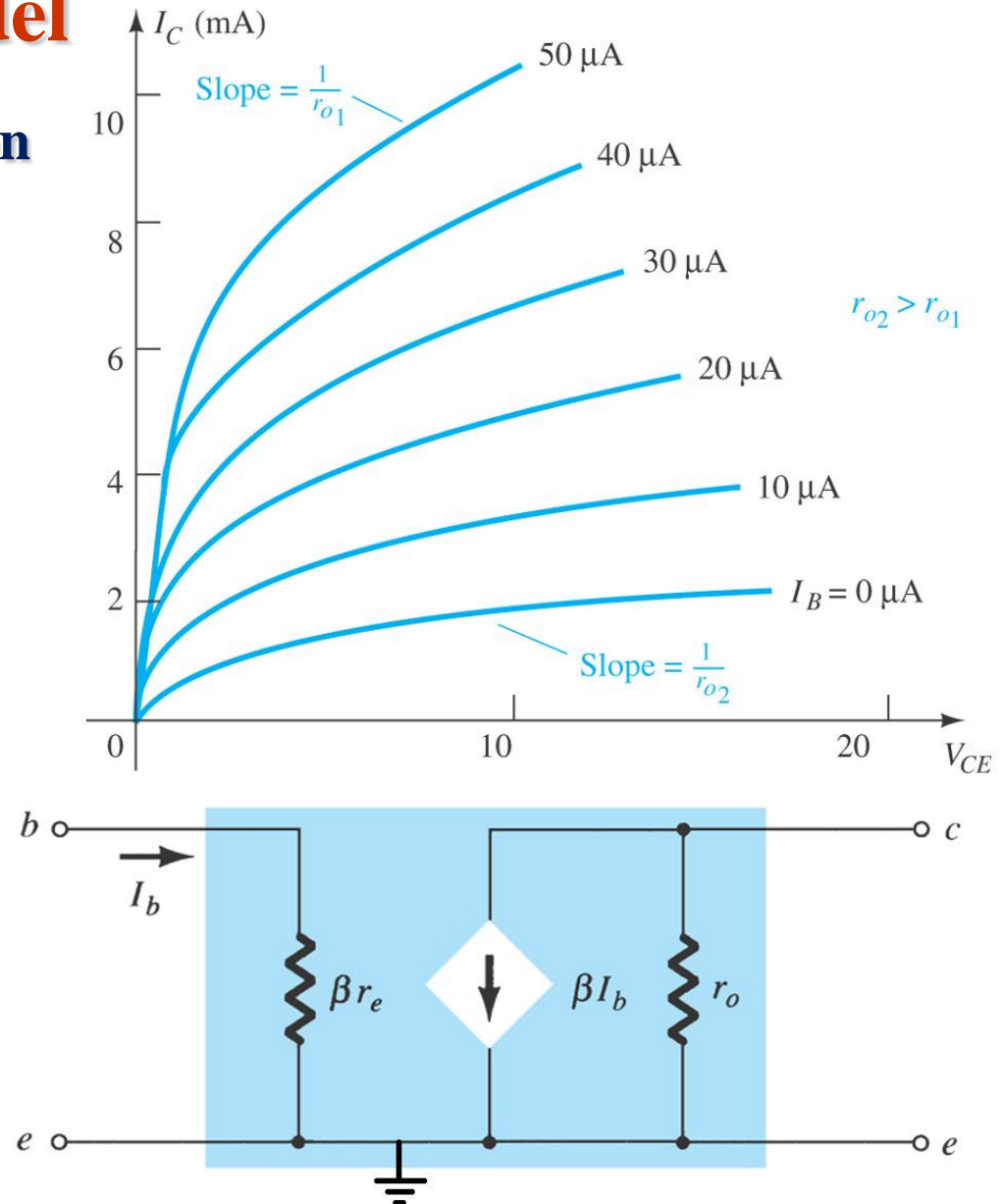
The output resistance r is typically in the range of 40 k Ω to 50 k Ω



Common-Base Configuration

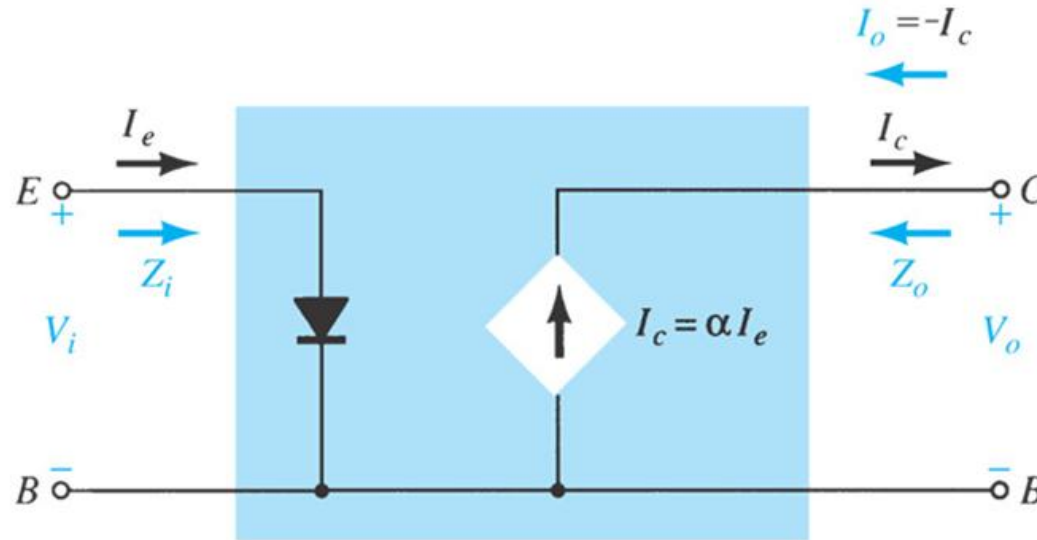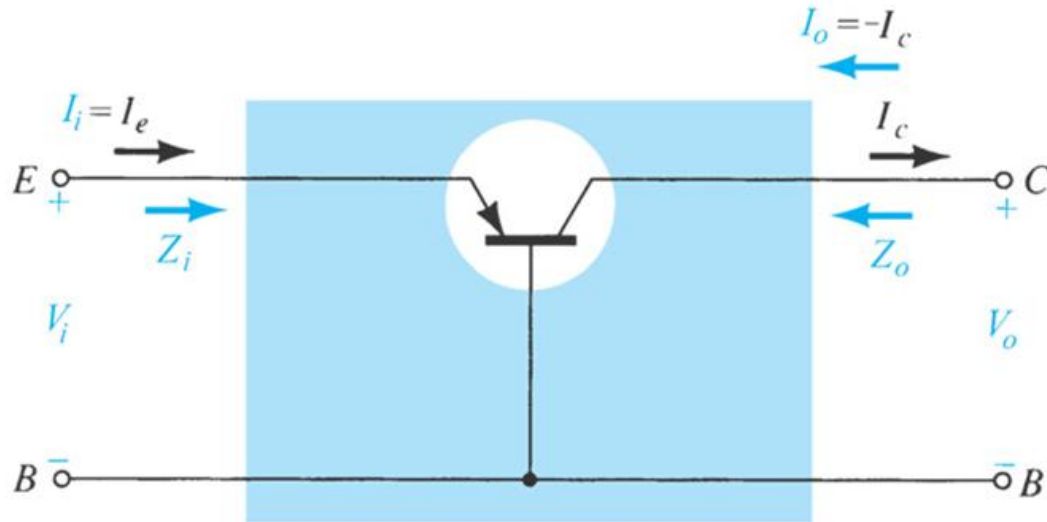


Common-Base Configuration

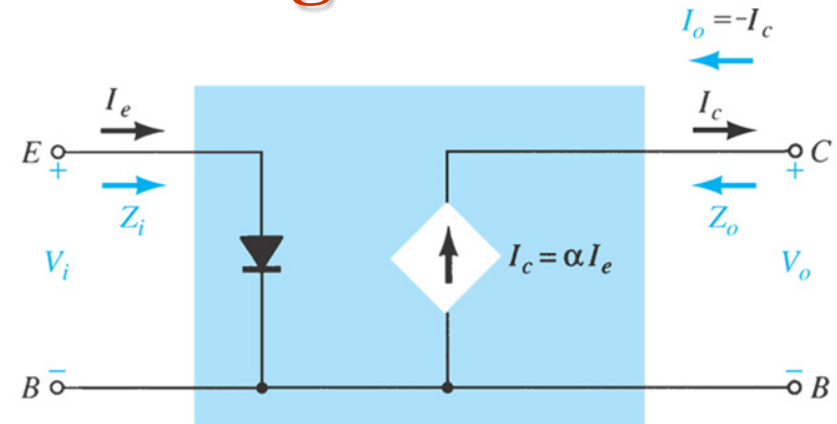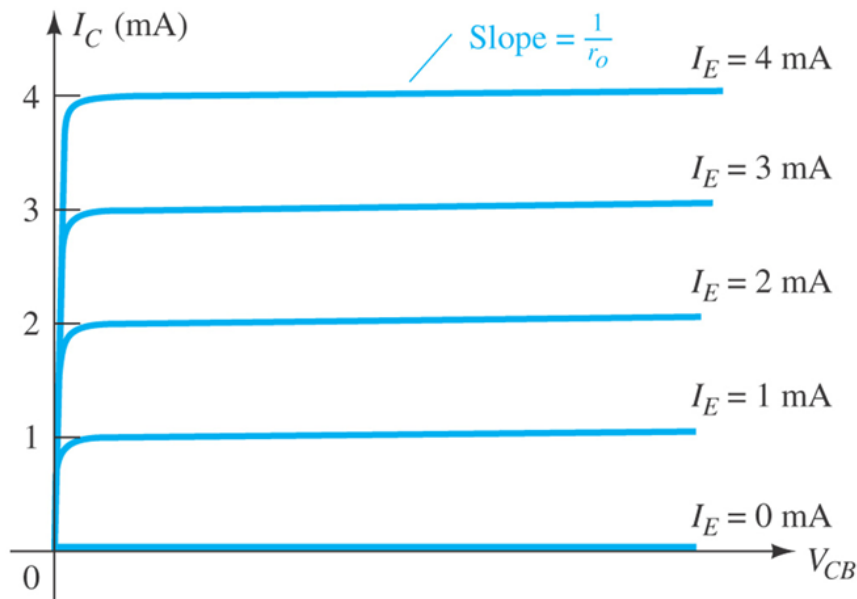


The output resistance r_o is quite high, typically extend into the megaohm range.


Common Base r_e equivalent circuit

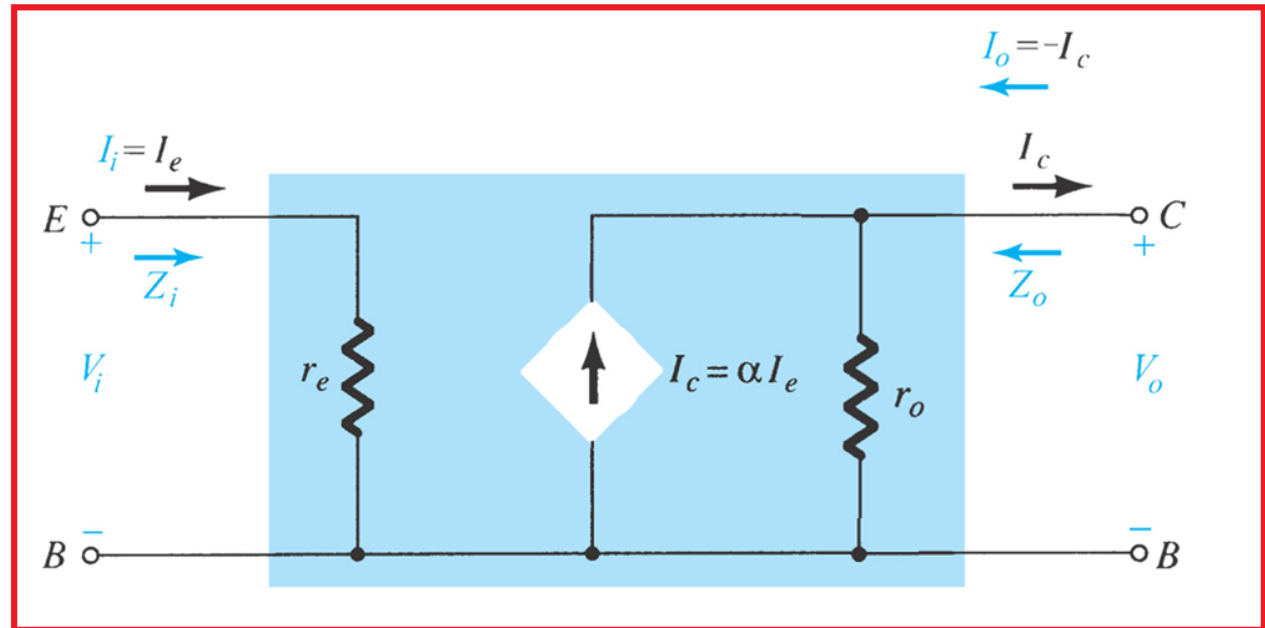

Common Emitter Fixed Bias Configuration

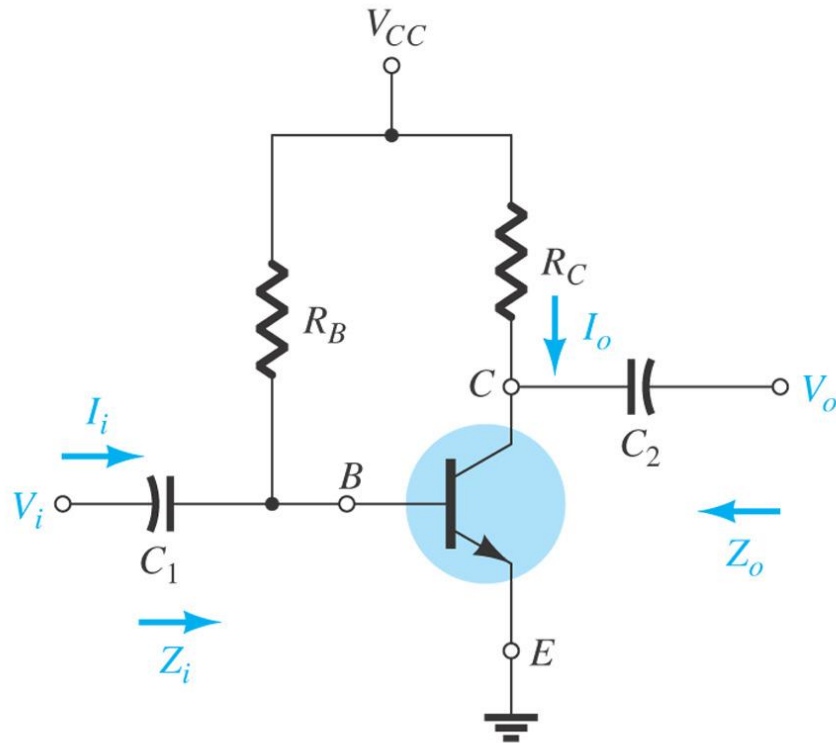


Common-emitter fixed-bias configuration.

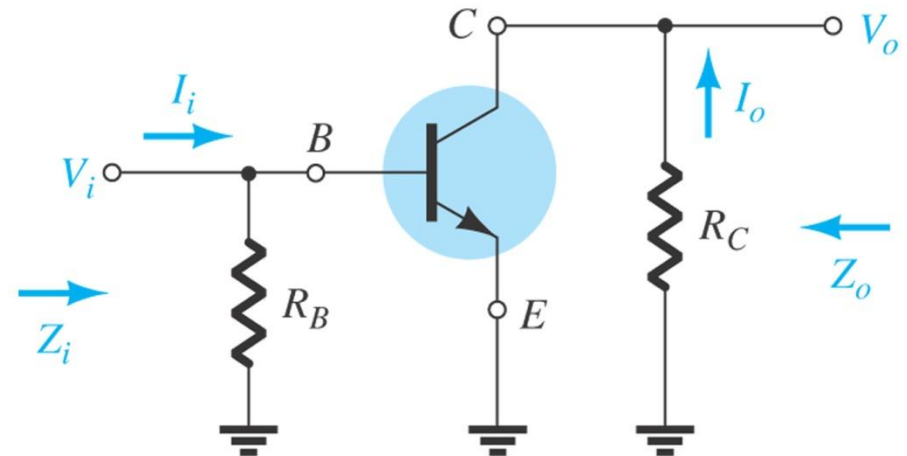

Network after the removal of the effects of V_{CC} , C_1 and C_2 .

Common Emitter Fixed Bias Configuration

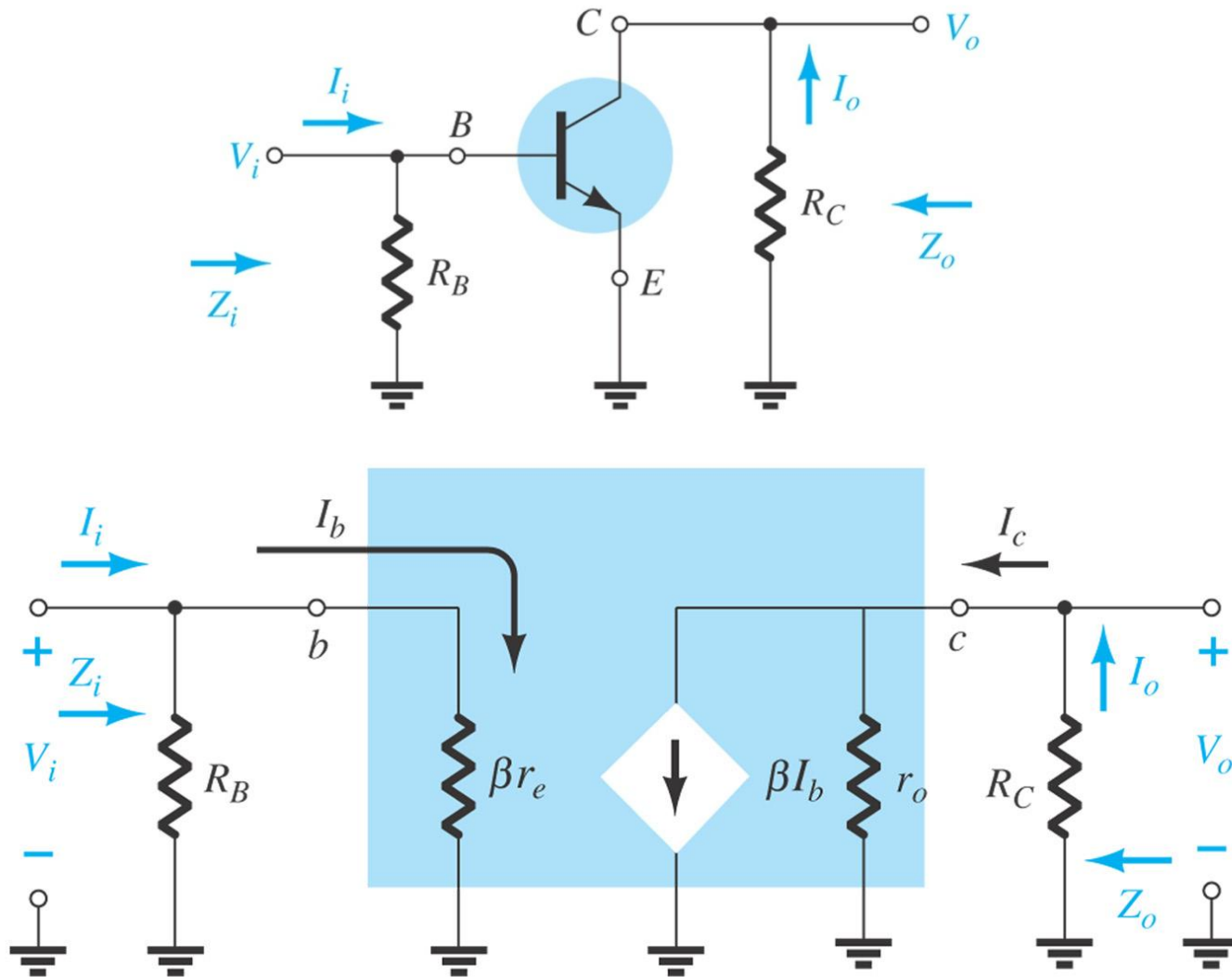

Substituting the r_e model into the network.

Common Emitter Fixed Bias Configuration

Input impedance:

$$Z_i = R_B \parallel \beta r_e$$

$$Z_i \cong \beta r_e \mid R_E \geq 10\beta r_e$$

Output impedance:


$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \mid r_o \geq 10R_C$$

Voltage gain:


$$V_o = -\beta I_b (R_C \parallel r_o) , \quad I_b = \frac{V_i}{\beta r_e} , \quad V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$
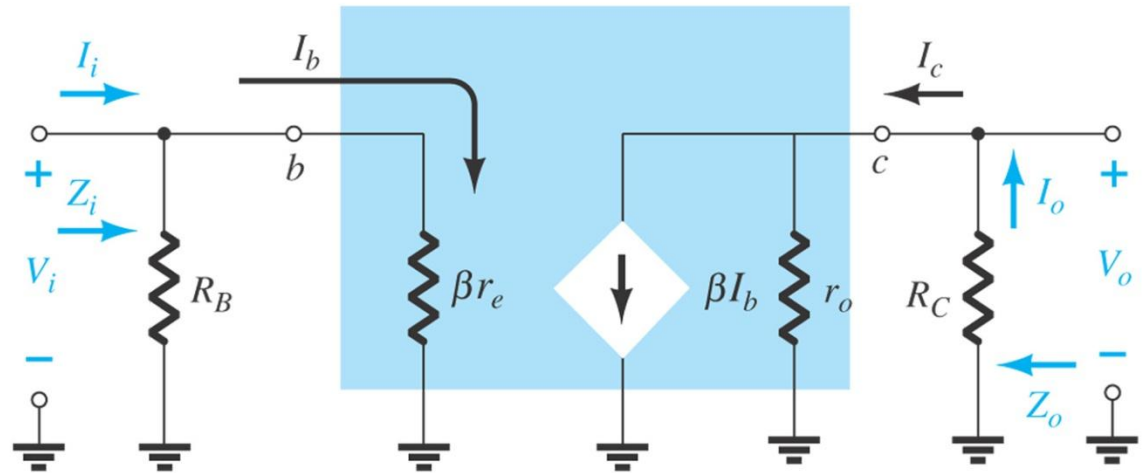
$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e} , \quad A_v = -\frac{R_C}{r_e} \mid r_o \geq 10R_C$$



Common Emitter Fixed Bias Configuration
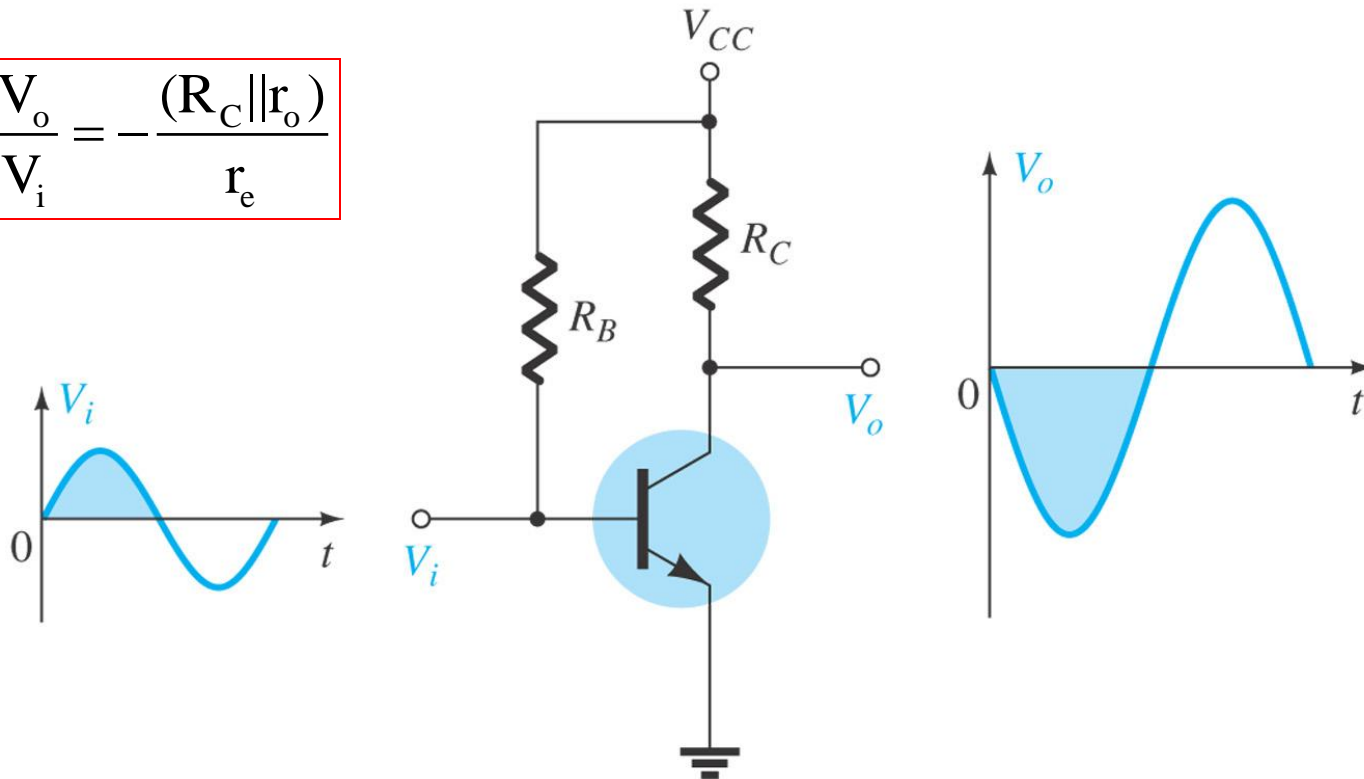
$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$




Demonstrating the 180° phase shift between input and output waveforms.


Example 5.1

Determine r_e , Z_i (with $r_o = \infty$), Z_o (with $r_o = \infty$), A_v (with $r_o = \infty$).



Repeat with $r_o = 50 \text{ k}\Omega$.

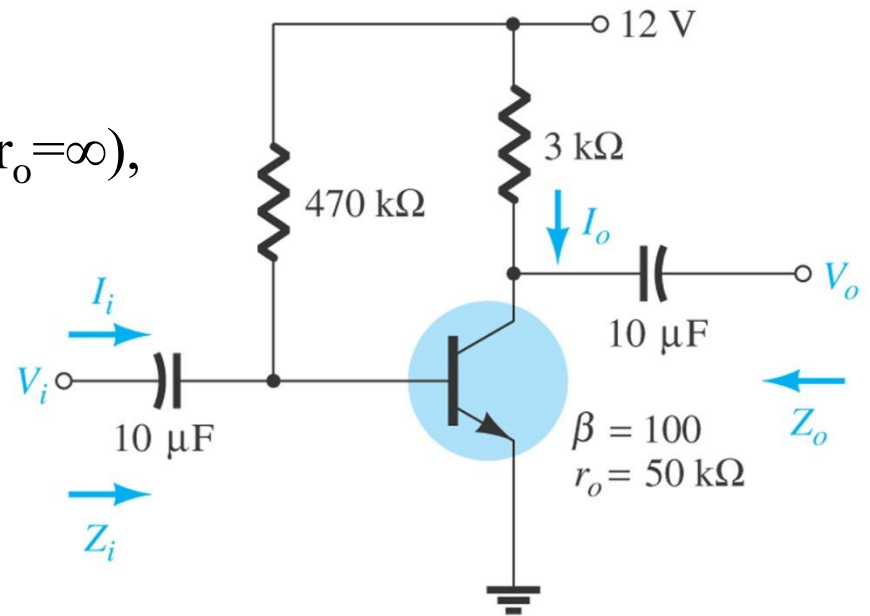

Example 5.1 - Solution

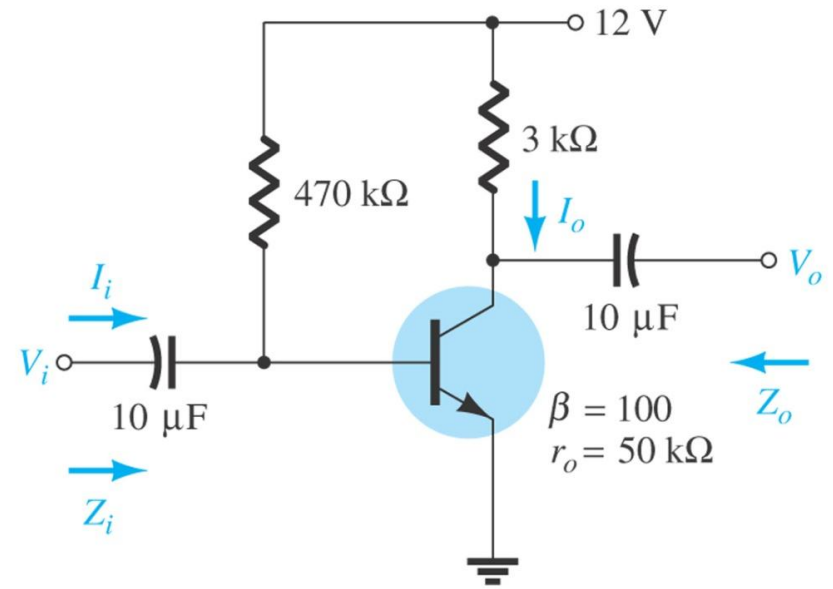

Common-Emitter Voltage-Divider Bias

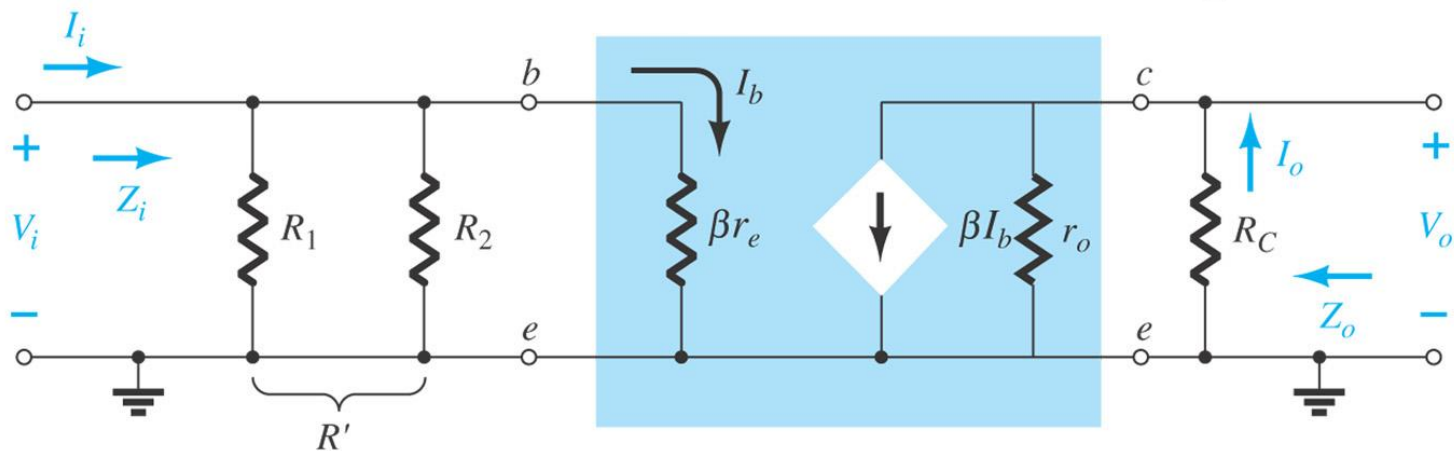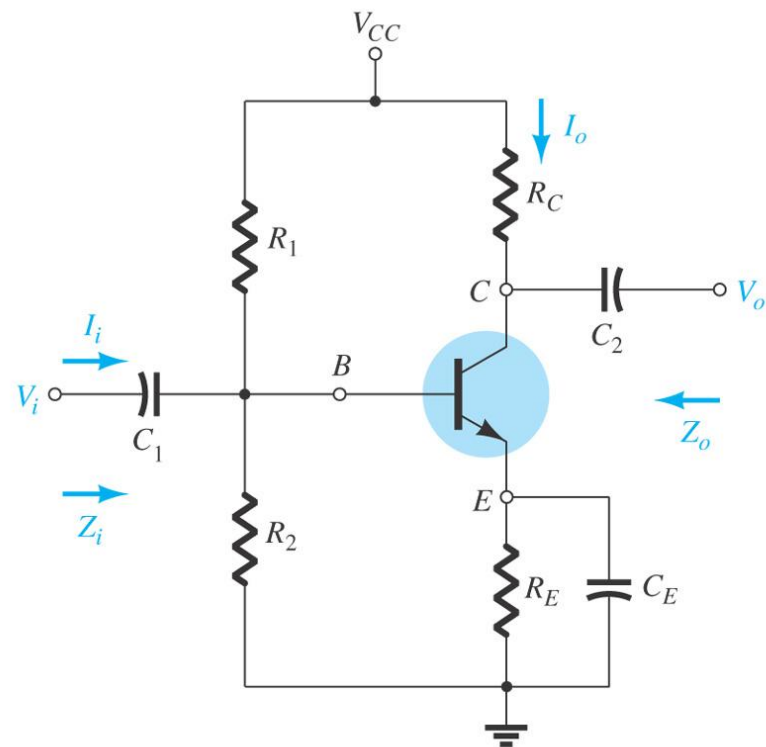


r_e model requires you to determine β , r_e , and r_o .

Common-Emitter Voltage-Divider Bias

Input impedance:

$$R' = R_1 \parallel R_2$$

$$Z_i = R' \parallel \beta r_e$$

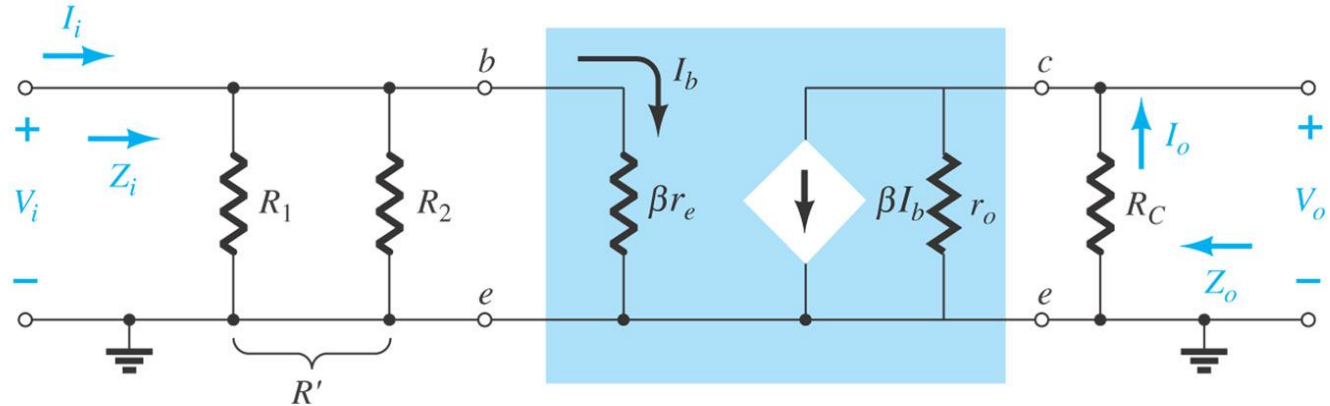

Output impedance:

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \big|_{r_o \geq 10R_C}$$


Voltage gain:

$$V_o = -\beta I_b (R_C \parallel r_o) , \quad I_b = \frac{V_i}{\beta r_e} , \quad V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$


$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e} , \quad A_v = -\frac{R_C}{r_e} \big|_{r_o \geq 10R_C}$$

Example 5.2



Determine r_e , Z_i , Z_o (with $r_o = \infty$), A_v (with $r_o = \infty$). Repeat with $r_o = 50 \text{ k}\Omega$.

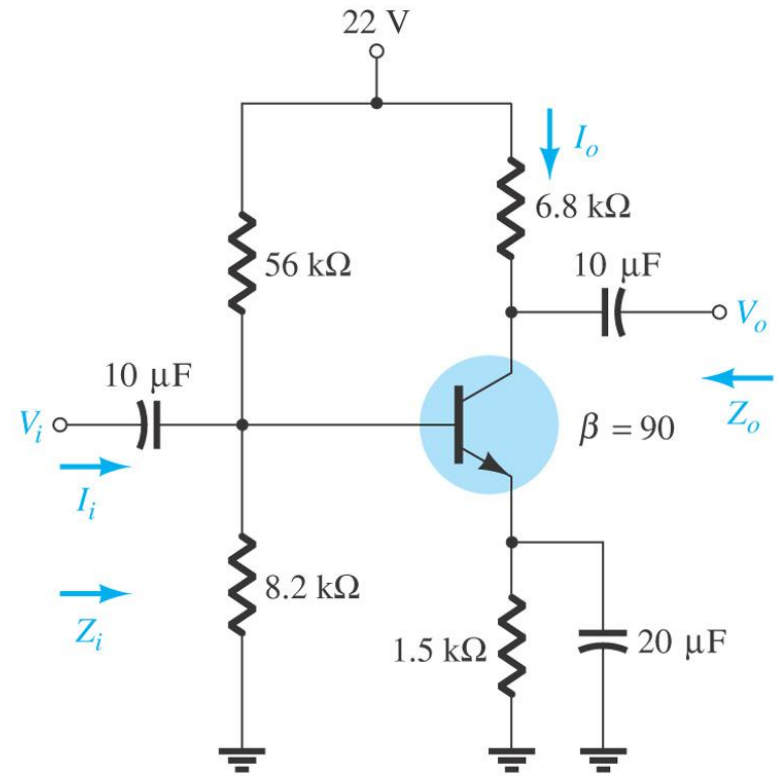

Example 5.2 - Solution

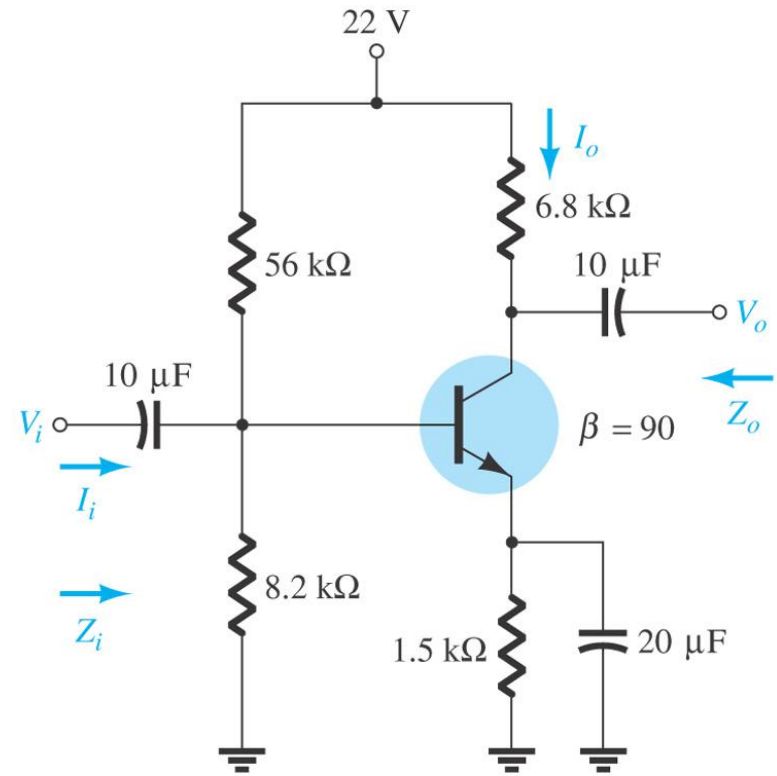

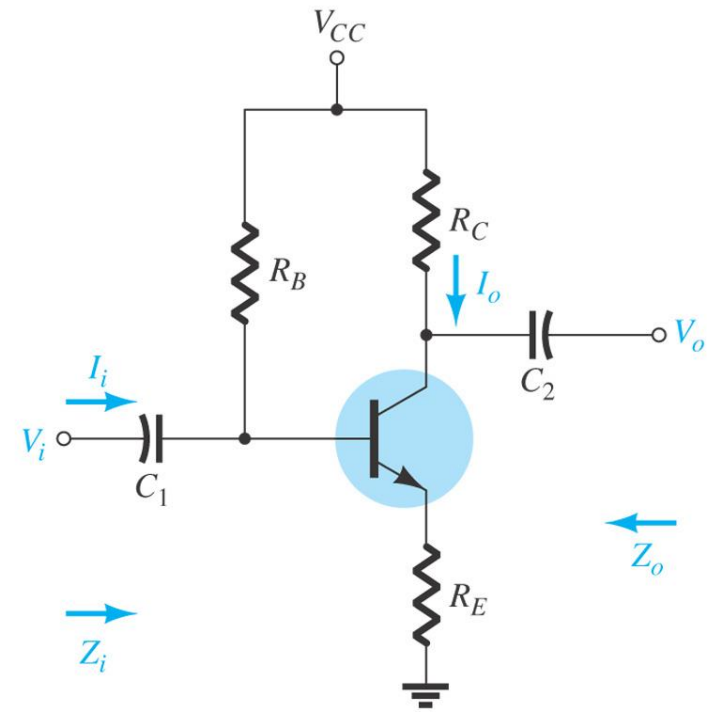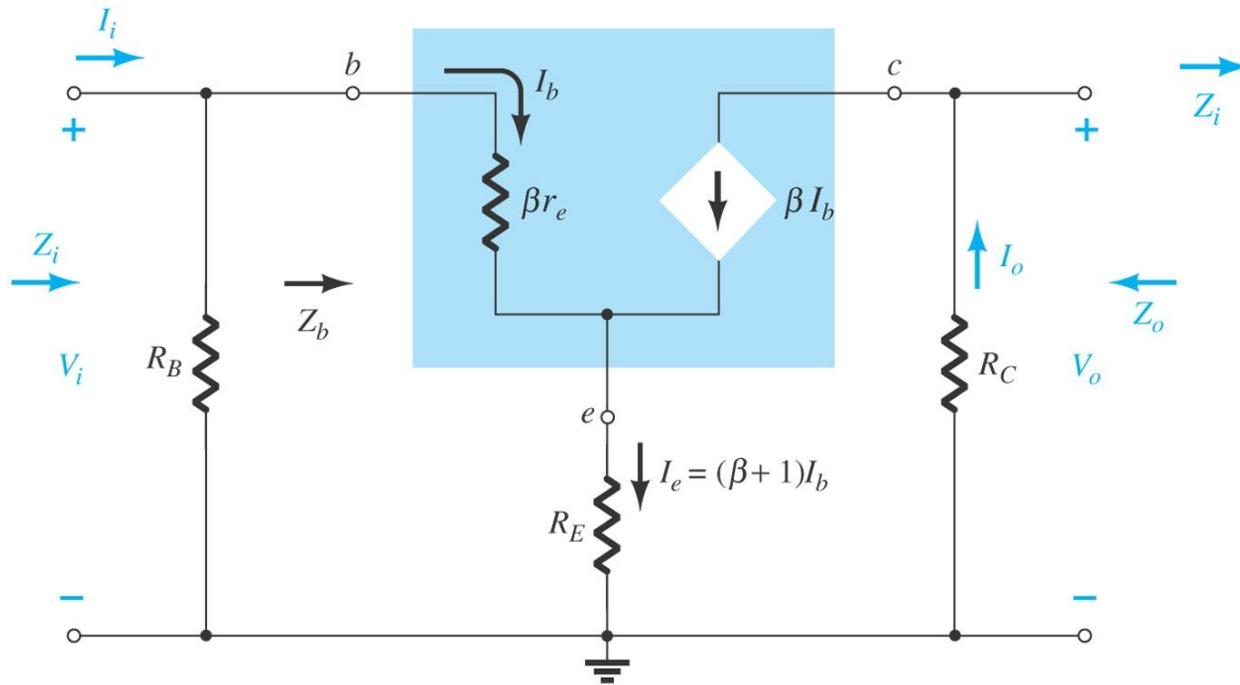Common-Emitter Emitter-Bias Configuration



Impedance Calculations

Input impedance:


$$V_i = I_b \beta r_e + I_e R_E$$

$$V_i = I_b \beta r_e + (\beta + 1) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1) R_E$$

$$Z_b \cong \beta r_e + \beta R_E = \beta (r_e + R_E)$$
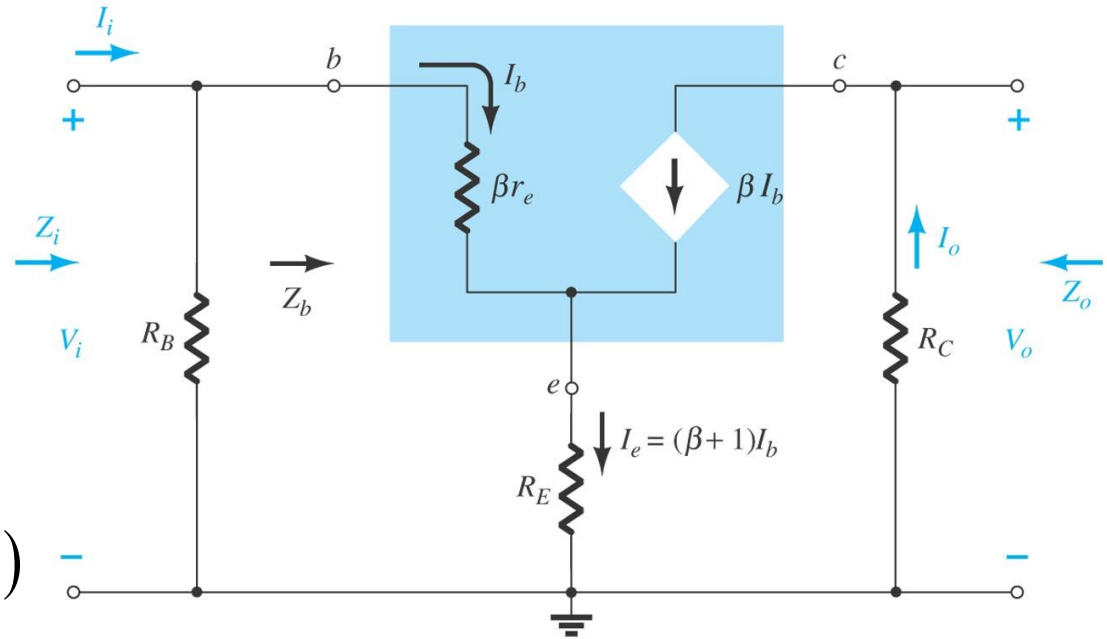
$$Z_b \cong \beta R_E \quad \text{for } R_E \gg r_e$$



Output impedance:

$$Z_i = R_B \parallel Z_b$$

$$Z_o = R_C$$

Gain Calculations

Voltage gain:

$$V_o = -I_o R_C = -\beta I_b R_C$$

$$V_o = -\beta \left(\frac{V_i}{Z_b} \right) R_C$$


$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

substituting $Z_b \cong \beta(r_e + R_E)$

$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e + R_E}$$


and for the approximation $Z_b \cong \beta R_E$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$$

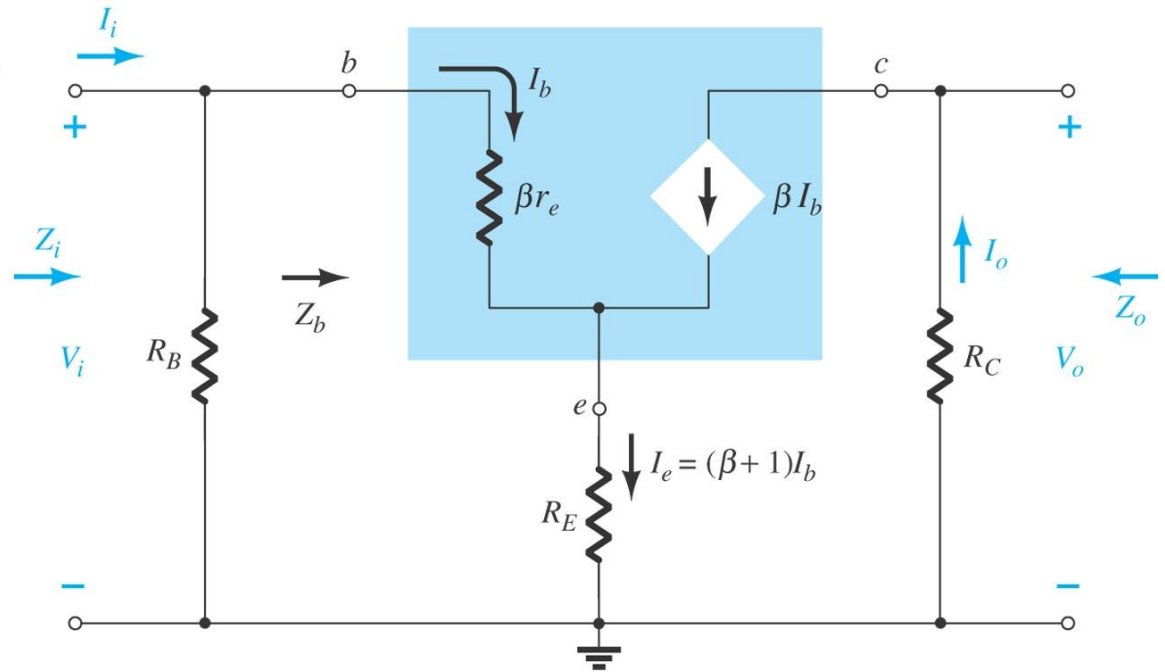


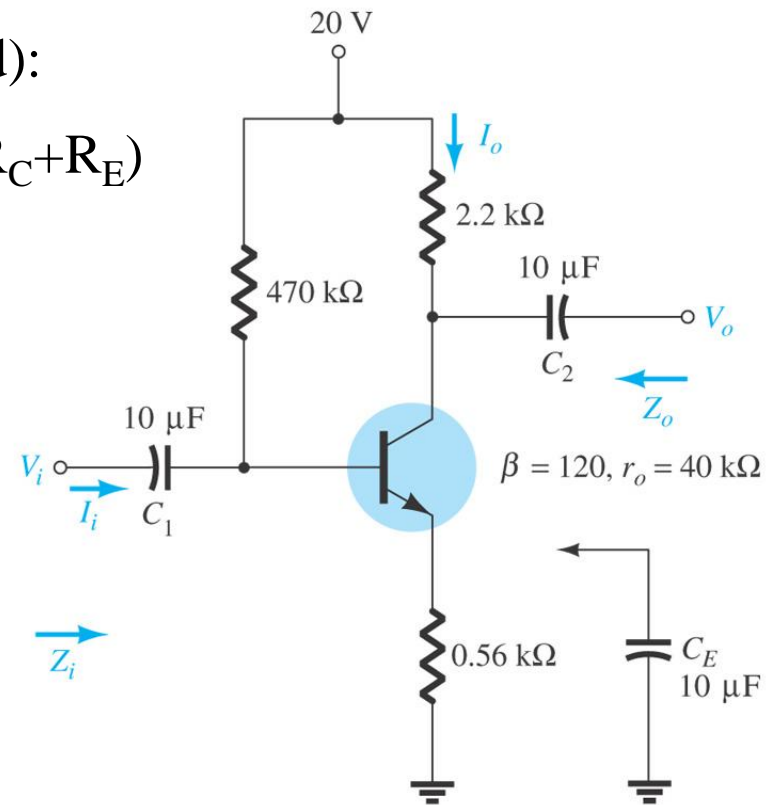Example 5.3 Without C_E (unbypassed):

Determine r_e , Z_i , Z_o , A_v . ignore r_o for $r_o \geq 10(R_C + R_E)$



Emitter-Follower Configuration

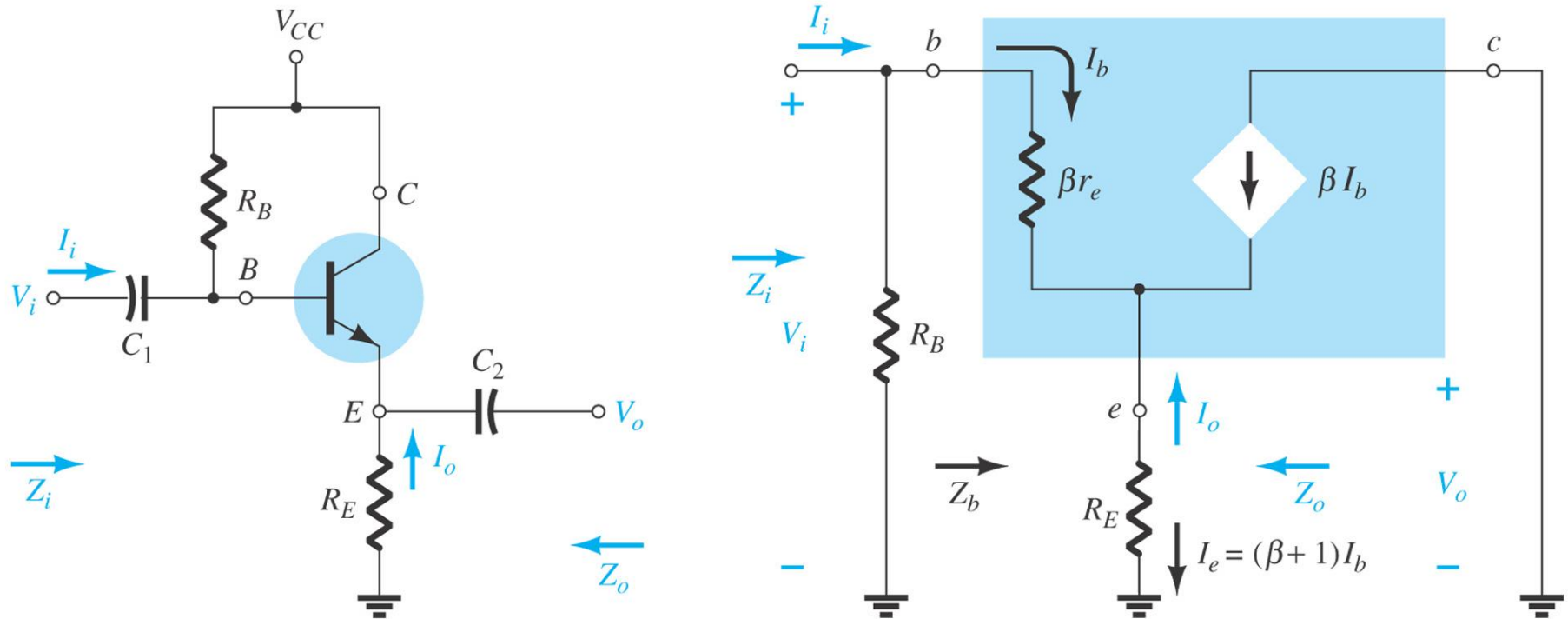

- This is also known as the common-collector configuration.
- The input is applied to the base and the output is taken from the emitter.
- There is no phase shift between input and output.

Impedance Calculations


Input impedance:

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E)$$
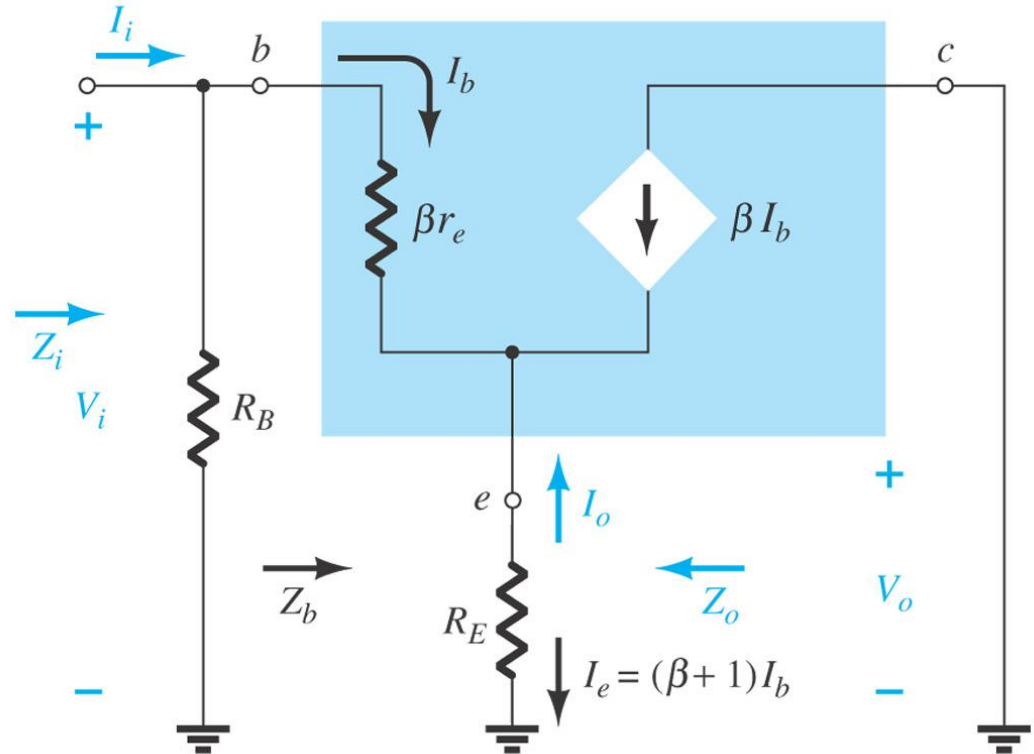
$$Z_b \cong \beta R_E \quad (\text{for } R_E \gg r_e)$$



Impedance Calculations

Output impedance:

$$I_b = \frac{V_i}{Z_b}, I_e = (\beta + 1)I_b$$

$$= (\beta + 1) \frac{V_i}{Z_b}$$



$$I_e = \frac{(\beta + 1)V_i}{\beta r_e + (\beta + 1)R_E}$$

since $(\beta + 1) \cong \beta$

$$I_e = \frac{V_i}{r_e + R_E}$$

To determine Z_o , V_i is set to zero
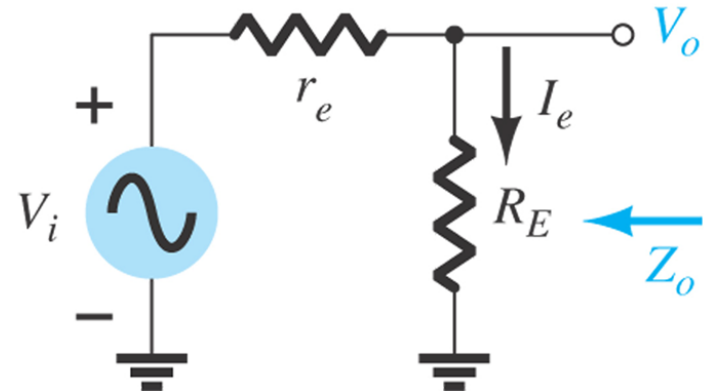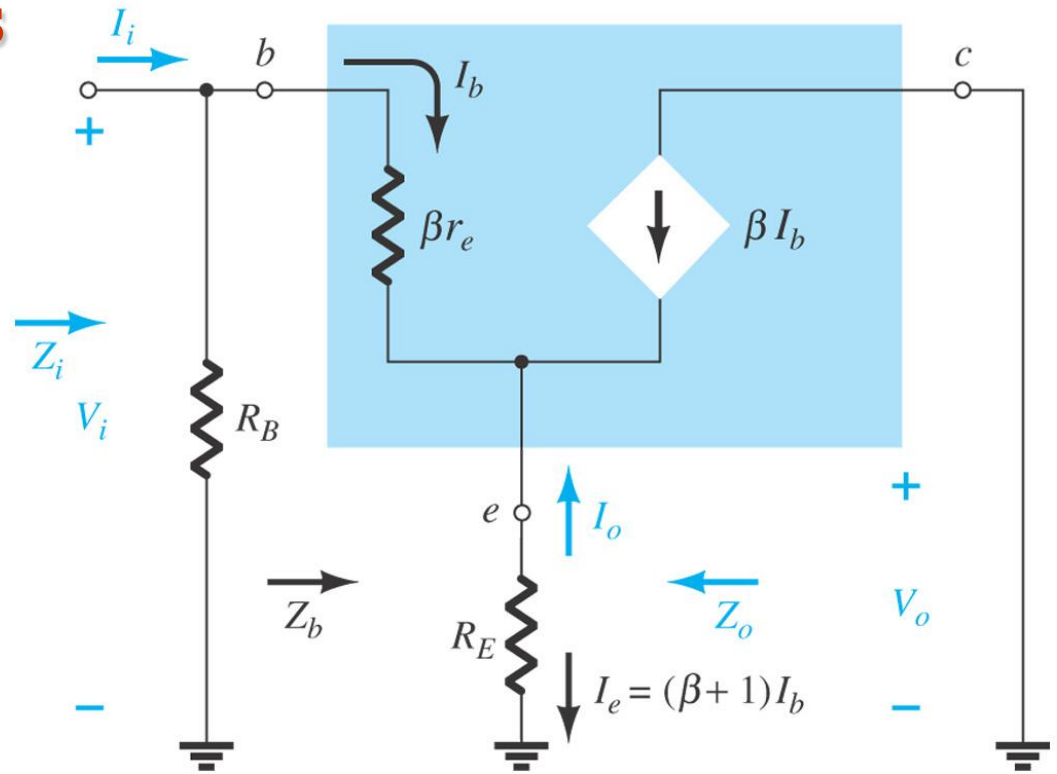
$$Z_o = R_E \parallel r_e, \quad Z_o \cong r_e \mid R_E \gg r_e$$





Gain Calculations

Voltage gain:


$$V_o = \frac{R_E}{R_E + r_e} V_i$$

$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$$

$$A_v = \frac{V_o}{V_i} \cong 1 \Big|_{R_E \gg r_e, R_E + r_e \cong R_E}$$

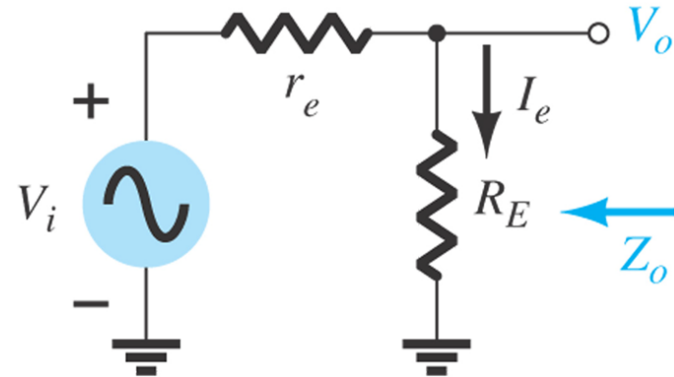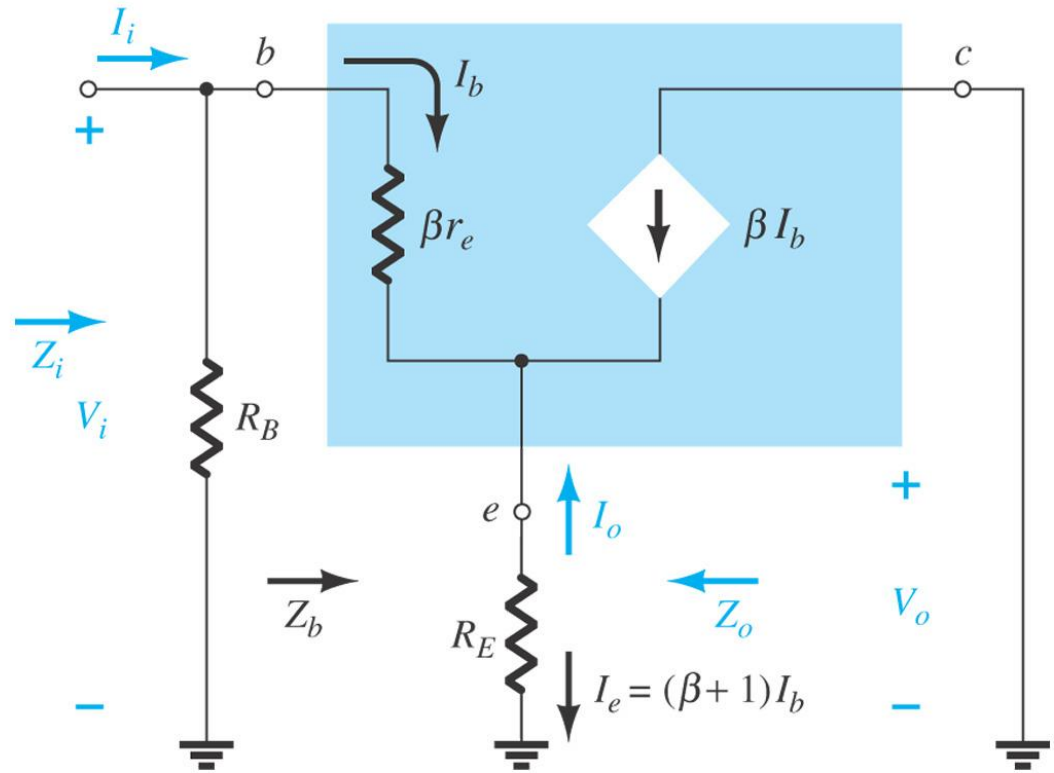

Example 5.7 Determine r_e , Z_i , Z_o , A_v .

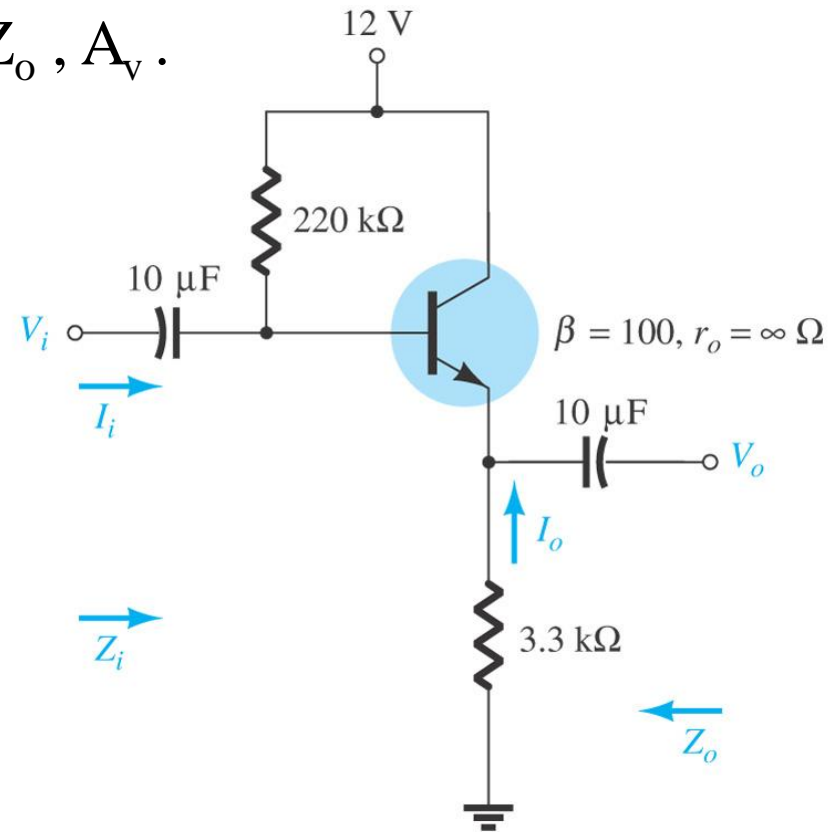

Example 5.7 - solution

