



# Buffer, Integrator, and Differentiator Op Amps

Produced by : Dr Musab T. S. Al-Kaltakchi

Electrical Engineering Department - Faculty of Engineering  
Mustansiriyah University

# Outline

Part1

- **Voltage Follower or Buffer**

part2

- **Integrator Op Amp**

part3

- **Differentiator Op Amp**

part4

part5

part6

part7


## Voltage Follower or Buffer

**What is a Voltage Follower?**

- A voltage follower is also known as a buffer amplifier, unity gain amplifier, or isolation amplifier
- Is an Op-Amp circuit whose output voltage is equal to the input voltage , so the output voltage follows the input voltage ( $V_{out}=V_{in}$ )
- A voltage follower Op Amp does not amplify the input signal and has a voltage gain of 1
- Gain with feedback or closed loop gain of this circuit is 1
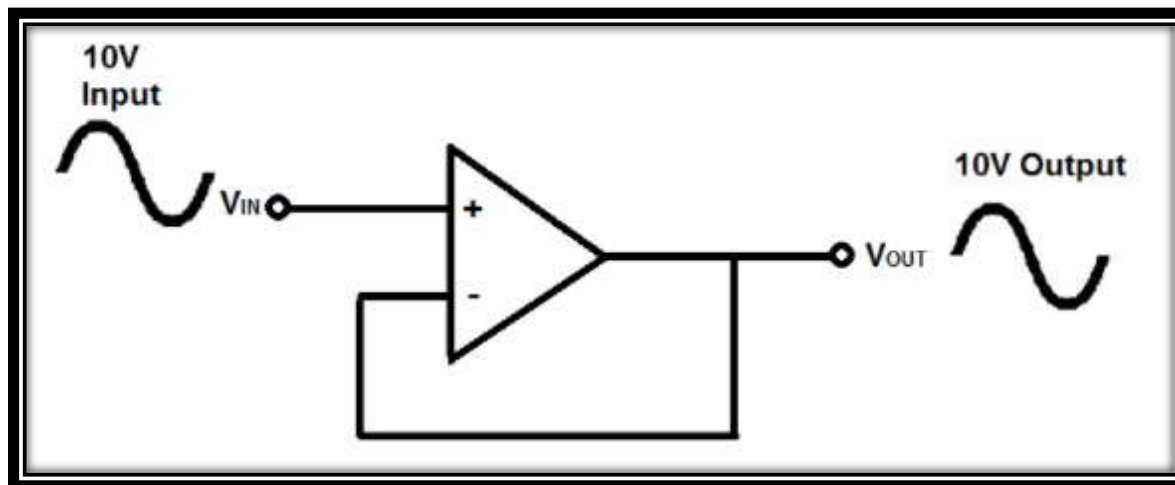
# Part1: Voltage Follower or Buffer

- ❑ The voltage follower provides no attenuation or amplification- only buffering
- ❑ It is a special case of non-inverting Op-Amp, therefore, in this circuit the output signal is in phase with the input signal
- ❑ The feedback resistance  $R_f = 0$  and the input resistance  $R_i = \infty$



# Part1: Voltage Follower or Buffer

## Advantages of Voltage Followers:


- 1) Provides power gain and current gain (voltage gain  $A_v = 1$ )
- 2) Low output impedance to the circuit, which uses the output of the voltage follower
- 3) High input impedance, Op-Amp takes no current from the input
- 4) Loading effects can be avoided
- 5) Isolator purpose, to isolate one circuits to another circuit
- 6) Impedance matching

# Part1: Voltage Follower or Buffer

## **Applications of Voltage Followers:**


- 1) Buffers for logic circuits**
- 2) Sample and hold circuits**
- 3) Active filters, voltage followers can be used to isolate filter stages from each other, when building multistage filters**
- 4) Bridge circuit via a transducer**

# Part1: Voltage Follower or Buffer

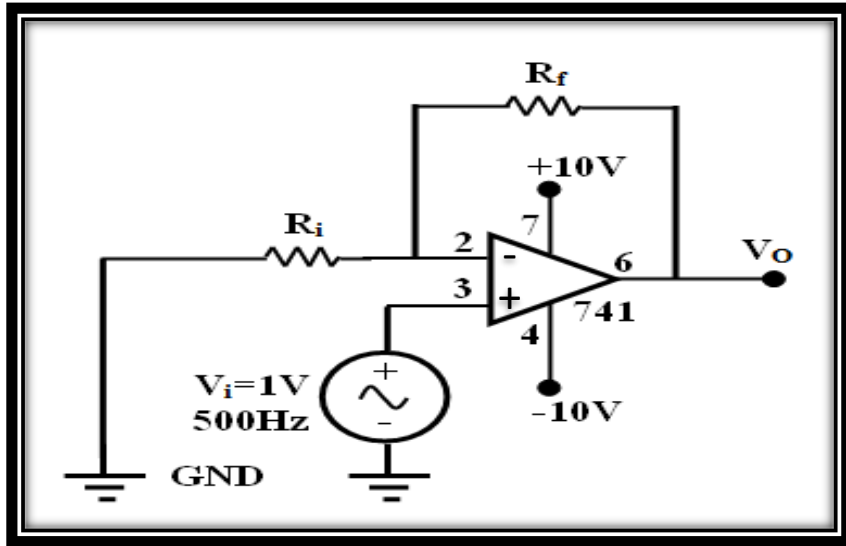

Non-Inverting Circuit
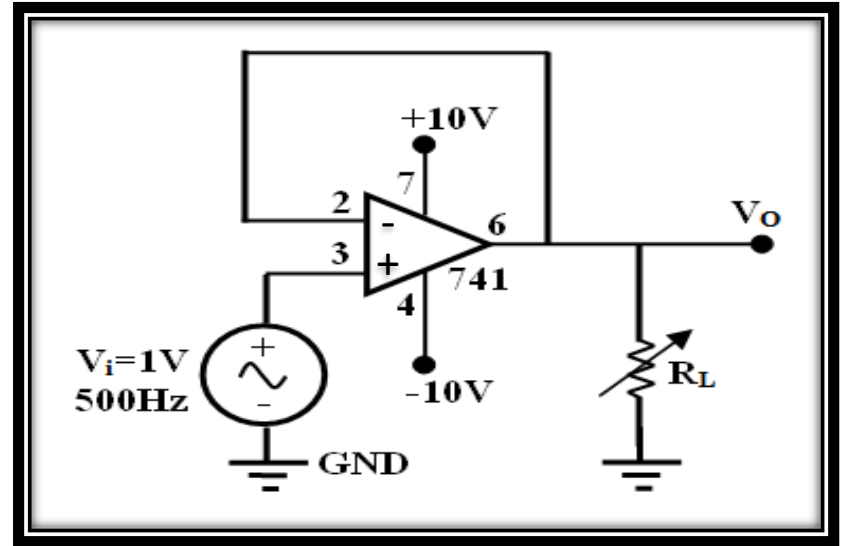
$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$
$$V_o = A_v V_i$$



Voltage Follower (Buffer) Circuit

$$A_v = \frac{V_o}{V_i} = 1 + \frac{0}{\infty} = 1$$
$$R_f = 0, R_i = \infty$$
$$V_o = V_i$$

# Part1: Voltage Follower or Buffer


The **input impedance** of the op-amp is **very high** when a voltage follower or unity gain configuration is used. Sometimes the input impedance is **much higher than 1 Megohm**. So, due to high input impedance, we can apply **weak signals** across the input and **no current** will flow in the input pin from the signal source to amplifier. On the other hand, the **output impedance** is **very low**, and it will produce the **same signal input**, in the output.

**Voltage follower** circuit is used to **create isolation** between two different kind of circuits. Due to high input impedance,, so the **input current is much lower than the output current** while the output voltage follows the input voltage. So the voltage follower provides **large power gain** across its output. Due to this behavior, Voltage follower used as a buffer circuit and can be used to isolate stages while building multistage filters or some other multistage circuit.


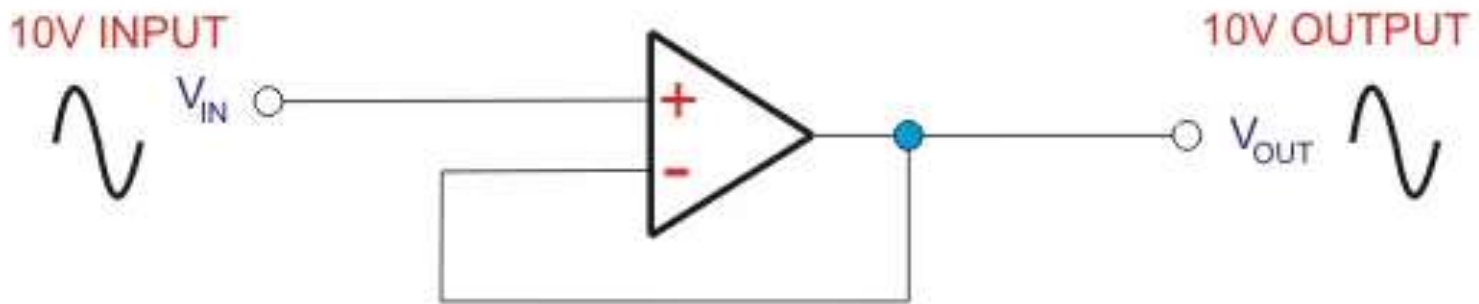
# Part1: Voltage Follower or Buffer

- A voltage follower circuit has a **very high input impedance**. This characteristic makes it a popular choice in many different types of circuits that require isolation between the input and output signal.
- A buffer is extremely useful because it prevents one stage's input impedance from loading the prior stage's output impedance, which causes undesirable loss of signal transfer. We covered this concept extensively in the Maximum Signal Transfer and Minimum Interstage Loading.



# Part1: Voltage Follower or Buffer

- Operational amplifiers have a **very high input impedance**, which means that they don't suck in much current (ideally, none) at the inputs. Op amps also have a **very low output impedance**. One application where this is useful is in a **voltage divider**. In a voltage divider (as in Figure 2), it's possible that the impedance load ( $R_o$ ) can vary quite a bit. Due to Ohm's Law ( $V=IR$ ), if  $R_o$  varies, it will affect  $V_{OUT}$ .

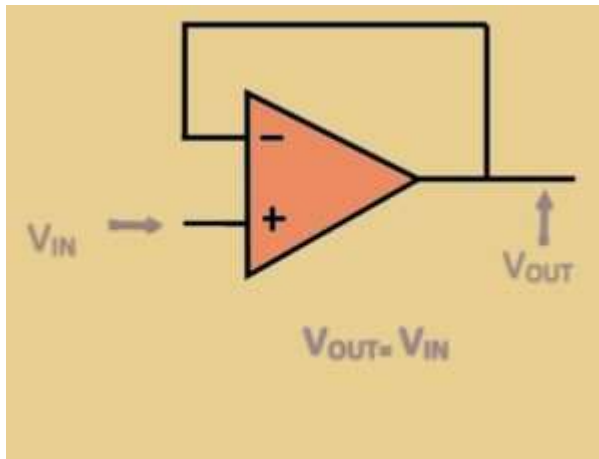


Figure 1: A voltage follower has a gain of one, so (theoretically) the output voltage is equal to the input voltage

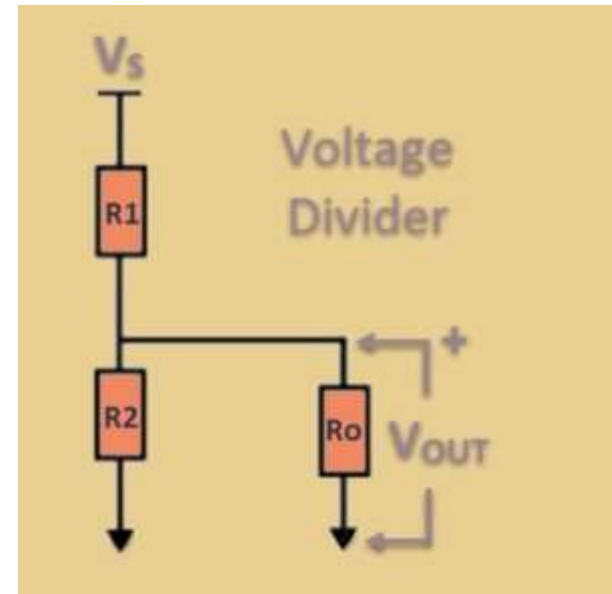


Figure 2: A voltage divider, but as  $R_o$  varies,  $V_{OUT}$  varies due to Ohm's Law

# Part1: Voltage Follower or Buffer

- In Figure 2, if  $R_o$  varies, then  $V_{OUT}$  would vary accordingly unless.... you were able to isolate the voltage divider's  $V_{OUT}$  by inserting a high impedance voltage follower between it and  $R_o$ , as in Figure 3. Adding a voltage follower to the voltage divider circuit isolates the load impedance ( $R_o$ ) so that  $V_{OUT}$  is dependent upon  $R1$  and  $R2$  (see figure 3), not  $R_o$ .

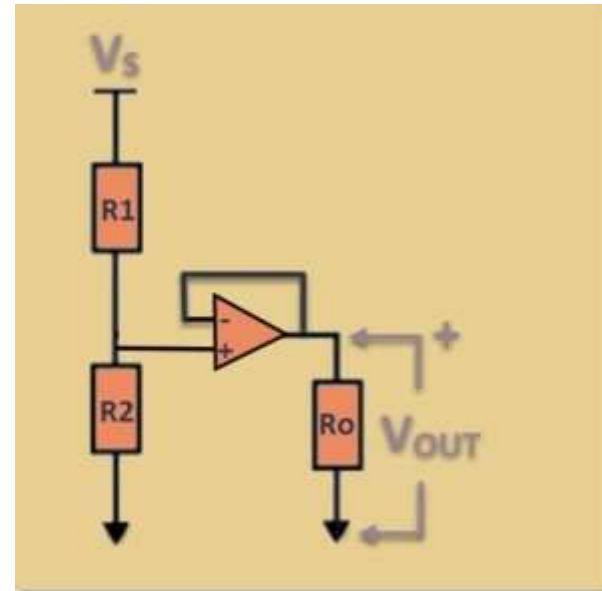


Figure 3: A voltage divider with a voltage follower (unity gain amp) that allows  $V_{OUT}$  to remain steady

# Part1: Voltage Follower or Buffer

- The voltage follower (Figure 1) allows us to move from one circuit to another and maintain the voltage level.
- It preserves the voltage source signal.
- This is why it's also called a **buffer or isolation amplifier**.
- You can use a **voltage divider circuit** to **switch** from **one logic level** (e.g. 5V) to **another logic level** (e.g., 3.3V).
- A cleaner switch is obtained when a **voltage follower (buffer amplifier)** is added to **the voltage divider circuit** (Figure 3).
- Another way to accomplish **logic level shifting** or **translation** is to use an **IC** called a **level shifter** to accomplish the same **buffered transition**. The high impedance of the op amp makes it possible for the voltage follower circuit to keep the load ( $R_o$ ) from affecting the output voltage.


# Part1: Voltage Follower or Buffer

- (**Logic levels** are used for binary signaling (**HI/LOW**), not for supplying power, so use a **voltage regulator** if you need to **step down** Power ( $P=VI$ ) to a load. A voltage divider is not a regulator and you could end up smoking a resistor if a voltage divider is used to step-down a power source.)
- With or without a voltage divider circuit, **the voltage follower, or voltage buffer, offers a means to transfer a voltage source signal from one impedance level to another without affecting current.**
- **Ohm's Law ( $V=IR$ )** dictates the relationship from there. **Voltage followers are used to match impedance** in other circuits, too. Note that there is also a **current buffer**, which preserves the current signal source, rather than voltage signal source.

# Part1: Voltage Follower or Buffer

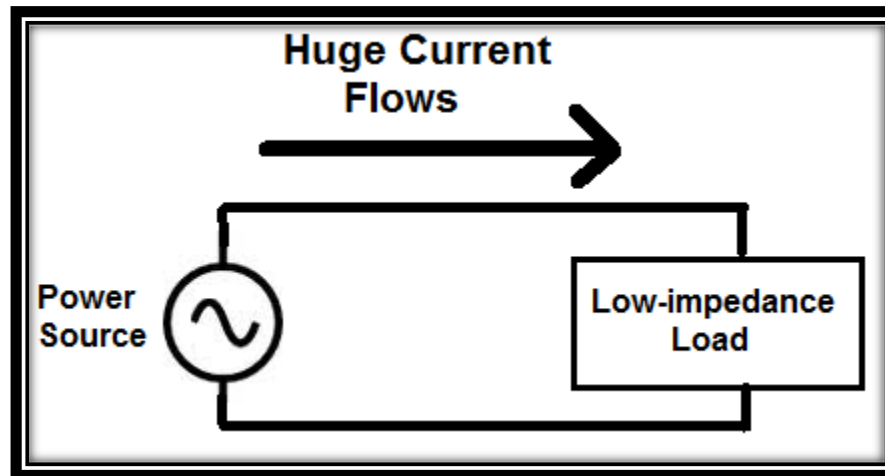
## Voltage Followers Draw Very Little Current

- According to ohm's law,  $I=V/R$ . When a circuit has a very high input impedance, very little current is drawn from the circuit. Thus, the power of the circuit isn't affected when current is feeding a high impedance load.
- The below circuit is a circuit in which a power source feeds a low-impedance load. According to ohm's law, again, current,  $I=V/R$ . If a load has very low resistance, it draws huge amounts of current. This causes huge amounts of power to be drawn from the power source and, because of this, causes high disturbances and use of the power source powering the load.


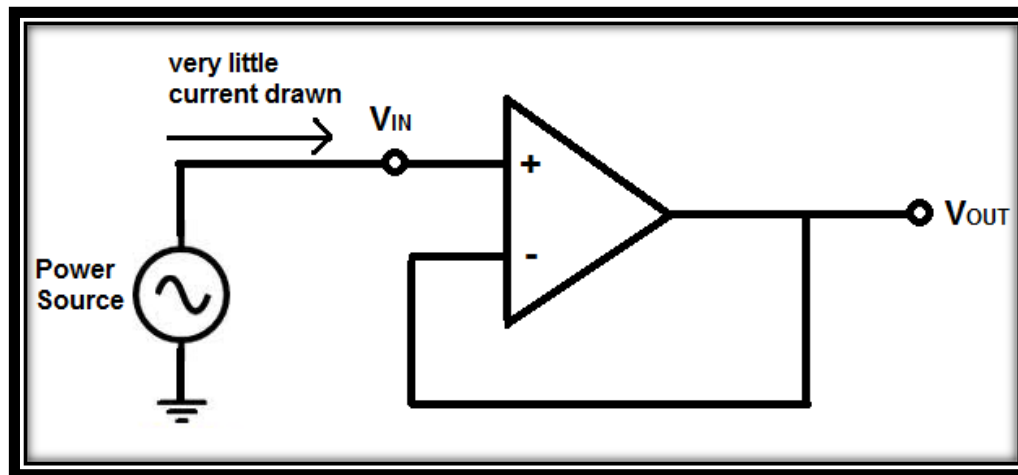
# Part1: Voltage Follower or Buffer

- This circuit below now draws very little current from the power source. Because the op amp has such **high impedance**, it draws **very little current**. And because an op amp that has **no feedback resistors** gives the **same output**, the circuit outputs the same signal that is fed in.
- This is one of the reasons voltage followers are used. **They draw very little current, not disturbing the original circuit**, and **give the same voltage signal as output**. They act as **isolation buffers**, isolating a circuit so that the power of the circuit is disturbed very little.



# Part1: Voltage Follower or Buffer

## Voltage Followers Are Important in Voltage Divider Circuits


- One of the reasons voltage followers are used, they simply don't draw a lot of current, so they do not load down the power source.
- Another reason voltage followers are used because of their importance in voltage divider circuits. So it's very valuable when used in a voltage divider circuit because strategically doing so can allow a designer to supply sufficient voltage to a load.
- Example:** So the following circuit will not work and it will be explained now why not.

1)  $10\text{K}\Omega \parallel 100\Omega = (10\text{K}\Omega)(100\Omega)/1.1\text{K}\Omega = 99.01\Omega \sim 99\Omega$ .

2) We next have a voltage divider between the  $10\text{K}\Omega$  resistor and the  $99\Omega$  resistor.

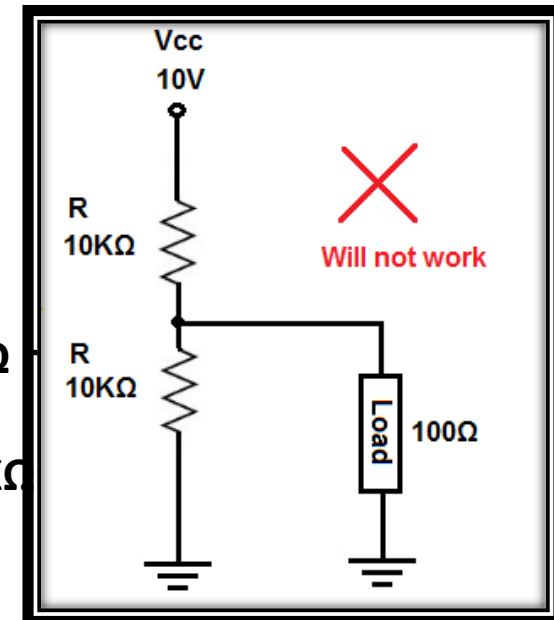3) The voltage divider formula for the voltage across the top  $10\text{K}\Omega$  resistor is,  $V = 10\text{V}(10\text{K}\Omega)/(10\text{K}\Omega + 99\Omega) = 9.9\text{V}$ .

The voltage divider formula for the voltage across the bottom  $10\text{K}\Omega$  resistor is,  $V = 10\text{V}(99\Omega)/(10,099\Omega) = 0.098\text{V}$  or  $98\text{mV}$ .





# Part1: Voltage Follower or Buffer

4) Remember, we use  $99\Omega$  because this is the equivalent resistance of the 2 resistors (the  $10K\Omega$  resistor and the  $100\Omega$  resistor in parallel).

Because the resistors are in parallel, they have the same voltage across each other, which is  $98mV$ .

- **Now let's say the load needs about 5V to operate.** You can see based on the calculation, there will **not be sufficient voltage at the output**. As we calculated, we had  **$98mV$**  as our voltage across the load at the output.
- The  $100\Omega$  resistance (load) carries down the resistance at the output too low. Therefore, in **a voltage divider circuit, the load gets very low voltage**, since voltage drops across loads in direct proportion to the resistance ( $V= IR$ ).

# Part1: Voltage Follower or Buffer


- However, if we take out the  $100\Omega$  load and instead connect an **op amp instead** (with its **high input impedance**), the resistance at the output (which ultimately powers the load) doesn't get drawn down. So the load can receive sufficient voltage.
- So this circuit above now works.

The op amp virtually offers infinite input impedance. Let's assume it's  $100M\Omega$ , though it can be much more. the equivalent parallel resistance of the  $10K\Omega \parallel 100M\Omega$   $(10K\Omega)(100M\Omega)/(10K\Omega + 100M\Omega) = 9999\Omega \sim 10K\Omega$ . So we have,  $10K\Omega \parallel 10K\Omega$ . the voltage divider formula,  $10V * (10K\Omega)/(10K\Omega + 10K\Omega) = 5V$ . So 5 volts falls across the top  $10K\Omega$  resistor and 5V falls across the bottom  $10K\Omega$  resistor and the  $100\Omega$ . Since the  $100\Omega$  and  $10K\Omega$  resistor are in parallel, they both receive the same 5V.

So you can see how the op amp allowed us to buffer the output of this circuit so that the load receives the voltage it needs.

So voltage followers are important to either isolate a circuit so that it

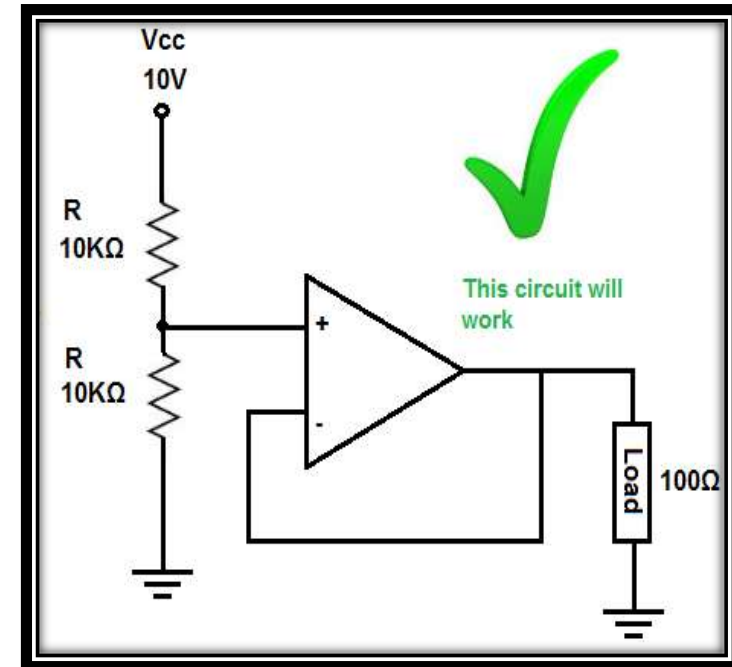**doesn't draw down power** or buffer a low impedance load so that it **receives sufficient voltage**.



# Part2: Integrator Op Amp Circuit

- An **integrator** is an electronic circuit that produces an output that is the integration of the applied input. This section discusses about the **op-amp based integrator**.
- An op-amp based integrator produces an output, which is an integral of the input voltage **applied to its inverting terminal**.
- It is a circuit designed with Op-Amp in such a way that it performs the **mathematical Integration operation**
- its **output** is proportional to the **amplitude** and **time duration** of the **input** applied.
- The integrator circuit layout is same as a **inverting amplifier** but the **feedback resistor** is replaced by a **capacitor** which make the circuit **frequency dependent**.

## Part2: Integrator Op Amp Circuit

- In this case the circuit is derived by the **time duration** of input applied which results in the **charging** and **discharging** of the **capacitor**.
- Initially when the voltage is applied to integrator the **uncharged capacitor** allows **maximum current to pass through it** and no current flows through the Op-Amp due to the presence of virtual ground,
- the capacitor starts to **charge** at the **rate of RC time constant** and its impedance starts to increase with time and a potential difference is develops across the capacitor resulting in charging current to decrease.
- This results in the ratio of capacitor's impedance and input resistance increasing causing a linearly increasing ramp output voltage that continues to increase until the capacitor becomes fully charged.

# Part2: Integrator Op Amp Circuit

Since, the Output voltage is the potential difference across capacitor.

$$V_C = \frac{Q}{C}, \quad Q = CV, \quad I_f = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

$$I_i = I_f$$


$$I_i = \frac{V_{in} - V_x}{R_{in}} = C \frac{d(V_x - V_{out})}{dt}$$

$$V^+ = V^- = V_x = 0$$

$$\frac{V_{in}}{R_{in}} = -C \frac{dV_{out}}{dt}$$

$$dV_{out} = -\frac{1}{R_{in}C} V_{in} dt$$
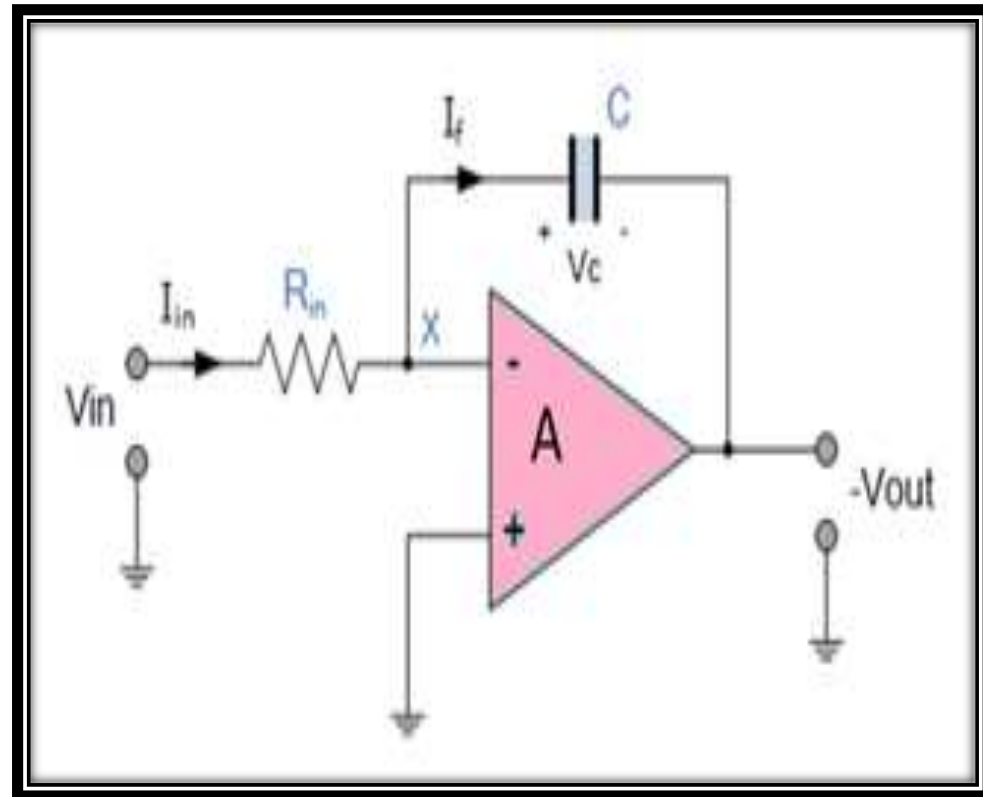
$$V_{out} = -\frac{1}{R_{in}C} \int V_{in} dt$$



$$V_o = -\frac{1}{RC} \int V_i dt$$

# Part3: Differentiator Op Amp Circuit

- A **differentiator** is an electronic circuit that produces an output equal to the **first derivative of its input**. This section discusses about the **op-amp based differentiator** in detail.
- An op-amp based differentiator produces an output, which is equal to the differential of input voltage that is applied to its **inverting terminal**.
- In the differentiator circuit **the input** is connected to the **inverting** output of the Op-Amp through a **capacitor(C)** and a **negative feedback** is provided to the **inverting input** terminal through a **resistor( $R_f$ )**
- which is **same as an integrator circuit** with feedback capacitor and input resistor being **replaced with each other**.
- Here the circuit **performs a mathematical differentiation operation**, and the **output is the first derivative** of the input signal, **180'** out of phase and **amplified** with a **factor  $R_f * C$** .

# Part3: Differentiator Op Amp Circuit

- The capacitor on the input allows only the AC component and restricts the DC, at low frequency the reactance of capacitor is very high causing a low gain and high frequency vice versa but at high frequency the circuit becomes unstable.

# Part3: Differentiator Op Amp Circuit

$$V_C = \frac{Q}{C}, \quad Q = CV,$$

$$I_i = \frac{dQ}{dt} = C \frac{dV_C}{dt}$$

$$I_i = I_f$$


$$I_i = C \frac{d(V_{in} - V_x)}{dt} = \frac{V_x - V_{out}}{R_f}$$

$$V^+ = V^- = V_x = 0$$

$$C \frac{dV_{in}}{dt} = - \frac{V_{out}}{R_f}$$

$$V_{out} = -R_f C \frac{dV_{in}}{dt}$$

$$V_{out} = -R C \frac{dV_{in}}{dt}$$

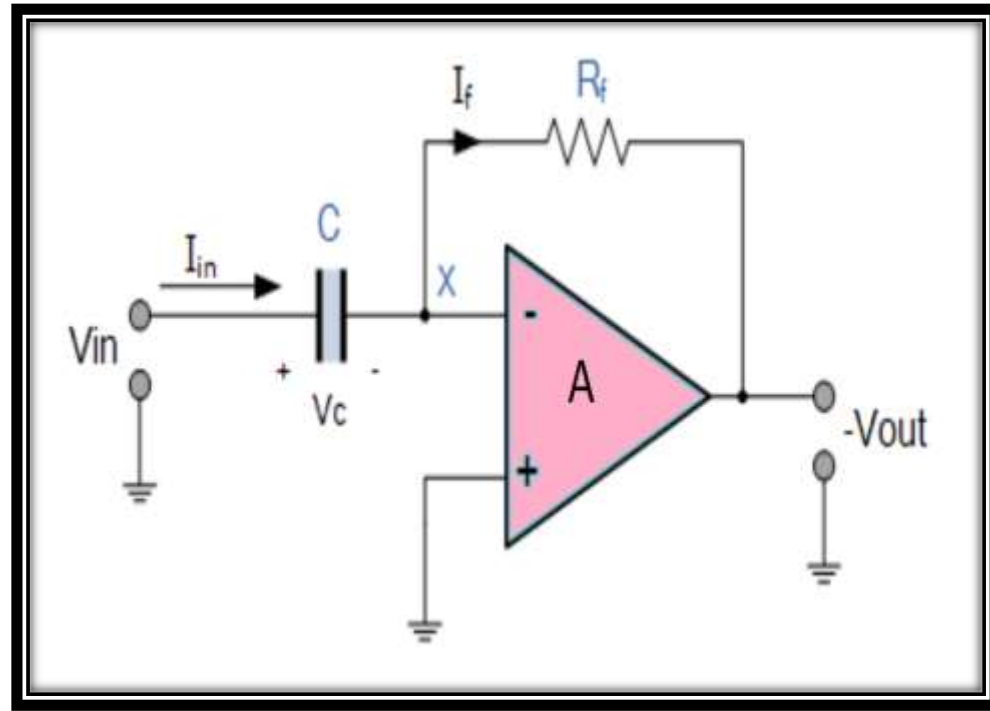

$$V_{out} = -R C \frac{dV_{in}}{dt}$$