



### 8.1 Resonance in A. C. Circuits:

In this chapter we will study the effect of varying the frequency of the sinusoidal source on different type of electric circuits, which refer to *frequency response* of the circuit (voltage or current w.r.t. frequency). According to ohm's law the frequency response represents a relationship between total impedance or admittance w.r.t. frequency.

There are three primary reasons for studying frequency response:

1. The ability to design circuits that are frequency selective circuits, like radio, telephone, and television communication systems.
2. We can predict the response of the circuit to any other *non-sinusoidal inputs*, so the engineer can carry out the design in terms of frequency specification and exert control over the response.
3. We can measure the frequency response in the laboratory and from these data; we can formulate a model for the circuit or device.

A network is in resonance (or resonant) when the voltage and current at the network input terminals are inphase. So the equivalent impedance or admittance consists of *real part* only and the power factor is *unity*. In other words the resonance occurs in electrical circuit at a frequency when the impedance between the input and output of the circuit is minimum (zero) or the transfer impedance is maximum (one). The energy will be oscillating between magnetic field of inductance and electrical field of capacitance. Resonance is a condition in an RLC circuit in which the capacitive and inductive reactances are equal in magnitude, thereby resulting in a purely resistive impedance. Resonant circuits (series or parallel) are useful for constructing filters, as their transfer functions can be highly frequency selective. They are used in many applications such as selecting the desired stations in radio and TV receivers.

**Resonant Frequency ( $\omega_0$ ):** is the frequency that makes the total impedance seen by the source is purely resistive and the corresponding total admittance purely conductive since  $Y_T = 1/Z_T$  (imaginary part equal to zero in both).

**Bandwidth ( $\beta$ ):** is the range of frequencies in which the amplitude of the output voltage or current is equal or greater than the maximum value divided by  $\sqrt{2}$ . So an acceptable output voltage or current has an amplitude is at least  $1/\sqrt{2} = 0.707$  times the maximum amplitude that can be transmitted by the circuit.

**Note:** because the amplitude is reduced by  $1/\sqrt{2}$ , so the average power delivered to the circuit is half its maximum value and this called half power frequency (HPF).

**Lower & Upper Side Frequencies ( $\omega_1$  &  $\omega_2$ ):** these are the two frequencies for which the output voltage or current amplitude is equal to  $1/\sqrt{2}$  from its maximum amplitude that can be transmitted by the circuit.

**Quality Factor (Q):** is the amount of sharpness of the response curve of any resonant (frequency selective) circuit (the circuit response are closely ideal).

$$Q = \text{quality factor} = 2\pi \times \frac{\text{maximum energy stored}}{\text{total energy lost per period (cycle)}}$$

### The Quality Factor for Some Circuits:


For series RL circuit:

The Sinusoidal Cycle Period =  $T = 1/f$

Maximum Energy (Power) Stored =  $\frac{1}{2}LI_{m\max}^2$

Average Energy (Power) Stored Per Cycle =  $\frac{1}{2}RI_{m\max}^2 \times 1/f$
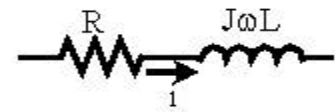
$$\therefore Q = 2\pi \times \frac{\frac{1}{2}LI_{m\max}^2}{\frac{1}{2}RI_{m\max}^2 \times \frac{1}{f_0}} = \frac{2\pi f_0 L}{R} = \frac{\omega_0 L}{R}$$




For series RC circuit:

The Sinusoidal Cycle Period =  $T = 1/f$

Maximum Energy (Power) Stored =  $\frac{1}{2}CV_{m\max}^2 = \frac{1}{2} \times \frac{1}{\omega^2 C} I_{m\max}^2$

Average Energy (Power) =  $\frac{1}{2}RI_{m\max}^2 \times 1/f$  stored per cycle
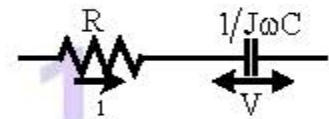
$$\therefore Q = 2\pi \times \frac{\frac{1}{2} \times \frac{1}{C\omega^2} I_{m\max}^2}{\frac{1}{2}RI_{m\max}^2 \times \frac{1}{f_0}} = \frac{1}{2\pi f_0 CR} = \frac{1}{\omega_0 CR}$$




For series RLC circuit:

The stored energy in RLC series circuit at resonance are constant, because when the capacitive voltage was maximum then the inductive current equal to zero and vice-versa.

$$\frac{1}{2}LI_{m\max}^2 = \frac{1}{2}CV_{m\max}^2$$
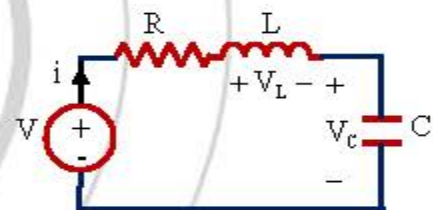
$$Q = 2\pi \times \frac{1/2 \times LV_{m\max}^2 / R^2}{1/2 \times RV_{m\max}^2 / R^2 \times 1/f} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$$




For parallel RLC circuit:

Like series circuit at resonance when the inductive current was maximum then the capacitive voltage equal to zero and vice-versa.

$$\frac{1}{2}LI_{m\max}^2 = \frac{1}{2}CV_{m\max}^2$$
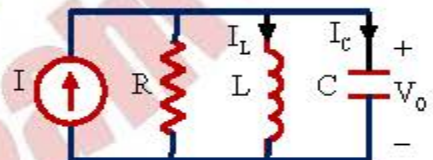
$$Q = 2\pi \times \frac{1/2 \times CV_{m\max}^2}{1/2 \times V_{m\max}^2 / R \times 1/f} = \frac{R}{\omega_0 L} = \omega_0 CR$$





## 8.2 Resonance in Series RLC Circuit:

First we need to change the voltage source frequency:  
R=Constant (will not be effected), while

$$X_L = \omega L = 2\pi fL \text{ or } X_L \propto f \quad \&$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} \text{ or } X_C \propto \frac{1}{f}$$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad \& \text{ at resonance imaginary part}=0$$

$$\therefore \omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s or } f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

$$\text{Resonant frequency } f_0 = \sqrt{f_1 f_2} \text{ or } \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\text{B.W}=\text{Band Width} =f_2-f_1 \text{ or } \beta = \omega_2 - \omega_1$$

Where:  $\beta = 2\pi \times \text{B.W}$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \text{ at } f_1 \text{ \& } f_2$$

$$I = \frac{I_m}{\sqrt{2}} = \frac{V_m}{\sqrt{2}R} \Rightarrow \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{2}R$$

Solve the equation for two positive values yields:

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \text{ and } \omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \text{ upper and lower side frequencies}$$

$$\therefore \beta = \omega_2 - \omega_1 = \frac{R}{L} \Rightarrow Q = \frac{\omega_0}{\beta} = \frac{f_0}{\text{B.W}} \text{ Quality factor}$$

$$Z = R + j\omega L \left(1 - \frac{1}{\omega^2 LC}\right) = R + j\omega L \left(1 - \left(\frac{\omega_0}{\omega}\right)^2\right)$$




$$Z = R \left[1 + j \frac{\omega L}{R} \left(1 - \left(\frac{\omega_0}{\omega}\right)^2\right)\right] = R \left[1 + jQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)\right] \text{ Total circuit normalized impedance}$$

Where:  $\omega/\omega_0$  =normalized frequency variable.

$$\text{At } f_1 \text{ or } f_2: I = \frac{I_m}{\sqrt{2}}, \text{ since } P_m = I_m^2 R \quad \therefore I^2 R = \frac{I_m^2}{2} R \Rightarrow P = \frac{P_m}{2} \text{ half power frequency}$$

$$\text{As a result } \omega_1 = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} \text{ and } \omega_2 = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$
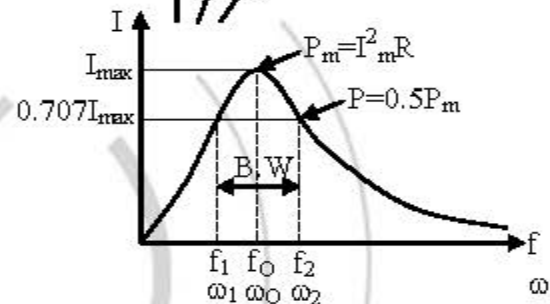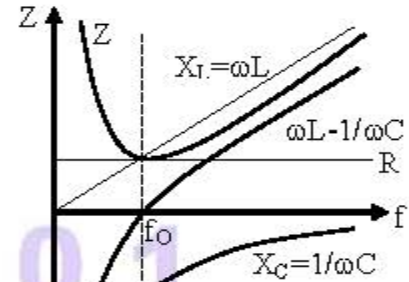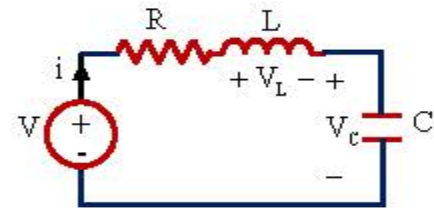
$$\text{, or using Quality factor: } \omega_1 = \omega_0 \left[-\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1}\right] \text{ and } \omega_2 = \omega_0 \left[\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1}\right]$$



### 8.3 Resonance in Parallel RLC Circuit:

First we need to change the voltage source frequency:  
R=Constant (will not be effected), while

$$X_L = \omega L = 2\pi fL \text{ or } X_L \propto f \text{ \&}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} \text{ or } X_C \propto \frac{1}{f}$$

$$Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) \text{ \& at resonance imaginary part}=0$$

$$\therefore \omega_0 C = \frac{1}{\omega_0 L} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ or } f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{Resonant frequency } f_0 = \sqrt{f_1 f_2} \text{ or } \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\text{B.W=Band Width} = f_2 - f_1 \text{ or } \beta = \omega_2 - \omega_1$$

$$\text{Where: } \beta = 2\pi \times \text{B.W}$$

$$Q = \omega_0 CR = \frac{R}{\omega_0 L} = R \sqrt{\frac{C}{L}}$$

$$V = \frac{I}{Y} = \frac{I}{\sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}} \text{ at } f_1 \text{ \& } f_2$$

$$V = \frac{V_m}{\sqrt{2}} = \frac{I_m R}{\sqrt{2}} \Rightarrow \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2} = \frac{\sqrt{2}}{R}$$

Solve the equation for two positive values yields:

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

and

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} \text{ upper \& lower side frequencies}$$

$$\therefore \beta = \omega_2 - \omega_1 = \frac{1}{RC} \Rightarrow Q = \frac{\omega_0}{\beta} = \frac{f_0}{\text{B.W}} \text{ Quality factor}$$

$$Y = \frac{1}{R} + j\omega C \left(1 - \frac{1}{\omega^2 LC}\right) = \frac{1}{R} + j\omega C \left(1 - \left(\frac{\omega_0}{\omega}\right)^2\right)$$




$$Y = \frac{1}{R} \left[1 + j\omega CR \left(1 - \left(\frac{\omega_0}{\omega}\right)^2\right)\right] = \frac{1}{R} \left[1 + jQ \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)\right] \text{ Total circuit normalized admittance}$$

Where:  $\omega/\omega_0$  =normalized frequency variable.

$$\text{At } f_1 \text{ or } f_2: V = \frac{V_m}{\sqrt{2}}, \text{ since } P_m = \frac{V_m^2}{R} \therefore \frac{V^2}{R} = \frac{V_m^2}{2R} \Rightarrow P = \frac{P_m}{2} \text{ half power frequency}$$

$$\text{As a result } \omega_1 = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} \text{ and } \omega_2 = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$
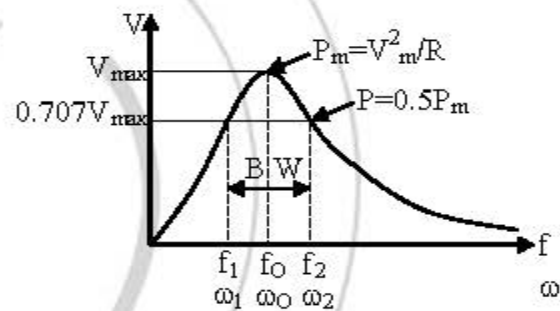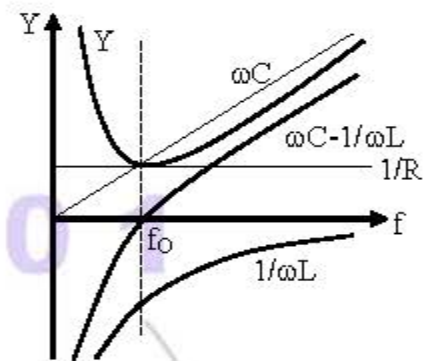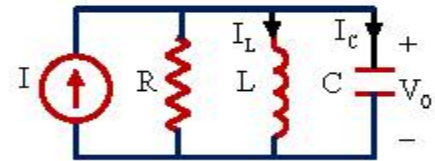
$$\text{, or using Quality factor: } \omega_1 = \omega_0 \left[-\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1}\right] \text{ and } \omega_2 = \omega_0 \left[\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1}\right]$$






**Example:** For the circuit shown, find the resonant frequency.

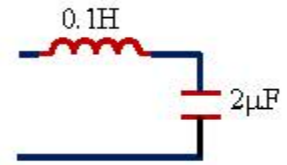**Solution:**

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 2 \times 10^{-6}}} = 356 \text{ Hz}$$



**Example:** A series circuit is desired that will resonate at 2MHz. if (10μH) inductor is available, what should be the value of capacitor used to form the circuit?

**Solution:**

$$C = \frac{1}{(2\pi f_0)^2 \times L} = \frac{1}{(2\pi \times 2 \times 10^6)^2 \times 10 \times 10^{-6}} = 633 \text{ PF}$$

**Example:** AM band radio station has a center frequency of 1010KHz and B.W of 15KHz. What is the value of Q for the radio transmitter circuit?

**Solution:**

$$Q = \frac{f_0}{\text{B.W}} = \frac{1010 \times 10^3}{15 \times 10^3} = 67.3$$

**Example:** For a series circuit with L/C=400 and  $f_0=2\text{MHz}$ :

1. Find the values of L & C.
2. What is the value of "R" needed so that  $Q=20$ .
3. Calculate the upper and lower cutoff frequencies.

**Solution:**

$$1. f_0 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow 2 \times 10^6 = \frac{1}{2\pi\sqrt{400C \times C}} \Rightarrow C = 3.979 \text{ nF and } L = 400 \times 3.979 \times 10^{-9} = 1.59 \mu\text{H}$$

$$2. R = \frac{1}{Q} \sqrt{\frac{L}{C}} = \frac{1}{20} \sqrt{\frac{1.59 \times 10^{-6}}{3.979 \times 10^{-9}}} = 0.9994 \Omega$$

$$3. \text{B.W} = \frac{f_0}{Q} = \frac{2 \times 10^6}{20} = 10^5 \text{ Hz}$$

$$\left. \begin{aligned} f_1 &= f_0 - \frac{\text{B.W}}{2} = 2 \times 10^6 - \frac{10^5}{2} = 1.95 \text{ MHz} \\ f_2 &= f_0 + \frac{\text{B.W}}{2} = 2 \times 10^6 + \frac{10^5}{2} = 2.05 \text{ MHz} \end{aligned} \right\} \text{ If } Q \geq 10$$

**Example:** A series resonant circuit has B.W=100Hz and  $f_0=2000\text{Hz}$ :

1. Find the value of Q for the circuit.
2. What is the value of "L" & "C" if  $R=10\Omega$ .
3. Calculate the upper and lower cutoff frequencies.

**Solution:**

$$1. Q = \frac{f_0}{\text{B.W}} = \frac{2000}{100} = 20$$

$$2. L = \frac{QR}{\omega_0} = \frac{20 \times 10}{2\pi \times 2000} = 15.9 \text{ mH and } C = \frac{1}{Q\omega_0 R} = \frac{1}{20 \times 2\pi \times 2000 \times 10} = 0.398 \mu\text{F}$$

$$\left. \begin{aligned} f_1 &= f_0 - \frac{\text{B.W}}{2} = 2000 - \frac{100}{2} = 1.95 \text{ KHz} \\ f_2 &= f_0 + \frac{\text{B.W}}{2} = 2000 + \frac{100}{2} = 2.05 \text{ KHz} \end{aligned} \right\} \text{ If } Q \geq 10$$

**Example:** Design a series resonant circuit with input voltage 2V, B.W=400Hz, and  $I_m=250\text{mA}$  at resonance, with  $f_0=10\text{KHz}$  find:

1. The value of Q for the circuit.
2. The value of "L" & "C".
3. The upper and lower cutoff frequencies.

**Solution:**

$$1. Q = \frac{f_0}{\text{B.W}} = \frac{10000}{400} = 25 \quad 2. \text{ at resonance } R = \frac{V}{I_m} = \frac{2}{250 \times 10^{-3}} = 8\Omega$$

$$L = \frac{QR}{\omega_0} = \frac{25 \times 8}{2\pi \times 10000} = 3.183\text{mH} \quad \text{and} \quad C = \frac{1}{Q\omega_0 R} = \frac{1}{25 \times 2\pi \times 10000 \times 8} = 0.0796\mu\text{F}$$

$$3. \left. \begin{aligned} f_1 &= f_0 - \frac{\text{B.W}}{2} = 10000 - \frac{400}{2} = 9.8\text{KHz} \\ f_2 &= f_0 + \frac{\text{B.W}}{2} = 10000 + \frac{400}{2} = 10.2\text{KHz} \end{aligned} \right\} \text{ IF } Q \geq 10$$

**Example:** Series RLC circuit with B.W=250Hz, and center frequency 750Hz. Use 100nF capacitor, compute Q, L, R,  $\omega_1$ , &  $\omega_2$ .

**Solution:**

$$Q = \frac{f_0}{\text{B.W}} = \frac{750}{250} = 3 \quad L = \frac{1}{(2\pi f_0)^2 \times C} = \frac{1}{(2\pi \times 750)^2 \times 100 \times 10^{-9}} = 450\text{mH}$$

$$R = \frac{\omega_0 L}{Q} = \frac{2\pi \times 750 \times 450 \times 10^{-3}}{3} = 707\Omega \quad \text{or} \quad \text{B.W} = \frac{R}{2\pi L}$$

$$\omega_1 = 2\pi \left[ -\frac{\text{B.W}}{2} + \sqrt{\left(\frac{\text{B.W}}{2}\right)^2 + f_0^2} \right] = 3992\text{rad/s} \quad \text{or} \quad \omega_1 = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

$$\omega_2 = 2\pi \left[ \frac{\text{B.W}}{2} + \sqrt{\left(\frac{\text{B.W}}{2}\right)^2 + f_0^2} \right] = 5562.8\text{rad/s} \quad \text{or} \quad \omega_2 = \omega_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

**Example:** Design the component values for series RLC circuit with center frequency 4KHz and Q=5, use 500nF capacitor.

**Solution:**

$$R = \frac{1}{Q\omega_0 C} = \frac{1}{5 \times 2\pi \times 4 \times 10^3 \times 500 \times 10^{-9}} = 15.92\Omega \quad L = \frac{QR}{\omega_0} = \frac{5 \times 15.92}{2\pi \times 4 \times 10^3} = 3.17\text{mH}$$

$$\text{B.W} = \frac{f_0}{Q} = \frac{4 \times 10^3}{5} = 800\text{Hz} \quad \text{or} \quad \text{B.W} = \frac{\omega_2 - \omega_1}{2\pi}$$

$$\omega_1 = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 2\pi \times 4 \times 10^3 \left[ -\frac{1}{2 \times 5} + \sqrt{\left(\frac{1}{2 \times 5}\right)^2 + 1} \right] = 22744.82\text{rad/s}$$

$$\omega_2 = \omega_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 2\pi \times 4 \times 10^3 \left[ \frac{1}{2 \times 5} + \sqrt{\left(\frac{1}{2 \times 5}\right)^2 + 1} \right] = 27771.37\text{rad/s}$$



**Example:** Design a component values for series RLC circuit with center frequency 20KHz and  $Q=5$ , use  $100\Omega$  resistor.

**Solution:**

$$L = \frac{QR}{\omega_0} = \frac{5 \times 100}{2\pi \times 20 \times 10^3} = 3.98\text{mH} \quad C = \frac{1}{Q\omega_0 R} = \frac{1}{5 \times 2\pi \times 20 \times 10^3 \times 100} = 15.92\text{nF}$$

$$\text{B.W} = \frac{f_0}{Q} = \frac{20 \times 10^3}{5} = 4\text{KHz} \quad \text{or} \quad \text{B.W} = f_2 - f_1 = \frac{R}{2\pi L}$$

$$f_1 = f_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 20 \times 10^3 \left[ -\frac{1}{2 \times 5} + \sqrt{\left(\frac{1}{2 \times 5}\right)^2 + 1} \right] = 18.1\text{KHz}$$

$$f_2 = f_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 20 \times 10^3 \left[ \frac{1}{2 \times 5} + \sqrt{\left(\frac{1}{2 \times 5}\right)^2 + 1} \right] = 22.1\text{KHz}$$

**Example:** Series-resonant circuit has resonant frequency 5MHz and lower half-power frequency 4.5MHz. Use  $0.01\mu\text{F}$  capacitor to find: B.W, Q, L, and R.

**Solution:**

$$f_2 = \frac{f_0^2}{f_1} = \frac{(5 \times 10^6)^2}{4.5 \times 10^6} = 5.56\text{MHz} \quad \text{B.W} = f_2 - f_1 = (5.56 - 4.5) \times 10^6 = 1.06\text{MHz}$$

$$Q = \frac{f_0}{\text{B.W}} = \frac{5 \times 10^6}{1.06 \times 10^6} = 4.74$$

$$L = \frac{1}{\omega_0^2 C} = \frac{1}{(2\pi \times 5 \times 10^6)^2 \times 0.01 \times 10^{-6}} = 0.101\mu\text{H}$$

$$R = \frac{\omega_0 L}{Q} = \frac{2\pi \times 5 \times 10^6 \times 0.101 \times 10^{-6}}{4.74} = 0.67\Omega$$

**Example:** For the series RLC circuit shown, calculate: resonant frequency, Q, B.W,  $f_1$ , and  $f_2$  (half-power frequencies).

**Solution:**


$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.2 \times 10^{-3} \times 5 \times 10^{-9}}} = 0.16\text{MHz}$$

$$Q = \frac{\omega_0 L}{R} = \frac{2\pi \times 0.16 \times 10^6 \times 0.2 \times 10^{-3}}{10} = 20 \quad \text{or} \quad Q = \frac{1}{\omega_0 CR}$$

$$\text{B.W} = \frac{f_0}{Q} = \frac{0.16 \times 10^6}{20} = 7.96\text{KHz} \approx 8\text{KHz}$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = 0.975\text{Mrad/s} \Rightarrow f_1 = \frac{\omega_1}{2\pi} = 0.155\text{MHz}$$
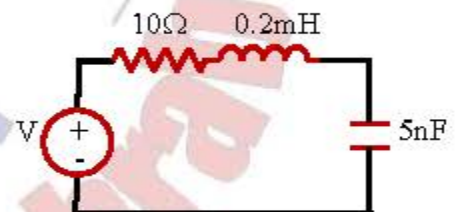
$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = 1.025\text{Mrad/s} \Rightarrow f_2 = \frac{\omega_2}{2\pi} = 0.163\text{MHz}$$



**Example:** If  $\frac{V_C}{V_S}|_{f_0} = 20$ ,  $f_0 = 20\text{KHz}$  and  $C = 0.001\mu\text{F}$  find: 1. "L" & "R". 2.  $V_C$ , if  $V_S = 1\text{V}$ ,  $2\text{KHz}$  voltage source. 3.  $V_L$  for the condition in "2".

**Solution:**

$$1. L = \frac{1}{\omega_0^2 \times C} = \frac{1}{(2\pi f_0)^2 \times C} = \frac{1}{(2\pi \times 20 \times 10^3)^2 \times 0.001 \times 10^{-6}} = 63.4\text{mH}$$

$$V_C|_{f_0} = I_0 X_C = \frac{V_S|_{f_0}}{R_T \omega_0 C}$$

$$\therefore \frac{V_C}{V_S}|_{f_0} = 20 = \frac{1}{R_T \times 2\pi \times 20 \times 10^3 \times 0.001 \times 10^{-6}} \Rightarrow R_T = 398\Omega$$

$$2. X_C = \frac{1}{2\pi \times 2 \times 10^3 \times 0.001 \times 10^{-6}} = 79.62\text{K}\Omega$$

$$X_L = 2\pi \times 2 \times 10^3 \times 63.4 \times 10^{-3} = 796.3\Omega$$

$$V_C = 1 \times \left| \frac{-jX_C}{R_T + j(X_L - X_C)} \right| = \left| \frac{-j79.62 \times 10^3}{398 + j(796.3 - 79.62 \times 10^3)} \right| = 1.01\text{V}$$

$$3. V_L = 1 \times \left| \frac{jX_L}{R_T + j(X_L - X_C)} \right| = \left| \frac{j796.3}{398 + j(796.3 - 79.62 \times 10^3)} \right| = 0.0101\text{V}$$

**Example:** A circuit is operate at  $100\text{KHz}$  with B.W of  $8\text{KHz}$ . If the magnitude of voltage source is  $1\text{V}$ , with internal resistance ( $25\Omega$ ), and the coil available has a resistance ( $20\Omega$ ) and ( $Q=50$ ). Find the values of R, L, and C, which make up the circuit. Also find current magnitude and voltage across capacitor, inductor, and resistor.

**Solution:**

$$Q_s = \frac{f_0}{\text{B.W}} = \frac{100 \times 10^3}{8 \times 10^3} = 12.5$$

For the coil:

$$\omega_0 L = Q_s \times R_c = 50 \times 20 = 1000\Omega$$

$$Q_s = \frac{\omega_0 L}{R_s + R + R_c} \text{ or } 12.5 = \frac{1000}{25 + R + 20}$$

$$\therefore R = 35\Omega$$

$$L = \frac{\omega_0 L}{2\pi f_0} = \frac{1000}{2\pi \times 100 \times 10^3} = 1.59\text{mH} \quad \text{at resonance } X_L = X_C$$

$$C = \frac{1}{2\pi f_0 \omega_0 L} = \frac{1}{2\pi \times 100 \times 10^3 \times 1000} = 1.59\text{nF}$$


$$I = \frac{V}{R_T} = \frac{1}{25 + 35 + 20} = 12.5\text{mA}$$

$$V_R = IR = 12.5 \times 10^{-3} \times 35 = 0.4375\text{V}$$

$$V_C = IX_C = 12.5 \times 10^{-3} \times 1000 = 12.5\text{V} = V_L$$

$$V_{R_c} = IR_c = 12.5 \times 10^{-3} \times 20 = 0.25\text{V}$$
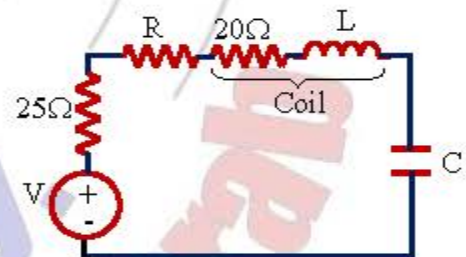
$$V_{\text{Coil}} = \sqrt{V_L^2 + V_{R_c}^2} = \sqrt{(12.5)^2 + (0.25)^2} = 12.502\text{V}$$





**Example:** Parallel-resonant circuit with resonant frequency 10KHz, B.W=400Hz, input current 20mA, and  $V_m=50V$  at resonance, find: Q, R, L, C,  $f_1$  and  $f_2$ .

**Solution:**

$$Q = \frac{f_0}{B.W} = \frac{10 \times 10^3}{400} = 25$$

$$R = \frac{V_m}{I_m} = \frac{50}{20 \times 10^{-3}} = 2.5K\Omega$$

$$L = \frac{R}{Q\omega_0} = \frac{2.5 \times 10^3}{25 \times 2\pi \times 10 \times 10^3} = 1.59mH$$

$$C = \frac{Q}{\omega_0 R} = \frac{25}{2\pi \times 10 \times 10^3 \times 2.5 \times 10^3} = 0.159\mu F$$

$$f_1 = f_0 - \frac{B.W}{2} = 10 \times 10^3 - \frac{400}{2} = 9.8KHz$$

$$f_2 = f_0 + \frac{B.W}{2} = 10 \times 10^3 + \frac{400}{2} = 10.2KHz$$

} IF  $Q \geq 10$

**Example:** If the resonant frequency of RLC parallel circuit is 100KHz, and B.W=1KHz, use 60nF capacitor, calculate Q, R, L,  $\omega_1$ , &  $\omega_2$ .

**Solution:**

$$Q = \frac{f_0}{B.W} = \frac{100 \times 10^3}{1 \times 10^3} = 100$$

$$R = \frac{Q}{\omega_0 C} = \frac{100}{2\pi \times 100 \times 10^3 \times 60 \times 10^{-9}} = 2652.6\Omega$$

$$L = \frac{R}{Q\omega_0} = \frac{2652.6}{100 \times 2\pi \times 100 \times 10^3} = 42.22\mu H$$

$$\omega_1 = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 2\pi \times 100 \times 10^3 \left[ -\frac{1}{200} + \sqrt{\left(\frac{1}{200}\right)^2 + 1} \right] = 625.2Krad/s = \omega_0 - \frac{\beta}{2}$$

$$\omega_2 = \omega_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 2\pi \times 100 \times 10^3 \left[ \frac{1}{200} + \sqrt{\left(\frac{1}{200}\right)^2 + 1} \right] = 631.5Krad/s = \omega_0 + \frac{\beta}{2}$$

**Note:**  $\omega_0 = 2\pi f_0$  and  $\beta = 2\pi B.W$

**Example:** Parallel RLC circuit with  $f_0=10MHz$ , B.W=100KHz, and  $R=100K\Omega$ , calculate Q, L, C,  $\omega_1$ , &  $\omega_2$ .

**Solution:**

$$Q = \frac{f_0}{B.W} = \frac{10 \times 10^6}{100 \times 10^3} = 100$$

$$L = \frac{R}{Q\omega_0} = \frac{100 \times 10^3}{100 \times 2\pi \times 10 \times 10^6} = 15.9\mu H$$


$$C = \frac{Q}{\omega_0 R} = \frac{100}{2\pi \times 10 \times 10^6 \times 100 \times 10^3} = 15.9PF$$

$$\omega_1 = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 2\pi \times 10 \times 10^6 \left[ -\frac{1}{200} + \sqrt{\left(\frac{1}{200}\right)^2 + 1} \right] = 62.52Mrad/s = \omega_0 - \frac{\beta}{2}$$

$$\omega_2 = \omega_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 2\pi \times 10 \times 10^6 \left[ \frac{1}{200} + \sqrt{\left(\frac{1}{200}\right)^2 + 1} \right] = 63.15Mrad/s = \omega_0 + \frac{\beta}{2}$$

**Example:** For the parallel RLC circuit shown, find:

1.  $\omega_0$ ,  $Q$ ,  $\omega_1$ ,  $\omega_2$ , and  $|V_o|$  at  $\omega_0$ ,  $\omega_1$ , and  $\omega_2$ .
2. Value of "R" for B.W of 80Hz.
3. Value of "Q" in "2".

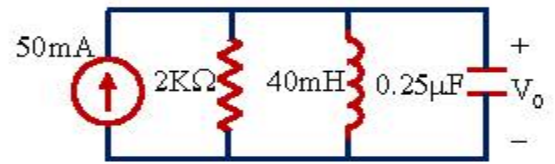

**Solution:**

$$1. \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{40 \times 10^{-3} \times 0.25 \times 10^{-6}}} = 10^4 \text{ rad/s} \quad \Rightarrow \quad f_0 = \frac{\omega_0}{2\pi} = 1591.55 \text{ Hz}$$

$$Q = \omega_0 CR = 10^4 \times 0.25 \times 10^{-6} \times 2 \times 10^3 = 5$$

$$\text{B.W} = \frac{f_0}{Q} = \frac{1591.55}{5} = 318.31 \text{ Hz} \quad \text{or} \quad \text{B.W} = \frac{1}{2\pi RC}$$

$$\omega_1 = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 9049.88 \text{ rad/s} = 2\pi \times \left[ -\frac{\text{B.W}}{2} + \sqrt{\left(\frac{\text{B.W}}{2}\right)^2 + f_0^2} \right]$$

$$\omega_2 = \omega_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right] = 11049.88 \text{ rad/s} = 2\pi \times \left[ \frac{\text{B.W}}{2} + \sqrt{\left(\frac{\text{B.W}}{2}\right)^2 + f_0^2} \right]$$

$$V_o(\omega_0) = I_m R = 50 \times 10^{-3} \times 2000 = 100 \text{ V}$$

$$V_o(\omega_1) = V_o(\omega_2) = 0.707 V_o(\omega_0) = 70.7 \text{ V}$$

$$2. R = \frac{1}{2\pi \text{B.W} C} = \frac{1}{2\pi \times 80 \times 0.25 \times 10^{-6}} = 7957.7 \Omega$$

$$3. Q = \frac{f_0}{\text{B.W}} = \frac{1591.55}{80} = 20$$

**Example:** For the parallel RLC circuit shown, if  $f_0 = 2 \text{ MHz}$  and  $Q = 10$ , calculate:  $C$ ,  $f_1$ ,  $f_2$ , B.W,  $V_o$ ,  $I_C$  and  $I_L$  at resonance.



**Solution:**

$$R = Q \omega_0 L = 10 \times 2\pi \times 2 \times 10^6 \times 25 \times 10^{-6} = 3140 \Omega$$

$$C = \frac{Q}{\omega_0 R} = \frac{10}{2\pi \times 2 \times 10^6 \times 3140} = 253 \text{ pF}$$

$$\text{B.W} = \frac{f_0}{Q} = \frac{2 \times 10^6}{10} = 0.2 \text{ MHz}$$

$$\left. \begin{aligned} f_1 &= f_0 - \frac{\text{B.W}}{2} = 2 \times 10^6 - \frac{0.2 \times 10^6}{2} = 1.9 \text{ MHz} \\ f_2 &= f_0 + \frac{\text{B.W}}{2} = 2 \times 10^6 + \frac{0.2 \times 10^6}{2} = 2.1 \text{ MHz} \end{aligned} \right\} \text{ If } Q \geq 10$$

$$V_o(\omega_0) = I_m R = 10 \times 10^{-3} \times 3140 = 31.4 \text{ V} \quad \text{output voltage at resonance}$$

$$I_C = V_o(\omega_0) Y_C = 31.4 \times 2\pi \times 2 \times 10^6 \times 253 \times 10^{-12} = 0.1 \text{ A} = I_L \quad (\text{phase difference } 180^\circ)$$



**Example:** For the circuit shown, find at resonance:  $f_0$ ,  $Q$ , B.W, output voltage, and the current in each element.

**Solution:**


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 10^{-3} \times 5 \times 10^{-9}}} = 3.16 \times 10^5 \text{ rad/s} \Rightarrow f_0 = \frac{\omega_0}{2\pi} = 50.3 \text{ KHz}$$

$$Q = \omega_0 CR = 3.16 \times 10^5 \times 5 \times 10^{-9} \times 10 \times 10^3 = 15.8$$

$$\text{B.W} = \frac{f_0}{Q} = \frac{50.3 \times 10^3}{15.8} = 3.19 \text{ KHz} \quad \text{or} \quad \text{B.W} = \frac{1}{2\pi RC}$$

$$V_o(\omega_0) = I_m R = 1 \times 10^{-3} \times 10^4 = 10 \text{ V} \quad \text{output voltage at resonance}$$
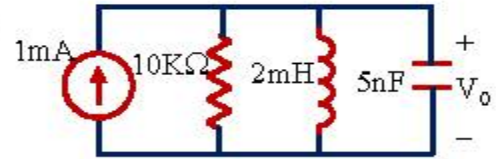
$$I_c = V_o(\omega_0) Y_c = 10 \times 2\pi \times 50.3 \times 10^3 \times 5 \times 10^{-9} = 15.8 \text{ mA} = I_L \quad (\text{phase difference } 180^\circ)$$



**Example:** For the circuit shown: 1. Estimate  $\omega_0$  w.r.t. circuit elements. 2. Find that resonance frequency.

**Solution:**

$$Y = \frac{1}{R_c - jX_c} + \frac{1}{R_L + jX_L}$$

$$Y = \left( \frac{R_c}{R_c^2 + X_c^2} + \frac{R_L}{R_L^2 + X_L^2} \right) + j \left( \frac{X_c}{R_c^2 + X_c^2} - \frac{X_L}{R_L^2 + X_L^2} \right)$$


Since at resonance imaginary part of total admittance=0

$$\therefore \frac{X_c}{R_c^2 + X_c^2} = \frac{X_L}{R_L^2 + X_L^2} \Rightarrow X_c(R_L^2 + X_L^2) = X_L(R_c^2 + X_c^2)$$

$$\frac{1}{\omega_0 C} (R_L^2 + \omega_0^2 L^2) = \omega_0 L (R_c^2 + \frac{1}{\omega_0^2 C^2}) \Rightarrow R_L^2 + \omega_0^2 L^2 - \omega_0^2 L C R_c^2 - \frac{L}{C} = 0$$

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_c^2 - L/C}} \quad \text{where: } \omega_0 = 2\pi f_0 \text{ for real frequency} \quad \boxed{R_L^2 > L/C \ \& \ R_c^2 > L/C}$$
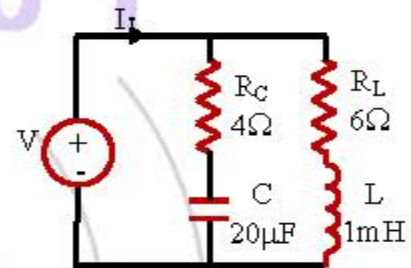
$$\therefore \omega_0 = \frac{1}{\sqrt{10^{-3} \times 20 \times 10^{-6}}} \sqrt{\frac{6^2 - 10^{-3} / 20 \times 10^{-6}}{4^2 - 10^{-3} / 20 \times 10^{-6}}} = 4537.42 \text{ rad/sec or } f_0 = \omega_0 / 2\pi = 722 \text{ Hz}$$




**Example:** For the circuit shown, estimate  $\omega_0$  w.r.t. circuit elements.

**Solution:**

$$Y = \frac{1}{R_g} + \frac{1}{R + j\omega L} + j\omega C$$

$$Y = \left( \frac{1}{R_g} + \frac{R}{R^2 + (\omega L)^2} \right) + j \left( \omega C - \frac{\omega L}{R^2 + (\omega L)^2} \right) \quad \text{at resonance imaginary part of } (Y) = 0$$

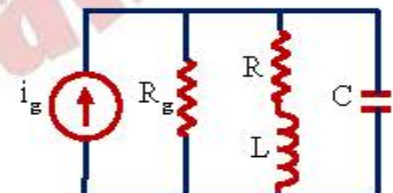
$$\therefore \omega_0 C = \frac{\omega_0 L}{R^2 + (\omega_0 L)^2} \Rightarrow \omega_0^2 = \frac{1}{LC} - \left( \frac{R}{L} \right)^2 \quad \text{or} \quad \boxed{\omega_0 = \sqrt{\frac{1}{LC} - \left( \frac{R}{L} \right)^2}}$$



### 8.4 More on Serial and Parallel Resonant Circuits:

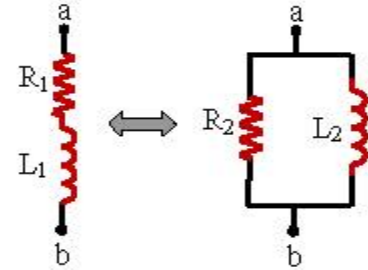a. RL Serial to Parallel:

$$\left. \begin{aligned} R_2 &= R_1(1 + Q_S^2) \\ L_2 &= L_1 \left(1 + \frac{1}{Q_S^2}\right) \end{aligned} \right\} Q_S = \frac{\omega_0 L_1}{R_1}$$




b. RL Parallel to Serial:

$$\left. \begin{aligned} R_1 &= R_2 \left(\frac{1}{1 + Q_P^2}\right) \\ L_1 &= L_2 \left(\frac{Q_P^2}{1 + Q_P^2}\right) \end{aligned} \right\} Q_P = \frac{R_2}{\omega_0 L_2}$$

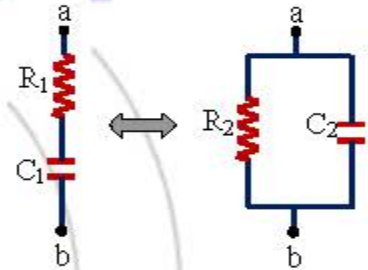c. RC Serial to Parallel:

$$\left. \begin{aligned} R_2 &= R_1(1 + Q_S^2) \\ C_2 &= C_1 \left(\frac{Q_S^2}{1 + Q_S^2}\right) \end{aligned} \right\} Q_S = \frac{1}{\omega_0 R_1 C_1}$$



d. RC Parallel to Serial:

$$\left. \begin{aligned} R_1 &= R_2 \left(\frac{1}{1 + Q_P^2}\right) \\ C_1 &= C_2 \left(1 + \frac{1}{Q_P^2}\right) \end{aligned} \right\} Q_P = \omega_0 R_2 C_2$$

**Example:** For the circuit shown, find the quality factor and Bandwidth.

**Solution:**

$$\omega_0 = \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2} = \sqrt{\frac{1}{5 \times 10^{-3} \times 0.02 \times 10^{-6}} - \left(\frac{25}{5 \times 10^{-3}}\right)^2}$$

$$= 100 \text{Krad/s} \quad \text{or} \quad f_0 = \frac{\omega_0}{2\pi} = 15.9 \text{KHz}$$

$$Q_S = \frac{\omega_0 L}{R} = \frac{100 \times 10^3 \times 5 \times 10^{-3}}{25} = 20$$


$$R_P = R(1 + Q_S^2) = 25(1 + (20)^2) = 10025 \Omega$$

$$R_T = \frac{R_g \times R_P}{R_g + R_P} = \frac{4.7 \times 10^3 \times 10025}{4.7 \times 10^3 + 10025} = 3.2 \text{K}\Omega$$

$$L_P = L \left(1 + \frac{1}{Q_S^2}\right) = 5 \times 10^{-3} \left(1 + \frac{1}{20^2}\right) = 5.0125 \text{mH}$$

$$Q_P = \frac{R_T}{\omega_0 L_P} = \frac{3.2 \times 10^3}{100 \times 10^3 \times 5.0125 \times 10^{-3}} = 6.38 = \omega_0 R_T C$$

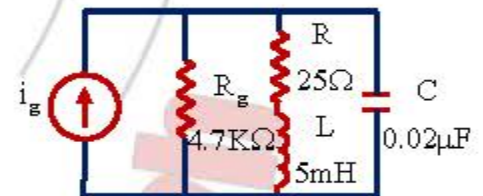
$$\text{B.W} = \frac{f_0}{Q_P} = \frac{15.9 \times 10^3}{6.38} = 2.49 \text{KHz}$$





**Example:** For the circuit shown, find:

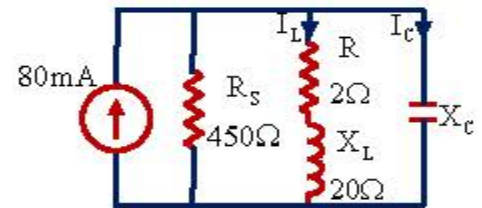1. The value of  $X_C$  at resonance.
2. The total circuit impedance at resonance.
3. The currents  $I_L$  &  $I_C$  at resonance.
4. The value of "L" & "C" at resonance frequency 20KHz.
5. Parallel quality factor and Bandwidth.



**Solution:**

$$1. Y = \frac{1}{R_S} + \frac{1}{R + j\omega L} + j\omega C = \left( \frac{1}{R_S} + \frac{R}{R^2 + (\omega L)^2} \right) + j \left( \omega C - \frac{\omega L}{R^2 + (\omega L)^2} \right)$$

At resonance the imaginary part of (Y)=0

$$\therefore \omega_0 C = \frac{\omega_0 L}{R^2 + (\omega_0 L)^2} = \frac{X_L}{R^2 + X_L^2} = \frac{20}{2^2 + 20^2} = 0.0495$$

$$X_C = \frac{1}{\omega_0 C} = 20.2 \Omega$$

$$2. Y = \frac{1}{450} + \frac{2}{2^2 + 20^2} = 0.00717 \text{ } \Omega^{-1} \quad \text{Just real part of (Y) or real value at resonance}$$

$$Z = \frac{1}{Y} = 139.42 \Omega$$

$$3. Q_S = \frac{\omega_0 L}{R} = \frac{X_L}{R} = \frac{20}{2} = 10$$

$$R_P = R (1 + Q_S^2) = 2(1 + 10^2) = 202 \Omega$$

$$R_T = \frac{R_S \times R_P}{R_S + R_P} = \frac{450 \times 202}{450 + 202} = 139.4 \Omega$$

$$V_o(\omega_0) = I_m R_T = 80 \times 10^{-3} \times 139.4 = 11.15 \text{ V}$$

$$I_C = V_o(\omega_0) Y_C = 11.15 \times 0.0495 = 0.552 \text{ A} = I_{LP} \quad (\text{phase difference } 180^\circ)$$

$$I_{RP} = \frac{V_o}{R_P} = \frac{11.15}{202} = 0.0552 \text{ A}$$

$$I_L = \sqrt{(I_{RP})^2 + (I_{LP})^2} = \sqrt{(0.0552)^2 + (0.552)^2} = 0.555 \text{ A}$$

$$4. L = \frac{Q_S R}{\omega_0} = \frac{10 \times 2}{2\pi \times 20 \times 10^3} = 0.159 \text{ mH}$$

$$L_P = L \left( 1 + \frac{1}{Q_S^2} \right) = 0.159 \times 10^{-3} \left( 1 + \frac{1}{10^2} \right) = 0.16 \text{ mH}$$

$$C = \frac{1}{\omega_0^2 L_P} = \frac{1}{(2\pi \times 20 \times 10^3)^2 \times 0.16 \times 10^{-3}} = 0.396 \mu\text{F}$$

$$5. Q_P = \frac{R_T}{\omega_0 L_P} = \frac{139.4}{2\pi \times 20 \times 10^3 \times 0.16 \times 10^{-3}} = 6.94 = \omega_0 R_T C$$

$$\text{B.W} = \frac{f_0}{Q_P} = \frac{20 \times 10^3}{6.94} = 2.9 \text{ KHz}$$

