

13.1 The Laplace Transform in Electric Circuits Transient:

Laplace Transform has two characteristics:

1. It transforms a set of linear constant-coefficient differential equations into a set of linear polynomial equations.
2. It automatically introduces into the polynomial equations the initial values of the current and voltage variables.

$$\mathcal{L}\{f(t)\} = F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

a. Step Function:

$$f(t) = u(t) = \begin{cases} 0, & t < 0 \\ A, & t \geq 0 \end{cases} \quad \text{Apply L.T method:}$$

$$\mathcal{L}\{u(t)\} = \int_0^{\infty} Ae^{-st} dt = \frac{A}{s} = \frac{1}{s} = F(s)$$

b. Ramp Function:

$$f(t) = \begin{cases} 0, & t < 0 \\ t, & t \geq 0 \end{cases} \quad \text{Apply L.T method:}$$

$$\mathcal{L}\{u(t)\} = \int_0^{\infty} te^{-st} dt = \frac{1}{s^2} = F(s)$$

c. Exponential Function:

$$f(t) = \begin{cases} e^{-at}, & t \geq 0 \\ 0, & t < 0 \end{cases} \quad \text{Apply L.T method:}$$

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} e^{-at}e^{-st} dt = \left[\frac{e^{-(a+s)t}}{-(a+s)} \right]_0^{\infty} = \frac{1}{s+a} = F(s)$$

d. Sine and Cosine Wave Functions:

$$f(t) = \begin{cases} \sin\omega t, & t \geq 0 \\ 0, & t < 0 \end{cases} \quad \text{Apply L.T method:}$$

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} \sin\omega te^{-st} dt \quad \text{where } e^{j\theta} = \cos\theta + j\sin\theta$$

$$\begin{aligned} \therefore \mathcal{L}\{f(t)\} &= \int_0^{\infty} \text{Im}e^{j\omega t} e^{-st} dt = \text{Im} \left[\frac{e^{-(s-j\omega)t}}{-(s-j\omega)} \right]_0^{\infty} \\ &= \text{Im} \left[\frac{1}{s-j\omega} \right] = \text{Im} \left[\frac{s}{s^2+\omega^2} + j \frac{\omega}{s^2+\omega^2} \right] = \frac{\omega}{s^2+\omega^2} = F(s) \end{aligned}$$

$$\text{in the same way. } \mathcal{L}\{\cos\omega t\} = \frac{s}{s^2+\omega^2} = F(s)$$

e. Special Functions:

$$\mathcal{L}\{te^{-at}\} = \frac{1}{(s+a)^2}$$

$$\mathcal{L}\{e^{-at}\sin\omega t\} = \frac{\omega}{(s+a)^2+\omega^2}$$

$$\mathcal{L}\{e^{-at}\cos\omega t\} = \frac{s+a}{(s+a)^2+\omega^2}$$

f. Differential Function:

$$\mathcal{L}\left\{\frac{df(t)}{dt}\right\} = sF(s) - f(0)$$





g. Integration Function:

$$\mathcal{L}\left\{\int_0^t f(x) dx\right\} = \frac{F(s)}{s} + \frac{1}{s} \int f(t)|_{t=0} dt$$

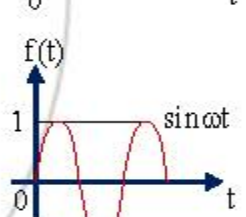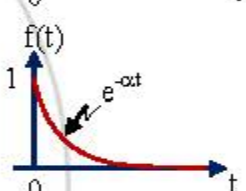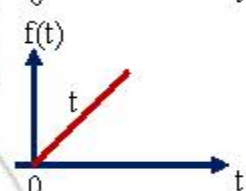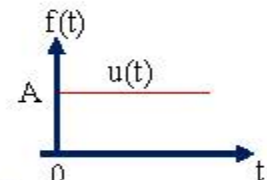Example: Find the Laplace Transform for 100V DC supply.

Solution:

$$\mathcal{L}\{f(t)\} = F(s) = \int_0^{\infty} 100e^{-st} dt = 100 \left[\frac{e^{-st}}{-s} \right]_0^{\infty} = \frac{100}{s}$$



13.2 Inverse Laplace Transform:

a. Using Properties:

$$\mathcal{L}^{-1}\left[\frac{100}{s}\right] = 100 \quad \mathcal{L}^{-1}\left[\frac{1}{s+\alpha}\right] = e^{-\alpha t} \quad \mathcal{L}^{-1}\left[\frac{\omega}{s^2+\omega^2}\right] = \sin\omega t$$

b. Using Partial-Fraction Expansion:

$$F(s) = \frac{s+6}{s(s+3)(s+1)^2} = \frac{K_1}{s} + \frac{K_2}{s+3} + \frac{K_3}{(s+1)^2} + \frac{K_4}{s+1}$$

$$\mathcal{L}^{-1}\left\{\frac{s+6}{s(s+3)(s+1)^2}\right\} = (K_1 + K_2e^{-3t} + K_3te^{-t} + K_4e^{-t})u(t)$$

$$K_1 = \left.\frac{s+6}{(s+3)(s+1)^2}\right|_{s=0} = 2$$

$$K_2 = \left.\frac{s+6}{s(s+1)^2}\right|_{s=-3} = \frac{-1}{4}$$

$$K_3 = \left.\frac{s+6}{s(s+3)}\right|_{s=-1} = \frac{-5}{2}$$

$$K_4 = \left.\frac{d}{ds}\left[\frac{s+6}{s(s+3)}\right]\right|_{s=-1} = \frac{-17}{4}$$

c. Using Long Division:

$$F(s) = \frac{s^4+13s^3+66s^2+200s+300}{s^2+9s+20} = s^2 + 4s + 10 + \frac{30s+100}{s^2+9s+20}$$

$$= s^2 + 4s + 10 - \frac{20}{s+4} + \frac{50}{s+5}$$

$$\therefore f(t) = \frac{d^2\delta}{dt^2} + 4\frac{d\delta}{dt} + 10\delta - (20e^{-4t} - 50e^{-5t})u(t)$$

13.3 Initial and Final Value Theorems:

a- Initial Value Theorem:

$$\mathcal{L}\left\{\frac{df(t)}{dt}\right\} = \int_0^{\infty} \frac{df(t)}{dt} e^{-st} dt = sF(s) - f(0)$$

$$\lim_{s \rightarrow \infty} \int_0^{\infty} \frac{df(t)}{dt} e^{-st} dt = \lim_{s \rightarrow \infty} [sF(s) - f(0)]$$

$$\text{as } s \rightarrow \infty \text{ then } \frac{df(t)}{dt} e^{-st} \rightarrow 0$$

$$\therefore \lim_{s \rightarrow \infty} [sF(s) - f(0)] = 0 \Rightarrow \lim_{s \rightarrow \infty} [sF(s)] = f(0)$$

$$\boxed{\lim_{t \rightarrow 0} [f(t)] = \lim_{s \rightarrow \infty} [sF(s)]}$$

b- Final Value Theorem:

$$\mathcal{L}\left\{\frac{df(t)}{dt}\right\} = \int_0^{\infty} \frac{df(t)}{dt} e^{-st} dt = sF(s) - f(0)$$

$$\lim_{s \rightarrow 0} \int_0^{\infty} \frac{df(t)}{dt} e^{-st} dt = \lim_{s \rightarrow 0} [sF(s) - f(0)]$$

$$\text{as } s \rightarrow 0 \text{ then } e^{-st} \rightarrow 1$$

$$\lim_{s \rightarrow 0} \int_0^{\infty} \frac{df(t)}{dt} dt = \lim_{s \rightarrow 0} \int_0^{\infty} df(t) = f(\infty) - f(0)$$

$$\therefore f(\infty) - f(0) = \lim_{s \rightarrow 0} [sF(s)] - f(0) \Rightarrow \lim_{s \rightarrow 0} [sF(s)] = f(\infty)$$

$$\boxed{\lim_{t \rightarrow \infty} [f(t)] = \lim_{s \rightarrow 0} [sF(s)]}$$


Example: Find the initial and final values of $I_1(s) = \frac{6.67(s+250)}{s(s+166.7)}$, $I_2(s) = \frac{5}{s+2000}$.

Solution:

$$i_1(0) = \lim_{s \rightarrow \infty} \frac{6.67s(s+250)}{s(s+166.7)} = 6.67 \text{ Amp.} \quad i_1(\infty) = \lim_{s \rightarrow 0} \frac{6.67s(s+250)}{s(s+166.7)} = 10 \text{ Amp.}$$

$$i_2(0) = \lim_{s \rightarrow \infty} \frac{5s}{s+2000} = 5 \text{ Amp.} \quad i_2(\infty) = \lim_{s \rightarrow 0} \frac{5s}{s+2000} = 0 \text{ Amp.}$$

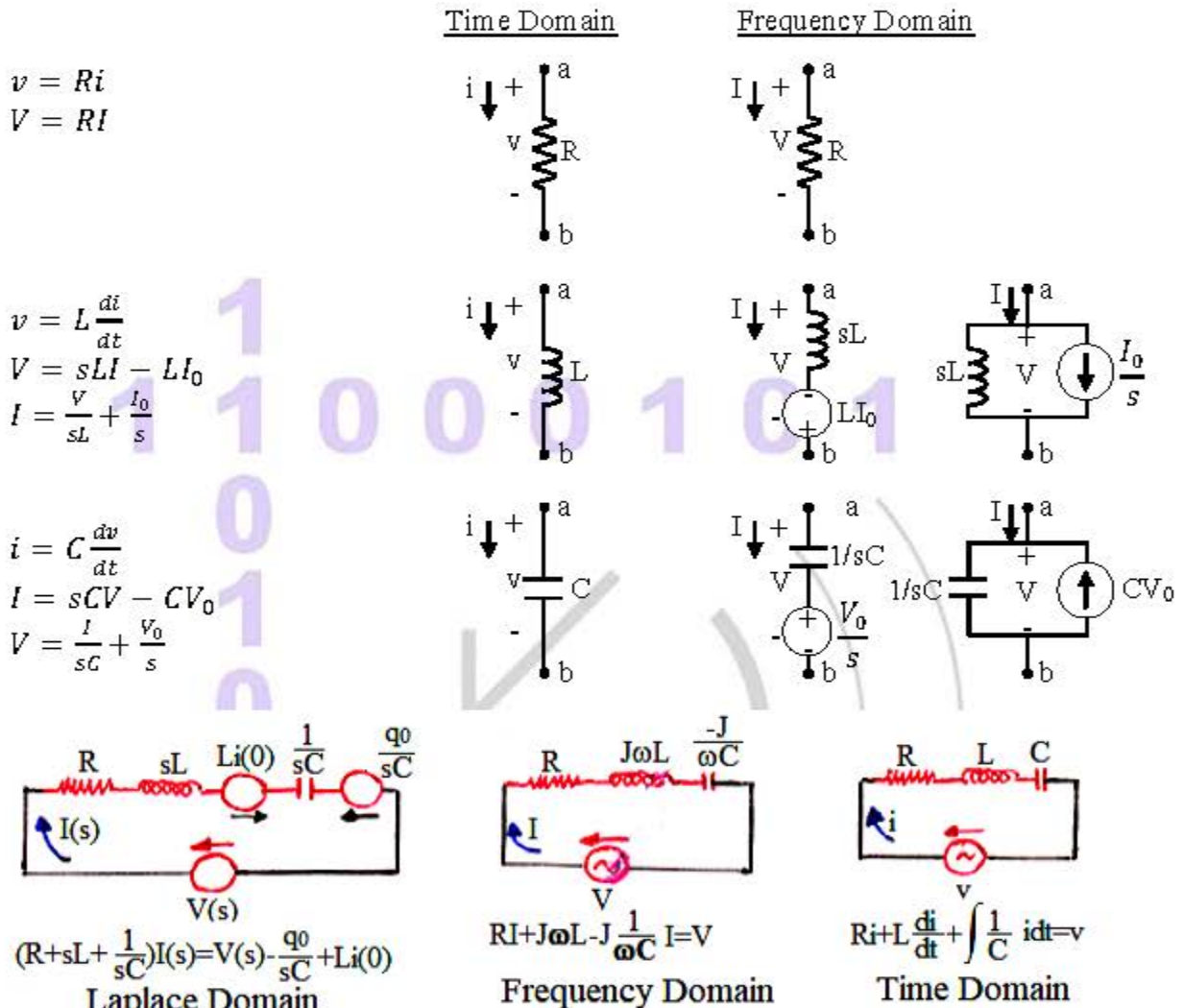13.4 The Laplace Transform in Circuit Analysis:



a. RLC Series Circuit:

$$v = v_R + v_L + v_C$$

$$v = Ri + L \frac{di}{dt} + \frac{1}{C} \int idt \quad \text{Take L.T. for both sides,}$$

$$V(s) = RI(s) + L(sI(s) - i(0)) + \frac{1}{C} \left(\frac{I(s)}{s} + \frac{\int idt|_{t=0}}{s} \right)$$

$$\left(R + Ls + \frac{1}{Cs} \right) I(s) = V(s) + Li(0) - \frac{q_0}{Cs}$$

$$\therefore I(s) = \frac{V(s) + Li(0) - \frac{q_0}{Cs}}{R + Ls + \frac{1}{Cs}}$$

b. RLC Parallel Circuit:

$$i = i_R + i_L + i_C$$

$$i = \frac{v}{R} + \frac{1}{L} \int vdt + C \frac{dv}{dt} \quad \text{Take L.T. for both sides,}$$

$$I(s) = \frac{V(s)}{R} + \frac{1}{L} \left(\frac{V(s)}{s} + \frac{\int vdt|_{t=0}}{s} \right) + C(sV(s) - v(0))$$

$$\left(\frac{1}{R} + \frac{1}{Ls} + Cs \right) V(s) = I(s) + Cv(0) - \frac{i_0}{Ls}$$

$$\therefore V(s) = \frac{I(s) + Cv(0) - \frac{i_0}{Ls}}{\frac{1}{R} + \frac{1}{Ls} + Cs}$$

Example: For the circuit shown, Assuming zero initial condition when the switch closed at $t=0$. Find:
1. The transient current equation and the voltage across each element.

2. The value of resistance to drop the inductance voltage to 25V at $t=25\text{msec}$.

Solution:

Apply L.T. to the circuit:

1. $i_0 = 0 = i(0)$ no initial energy stored in the coil

$$I(s) = \frac{V/s}{R+Ls} = \frac{100/s}{50+10s} = \frac{10}{s(s+5)} = \frac{A}{s} + \frac{B}{s+5}$$

$$A = \frac{V/L}{s+R/L} \Big|_{s=0} = \frac{10}{s+5} \Big|_{s=0} = 2 = \frac{V}{R}$$

$$B = \frac{V/L}{s} \Big|_{s=-R/L} = \frac{10}{s} \Big|_{s=-5} = -2 = -\frac{V}{R}$$

$$\therefore I(s) = \frac{V}{R} \left(\frac{1}{s} - \frac{1}{s+\frac{R}{L}} \right) = 2 \left(\frac{1}{s} - \frac{1}{s+5} \right)$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\} = \frac{V}{R} (1 - e^{-\frac{R}{L}t}) = 2(1 - e^{-5t}) \text{ Amp. } t \geq 0$$

$$V_R = 50 * I(s) = \frac{500}{s(s+5)} = \frac{100}{s} - \frac{100}{s+5}$$

$$\therefore V_R(t) = \mathcal{L}^{-1}\{V_R(s)\} = V (1 - e^{-\frac{R}{L}t}) = 100(1 - e^{-5t}) \text{ Volt } t \geq 0$$

$$V_L = 10s * I(s) = \frac{100}{s+5} \Rightarrow V_L(t) = \mathcal{L}^{-1}\{V_L(s)\} = Ve^{-\frac{R}{L}t} = 100e^{-5t} \text{ Volt } t \geq 0$$

2. $V_L(25\text{msec}) = 25 = 100e^{-\frac{R}{10} \cdot 25 \cdot 10^{-3}} \Rightarrow R = 554.52\Omega$

Example: For the circuit shown, find the transient current equation and the voltage across each element when the switch closed at $t=0$ with $q_0=10\mu\text{Coulomb}$. Also find the value of resistance to drop the capacitance voltage to 25V at $t=25\text{msec}$.

Solution:

Apply L.T. to the circuit:

$$I(s) = \frac{\frac{V}{s} - \frac{q_0}{Cs}}{R + \frac{1}{Cs}} = \frac{\frac{50}{s} - \frac{10^{-6}}{50s}}{10 \times 10^3 + \frac{10^6}{50s}} = \frac{0.00498}{s+2} = \frac{v - \frac{q_0}{C}}{R} \times \frac{1}{s + \frac{1}{RC}}$$

$$i(t) = \mathcal{L}^{-1}\{I(s)\} = \frac{V - \frac{q_0}{C}}{R} e^{-\frac{1}{RC}t} = 5e^{-2t} \text{ mA } t \geq 0$$





$$\therefore i(t)|_{q_0=0} = \frac{V}{R} e^{-\frac{1}{RC}t} \text{ A } t \geq 0 \text{ and } V_R = 10 * 10^3 * I(s) = \frac{50}{s+2}$$

$$\therefore V_R(t) = \mathcal{L}^{-1}\{V_R(s)\} = (V - \frac{q_0}{C}) e^{-\frac{1}{RC}t} = 50e^{-2t} \text{ Volt } t \geq 0$$


$$V_C = \frac{1}{5s} - \frac{10^6}{50s} * I(s) = \frac{s-498}{5s(s+2)} = \frac{50}{s} - \frac{50}{s+2} \text{ with approximated values}$$

$$\therefore V_C(t) = \mathcal{L}^{-1}\{V_C(s)\} = (V - \frac{q_0}{C}) e^{-\frac{1}{RC}t} = 50(1 - e^{-2t}) \text{ Volt } t \geq 0$$
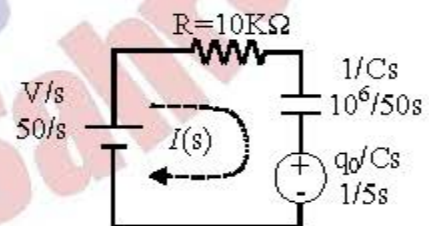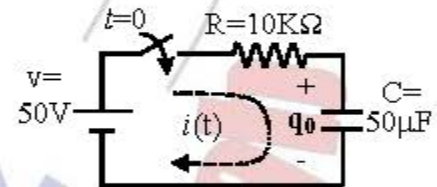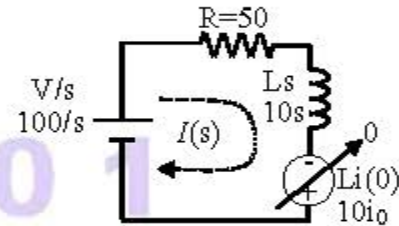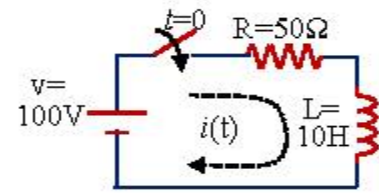
$$V_C(25\text{msec}) = 25 = 50 \left(1 - e^{-\frac{25 \cdot 10^{-3}}{R \cdot 50 \cdot 10^{-6}}} \right) \Rightarrow R = 721.35\Omega$$



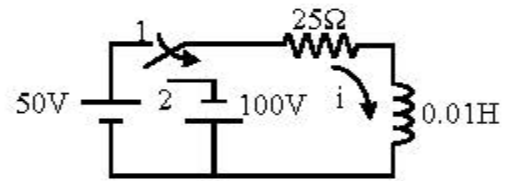Example: In the circuit shown, if the switch was be in position "1" for a long time then at $t=0$ moved to position "2". Find the transient current equation in each case using L.T. method.



Solution:

The switch in position "1"; Apply L.T. to the circuit:

$$I(s) = \frac{V/s}{R+Ls} = \frac{50/s}{25+0.01s} = \frac{5000}{s(s+2500)} = \frac{A}{s} + \frac{B}{s+2500}$$

$$A = \left. \frac{5000}{s+2500} \right|_{s=0} = 2 \text{ and } B = \left. \frac{5000}{s} \right|_{s=-2500} = -2$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\} = 2(1 - e^{-2500t}) \text{ Amp. } t < 0$$



$$\lim_{s \rightarrow 0} sI(s) = 2 \text{ Amp.} = \lim_{t \rightarrow \infty} i(t) \text{ steady-state}$$

The switch in position "2"; Apply L.T. to the circuit:


$$I(s) = \frac{V/s - Li_0}{R+Ls} = \frac{100/s - 0.02}{25+0.01s} = \frac{-2s+10000}{s(s+2500)} = \frac{A}{s} + \frac{B}{s+2500}$$

$$A = \left. \frac{-2s+10000}{s+2500} \right|_{s=0} = 4 \text{ and } B = \left. \frac{-2s+10000}{s} \right|_{s=-2500} = -6$$
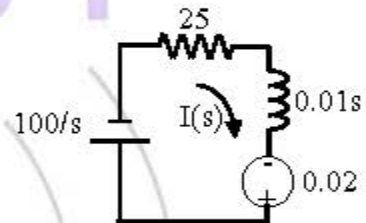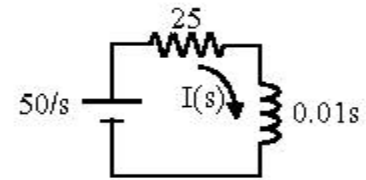
$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\} = 4 - 6e^{-2500t} \text{ Amp. } t \geq 0$$



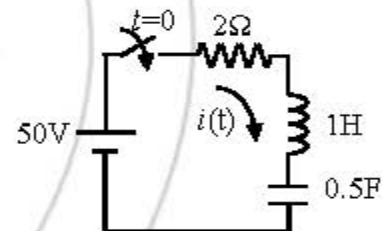Example: For the circuit shown, when the switch closed at $t=0$ and by assuming zero initial charge on the capacitor terminals. Find the transient current equation w.r.t. time and the voltage across each element.



Solution:

Apply L.T. to the circuit:

$$I(s) = \frac{V/s}{R+Ls+\frac{1}{Cs}} = \frac{50/s}{2+s+\frac{2}{s}} = \frac{50}{s^2+2s+2} = \frac{A}{s+1+j} + \frac{B}{s+1-j}$$

$$A = \left. \frac{50}{s+1-j} \right|_{s=-1-j} = 25j \text{ and } B = \left. \frac{50}{s+1+j} \right|_{s=-1+j} = -25j$$

$$\therefore i(t) = \mathcal{L}^{-1}\{I(s)\} = j25(e^{-(1+j)t} - e^{-(1-j)t})$$

$$= 50e^{-t} \left[\frac{e^{jt} - e^{-jt}}{2j} \right] = 50e^{-t} \sin t \text{ Amp. } t \geq 0$$

$$V_R = R * I(s) = \frac{100}{s^2+2s+2} = \frac{100}{(s+1)^2+1}$$


$$\therefore V_R(t) = \mathcal{L}^{-1}\{V_R(s)\} = 100e^{-t} \sin t \text{ Volt } t \geq 0$$

$$V_L = Ls * I(s) = \frac{50s}{s^2+2s+2} = \frac{50(s+1)}{(s+1)^2+1} - \frac{50}{(s+1)^2+1}$$

$$\therefore V_L(t) = \mathcal{L}^{-1}\{V_L(s)\} = 50e^{-t} \cos t - 50e^{-t} \sin t = 50e^{-t} (\cos t - \sin t) \text{ Volt } t \geq 0$$

$$V_C = \frac{2}{s} * I(s) = \frac{100}{s(s^2+2s+2)} = \frac{A}{s} + \frac{Bs+C}{(s+1)^2+1} = \frac{50}{s} - \frac{50s+100}{(s+1)^2+1}$$
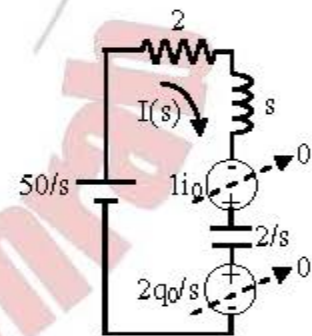
$$\therefore V_C(t) = \mathcal{L}^{-1}\{V_C(s)\} = 50(1 - e^{-t} \cos t - e^{-t} \sin t) \text{ Volt } t \geq 0$$



Note:

$$\mathcal{L}\{\sin(\omega t + \psi)\} = \frac{s \sin \psi + \omega \cos \psi}{s^2 + \omega^2} \quad \dots(*)$$

$$\mathcal{L}\{\cos(\omega t + \psi)\} = \frac{s \cos \psi - \omega \sin \psi}{s^2 + \omega^2} \quad \dots(**)$$