

Simplification of Boolean Functions

Another method of simplification of Boolean function is Karnaugh – Map (K-Map). This map is a diagram made of squares, each square represent one minterms, and there are several types of K-Map depending on the number of variables in Boolean function.

1-Two – variable K-Map

		Y	0	1
X	0	M0	M1	
	1	M2	M3	

		Y	0	1
X	0	$\bar{X}\bar{Y}$	$\bar{X}Y$	
	1	$X\bar{Y}$	XY	

2 – Three – variable K – Map

		YZ	00	01	11	10
X	0	M0	M1	M3	M2	
	1	M4	M5	M7	M6	

		YZ	00	01	11	10
X	0	$\bar{X}\bar{Y}\bar{Z}$	$\bar{X}\bar{Y}Z$	$\bar{X}YZ$	$\bar{X}Y\bar{Z}$	
	1	$X\bar{Y}\bar{Z}$	$X\bar{Y}Z$	XYZ	$XY\bar{Z}$	

3 – Four – variable K-Map

		ZW	00	01	11	10
XY	00	0	1	3	2	
	01	4	5	7	6	
	11	12	13	15	14	
	10	8	9	11	10	

		ZW	00	01	11	10
XY	00					
	01					
	11					
	10					

3 – Five and Six variables K-Map

		CDE							
		000	001	011	010	110	111	101	100
AB	00	0	1	3	2	6	7	5	4
	01	8	9	11	10	14	15	13	12
	11	24	25	27	26	30	31	29	28
	10	16	17	19	18	22	23	21	20

		DEF							
		000	001	011	010	110	111	101	100
ABC	000	0	1	3	2	7	6	5	4
	001	8	9	11	10	14	15	13	12
	011	24	25	27	26	30	31	29	28
	010	16	17	19	18	22	23	21	20
	110	48	49	51	50	54	55	53	52
	111	56	57	59	58	62	63	61	60
	101	40	41	43	42	46	47	45	44
	100	32	33	35	34	38	39	37	36

Ex Simply the following Boolean functions using K –Map?

$$1 - F = \overline{X}YZ + X\overline{Y}\overline{Z} + X\overline{Y}Z + \overline{X}Y\overline{Z}$$

		YZ			
	X	00	01	11	10
	0			1	1
	1	1	1		

$$F = \overline{X}Y + \overline{X}Y$$

If the function is simplified using Boolean- algebra

$$F = \overline{X}YZ + X\overline{Y}\overline{Z} + X\overline{Y}Z + \overline{X}Y\overline{Z}$$

$$\overline{X}Y(Z + \overline{Z}) + X\overline{Y}(Z + \overline{Z}) = \overline{X}Y + X\overline{Y}$$

$$2 - F = \overline{X}YZ + X\overline{Y}\overline{Z} + X\overline{Y}Z + X\overline{Y}\overline{Z}$$

		YZ			
	X	00	01	11	10
	0			1	
	1	1		1	1

$$F = YZ + X\overline{Z}$$

$$3 - F = \overline{A}C + \overline{A}B + A\overline{B}C + BC$$

In this function each term must expressed by all variables in the function (A,B,C)

$$F(A,B,C) = \overline{A}C.1 + \overline{A}B.1 + A\overline{B}C + BC.1$$

$$= \overline{A}C(B + \overline{B}) + \overline{A}B(C + \overline{C}) + A\overline{B}C + BC(A + \overline{A})$$

$$= \overline{A}BC + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}B\overline{C} + A\overline{B}C + A\overline{B}C + \overline{A}BC + \overline{A}BC$$

$$= \overline{A} B C + \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} C + A B C$$

		BC			
		00	01	11	10
A	0		1	1	1
	1		1	1	

$$F = C + \overline{A} B$$

4 - $F(X,Y,Z) = \sum(0, 2, 4, 5, 6)$

		YZ			
		00	01	11	10
X	0	1			1
	1	1	1		1

$$F(X,Y,Z) = \overline{Z} + X \overline{Y}$$

5 - $F(X,Y,Z,W) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$

		ZW			
		00	01	11	10
XY	00	1	1		1
	01	1	1		1
	11	1	1		1
	10	1	1		

$$F(X,Y,Z,W) = \overline{Z} + \overline{X} \overline{W} + Y \overline{W}$$

$$6 - F = \overline{A} \overline{B} \overline{C} + \overline{B} C \overline{D} + \overline{A} B C \overline{D} + A \overline{B} \overline{C}$$

		CD			
		00	01	11	10
AB	00	1	1		1
	01				1
	11				
	10	1	1		1

$$F(A,B,C,D) = \overline{B} \overline{D} + \overline{B} \overline{C} + \overline{A} C \overline{D}$$

$$7 - F(A,B,C,D,E) = \sum (0,2,4,6,9,11,13,15,,17,21,25,27,29,31)$$

		CDE							
		000	001	011	010	110	111	101	100
AB	00	1			1	1			1
	01		1	1			1	1	
	11		1	1			1	1	
	10		1					1	

$$F(A,B,C,D) = \overline{A} \overline{B} \overline{E} + B E + A \overline{D} E$$

H.W

Simplify the following functions in sum of product using K-map

$$1- F = \overline{X} Y + X \overline{Y} \overline{W} + W (\overline{X} Y + X \overline{Y})$$

$$2 - F = A B D + \overline{A} \overline{C} \overline{D} + \overline{A} B + \overline{A} C \overline{D} + A \overline{B} \overline{D}$$

$$3 - F(A, B, C, D) = \Pi(2, 3, 6, 7, 8, 9, 10, 11, 12, 13, 14)$$

Product of Sum simplification

In previous examples the simplification in **Sum of Product** form and each minterms represented by 1 (one) in K-map and each missing term in the function is a complement of the function and represented by 0 (zero) in k-map and the simplified expression obtained F (the complement of the function).

Ex simplify the following function in

1 – Sum of products 2 – product of Sums

$$F(A,B,C,D) = \sum (0,1, 2, 5, 8, 9, 10)$$

Sol : 1 – Sum of Products (minterms)

		CD			
		00	01	11	10
AB	00	1	1		1
	01		1		
	11				
	10	1	1		1

$$F = \bar{B} \bar{D} + \bar{B} \bar{C} + \bar{A} \bar{C} D$$

2 – Product of Sums

In this case the missing terms is represented by 0 in K-map and simplified to obtained F (complement of the function).

		CD			
		00	01	11	10
AB	00			0	
	01	0		0	0
	11	0	0	0	0
	10			0	

$$\overline{F} = A \overline{B} + C \overline{D} + B \overline{D}$$

And the basic function

$$F = (\overline{A} + \overline{B}) (\overline{C} + \overline{D}) (\overline{B} + D)$$

Ex Simplify the function F in 1 – Sum of Products 2 – Product of Sums

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Note

If the function in **Product of Sums** form then the complement of the function must take first and then the 0 is represented in k-map.

Ex: $(\bar{A} + \bar{B} + C)(B + D)$

The function in Product of Sum form, therefore the complement is take first

$$\bar{F} = A B \bar{C} + \bar{B} \bar{D}$$

Then these minterms will be assign in the map by 0 because the function is complement.

Ex : Obtained the simplified expression in Product of Sums

$$F = (\bar{A} + \bar{B} + D)(\bar{A} + \bar{D})(A + B + \bar{D})(A + \bar{B} + C + D)$$

Sol

$$\bar{F} = A B \bar{D} + A D + \bar{A} \bar{B} D + \bar{A} B \bar{C} \bar{D}$$

		CD			
		00	01	11	10
AB	00		0	0	
	01	0			
	11	0	0	0	0
	10		0	0	

$$\bar{F} = A B + \bar{B} D + B \bar{C} \bar{D}$$

$$F = (\bar{A} + \bar{B})(B + \bar{D})(\bar{B} + C + D)$$

Ex Obtain the simplified expression in Product of Sums

$$F(A, B, C, D) = \Pi(0, 1, 2, 3, 4, 10, 11)$$

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0			
	11				
	10			0	0

$$\bar{F} = \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D} + \bar{B}C$$

$$F = (A + B)(A + C + D)(B + \bar{C})$$

H.W.

Obtain the simplified expression of the following functions in 1 – Sum of Products 2 – Product of Sums

1 - $F = \bar{X}\bar{Y} + \bar{Y}\bar{Z} + Y\bar{Z} + XYZ$

2 - $F(X, Y, Z, W) = \prod(1, 3, 5, 7, 13, 15)$

3 - $F = (A + \bar{B} + D)(\bar{A} + B + D)(C + D)(\bar{C} + \bar{D})$

Don't- Care Condition

Sometimes a function table or map contains entries for which it is known:

- The input values for the minterm will never occur, or
- The output value for the minterm is not used

In these cases, the output value need not be defined, Instead, the output value is defined as a “don't care” these values are:

- 1 - Placing “don't cares” (an “x” entry) in the function table or map,
- 2 - These values used in simplification with F and \bar{F} .
- 3 - These values may be not used in simplification.

Ex simplify the Boolean function F in 1 – Sum of Products 2 – Product of Sums

$$F(X,Y,Z,W) = \Sigma(1, 3, 7, 11, 15) \quad d(X,Y,Z,W) = \Sigma(0, 2, 5)$$

Sol

1- Sum of Products

		CD			
		00	01	11	10
AB	00	X	1	1	X
	01		X	1	
	11			1	
	10			1	

$$F(X,Y,Z,W) = ZW + \bar{X}\bar{Y}$$

2 – Product of Sums

		CD			
		00	01	11	10
AB	00	X			X
	01	0	X		0
	11	0	0		0
	10	0	0		0

$$F(X,Y,Z,W) = \bar{W} + X\bar{Z}$$

$$F(X,Y,Z,W) = W(\bar{X} + \bar{Z})$$

Ex Simplify the Boolean function F in 1 – Sum of Products 2 Product of Sums using don't care condition

$$F = ACE + \bar{A}C\bar{D}\bar{E} + \bar{A}\bar{C}DE$$

$$D = D\bar{E} + \bar{A}\bar{D}E + A\bar{D}\bar{E}$$

Sol

$$F = ACE \cdot 1 + ACE + ACE + ACE$$

$$= ACE + ACE + \bar{A}C\bar{D}\bar{E} + \bar{A}\bar{C}DE$$

$$D = D\bar{E}(A + \bar{A}) + \bar{A}\bar{D}E(C + \bar{C}) + A\bar{D}\bar{E}(C + \bar{C})$$

$$= AD\bar{E}(C + \bar{C}) + \bar{A}D\bar{E}(C + \bar{C}) + \bar{A}C\bar{D}E + \bar{A}\bar{C}\bar{D}E + ACE + \bar{A}\bar{C}\bar{D}\bar{E}$$

$$= AC\bar{D}\bar{E} + \bar{A}\bar{C}\bar{D}\bar{E} + \bar{A}C\bar{D}\bar{E} + \bar{A}\bar{C}\bar{D}\bar{E} + \bar{A}C\bar{D}E + \bar{A}\bar{C}\bar{D}E + ACE + \bar{A}\bar{C}\bar{D}\bar{E}$$

1 – Sum of Products

DE AC		00	01	11	10
AC	00		X	1	X
	01	1	X		X
	11	X	1	1	X
	10	X			X

S.O.P

$$F(A,C,D,E) = AC + C\bar{E} + \bar{A}\bar{C}D$$

2 – Product of Sums

DE AC		00	01	11	10
AC	00	0	X		X
	01		X	0	X
	11	X			X
	10	X	0	0	X

P.O.S.

$$\bar{F}(A,C,D,E) = A\bar{C} + \bar{C}\bar{D} + \bar{A}CD$$

$$F(A,C,D,E) = (\bar{A} + C)(C + D)(A + \bar{C} + \bar{D})$$


Ex Simplify the Boolean function F in Sum of Products using don't care condition

$$F = \bar{B}\bar{C}\bar{D} + B\bar{C}\bar{D} + A\bar{B}\bar{C}D$$

$$D = \bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D}$$

Combinational Logic Circuit

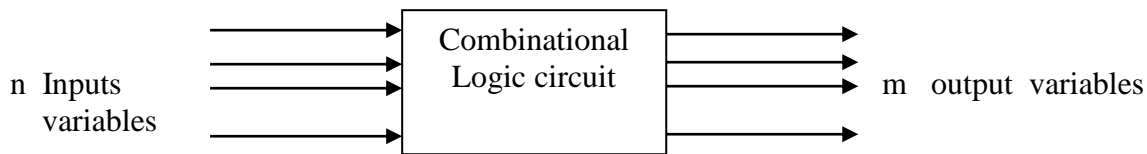A combinational circuit consist of inputs variables, logic gates and output variables. The logic gates accepts signal from the inputs and generate signal to the output. A block diagram of a combinational circuit is:



Design Procedure

The design procedure involves the following steps:-

- 1 – The problem is stated.
- 2 – The number of available input variable and required output variable is determined.
- 3- The input and output variables are assigned letter symbols.
- 4 – The truth table that defines the required relationships between inputs and outputs is derived.
- 5 – The simplified Boolean function for each output is obtained.
- 6 – The logic diagram is drowning.

The ADDERS

دوائر الجمع

1- Half Adder

It is a combinational circuit that perform the addition of two bits

$$0 + 0 = 0 \quad 0 + 1 = 1 \quad 1 + 0 = 1 \quad 1 + 1 = 0 \text{ and carry } 1$$


The circuit needs two binary inputs and two binary outputs. The truth table of half adder is:

Input		output	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


$$S = \text{Sum} \quad , \quad C = \text{Carry}$$

Truth Table

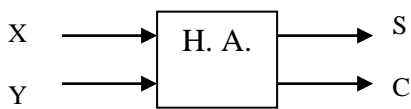The logic equations $S = \overline{X}Y + X\overline{Y} = X \oplus Y$, $C = XY$



The Block Diagram

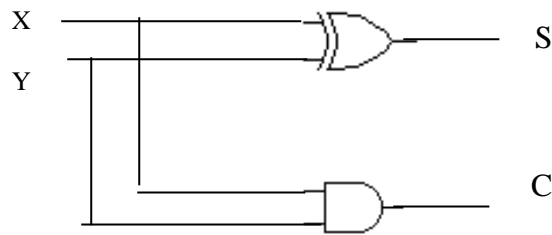

Logic Circuit


2- Full Adder

A full adder is a combinational circuit that forms the arithmetic sum of three inputs bits. It consists of three inputs and two outputs. Two of the inputs variables, X and Y, represent the two bits to be added, the third input Z, represent the carry from the previous step. The two output S (for sum) and C (for carry).

Input			Output	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table

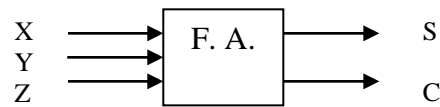To find the logic equations K- map is used



Block Diagram


		YZ				
		00	01	11	10	
X	0		1		1	=
	1	1		1		=

$$\begin{aligned}
 S &= \bar{X} \bar{Y} Z + \bar{X} Y \bar{Z} + X \bar{Y} \bar{Z} + X Y Z \\
 &= Z(\bar{X} \bar{Y} + X Y) + \bar{Z}(\bar{X} Y + X \bar{Y}) \\
 &= Z(\bar{X} \odot Y) + \bar{Z}(X \oplus Y) \\
 &= Z(\overline{X \oplus Y}) + \bar{Z}(X \oplus Y) \\
 &= X \oplus Y \oplus Z
 \end{aligned}$$

		YZ		
X \	00	01	11	10
0			1	
1		1	1	1

$$C = XY + XZ + YZ$$

The logic circuit

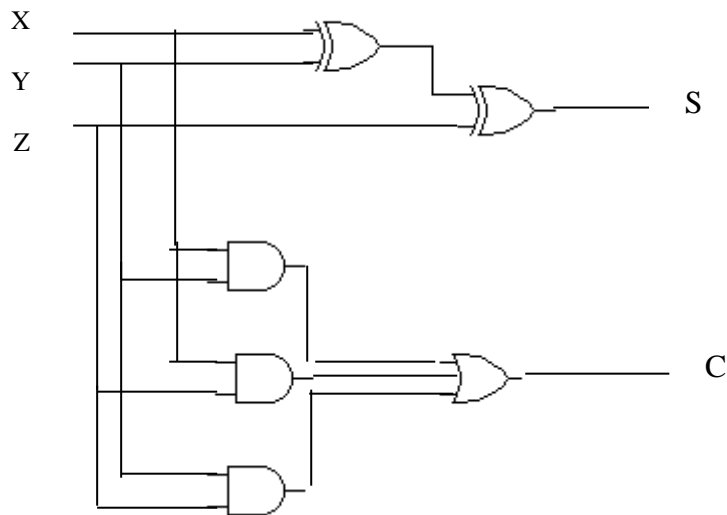

The Subtractors

1 – Half Subtractor

A half subtractor is combinational circuits that subtract two bits and produce their differences.

To perform (X-Y) the truth table is:

Input		output	
X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

D = difference , B = Borrow



Truth Table

The logic equations

$$D = \bar{X} Y + X \bar{Y} = X \oplus Y$$

$$B = \bar{X} Y$$


The Block Diagram

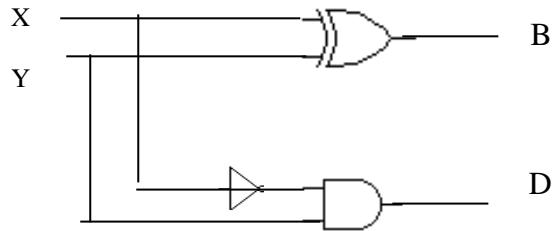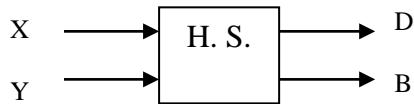

2 – Full – Subtractor

A full subtractor is a combinational circuit that perform a subtraction between two bits, taking into account that a 1 may have been borrowed. The truth table:

Input			Output	
X	Y	Z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

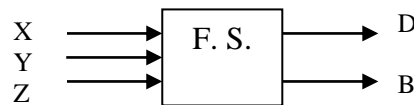


the block diagram

Truth Table

To find the logic equations K- map is used

$$B = \bar{X} Y + \bar{X} Z + Y Z$$

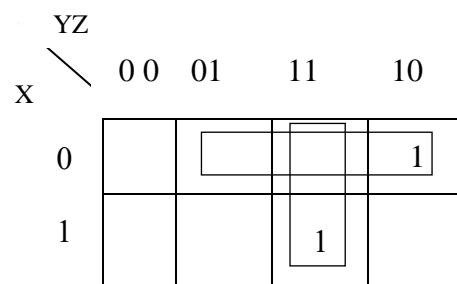

	YZ			
X	00	01	11	10
0		1		1
1	1		1	

$$D = X \bar{Y} \bar{Z} + \bar{X} \bar{Y} Z + X Y Z + \bar{X} Y \bar{Z}$$


$$= \bar{Z}(X \bar{Y} + \bar{X} Y) + Z(\bar{X} \bar{Y} + X Y)$$

$$= \bar{Z}(X \oplus Y) + Z(\overline{X \oplus Y})$$

$$= \bar{Z}(X \oplus Y) + Z(X \oplus Y)$$

$$= X \oplus Y \oplus Z$$

The logic circuit

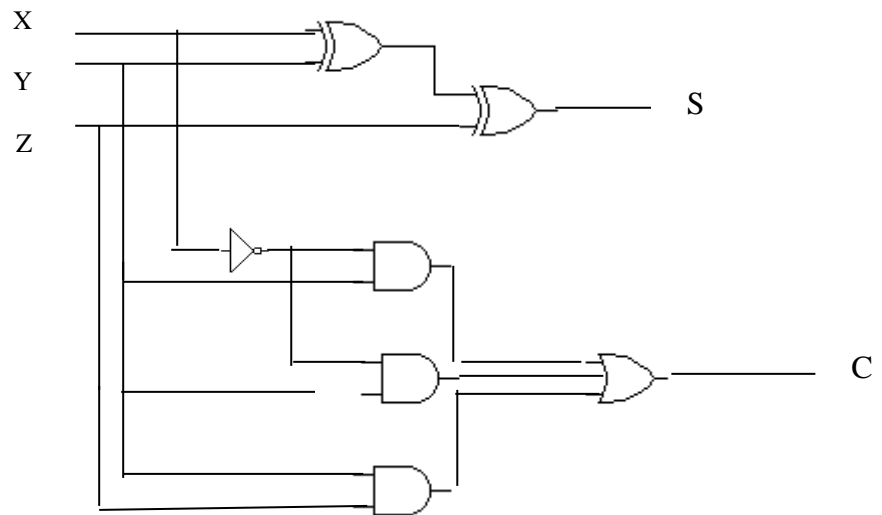

Code Conversion

To convert from binary code to another code, a combinational circuit performs this transformation by means of logic gates.

Ex Design a combinational circuit that convert a BCD code to Excess-3 code.

Sol

The truth table consists of 4 inputs and 4 outputs

Input				Output			
A	B	C	D	X	Y	Z	W
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

		CD			
		00	01	11	10
AB	00				
	01		1	1	1
	11		X	X	
	10	1	1	X	

$$\begin{aligned}
 X &= A + BD + BC \\
 &= A + B(D + C)
 \end{aligned}$$

		CD			
		00	01	11	10
AB	00		1	1	1
	01	1			
	11	X		X	X
	10			X	X

$$\begin{aligned}
 Y &= B\bar{C}\bar{D} + \bar{B}D + \bar{B} + C \\
 &= B\bar{C}\bar{D} + \bar{B}(D + C)
 \end{aligned}$$

	CD			
	00	01	11	10
AB				
00	1		1	
01	1		1	
11	X	X	X	X
10	1		X	X


	CD			
	00	01	11	10
AB				
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X

$$Z = \overline{C} \overline{D} + C D$$

$$= C \odot D$$

$$W = \overline{D}$$

The logic circuit

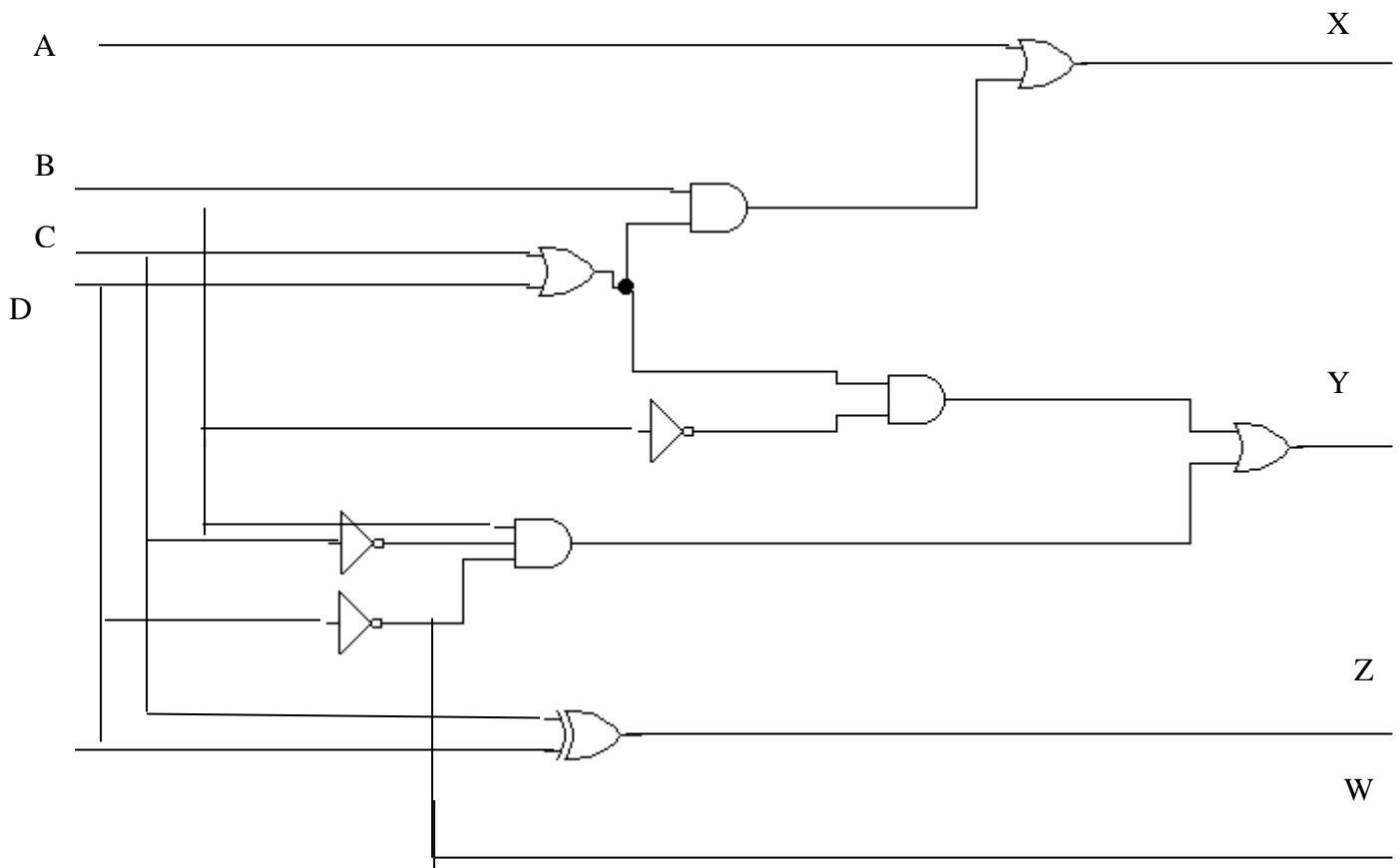

Ex A combinational circuit has four inputs and one output, the output equal 1 when:

- 1 – all the inputs are equal to 1 or
- 2 – non of the inputs are equal to 1 or
- 3 – an odd number of inputs are equal to 1.

Design the logic circuit.

Sol

Input				Output
X	Y	Z	W	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

		ZW			
		00	01	11	10
XY	00	1	1		1
	01	1		1	
	11		1	1	1
	10	1		1	

$$F = \overline{Y} \overline{Z} \overline{W} + \overline{X} \overline{Y} \overline{W} + \overline{X} \overline{Y} \overline{Z} + \overline{X} Z W$$

$$+ Y Z W + X Y W + X Y Z + \overline{Y} \overline{Z} \overline{W}$$

Ex Design a combinational circuit that inputs is three – bit numbers and the output is equal to the squared of the input numbers in binary?

Sol

Input			Output					
X	Y	Z	F ₅	F ₄	F ₃	F ₂	F ₁	F ₀
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

		YZ			
X \		00	01	11	10
0			1	1	
1			1	1	

$$F_0 = Z$$

		YZ			
X \		00	01	11	10
0					1
1					1

$$F_2 = Y \bar{Z}$$

		YZ			
X \		00	01	11	10
0				1	
1			1		

$$F_3 = \bar{X} Y Z + X \bar{Y} Z$$

		YZ			
X \		00	01	11	10
0					
1		1	1	1	


$$F_4 = X \bar{Y} + X Z$$

		YZ			
X \		00	01	11	10
0					
1				1	1


$$F_5 = X Y$$

Ex Design a Full – Adder using two Half - Adder and OR gate, draw the Block diagram and logic circuit ?

The block diagram


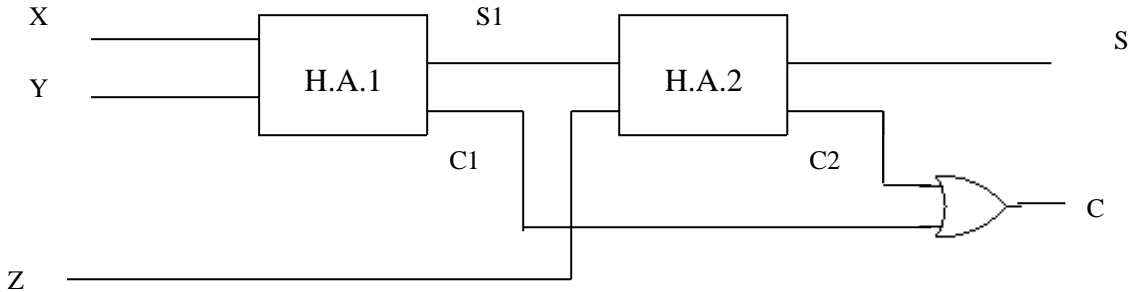


The logic circuit

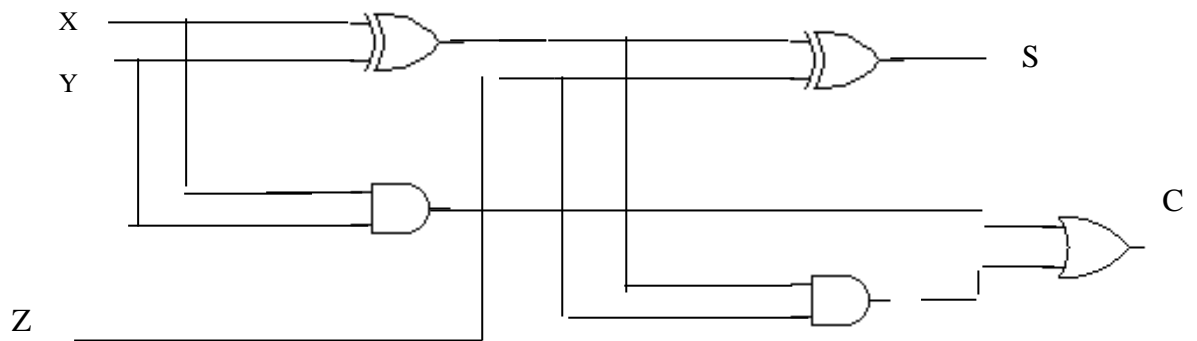

$$\begin{aligned}
 C &= C1 + C2 = X Y + (X \bar{Y} + \bar{X} Y) \cdot Z \\
 &= X Y + (X \bar{Y} + \bar{X} Y) \cdot Z \\
 &= X Y Z + X \bar{Y} Z + \bar{X} Y Z
 \end{aligned}$$

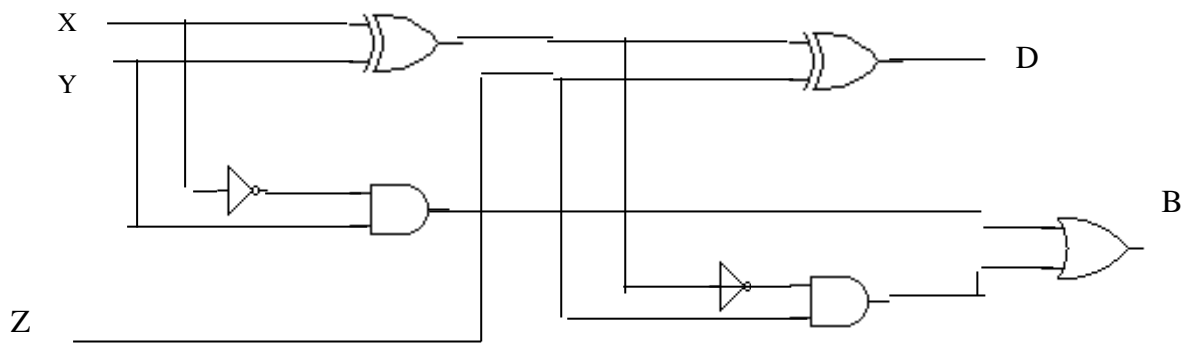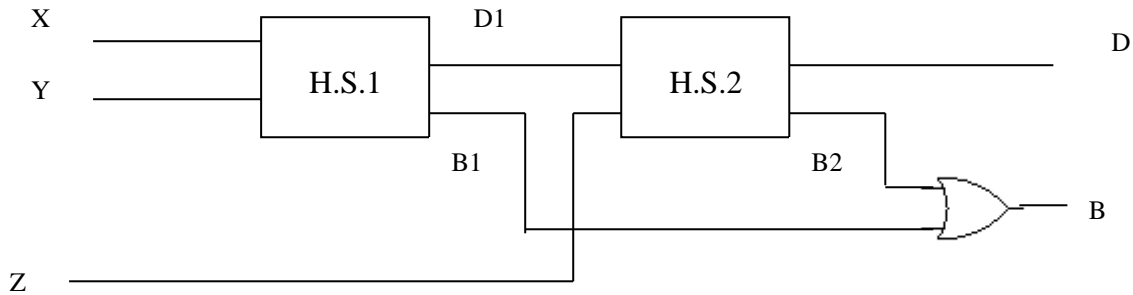Ex Design Full- Subtractor using two Half – Subtractor and OR gate, draw the Block diagram and logic circuit ?



$$B = B1 + B2 = \bar{X} Y + (\bar{X} \bar{Y}) Z = \bar{X} Y + (\bar{X} \bar{Y} + X Y) . Z$$

$$= \bar{X} Y + \bar{X} \bar{Y} Z + X Y Z = \bar{X} (Y + \bar{Y} Z) + X Y Z$$

$$\begin{aligned} &= \bar{X} (Y + \bar{Y}) (Y + Z) + X Y Z \\ &= \bar{X} Y + \bar{X} Z + X Y Z \\ &= Y (\bar{X} + X Z) + \bar{X} Z \\ &= Y (\bar{X} + X) (\bar{X} + Z) + \bar{X} Z \\ &= \bar{X} Y + Y Z + \bar{X} Z \end{aligned}$$

Ex Show that a Full-Subtractor can be obtained from a Full – adder and one inverter?