



Mustansiriyah University  
College of Sciences  
Department of Computer Science


# Logic Design

## Karnaugh Map


By: Dr. Bassam B. AlKindy

10 March 2020


# Lecture Outlines

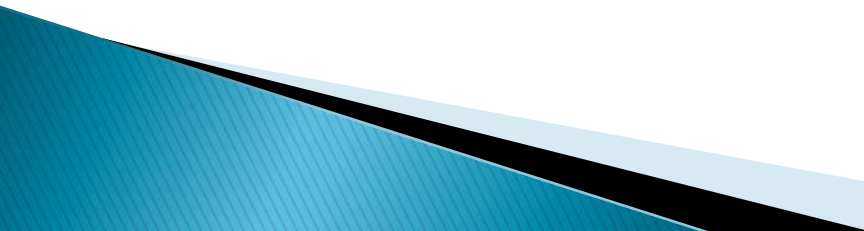- ▶ What is K-Map?
  - ▶ Why needs K-Map?
  - ▶ How to represent K-Map?
    - 2-variables function
    - 3-variables function – example
    - 4-variables function –example
    - 5-variables function – example
  - ▶ Simplify expressions using K-Maps
    - Grouping
  - ▶ Some Examples
  - ▶ Quiz
- 

# What is K-Map?

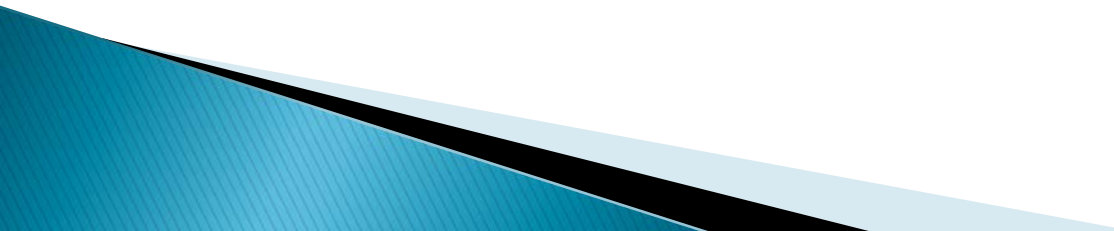- ▶ Karnaugh map or shortly K-Map, is a two dimensional graphical representation technique used to simplify the Boolean algebra expressions or from truth tables
  - ▶ It can be used to written minimal boolean expressions representing the required logic.
- 

# Why needs K-Map?

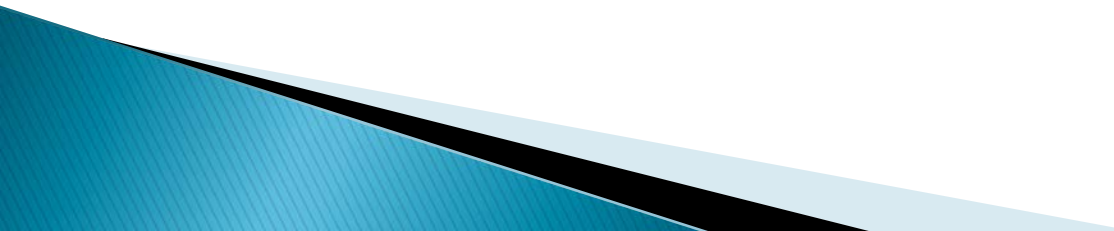- ▶ Simplify using boolean algebra is more complex than using K-Map
  - ▶ The result expression is perfectly simplified
  - ▶ Working within SOP and POS
  - ▶ Unknown truth table case(s) can be considered as don't care (**in Next Lecture**)
- 

# How to represent K-Map?

## ▶ 2-Variables function

➤ A two-variable function has four possible minterms. We can re-arrange these minterms into a **Karnaugh map**.

x	y	minterm
0	0	$x'y'$
0	1	$x'y$
1	0	$xy'$
1	1	$xy$



		y	
		0	1
x	0	$x'y'$	$x'y$
	1	$xy'$	$xy$

- Now we can easily see which minterms contain common literals.
  - Minterms on the left and right sides contain  $y'$  and  $y$  respectively.
  - Minterms in the top and bottom rows contain  $x'$  and  $x$  respectively

		y	
		0	1
x	0	$x'y'$	$x'y$
	1	$xy'$	$xy$

	$y'$	$y$
	$x'$	$x'y'$
$x$	$xy'$	$xy$

# How to represent K-Map?

- ▶ 3-Variables function

- For a three-variable expression with inputs  $x$ ,  $y$ ,  $z$ , the arrangement of minterms is more tricky:

			y	
	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
X	$xy'z'$	$xy'z$	$xyz$	$xyz'$

$z$

		YZ			
		00	01	11	10
x	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

# How to represent K-Map?

- ▶ Example of three variables K-Map: given

$$F(a,b,c) = \sum m(1, 2, 3, 4, 5, 6)$$

	B'C'	B'C	BC	BC'
A'	0 0	1 1	3 1	2 1
A	4 1	5 1	7 0	6 1

$$F = A'C + BC' + AB'$$

# How to represent K-Map?

- ▶ 4-variables function:  $F(W,X,Y,Z)$ 
  - Grouping minterms is similar to the three-variable case, but:  
We can have rectangular groups of 1, 2, 4, 8 or 16 minterms.

		y			
		w'x'y'z'	w'x'y'z	w'x'yz	w'xyz'
w		w'x'y'z'	w'x'y'z	w'x'yz	w'xyz'
		w'x'y'z'	w'x'y'z	w'xyz	w'xyz'
	x	wxy'z'	wxy'z	wxyz	wxyz'
		wx'y'z'	wx'y'z	wx'yz	wxyz'
		z			

		y			
		m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
w		m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
		m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>
	x	m <sub>12</sub>	m <sub>13</sub>	m <sub>15</sub>	m <sub>14</sub>
		m <sub>8</sub>	m <sub>9</sub>	m <sub>11</sub>	m <sub>10</sub>
		z			



# How to represent K-Map?

- ▶ Example: simplify the following (SOMs):

$$F(w,x,y,z) = \Sigma(m_0, m_2, m_5, m_8, m_{10}, m_{13})$$

- The expression is already a sum of minterms, so here's the K-map:

		y		
	1	0	0	1
	0	1	0	0
w	0	1	0	0
	1	0	0	1
		z		

		y		
	$m_0$	$m_1$	$m_3$	$m_2$
	$m_4$	$m_5$	$m_7$	$m_6$
w	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	$m_8$	$m_9$	$m_{11}$	$m_{10}$
		z		

Result,  $F = x'z' + xy'z$ .

# How to represent K-Map?

- ▶ 5-variables function
  - The #of locations needed is  $2^n$ ,  $n$ =#of variables
  - $2^5 = 2 \times 2 \times 2 \times 2 \times 2 = 32$  locations
  - We need 2x16 K-Maps for represents these 5-var.

$$F(A, B, C, D, E) = \sum m(0, 2, 3, 5, 7, 8, 11, 13, 17, 19, 23, 24, 29, 30)$$


	A'				A			
	D'E'	D'E	DE	DE'	D'E'	D'E	DE	DE'
B'C'	0	1	3	2	16	17	19	18
B'C	4	5	7	6	20	21	23	22
BC	12	13	15	14	28	29	31	30
BC'	8	9	11	10	24	25	27	26

$$F = B'DE + A'C'DE + A'B'C'E' + A'B'CE + AB'C'E + BCD'E + BC'D'E' + ABCDE'$$


# Simplify expressions using K-Maps

- ▶ K-Map uses the following rules for simplifying expressions by grouping the cells containing ONES only.

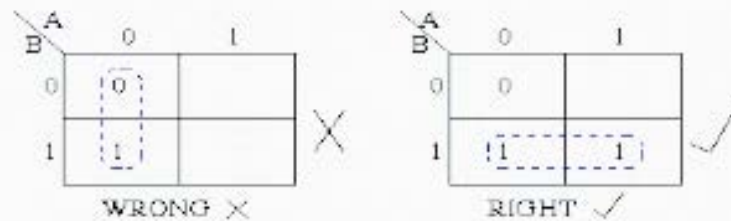**1. Groups may not include any cell containing a zero.**







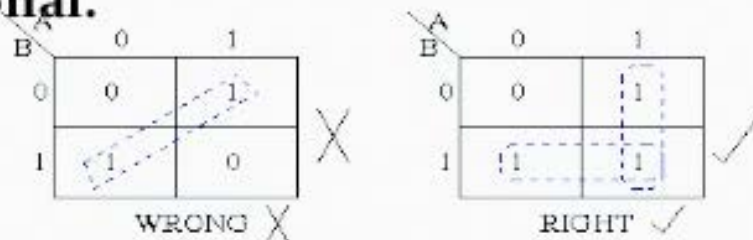**2. Groups may be horizontal or vertical, but not diagonal.**


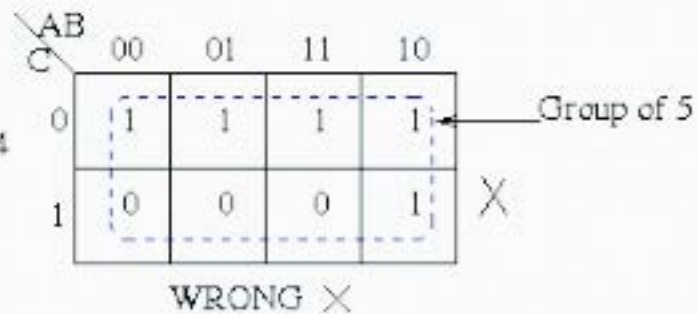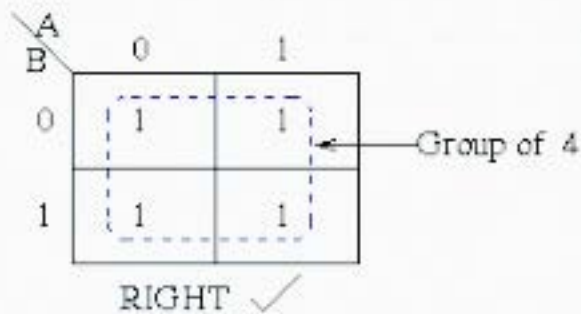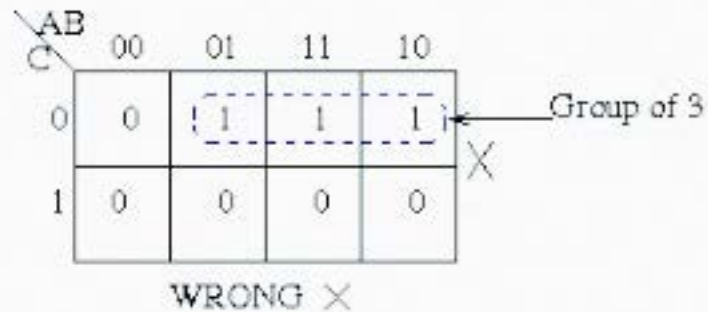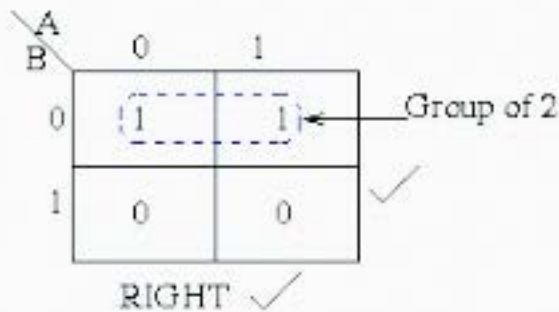
# Simplify expressions using K-Maps

- ▶ Groups made using  $2^n$  cells only.
  - If  $n=1$ , a group contains two 1's since  $2^1=2$
  - If  $n=2$ , a group contains four 1's since  $2^2=4$



# Simplify expressions using K-Maps

4. Each group should be as large as possible.

$\backslash$ AB C	00	01	11	10
0	1	1	1	1
1	0	0	1	1

RIGHT ✓

$\backslash$ AB C	00	01	11	10
0	1	1	1	1
1	0	0	1	1

WRONG ✗

(Note that no Boolean laws broken,  
but not sufficiently minimal)


5. Each cell containing a one must be in at least one group.

$\backslash$ AB C	00	01	11	10
0	0	0	1	1
1	0	0	0	1


Group I  
Group II  
1 present in at least one group.

# Simplify expressions using K-Maps

## 6. Groups may Overlap.

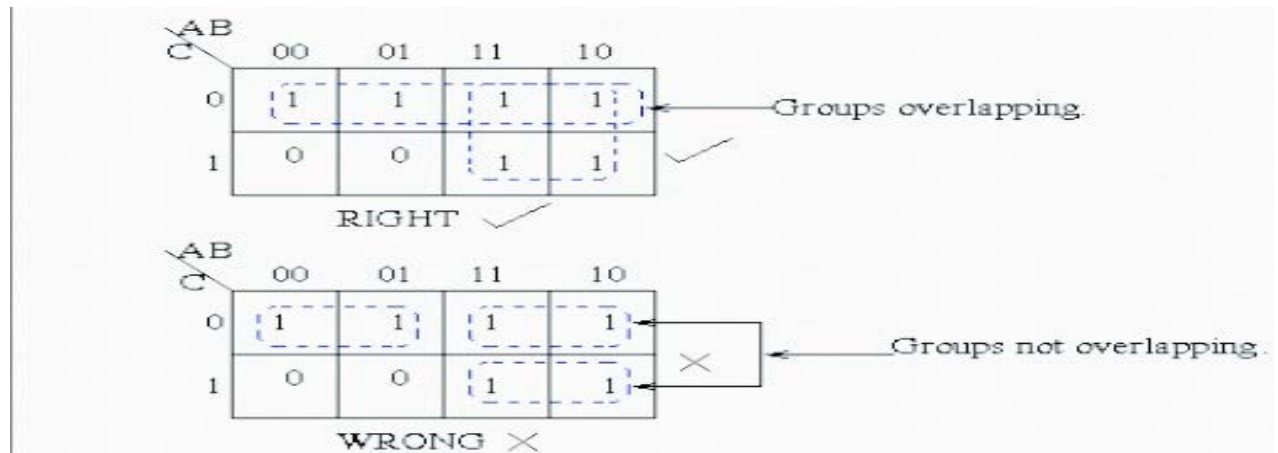

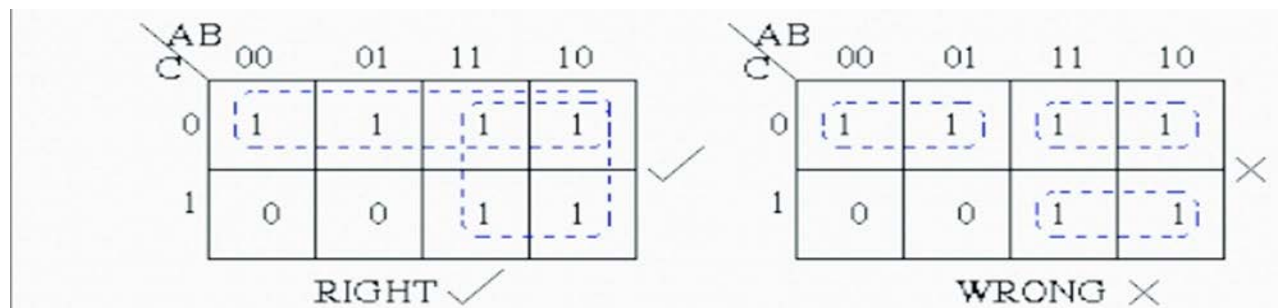
## 7. there should be as few groups as possible.



# Simplify expressions using K-Maps

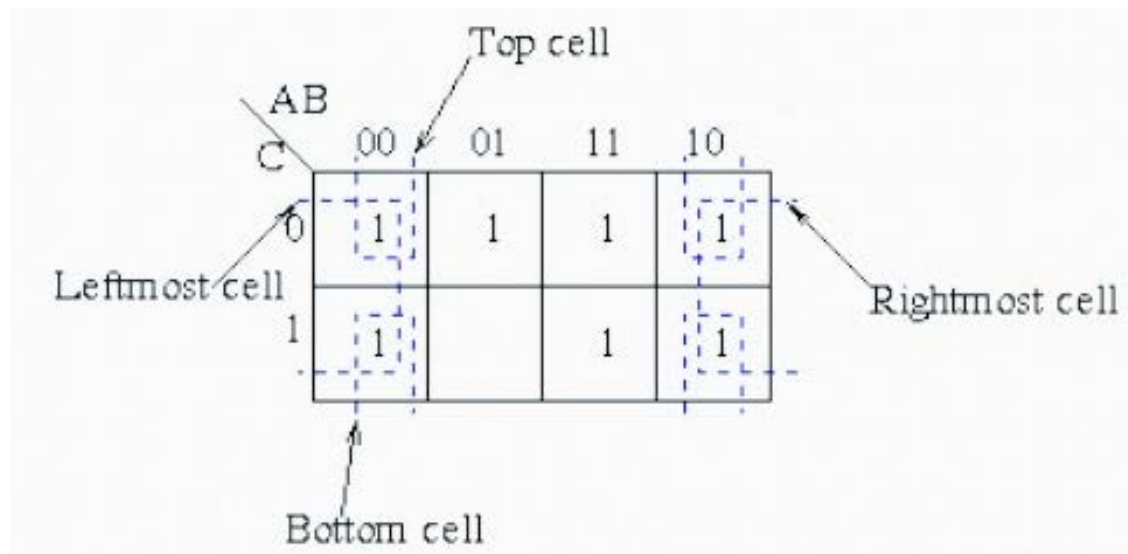8. groups may wrap around the table.

- The leftmost cell in a row may be grouped with the rightmost cell and the top cell in a column may be grouped with the bottom cell.



# Examples:

- ▶ Simplify the following expression using: (a) boolean algebra, (b) K-Map.

$$F(x, y) = x + xy$$

Sol.

- a. Using boolean algebra

$$F = X + XY \rightarrow F = X(1 + Y) \quad \text{since } (1 + Y) = 1 \text{ in Boolean Rules}$$

$$\rightarrow F = X$$


- b. Using K-Map: we need first to get Minterms:

Express the function in SOMs:

- a.  $F = x + xy \rightarrow F = x \cdot 1 + xy$
- $\rightarrow F = x(y + y') + xy$
- $\rightarrow F = xy + xy' + xy$  since  $xy + xy = xy$ ,
- $\rightarrow F = xy' + xy \rightarrow F(x, y) = \Sigma(m_2, m_3)$

**Simplified Function  $F(x, y) = x$**

- b. Using Truth Table

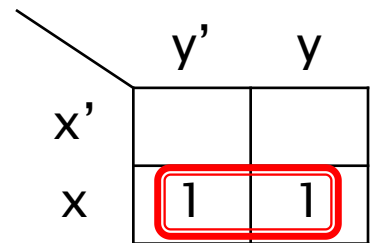

x	y	F
0	0	0
0	1	0
1	0	1
1	1	1



$$F(x, y) = x$$



# Examples:

- ▶ Simplify the following expression using K-Map in a. SOP, b. POS

$$F(A,B,C,D)=\Sigma(0, 2, 3, 6, 8, 9,10, 12)$$

Sol.

$$F=A'B'C'D'+A'B'CD'+A'B'CD+A'BCD'+AB'C'D'+AB'C'D+AB'CD'+ABC'D'$$

	C'D'	C'D	CD	CD'
A'B'	1	0	1	1
A'B	0	0	0	1
AB	1	0	0	0
AB'	1	1	0	1

SOP:

F=

POS:

F' =

F=

# Quiz

- ▶ Try yourself to solve this question:
  - Simplify the following function's truth table using K-Map in SOP and POS, then draw the SOP circuit?

x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

# End of this Lecture!

## Any Questions?

Join our Logic Design google classroom at

<https://classroom.google.com/u/0/h>

class join code: upoi4fe

