


Current and Voltage

Charge: the electrical charge is an electrical property of atomic particles of which matter consists, measured in coulombs (C). The charge of an electron is $(-1.602 \times 10^{-19} \text{ C})$.

Electrical current: is the rate of change of charge, measured in amperes (A). The current (I) is defined mathematically as:

$$I = \frac{Q}{t}$$

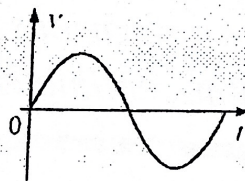- **Direct current (DC):** is the current that remains constant with time. The symbol (I) is usually used to represent such a constant current.
- **Alternating current (AC):** is a current that is varying sinusoidally with time. A time varying current is represented by the symbol (i).



Sinusoidal

Voltage: the voltage (or potential difference) is the energy required to move a unit of charge through an element, measured in volts (V).

* For the voltage V_{ab} , this mean that the potential of point a is higher than that of point b.

$$V_{ab} = V_a - V_b$$

Power: is the time rate of expending or absorbing energy, measured in watt (W).

$$P = \frac{w}{t}$$

Where P is the power in watt (W), w is the energy in joules (J), and t is the time in seconds (s).


The power (P) is defined mathematically as:

$$P = VI$$

$$P = \frac{V^2}{R}$$

$$P = I^2 R$$

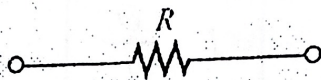Resistance: the resistance R denotes the ability of an element to resist the flow of electrical current, it is measured in Ohms (Ω).



For the material, the resistance R depends of the physical dimensions as follows:

$$R = \rho \frac{l}{A}$$

Where ρ is the receptivity of material.

Resistivity (ρ) of various materials in ohm-centimeters.

Silver	1.645×10^{-6}
Copper	1.723×10^{-6}
Gold	2.443×10^{-6}
Aluminum	2.825×10^{-6}
Tungsten	5.485×10^{-6}
Nickel	7.811×10^{-6}
Iron	12.299×10^{-6}
Tantalum	15.54×10^{-6}
Nichrome	99.72×10^{-6}
Tin oxide	250×10^{-6}
Carbon	3500×10^{-6}



EXAMPLE: Determine the resistance of 30.48 m of copper telephone wire if the diameter is 0.032 cm.

Solution:

$$A = \frac{\pi d^2}{4} = \frac{(3.1416)(0.032 \text{ cm})^2}{4} = 8.04 \times 10^{-4} \text{ cm}^2$$

$$R = \rho \frac{l}{A} = \frac{(1.723 \times 10^{-6} \Omega \cdot \text{cm})(3048 \text{ cm})}{8.04 \times 10^{-4} \text{ cm}^2} \approx 6.5 \Omega$$

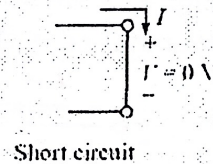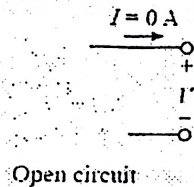- The resistance of a short circuit element is approaching zero.
- The resistance of an open circuit element is approaching infinity.



Conductance: the conductance can be explained as the ability of an element to conduct electrical current, it is measured in siemens (S).

$$G = \frac{1}{R}$$

$$G = \frac{A}{\rho l}$$

OHM'S LAW: Ohm's law states that the voltage V across a resistor is directly proportional to the current I flowing through the resistor.

$$V = IR \quad I = \frac{V}{R} \quad R = \frac{V}{I}$$

EXAMPLE: Determine the current resulting from the application of a 9-V battery across a network with a resistance of 2.2Ω .

Solution:


$$I = \frac{V}{R} = \frac{9V}{2.2\Omega} = 4.09 A$$

EXAMPLE: Calculate the resistance of a 60-W bulb if a current of 500 mA results from an applied voltage of 120 V.

Solution:

$$R = \frac{V}{I} = \frac{120}{500 \times 10^{-3}} = 240 \Omega$$

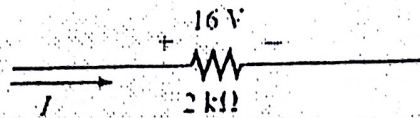
EXAMPLE: Calculate the current through the 2-k Ω resistor of Figure below if the voltage drop across it is 16 V.



Solution:

$$I = \frac{V}{R} = \frac{16 \text{ V}}{2 \times 10^3 \Omega} = 8 \text{ mA}$$

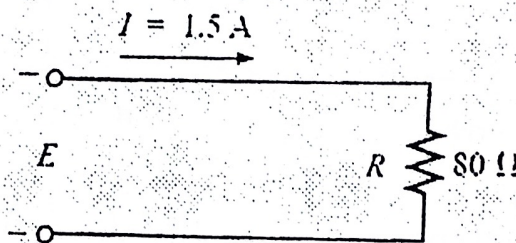EXAMPLE: Calculate the voltage that must be applied across the soldering iron of Figure below to establish a current of 1.5 A through the iron if its internal resistance is 80 Ω .



Solution:

$$E = IR = (1.5 \text{ A})(80 \Omega) = 120 \text{ V}$$

EXAMPLE: What is the power dissipated by a 5 Ω resistor if the current is 4 A?

Solution:

$$P = I^2 R = (4 \text{ A})^2 (5 \Omega) = 80 \text{ W}$$

EXAMPLE: Determine the current through a 5-k Ω resistor when the power dissipated by the element is 20 mW.

Solution:

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{20 \times 10^{-3} \text{ W}}{5 \times 10^3 \Omega}} = \sqrt{4 \times 10^{-6}} = 2 \times 10^{-3} \text{ A} \\ = 2 \text{ mA}$$