

VOLTAGE DIVIDER RULE:

In a series circuit, the voltage across a resistor in a series circuit is equal to the value of that resistor times the total impressed voltage across the series elements divided by the total resistance of the series elements.


$$V_x = \frac{R_x E}{R_T}$$

Where V_x is the voltage across R_x .


For example:

$$V_1 = IR_1 = \left(\frac{E}{R_T}\right)R_1 = \frac{R_1 E}{R_T}$$
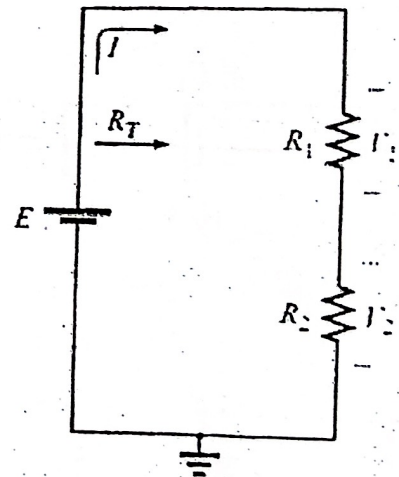
$$V_2 = IR_2 = \left(\frac{E}{R_T}\right)R_2 = \frac{R_2 E}{R_T}$$



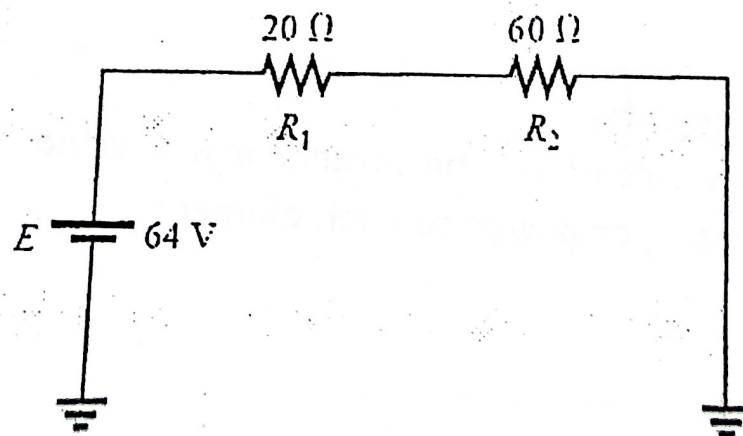
EXAMPLE: Determine the voltage V_1 for the network of Figure below.



Solution:

$$V_1 = \frac{R_1 E}{R_T} = \frac{R_1 E}{R_1 + R_2} = \frac{(20 \Omega)(64 \text{ V})}{20 \Omega + 60 \Omega} = \frac{1280 \text{ V}}{80} = 16 \text{ V}$$

EXAMPLE: Using the voltage divider rule, determine the voltages V_1 and V_3 for the series circuit of Figure below.

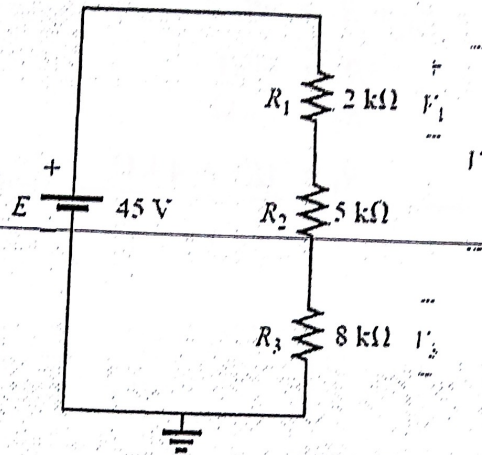**Solution:**


$$V_1 = \frac{R_1 E}{R_T} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{2 \text{ k}\Omega + 5 \text{ k}\Omega + 8 \text{ k}\Omega} = \frac{(2 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega}$$

$$= \frac{(2 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega} = \frac{90 \text{ V}}{15} = 6 \text{ V}$$

$$V_3 = \frac{R_3 E}{R_T} = \frac{(8 \text{ k}\Omega)(45 \text{ V})}{15 \text{ k}\Omega} = \frac{(8 \times 10^3 \Omega)(45 \text{ V})}{15 \times 10^3 \Omega}$$

$$= \frac{360 \text{ V}}{15} = 24 \text{ V}$$

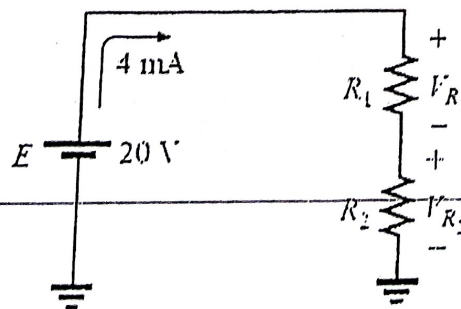EXAMPLE: Design the voltage divider of Figure below such that $V_{R1} = 4 V_{R2}$.



Solution: The total resistance is defined by

$$R_T = \frac{E}{I} = \frac{20 \text{ V}}{4 \text{ mA}} = 5 \text{ k}\Omega$$

Since $I'_{R_1} = 4I'_{R_2}$,

$$R_1 = 4R_2$$

Thus

$$R_T = R_1 + R_2 = 4R_2 + R_2 = 5R_2$$

and



$$5R_2 = 5 \text{ k}\Omega$$



$$R_2 = 1 \text{ k}\Omega$$

and


$$R_1 = 4R_2 = 4 \text{ k}\Omega$$

NOTATION:

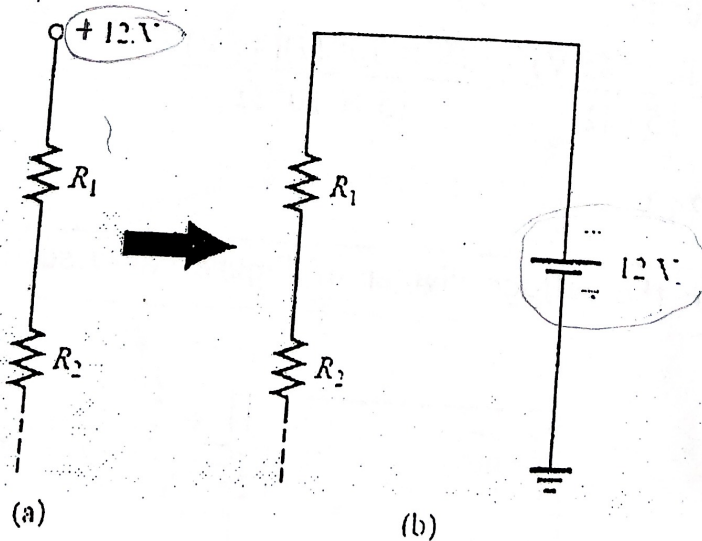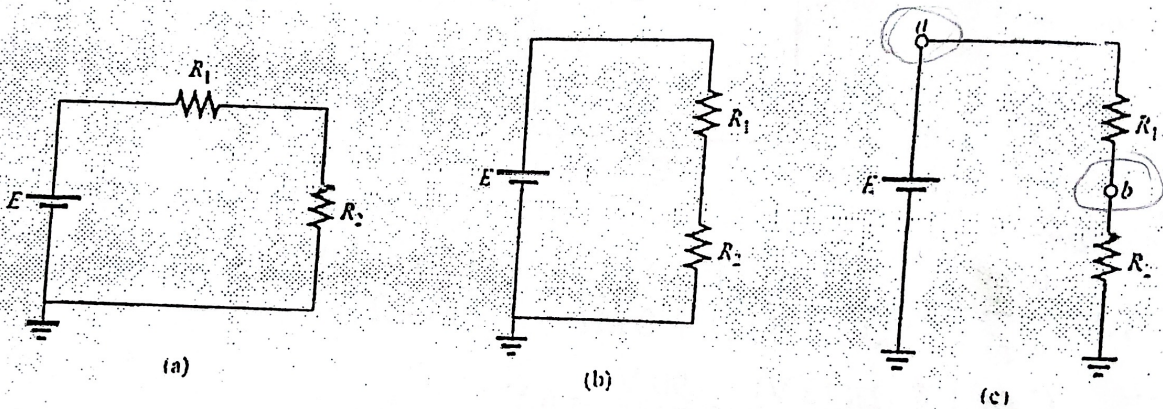

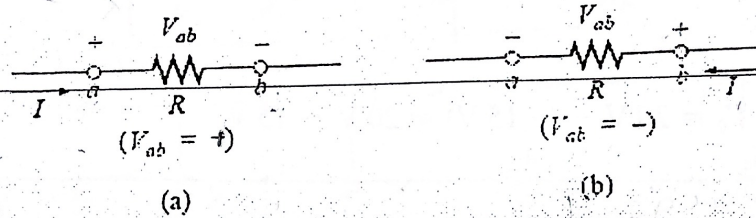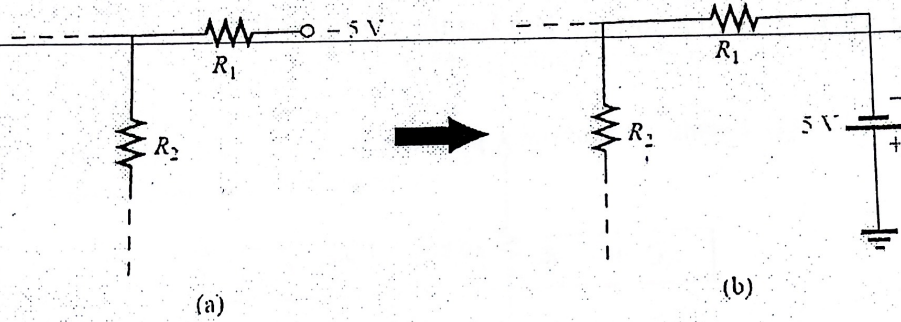

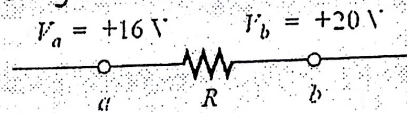
EXAMPLE: Find the voltage V_{ab} for the conditions.



Solution:

$$V_{ab} = V_a - V_b = 16\text{ V} - 20\text{ V} \\ = -4\text{ V}$$

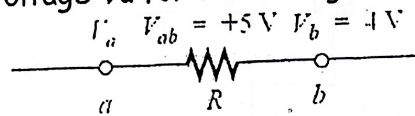EXAMPLE: Find the voltage V_a for the configuration.




Solution:

$$V_{ab} = V_a - V_b$$

$$V_a = V_{ab} + V_b = 5\text{ V} + 4\text{ V} \\ = 9\text{ V}$$

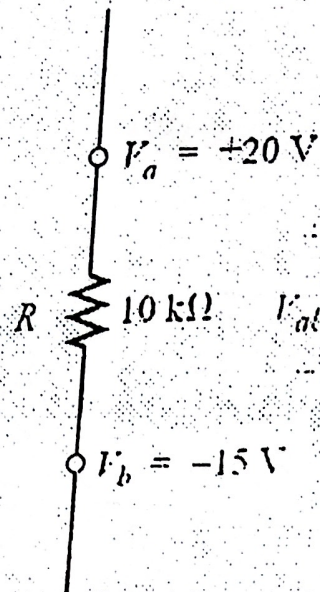EXAMPLE: Find the voltage V_{ab} for the configuration.



Solution:

$$\begin{aligned} V_{ab} &= V_a - V_b = 20 \text{ V} - (-15 \text{ V}) = 20 \text{ V} + 15 \text{ V} \\ &= 35 \text{ V} \end{aligned}$$