
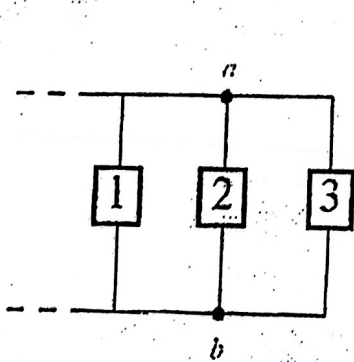


Parallel Circuits:

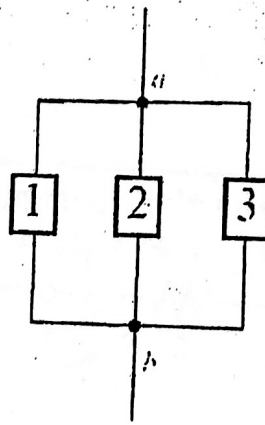
Two elements, branches, or networks are in parallel if they have two points in common.



(a)




(b)

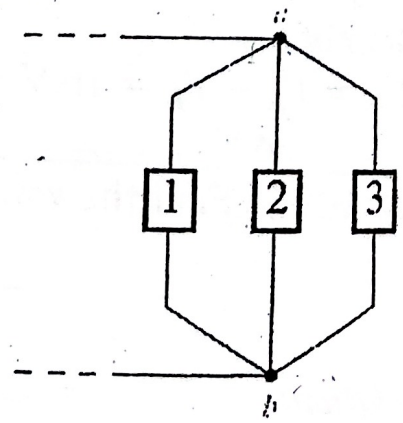

(c)

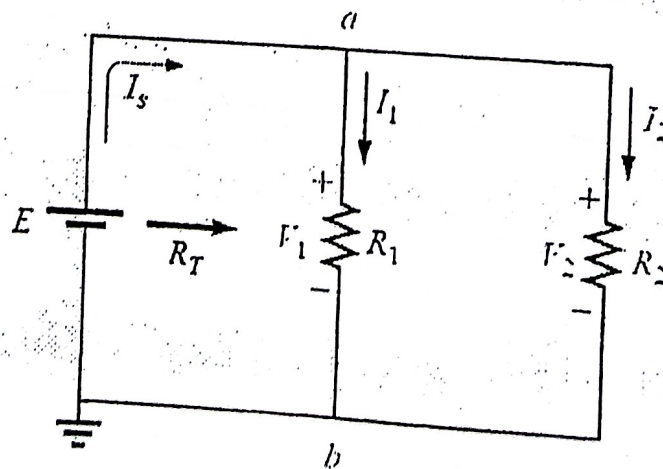- The voltage across parallel elements is the same, but the current is different.




$$E = V_1 = V_2$$


- For parallel elements, the total conductance is the sum of the individual conductances.
- The total resistance of parallel resistors is always less than the value of the smallest resistor.

$$G_T = G_1 + G_2 + G_3 + \dots + G_N$$
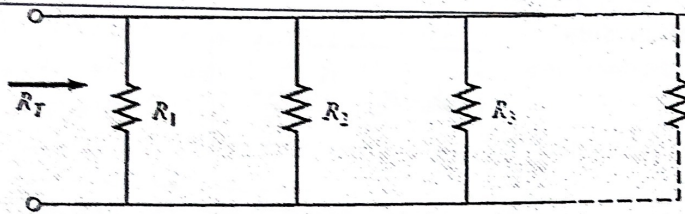
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$



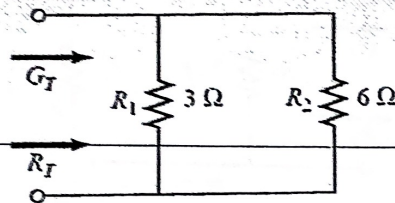EXAMPLE: Determine the total conductance and resistance for the parallel network.




Solution:

$$G_T = G_1 + G_2 = \frac{1}{3\ \Omega} + \frac{1}{6\ \Omega} = 0.333\ \text{S} + 0.167\ \text{S} = 0.5\ \text{S}$$

and

$$R_T = \frac{1}{G_T} = \frac{1}{0.5\ \text{S}} = 2\ \Omega$$

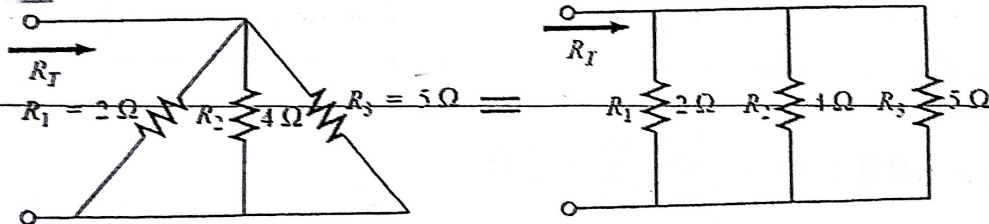EXAMPLE: Determine the total resistance for the network.



Solution:


$$\begin{aligned}
 \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\
 &= \frac{1}{2\ \Omega} + \frac{1}{4\ \Omega} + \frac{1}{5\ \Omega} = 0.5\ \text{S} + 0.25\ \text{S} + 0.2\ \text{S} \\
 &= 0.95\ \text{S}
 \end{aligned}$$

and $R_T = \frac{1}{0.95\ \text{S}} = 1.053\ \Omega$

* The total resistance of two parallel resistors is the product of the two divided by their sum.


$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

EXAMPLE: Determine the total conductance and resistance for the parallel network.

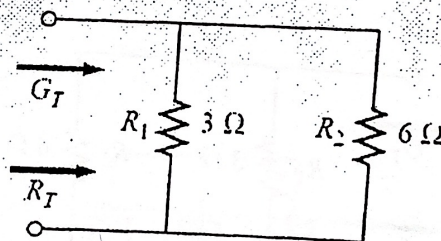**Solution:**

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(3\ \Omega)(6\ \Omega)}{3\ \Omega + 6\ \Omega} = \frac{18\ \Omega}{9} = 2\ \Omega$$


EXAMPLE: Determine the total resistance for the network.

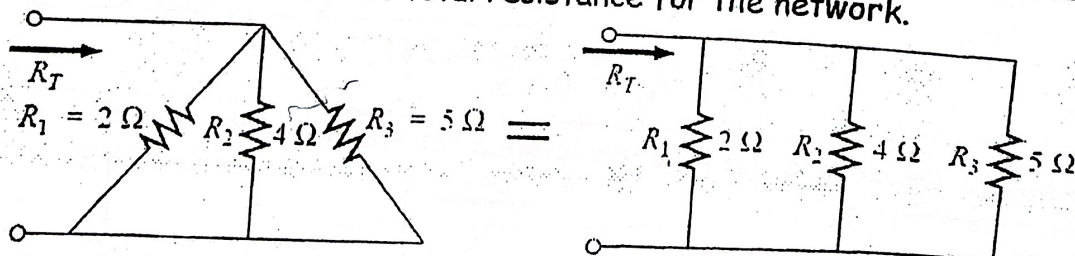**Solution:**

$$R'_T = 2\ \Omega \parallel 4\ \Omega = \frac{(2\ \Omega)(4\ \Omega)}{2\ \Omega + 4\ \Omega} = \frac{4}{3}\ \Omega$$

$$R_T = R'_T \parallel 5\ \Omega = \frac{\left(\frac{4}{3}\ \Omega\right)(5\ \Omega)}{\frac{4}{3}\ \Omega + 5\ \Omega} = 1.053\ \Omega$$

EXAMPLE: For the parallel network.

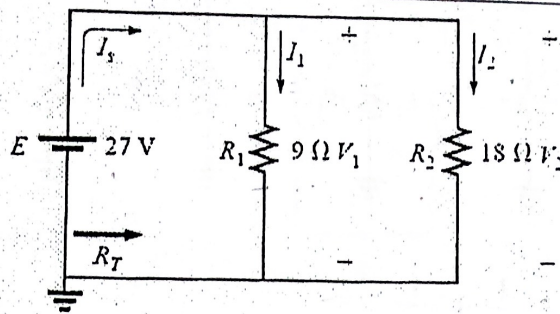

- Calculate R_T .
- Determine I_s .
- Calculate I_1 and I_2 , and demonstrate that $I_s = I_1 + I_2$.
- Determine the power to each resistive load.
- Determine the power delivered by the source, and compare it to the total power dissipated by the resistive elements.

Solution:

$$a. R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{(9\ \Omega)(18\ \Omega)}{9\ \Omega + 18\ \Omega} = \frac{162\ \Omega}{27} = 6\ \Omega$$

$$b. I_s = \frac{E}{R_T} = \frac{27\text{ V}}{6\ \Omega} = 4.5\text{ A}$$

$$c. I_1 = \frac{V_1}{R_1} = \frac{E}{R_1} = \frac{27\text{ V}}{9\ \Omega} = 3\text{ A}$$

$$I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{27\text{ V}}{18\ \Omega} = 1.5\text{ A}$$

$$I_s = I_1 + I_2$$

$$4.5\text{ A} = 3\text{ A} + 1.5\text{ A}$$

$$4.5\text{ A} = 4.5\text{ A} \quad (\text{checks})$$

$$d. P_1 = V_1 I_1 = E I_1 = (27\text{ V})(3\text{ A}) = 81\text{ W}$$


$$P_2 = V_2 I_2 = E I_2 = (27\text{ V})(1.5\text{ A}) = 40.5\text{ W}$$

$$e. P_s = E I_s = (27\text{ V})(4.5\text{ A}) = 121.5\text{ W}$$

$$= P_1 + P_2 = 81\text{ W} + 40.5\text{ W} = 121.5\text{ W}$$

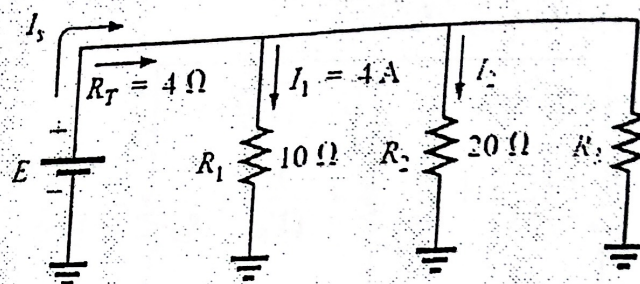EXAMPLE: Given the information provided.

- Determine R_3 .
- Calculate E .
- Find I_s .
- Find I_2 .
- Determine P_2 .



Solution:

$$a. \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{4 \Omega} = \frac{1}{10 \Omega} + \frac{1}{20 \Omega} + \frac{1}{R_3}$$

$$0.25 \text{ S} = 0.1 \text{ S} + 0.05 \text{ S} + \frac{1}{R_3}$$

$$0.25 \text{ S} = 0.15 \text{ S} + \frac{1}{R_3}$$

$$\frac{1}{R_3} = 0.1 \text{ S}$$

$$R_3 = \frac{1}{0.1 \text{ S}} = 10 \Omega$$

$$b. \quad E = V_1 = I_1 R_1 = (4 \text{ A})(10 \Omega) = 40 \text{ V}$$


$$c. \quad I_s = \frac{E}{R_T} = \frac{40 \text{ V}}{4 \Omega} = 10 \text{ A}$$

$$d. \quad I_2 = \frac{V_2}{R_2} = \frac{E}{R_2} = \frac{40 \text{ V}}{20 \Omega} = 2 \text{ A}$$

$$e. \quad P_2 = I_2^2 R_2 = (2 \text{ A})^2 (20 \Omega) = 80 \text{ W}$$

CURRENT DIVIDER RULE:

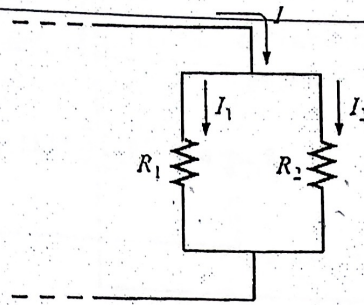- For two parallel elements of equal value, the current will divide equally.
- For parallel elements with different values, the smaller the resistance, the greater the share of input current.
- For parallel elements of different values, the current will split with a ratio equal to the inverse of their resistor values.




Note difference in subscripts.

$$I_1 = \frac{R_2 I}{R_1 + R_2}$$

$$I_2 = \frac{R_1 I}{R_1 + R_2}$$

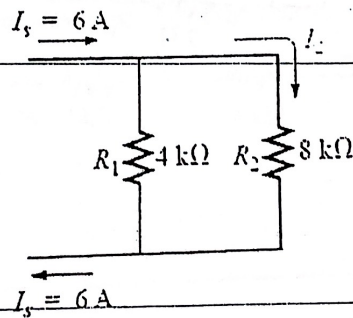EXAMPLE: Determine the current I_2 for the network using the current divider rule.




Solution:

$$I_2 = \frac{R_1 I_s}{R_1 + R_2} = \frac{(4 \text{ k}\Omega)(6 \text{ A})}{4 \text{ k}\Omega + 8 \text{ k}\Omega} = \frac{4}{12}(6 \text{ A}) = \frac{1}{3}(6 \text{ A})$$

$$= 2 \text{ A}$$

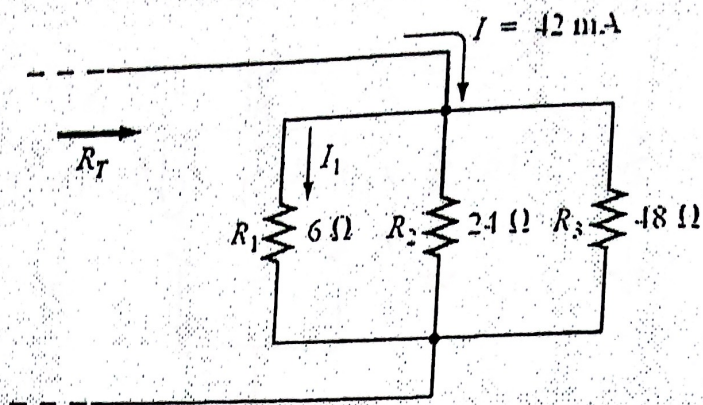EXAMPLE: Find the current I_1 for the network.




Solution:

$$24\ \Omega \parallel 48\ \Omega = \frac{(24\ \Omega)(48\ \Omega)}{24\ \Omega + 48\ \Omega} = 16\ \Omega$$

$$I_1 = \frac{16\ \Omega(42\ \text{mA})}{16\ \Omega + 6\ \Omega} = 30.54\ \text{mA}$$

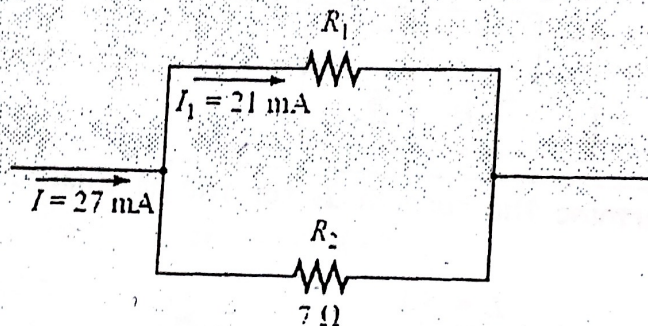EXAMPLE: Determine the resistance R_1 to effect the division of current.



Solution:

$$I_1 = \frac{R_2 I}{R_1 + R_2}$$

$$(R_1 + R_2)I_1 = R_2 I$$

$$R_1 I_1 + R_2 I_1 = R_2 I$$

$$R_1 I_1 = R_2 I - R_2 I_1$$

$$R_1 = \frac{R_2(I - I_1)}{I_1}$$

$$R_1 = \frac{7\ \Omega(27\ \text{mA} - 21\ \text{mA})}{21\ \text{mA}}$$

$$= 7\ \Omega \left(\frac{6}{21} \right) = \frac{42\ \Omega}{21} = 2\ \Omega$$