
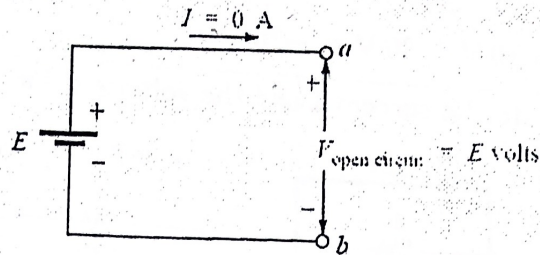


Open and Short Circuits:

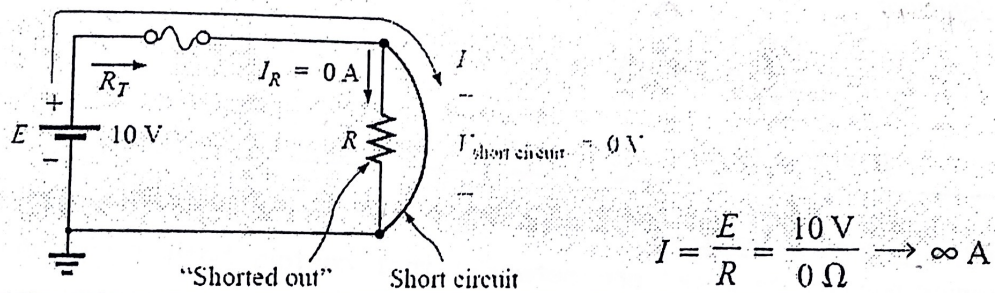
An open circuit can have a potential difference (voltage) across its terminals, but the current is always zero amperes.



A short circuit can carry a current of a level determined by the external circuit, but the potential difference (voltage) across its terminals is always zero volts.



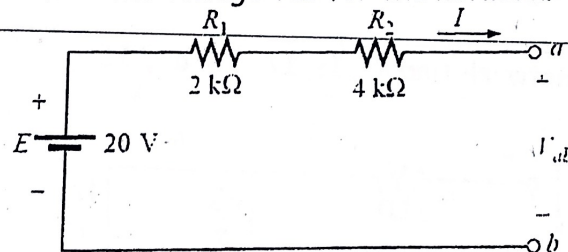
EXAMPLE: Determine the voltage V_{ab} for the network.



Solution:

$$V_{ab} = E = 20 \text{ V}$$

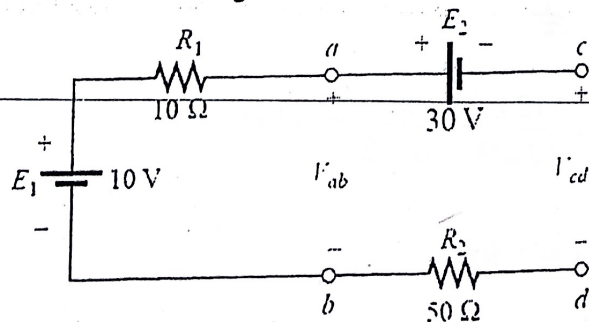EXAMPLE: Determine the voltages V_{ab} and V_{cd} for the network.





Solution:

$$V_{ab} = E_1 = 10 \text{ V}$$

$$+E_1 - E_2 - V_{cd} = 0$$

$$V_{cd} = E_1 - E_2 = 10 \text{ V} - 30 \text{ V} = -20 \text{ V}$$

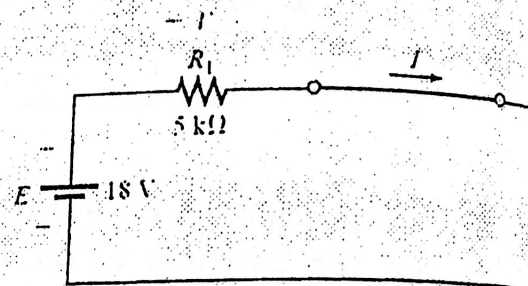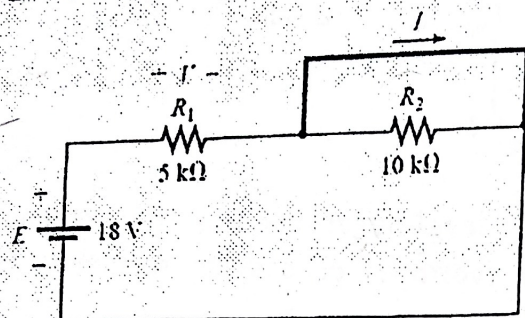EXAMPLE: Calculate the current I and the voltage V for the network.



Solution:


$$I = \frac{E}{R_1} = \frac{18 \text{ V}}{5 \text{ k}\Omega} = 3.6 \text{ mA}$$

$$V = E = 18 \text{ V}$$

Series-Parallel Networks:

Series-parallel networks are networks that contain both series and parallel circuit configurations.

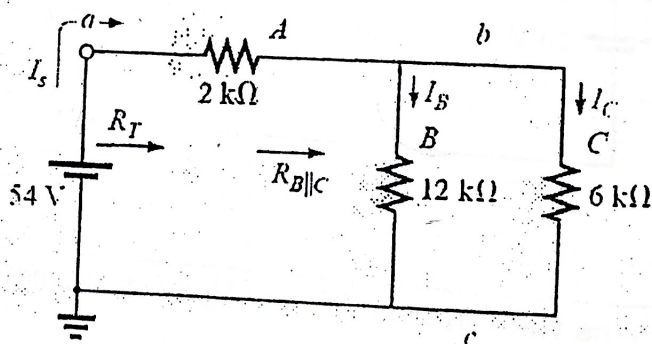
EXAMPLE: for the network find R_T , I_s , I_A , I_B , and I_C .



Solution:

$$R_{B||C} = R_B \parallel R_C = \frac{(12 \text{ k}\Omega)(6 \text{ k}\Omega)}{12 \text{ k}\Omega + 6 \text{ k}\Omega} = 4 \text{ k}\Omega$$

$$\begin{aligned} R_T &= R_A + R_{B||C} \\ &= 2 \text{ k}\Omega + 4 \text{ k}\Omega = 6 \text{ k}\Omega \end{aligned}$$

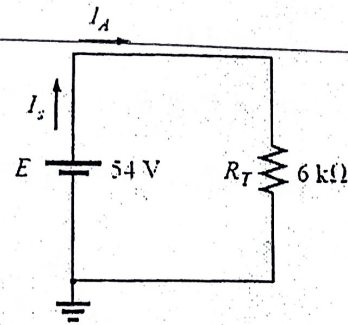


$$I_s = \frac{E}{R_T} = \frac{54 \text{ V}}{6 \text{ k}\Omega} = 9 \text{ mA}$$


$$I_A = I_s = 9 \text{ mA}$$

$$I_B = \frac{6 \text{ k}\Omega(I_s)}{6 \text{ k}\Omega + 12 \text{ k}\Omega} = \frac{6}{18} I_s = \frac{1}{3} (9 \text{ mA}) = 3 \text{ mA}$$
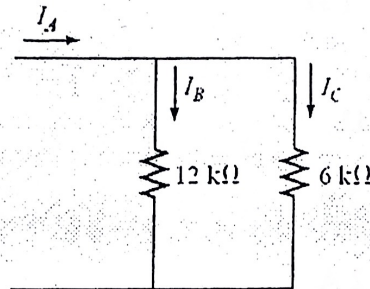
$$I_C = \frac{12 \text{ k}\Omega(I_s)}{12 \text{ k}\Omega + 6 \text{ k}\Omega} = \frac{12}{18} I_s = \frac{2}{3} (9 \text{ mA}) = 6 \text{ mA}$$



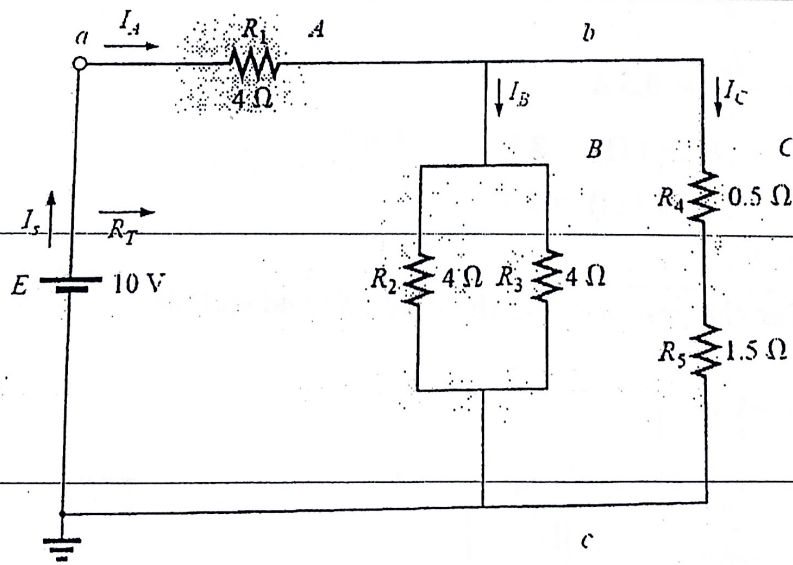EXAMPLE: for the network find the currents and voltage for each element.




Solution:

$$A: R_A = 4 \Omega$$

$$B: R_B = R_2 \parallel R_3 = R_{2 \parallel 3} = \frac{R}{N} = \frac{4 \Omega}{2} = 2 \Omega$$
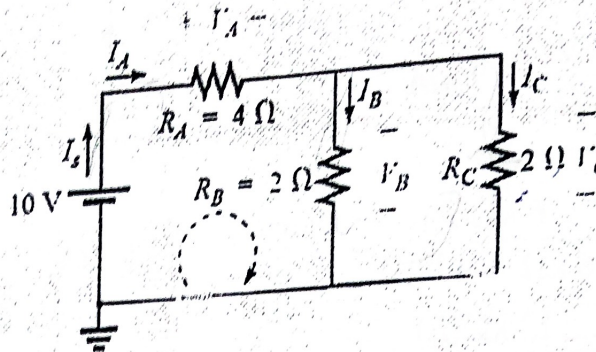
$$C: R_C = R_4 + R_5 = R_{4.5} = 0.5 \Omega + 1.5 \Omega = 2 \Omega$$



$$R_{B \parallel C} = \frac{R}{N} = \frac{2 \Omega}{2} = 1 \Omega$$

$$R_T = R_A + R_{B \parallel C} = 4 \Omega + 1 \Omega = 5 \Omega$$

$$I_s = \frac{E}{R_T} = \frac{10 \text{ V}}{5 \Omega} = 2 \text{ A}$$

$$I_A = I_s = 2 \text{ A}$$

$$I_B = I_C = \frac{I_A}{2} = \frac{I_s}{2} = \frac{2 \text{ A}}{2} = 1 \text{ A}$$



$$I_{R_2} = I_{R_3} = \frac{I_B}{2} = 0.5 \text{ A}$$

$$V_A = I_A R_A = (2 \text{ A})(4 \Omega) = 8 \text{ V}$$

$$V_B = I_B R_B = (1 \text{ A})(2 \Omega) = 2 \text{ V}$$

$$V_C = I_C R_C = 2 \text{ V}$$

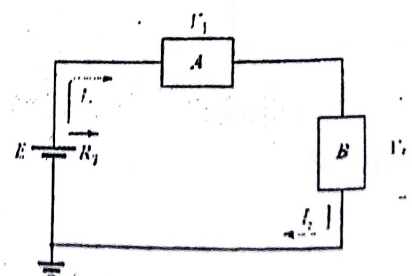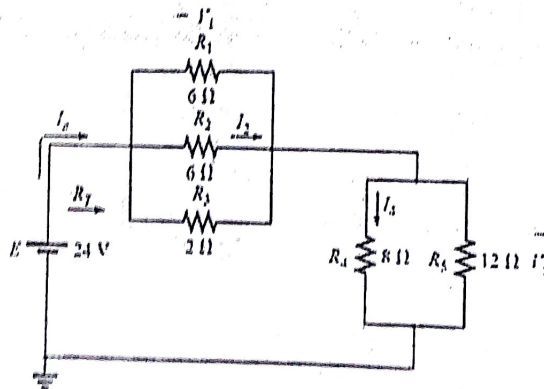EXAMPLE: for the network find the currents and voltage for each element.




Solution:

$$R_{1\parallel 2} = \frac{R}{N} = \frac{6\ \Omega}{2} = 3\ \Omega$$

$$R_A = R_{1\parallel 2\parallel 3} = \frac{(3\ \Omega)(2\ \Omega)}{3\ \Omega + 2\ \Omega} = \frac{6\ \Omega}{5} = 1.2\ \Omega$$
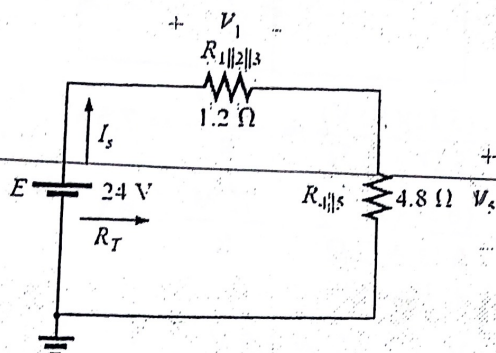
$$R_B = R_{4\parallel 5} = \frac{(8\ \Omega)(12\ \Omega)}{8\ \Omega + 12\ \Omega} = \frac{96\ \Omega}{20} = 4.8\ \Omega$$



$$R_T = R_{1\parallel 2\parallel 3} + R_{4\parallel 5} = 1.2\ \Omega + 4.8\ \Omega = 6\ \Omega$$

$$I_s = \frac{E}{R_T} = \frac{24\ \text{V}}{6\ \Omega} = 4\ \text{A}$$

$$V_1 = I_s R_{1\parallel 2\parallel 3} = (4\ \text{A})(1.2\ \Omega) = 4.8\ \text{V}$$


$$V_5 = I_s R_{4\parallel 5} = (4\ \text{A})(4.8\ \Omega) = 19.2\ \text{V}$$

$$I_4 = \frac{V_5}{R_4} = \frac{19.2\ \text{V}}{8\ \Omega} = 2.4\ \text{A}$$


$$I_2 = \frac{V_2}{R_2} = \frac{V_1}{R_2} = \frac{4.8\ \text{V}}{6\ \Omega} = 0.8\ \text{A}$$

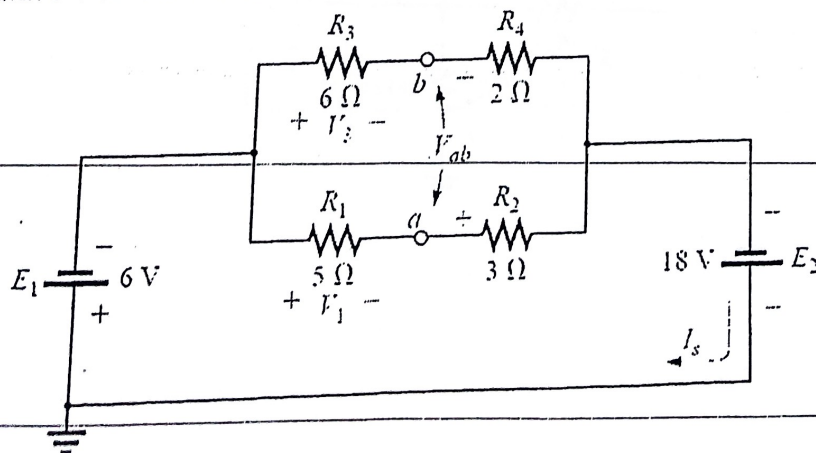EXAMPLE:

- Find the voltages V_1 , V_3 , and V_{ab} for the network.
- Calculate the source current I_s .



Solution:

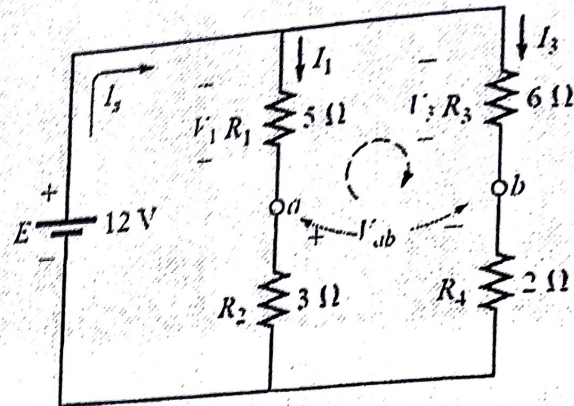

$$V_1 = \frac{R_1 E}{R_1 + R_2} = \frac{(5 \Omega)(12 \text{ V})}{5 \Omega + 3 \Omega} = \frac{60 \text{ V}}{8} = 7.5 \text{ V}$$

$$V_3 = \frac{R_3 E}{R_3 + R_4} = \frac{(6 \Omega)(12 \text{ V})}{6 \Omega + 2 \Omega} = \frac{72 \text{ V}}{8} = 9 \text{ V}$$

$$+V_1 - I_3 + I_{ab} = 0$$


$$I_{ab} = V_3 - V_1 = 9 \text{ V} - 7.5 \text{ V} = 1.5 \text{ V}$$

$$I_1 = \frac{V_1}{R_1} = \frac{7.5 \text{ V}}{5 \Omega} = 1.5 \text{ A}$$


$$I_3 = \frac{V_3}{R_3} = \frac{9 \text{ V}}{6 \Omega} = 1.5 \text{ A}$$

$$I_s = I_1 + I_3 = 1.5 \text{ A} + 1.5 \text{ A} = 3 \text{ A}$$

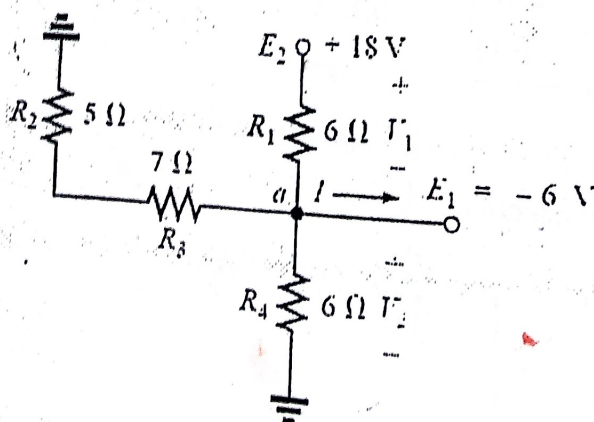EXAMPLE: For the network, determine the voltages V_1 and V_2 and the current I .



Solution:

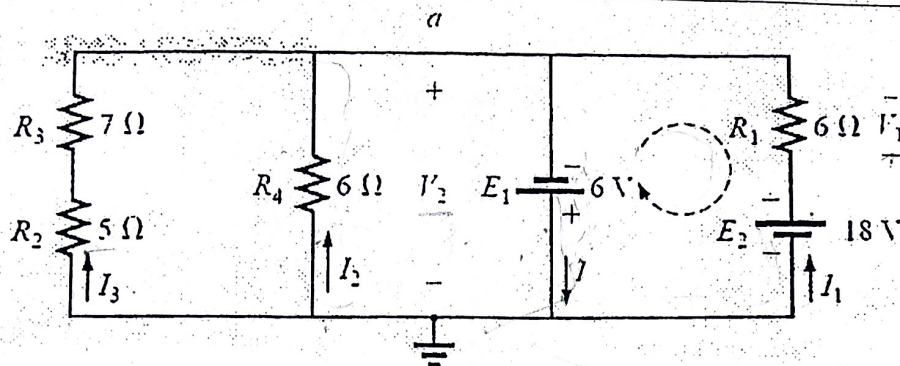

$$V_2 = -E_1 = -6 \text{ V}$$

$$-E_1 + V_1 - E_2 = 0$$

$$V_1 = E_2 + E_1 = 18 \text{ V} + 6 \text{ V} = 24 \text{ V}$$

$$I = I_1 + I_2 + I_3$$

$$= \frac{V_1}{R_1} + \frac{E_1}{R_4} + \frac{E_1}{R_2 + R_3}$$

$$= \frac{24 \text{ V}}{6 \Omega} + \frac{6 \text{ V}}{6 \Omega} + \frac{6 \text{ V}}{12 \Omega}$$

$$= 4 \text{ A} + 1 \text{ A} + 0.5 \text{ A}$$

$$I = 5.5 \text{ A}$$