


Kirchoff's Laws

* Kirchhoff's current law (KCL) states that the algebraic sum of the currents entering and leaving an area, system, or junction is zero.

Or,

* The sum of the currents entering an area, system, or junction must equal the sum of the currents leaving the area, system, or junction.

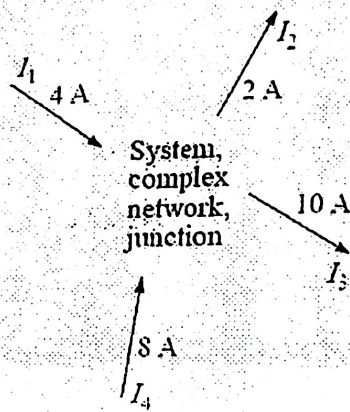
$$\Sigma I_{\text{entering}} = \Sigma I_{\text{leaving}}$$



$$\begin{aligned}
 I_1 + I_4 &= I_2 + I_3 \\
 4 \text{ A} + 8 \text{ A} &= 2 \text{ A} + 10 \text{ A} \\
 12 \text{ A} &= 12 \text{ A}
 \end{aligned}$$

* Kirchhoff's voltage law (KVL) states that the algebraic sum of the potential rises and drops around a closed loop (or path) is zero.


$$\sum_C V = 0$$

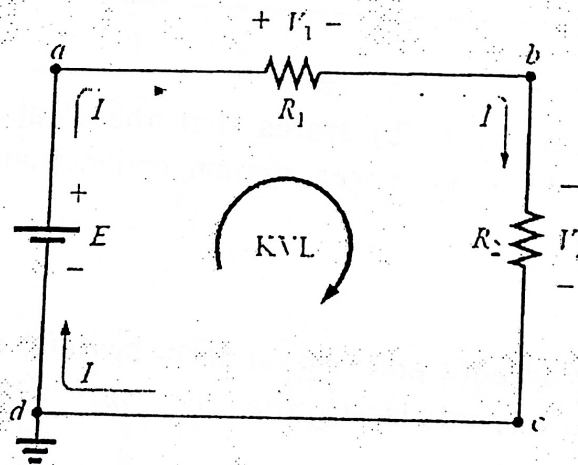

$$+E - V_1 - V_2 = 0$$

$$E = V_1 + V_2$$

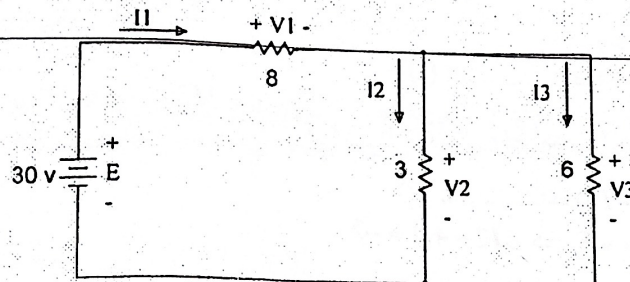EXAMPLE: using Kirchhoff's laws. Find the currents and voltages in the circuit shown.



Solution:

$$E - V1 - V2 = 0 \Rightarrow 30 - V1 - V2 = 0$$

$$30 - 8I1 - 3I2 = 0 \Rightarrow I1 = \frac{30 - 3I2}{8}$$

$$V2 - V3 = 0 \Rightarrow V2 = V3$$

$$6I3 = 3I2 \Rightarrow I3 = \frac{I2}{3}$$

$$I1 = I2 + I3 \Rightarrow I1 - I2 - I3 = 0$$

By substitute $I1$ and $I3$

$$\frac{30 - 3I2}{8} - I2 - \frac{I2}{3} = 0 \Rightarrow I2 = 2A$$

$$I1 = \frac{30 - 3I2}{8} = \frac{30 - 3(2)}{8} = 3A$$


$$I3 = \frac{I2}{3} = \frac{2}{3} = 1A$$

$$V1 = 8I1 \Rightarrow V1 = 8(3) = 24V$$

$$V2 = 3I2 \Rightarrow V2 = 3(2) = 6V$$

$$V3 = 6I3 \Rightarrow V3 = 6(1) = 6V$$

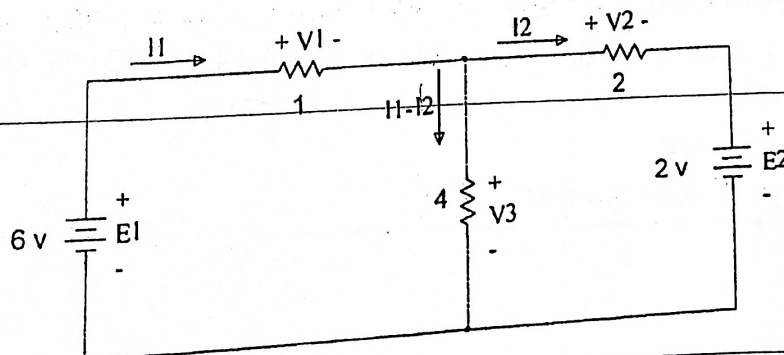EXAMPLE: using Kirchhoff's laws. Find the currents and voltages in the circuit shown.



Solution:

$$I_1 + 4(I_1 - I_2) - E_1 = 0 \dots\dots\dots(1)$$

$$I_1 + 4I_1 - 4I_2 = E_1 \Rightarrow 5I_1 - 4I_2 = 6 \Rightarrow I_1 = \frac{6 + 4I_2}{5}$$

$$2I_2 + E_2 - 4(I_1 - I_2) = 0 \dots\dots\dots(2)$$

$$2I_2 - 4I_1 + 4I_2 = -E \Rightarrow 6I_2 - 4I_1 = -2$$

By substitute I_1

$$6I_2 - 4\left(\frac{6 + 4I_2}{5}\right) = -2 \Rightarrow 6I_2 - \frac{24}{5} - \frac{16I_2}{5} = -2 \Rightarrow 30I_2 - 24 - 16I_2 = -10$$

$$14I_2 = 14 \Rightarrow I_2 = \frac{14}{14} = 1A$$


$$I_1 = \frac{6 + 4(1)}{5} = 2A$$

$$V_1 = 1I_1 = 2V$$

$$V_2 = 2I_2 = 2(1) = 2V$$

$$V_3 = 4(I_1 - I_2) = 4(2 - 1) = 4V$$

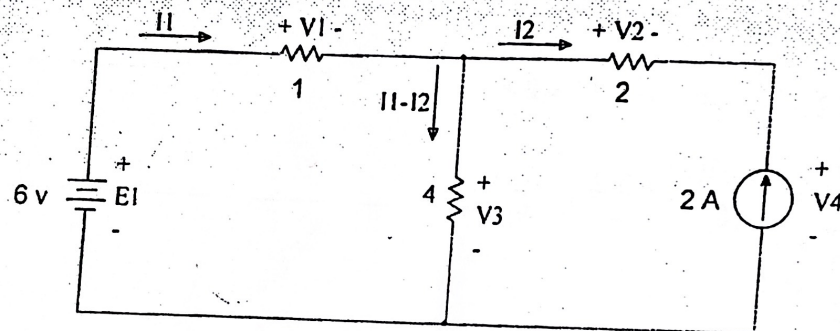EXAMPLE: using Kirchhoff's laws. Find the currents and voltages in the circuit shown.



Solution:

From the circuit $I_2 = -2A$

$$I_1 + 4(I_1 - I_2) - E_1 = 0 \dots\dots\dots(1)$$

$$I_1 + 4I_1 - 4I_2 = E_1 \Rightarrow 5I_1 - 4I_2 = 6 \Rightarrow I_1 = \frac{6 + 4I_2}{5} = \frac{6 + 4(-2)}{5} = -0.4A$$

$$2I_2 + V_4 - 4(I_1 - I_2) = 0 \dots\dots\dots(2)$$

$$2I_2 - 4I_1 + 4I_2 + V_4 = 0 \Rightarrow 6I_2 - 4I_1 + V_4 = 0 \Rightarrow V_4 = 4I_1 - 6I_2 = 4(-0.4) - 6(-2) = 10.4$$


$$V_1 = 1I_1 = -0.4V$$

$$V_2 = 2I_2 = 2(-2) = -4V$$

$$V_3 = 4(I_1 - I_2) = 4(-0.4 + 2) = 6.4V$$


Current Sources in Parallel

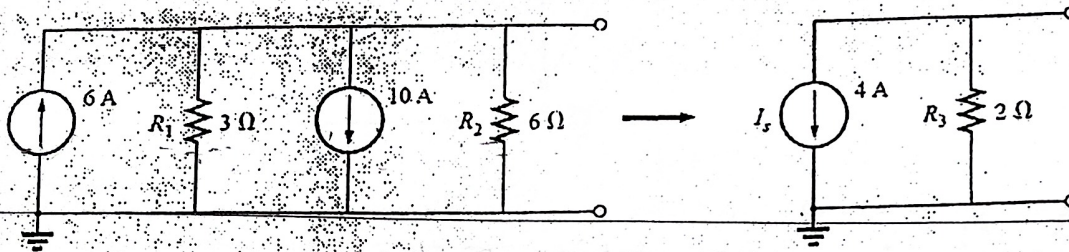If two or more current sources are in parallel, they may all be replaced by one current source having the magnitude and direction of the resultant



$$I_s = 10\text{ A} - 6\text{ A} = 4\text{ A}$$
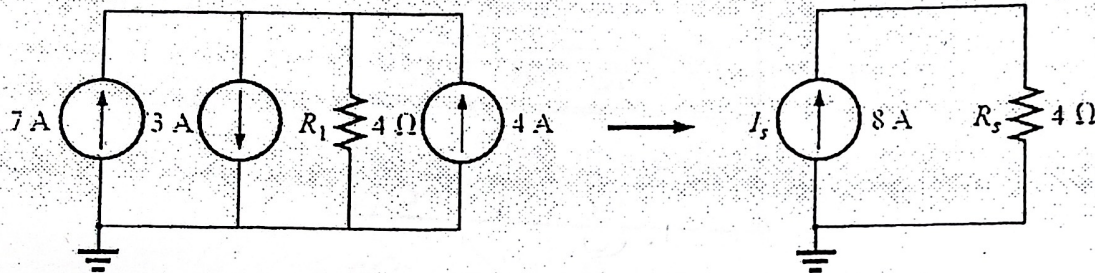
$$R_s = 3\ \Omega \parallel 6\ \Omega = 2\ \Omega \Rightarrow R_s = \frac{R_1 * R_2}{R_1 + R_2}$$



$$I_s = 7\text{ A} + 4\text{ A} - 3\text{ A} = 8\text{ A}$$

$$R_s = R_1 = 4\ \Omega$$

$$R_s = \frac{3 * 6}{3 + 6} = \frac{18}{9} = 2$$