
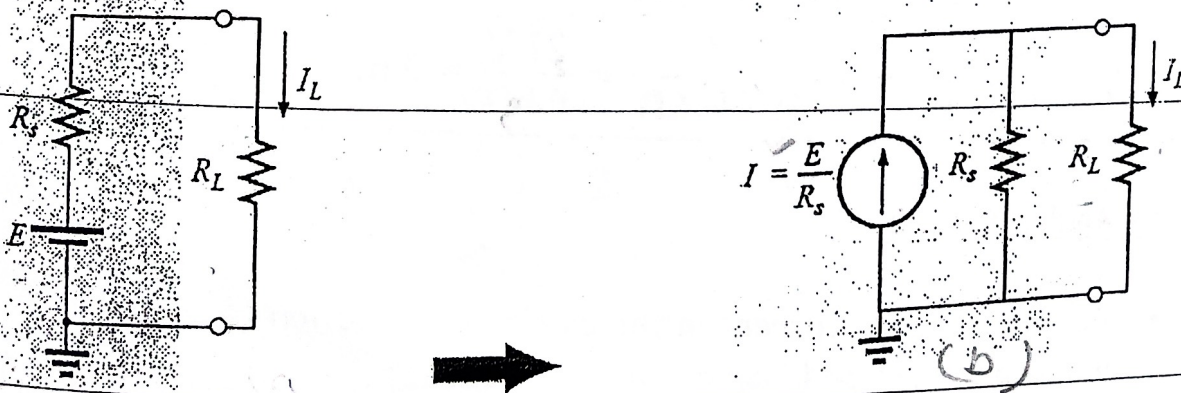


Methods of Analysis


Source Conversions

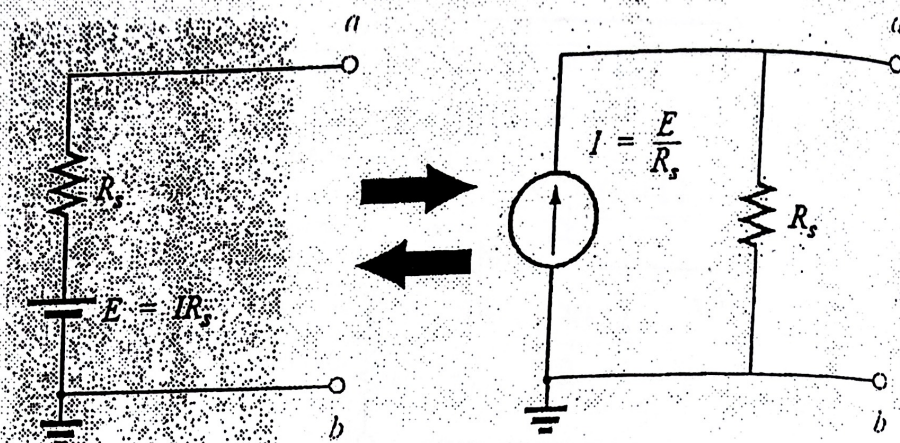To perform a conversion from one type of source to another, a voltage source must have a resistor in series with it, and a current source must have a resistor in parallel.





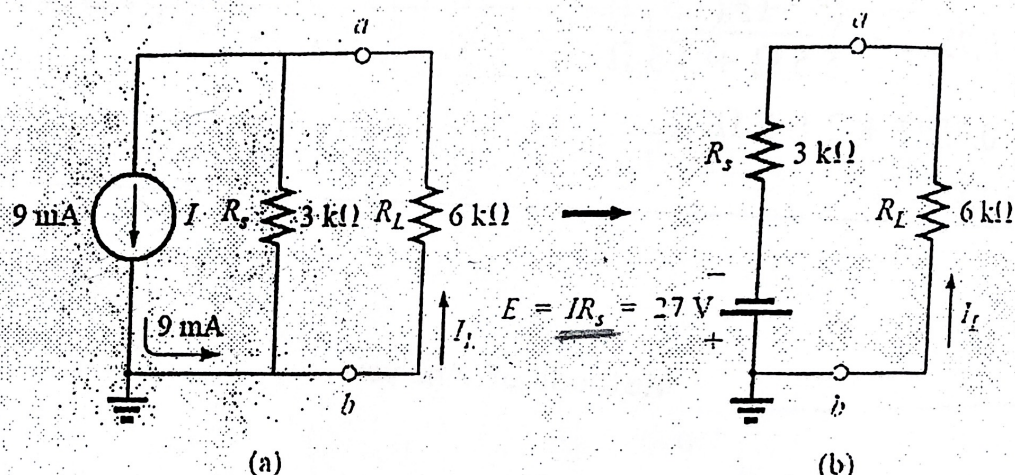EXAMPLE: Convert the current source of the circuit below to a voltage source, and find the load current for each source.



Solution:


$$(a): I_L = \frac{R_s I}{R_s + R_L} = \frac{(3 \text{ k}\Omega)(9 \text{ mA})}{3 \text{ k}\Omega + 6 \text{ k}\Omega} = 3 \text{ mA}$$

$$(b): I_L = \frac{E}{R_s + R_L} = \frac{27 \text{ V}}{3 \text{ k}\Omega + 6 \text{ k}\Omega} = \frac{27 \text{ V}}{9 \text{ k}\Omega} = 3 \text{ mA}$$

Mesh Analysis (Loop)

- Assign a distinct current in the clockwise direction to each independent, closed loop of the network.
- Indicate the polarities within each loop for each resistor as determined by the assumed direction of loop current for that loop.
- Write the linear equations for each loop.
- Solve the resulting linear equations for the assumed loop currents.

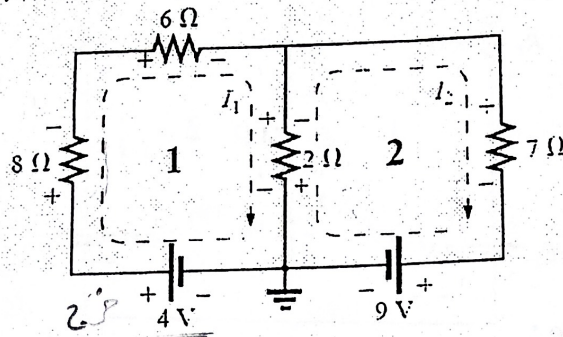EXAMPLE: Write the mesh equations for the network, and find the current through the 7-Ω resistor.



Solution:

$$I_1: (8\Omega + 6\Omega + 2\Omega)I_1 - (2\Omega)I_2 = 4\text{ V}$$

$$I_2: (7\Omega + 2\Omega)I_2 - (2\Omega)I_1 = -9\text{ V}$$

$$16I_1 - 2I_2 = 4$$

$$9I_2 - 2I_1 = -9$$


$$16I_1 - 2I_2 = 4$$

$$-2I_1 + 9I_2 = -9$$

$$I_2 = I_{7\Omega} = \frac{\begin{vmatrix} 16 & 4 \\ -2 & -9 \end{vmatrix}}{\begin{vmatrix} 16 & -2 \\ -2 & 9 \end{vmatrix}} = \frac{-144 + 8}{144 - 4} = \frac{-136}{140}$$

$$= -0.971\text{ A}$$

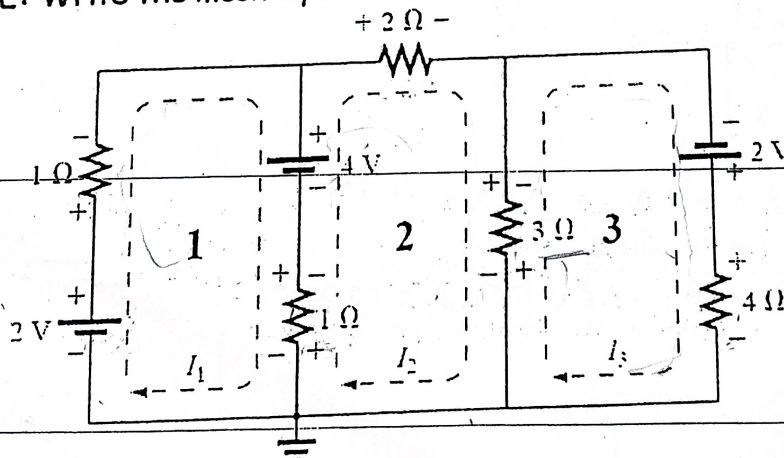EXAMPLE: Write the mesh equations for the network




Solution:

$$2I_1 - I_2 + 0 = -2$$

$$6I_2 - I_1 - 3I_3 = 4$$

$$7I_3 - 3I_2 + 0 = 2$$

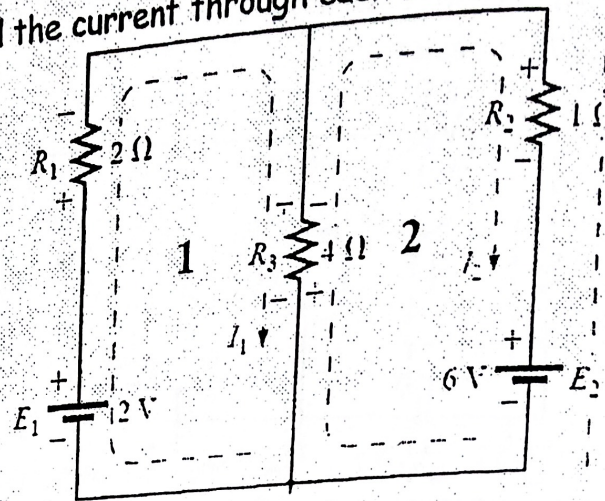EXAMPLE: Find the current through each branch of the network



Solution:

$$6I_1 - 4I_2 = 2 \quad \text{.....(1)}$$

$$5I_2 - 4I_1 = -6 \quad \text{.....(2)}$$

$$6I_1 - 4I_2 = 2$$


$$-4I_1 + 5I_2 = -6$$

$$I_1 = \frac{\begin{bmatrix} 2 & -4 \\ -6 & 5 \end{bmatrix}}{\begin{bmatrix} 6 & -4 \\ -4 & 5 \end{bmatrix}} = \frac{(2 \times 5) - (-4 \times -6)}{(6 \times 5) - (-4 \times -4)} = \frac{10 - 24}{30 - 16} = \frac{-14}{14} = -1 \text{ A}$$

$$I_2 = \frac{\begin{bmatrix} 6 & 2 \\ -4 & -6 \end{bmatrix}}{\begin{bmatrix} 6 & -4 \\ -4 & 5 \end{bmatrix}} = -2 \text{ A}$$

$$I_{4\Omega} = I_1 - I_2 = -1 \text{ A} - (-2 \text{ A}) = -1 \text{ A} + 2 \text{ A} = 1 \text{ A} \quad (\text{in the direction of } I_1)$$

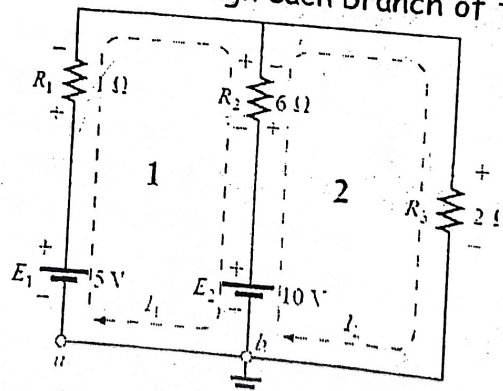EXAMPLE: Find the current through each branch of the network



Solution:

$$7I_1 - 6I_2 = 5 - 10 \dots\dots\dots(1)$$

$$8I_2 - 6I_1 = 10 \dots\dots\dots(2)$$

$$-7I_1 + 6I_2 = 5$$


$$+6I_1 - 8I_2 = -10$$

$$I_1 = \frac{\begin{vmatrix} 5 & 6 \\ -10 & -8 \end{vmatrix}}{\begin{vmatrix} -7 & 6 \\ 6 & -8 \end{vmatrix}} = \frac{-40 + 60}{56 - 36} = \frac{20}{20} = 1 \text{ A}$$

$$I_2 = \frac{\begin{vmatrix} -7 & 5 \\ 6 & -10 \end{vmatrix}}{20} = \frac{70 - 30}{20} = \frac{40}{20} = 2 \text{ A}$$

$$I_{R_2} = I_2 - I_1 = 2 \text{ A} - 1 \text{ A} = 1 \text{ A} \text{ in the direction of } I_2$$

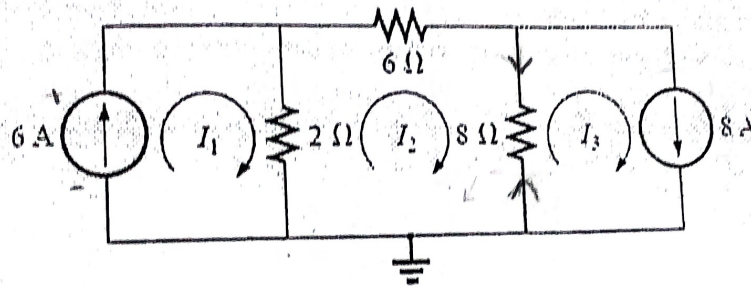EXAMPLE: Using mesh analysis, determine the currents of the network



Solution:

$$I_1 = 6 \text{ A}$$

$$I_3 = 8 \text{ A}$$

$$2I_1 - 16I_2 + 8I_3 = 0$$


$$2(6 \text{ A}) - 16I_2 + 8(8 \text{ A}) = 0$$

$$I_2 = \frac{76 \text{ A}}{16} = 4.75 \text{ A}$$

$$I_{2\Omega} \downarrow = I_1 - I_2 = 6 \text{ A} - 4.75 \text{ A} = 1.25 \text{ A}$$

$$I_{8\Omega} \uparrow = I_3 - I_2 = 8 \text{ A} - 4.75 \text{ A} = 3.25 \text{ A}$$

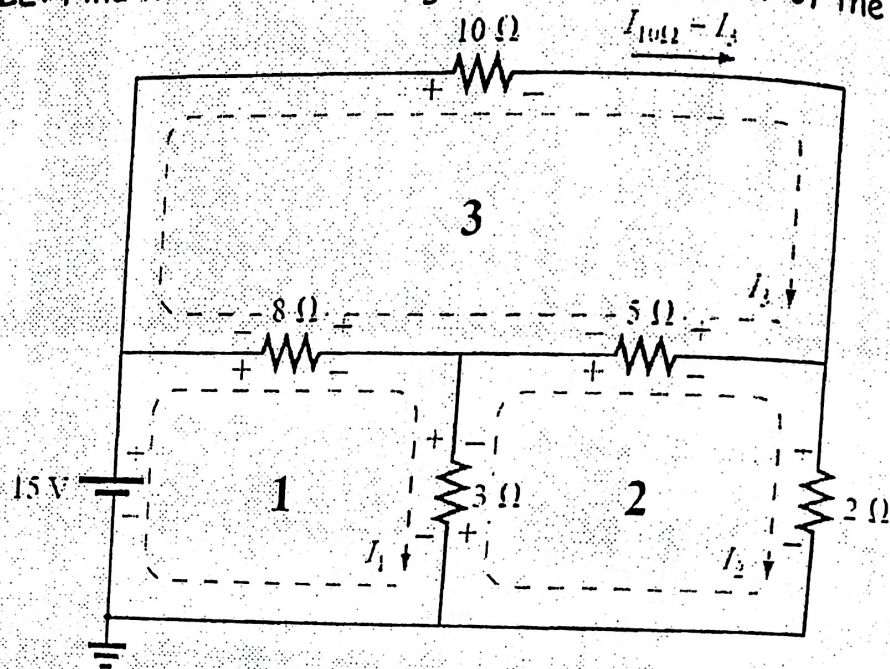EXAMPLE: Find the current through the $10\text{-}\Omega$ resistor of the network



Solution:

$$I_1: (8\Omega + 3\Omega)I_1 - (8\Omega)I_3 - (3\Omega)I_2 = 15\text{ V}$$

$$I_2: (3\Omega + 5\Omega + 2\Omega)I_2 - (3\Omega)I_1 - (5\Omega)I_3 = 0$$

$$I_3: (8\Omega + 10\Omega + 5\Omega)I_3 - (8\Omega)I_1 - (5\Omega)I_2 = 0$$

$$11I_1 - 8I_3 - 3I_2 = 15$$

$$10I_2 - 3I_1 - 5I_3 = 0$$

$$23I_3 - 8I_1 - 5I_2 = 0$$

$$11I_1 - 3I_2 - 8I_3 = 15$$

$$-3I_1 + 10I_2 - 5I_3 = 0$$

$$-8I_1 - 5I_2 + 23I_3 = 0$$

$$I_3 = I_{10\Omega} = \frac{\begin{vmatrix} 11 & -3 & 15 \\ -3 & 10 & 0 \\ -8 & -5 & 0 \end{vmatrix}}{\begin{vmatrix} 11 & -3 & -8 \\ -3 & 10 & -5 \\ -8 & -5 & 23 \end{vmatrix}} = 1.220\text{ A}$$