
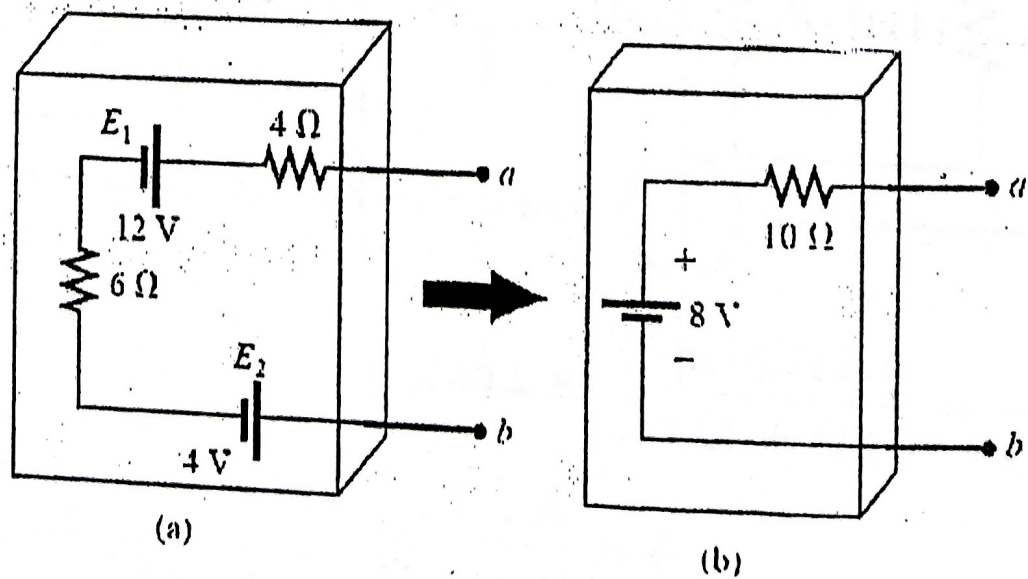


Thevenin's Theorem

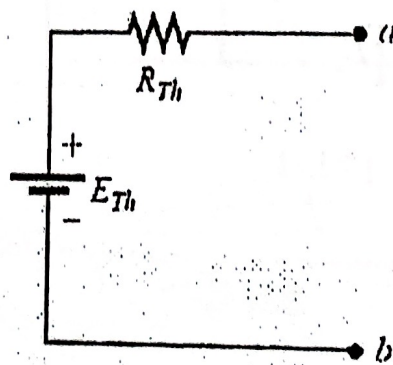Any two-terminal, linear bilateral dc network can be replaced by an equivalent circuit consisting of a voltage source and a series resistor,




The following sequence of steps will lead to the proper value of R_{Th} and E_{Th} .

- 1) Remove that portion of the network across which the Thévenin equivalent circuit is to be found.
- 2) Mark the terminals of the remaining two-terminal network.
- 3) Calculate R_{Th} by first setting all sources to zero (voltage sources are replaced by short circuits and current sources by open circuits) and then finding the resultant resistance between the two marked terminals.
- 4) Calculate E_{Th} by first returning all sources to their original position and finding the open-circuit voltage between the marked terminals.
- 5) Draw the Thévenin equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.


So the load current will be equal to


$$I_L = \frac{E_{th}}{R_{th} + R_L}$$

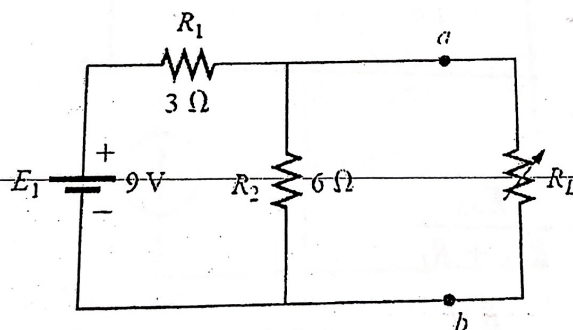EXAMPLE: Find the Thévenin equivalent circuit for the network in the shaded area of the network. Then find the current through R_L for values of 2Ω , 10Ω , and 100Ω .




Solution:

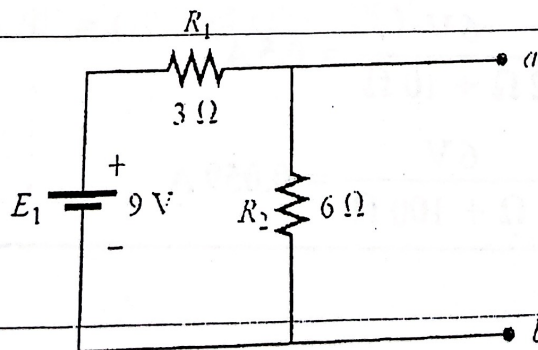


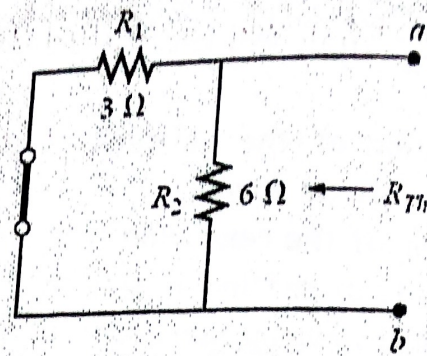
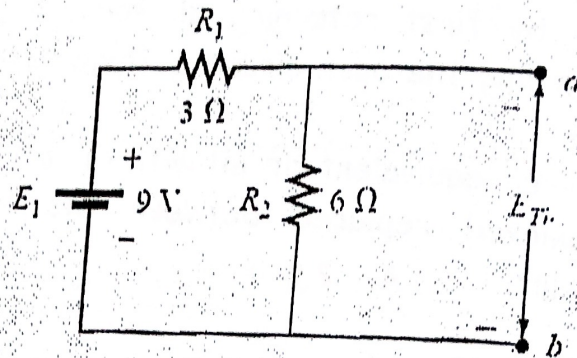
$$R_{Th} = R_1 \parallel R_2 = \frac{(3 \Omega)(6 \Omega)}{3 \Omega + 6 \Omega} = 2 \Omega$$


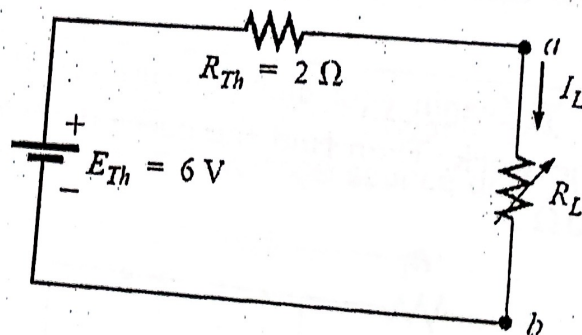
$$E_{Th} = \frac{R_2 E_1}{R_2 + R_1} = \frac{(6 \Omega)(9 \text{ V})}{6 \Omega + 3 \Omega} = \frac{54 \text{ V}}{9} = 6 \text{ V}$$




$$I_L = \frac{E_{Th}}{R_{Th} + R_L}$$

$$R_L = 2 \Omega: \quad I_L = \frac{6 \text{ V}}{2 \Omega + 2 \Omega} = 1.5 \text{ A}$$



$$R_L = 10 \Omega: \quad I_L = \frac{6 \text{ V}}{2 \Omega + 10 \Omega} = 0.5 \text{ A}$$

$$R_L = 100 \Omega: \quad I_L = \frac{6 \text{ V}}{2 \Omega + 100 \Omega} = 0.059 \text{ A}$$

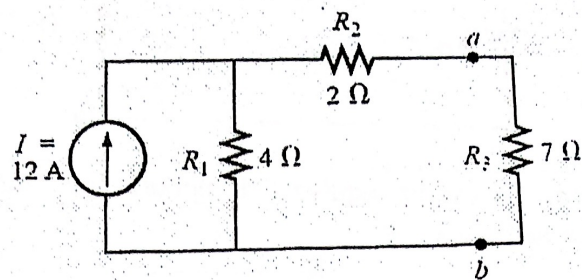
EXAMPLE: Find the Thévenin equivalent circuit for the network in the shaded area of the network



Solution:

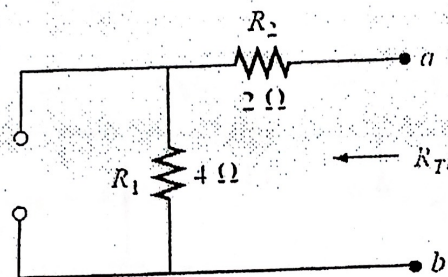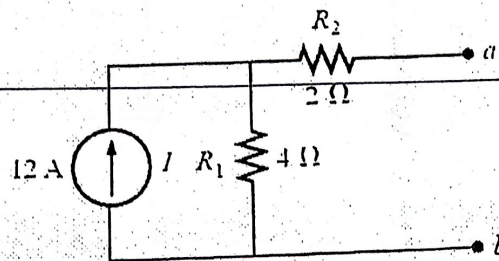

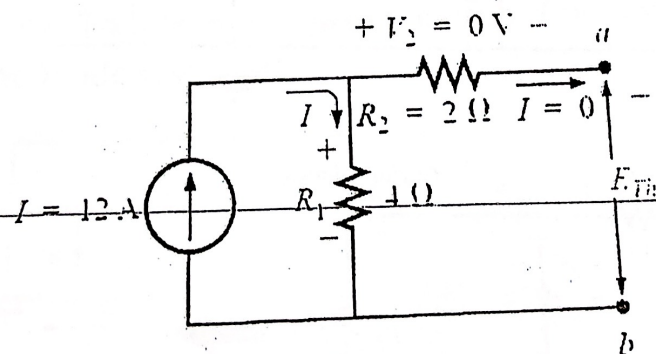
$$R_{Th} = R_1 + R_2 = 4 \Omega + 2 \Omega = 6 \Omega$$




$$V_2 = I_2 R_2 = (0) R_2 = 0 \text{ V}$$


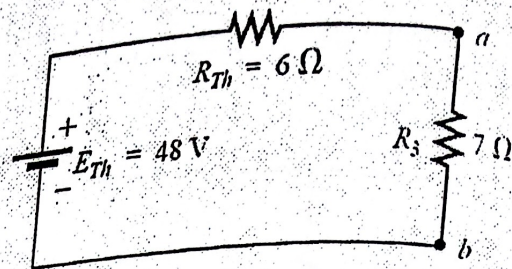
$$E_{Th} = V_1 = I_1 R_1 = I R_1 = (12 \text{ A})(4 \Omega) = 48 \text{ V}$$




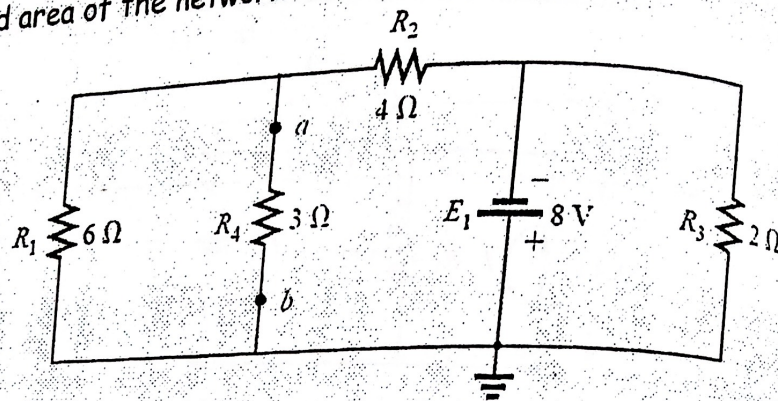
EXAMPLE: Find the Thévenin equivalent circuit for the network in shaded area of the network




Solution:

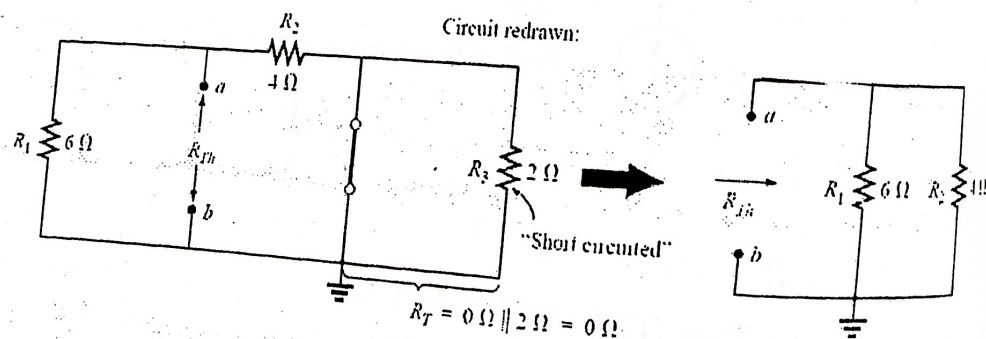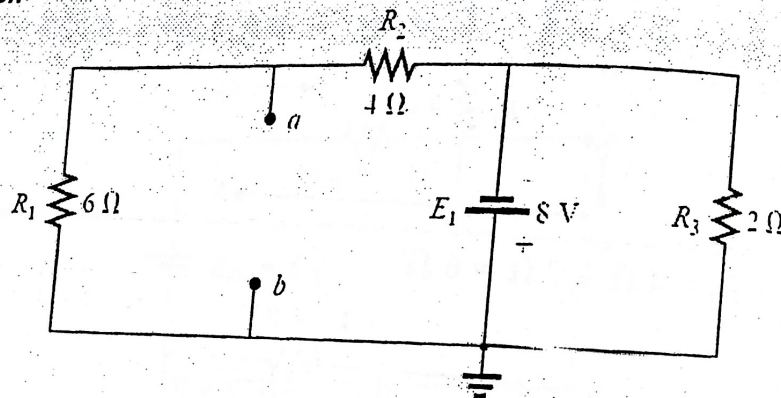
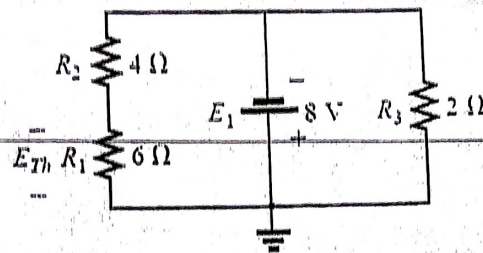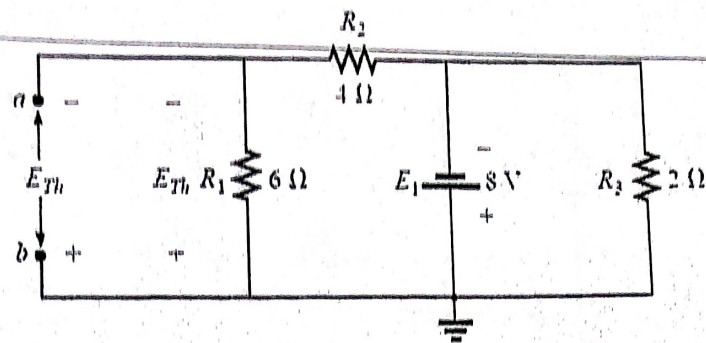
$$R_{Th} = R_1 \parallel R_2 = \frac{(6 \Omega)(4 \Omega)}{6 \Omega + 4 \Omega} = \frac{24 \Omega}{10} = 2.4 \Omega$$


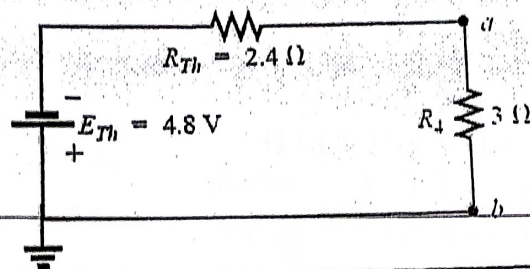
$$E_{Th} = \frac{R_1 E_1}{R_1 + R_2} = \frac{(6 \Omega)(8 \text{ V})}{6 \Omega + 4 \Omega} = \frac{48 \text{ V}}{10} = 4.8 \text{ V}$$



EXAMPLE: Find the Thévenin equivalent circuit for the network in the shaded area of the bridge network

